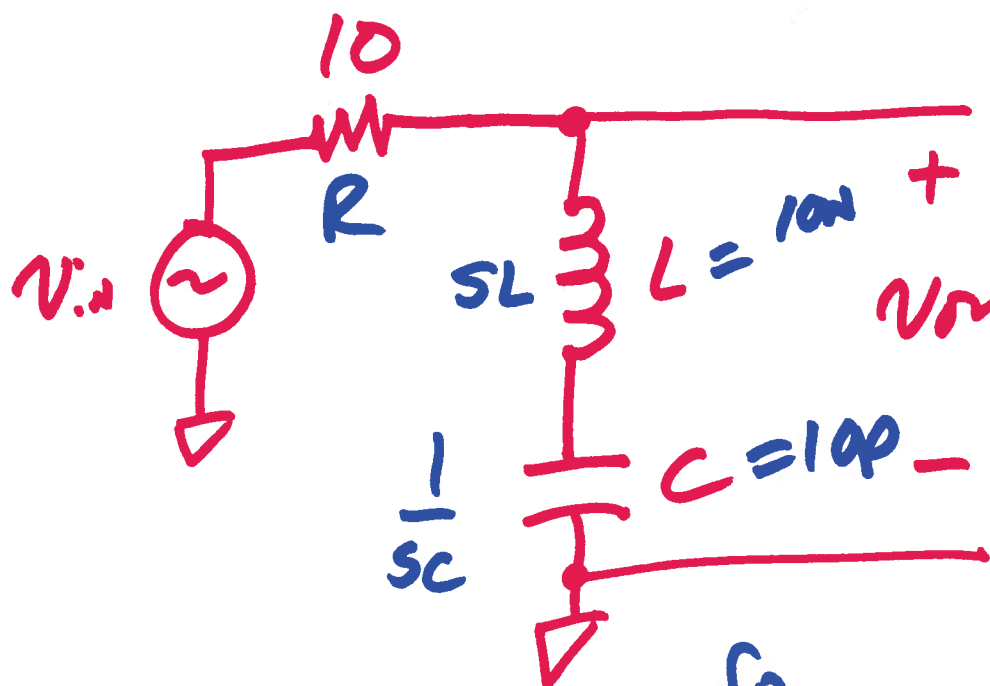


EE 421 / ECE 621

Lecture 3

Sept. 5, 2018




$$= V_{in} \cdot \frac{s^2 LC + 1}{s^2 LC + sCR + 1}$$

$$= V_{in} \cdot \frac{1}{sL + \frac{1}{sC}}$$

$$= V_{in} \cdot \frac{1}{R + sL + \frac{1}{sC}}$$

f_0
 $f_{3dB} - f_{-3dB}$

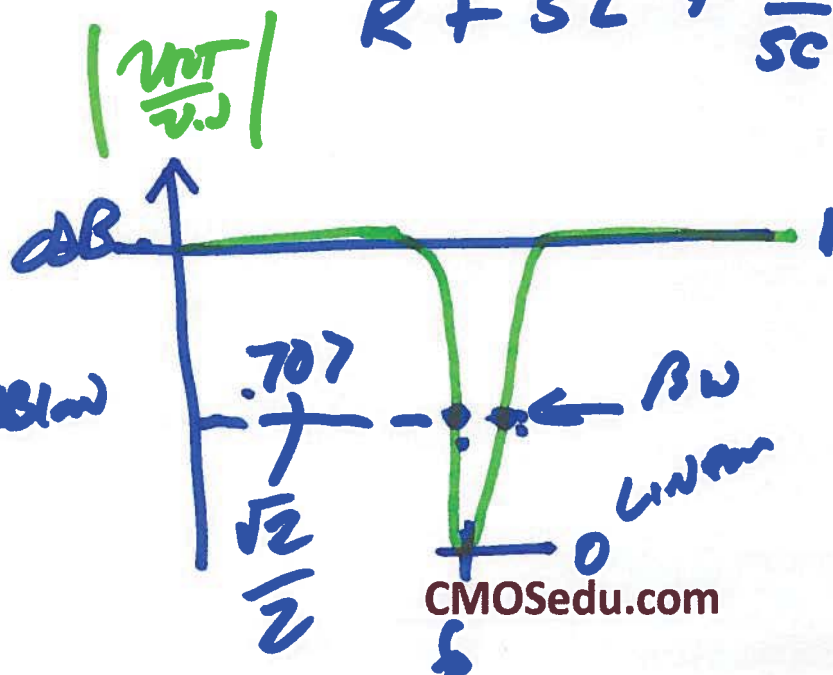

$$\frac{v_{NT}}{v_N} = \frac{s^2 + \frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

At f_0 $\frac{v_{NT}}{v_N} = 0 = \left(\frac{s^2 + \frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}} \right)$


$$\frac{1}{2\pi\sqrt{LC}} = f_0$$

$$s \rightarrow j \cdot 2\pi \cdot \frac{1}{\sqrt{LC} \cdot 2\pi} = f_0$$

$$\frac{\pm \sqrt{-4 \frac{1}{LC}}}{2} = \pm \frac{j}{\sqrt{LC}} \quad \text{root} =$$

$$\left. \begin{array}{l} s_{3dB}^2 + \frac{1}{LC} \\ s_{3dB}^2 + s_{3dB} \frac{R}{L} + \frac{1}{LC} \end{array} \right|$$
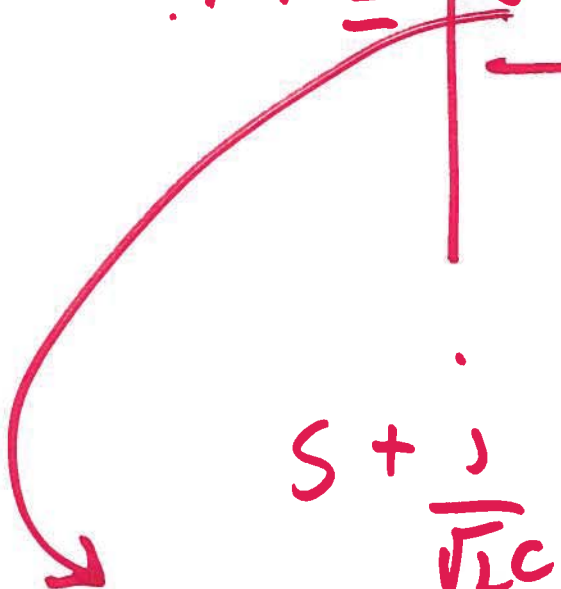
$$707 = \left(s_{3dB} + \frac{j}{\sqrt{LC}} \right) \left(s_{3dB} - \frac{j}{\sqrt{LC}} \right)$$






$$s + \frac{j}{\sqrt{LC}}$$

$$= j \cdot 2\pi f + \frac{j}{\sqrt{LC}}$$


$$= j \left(2\pi f + \frac{1}{\sqrt{LC}} \right)$$

$$f_{3dB} \pm \frac{1}{\sqrt{LC}} \cdot 2\pi$$

3)

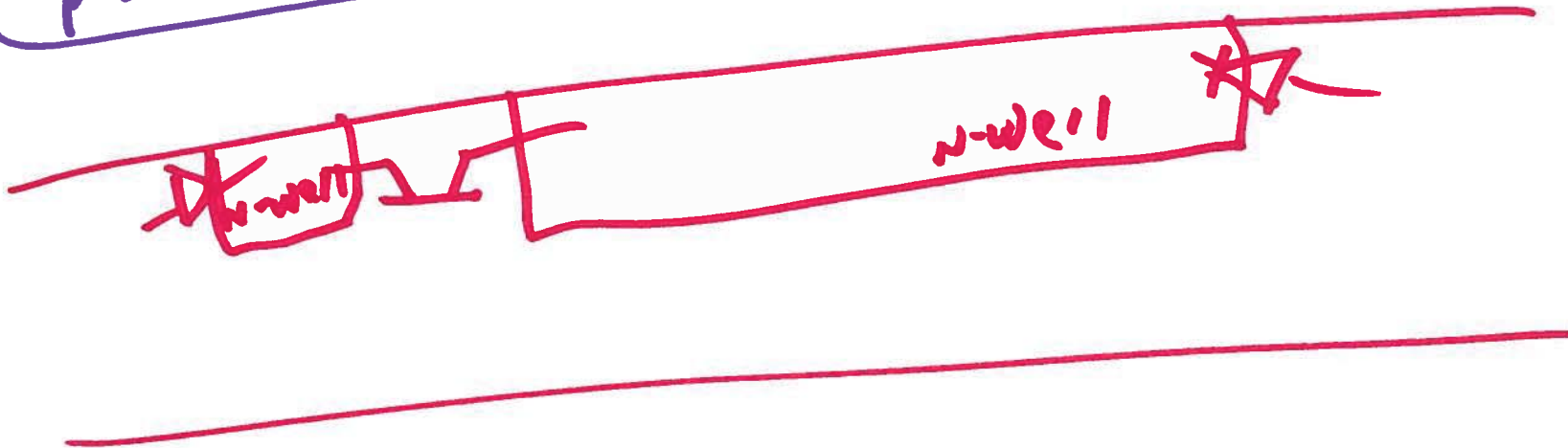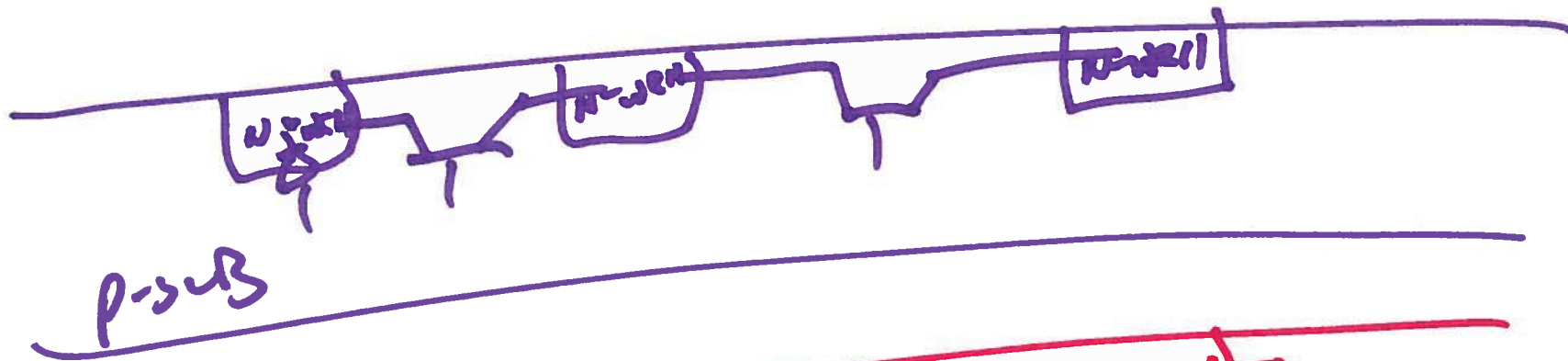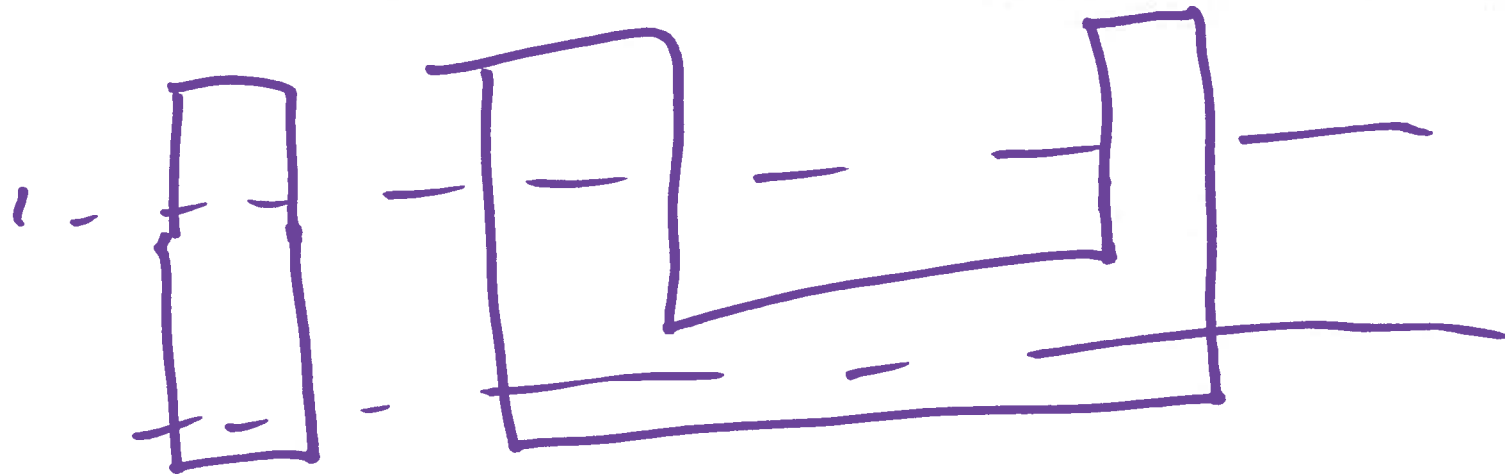


4)


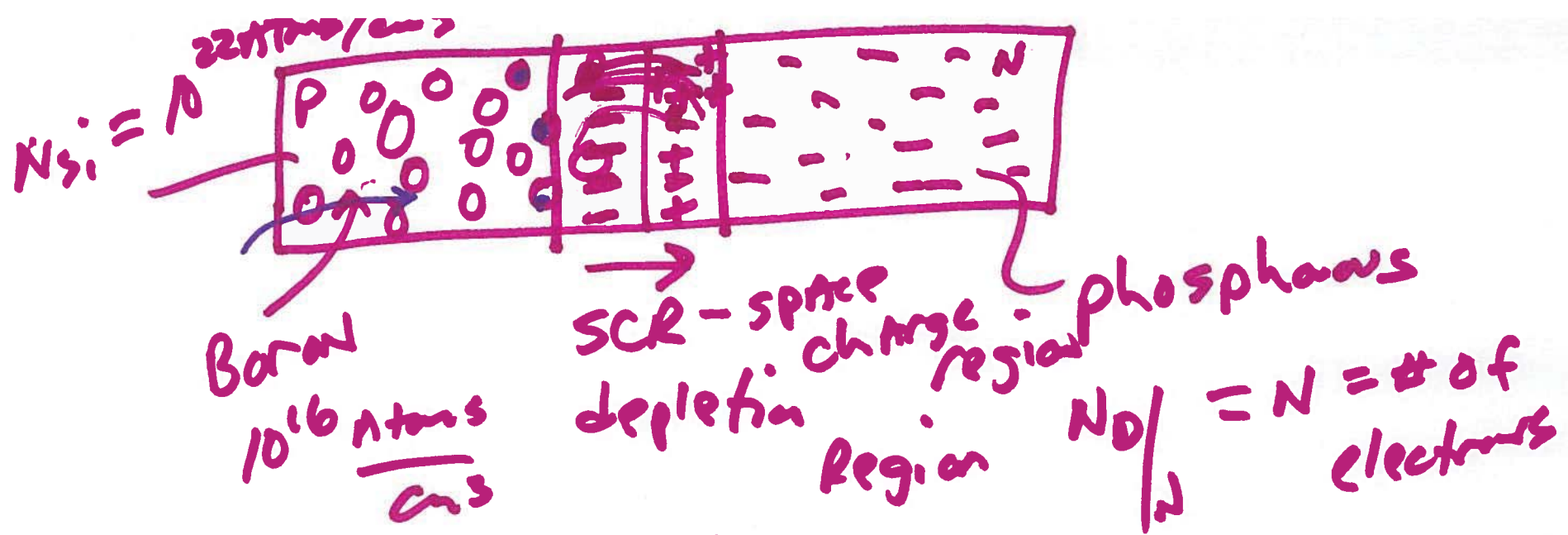


$N_A = p = \# \text{ of holes}$
 $N_D = n = \# \text{ of electrons}$

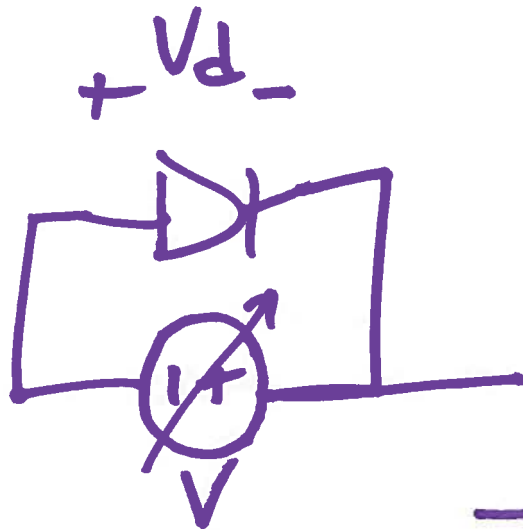$C = \epsilon \cdot \frac{A}{t}$
 $C_j(V_0)$



5)

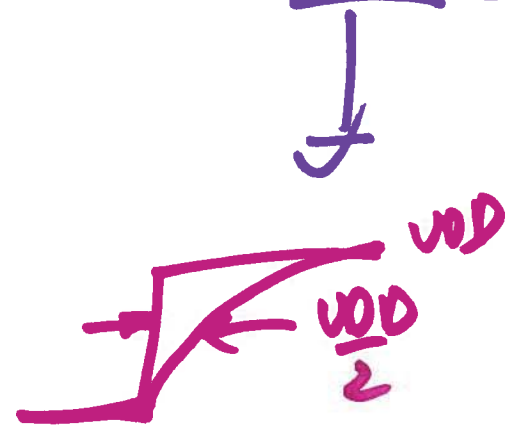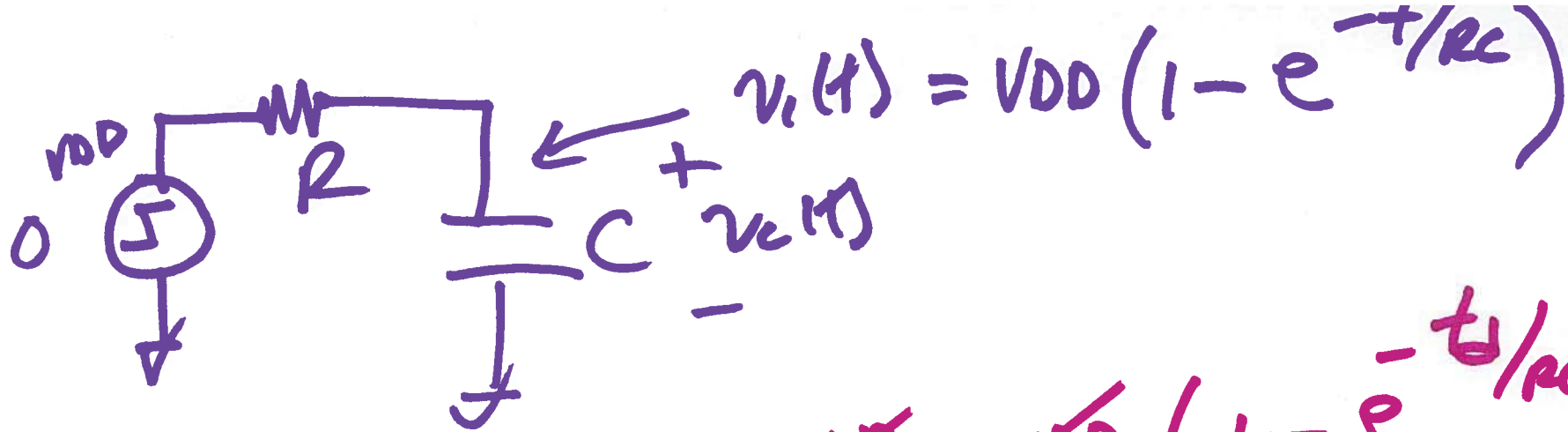


$$\frac{VDD}{2} = VDD(1 - e^{-t_d/RC})$$

$$-\frac{1}{2} = -e^{-t_d/RC}$$

$$RC(-\ln \frac{1}{2}) = t_d$$

$$t_d = 0.7RC$$

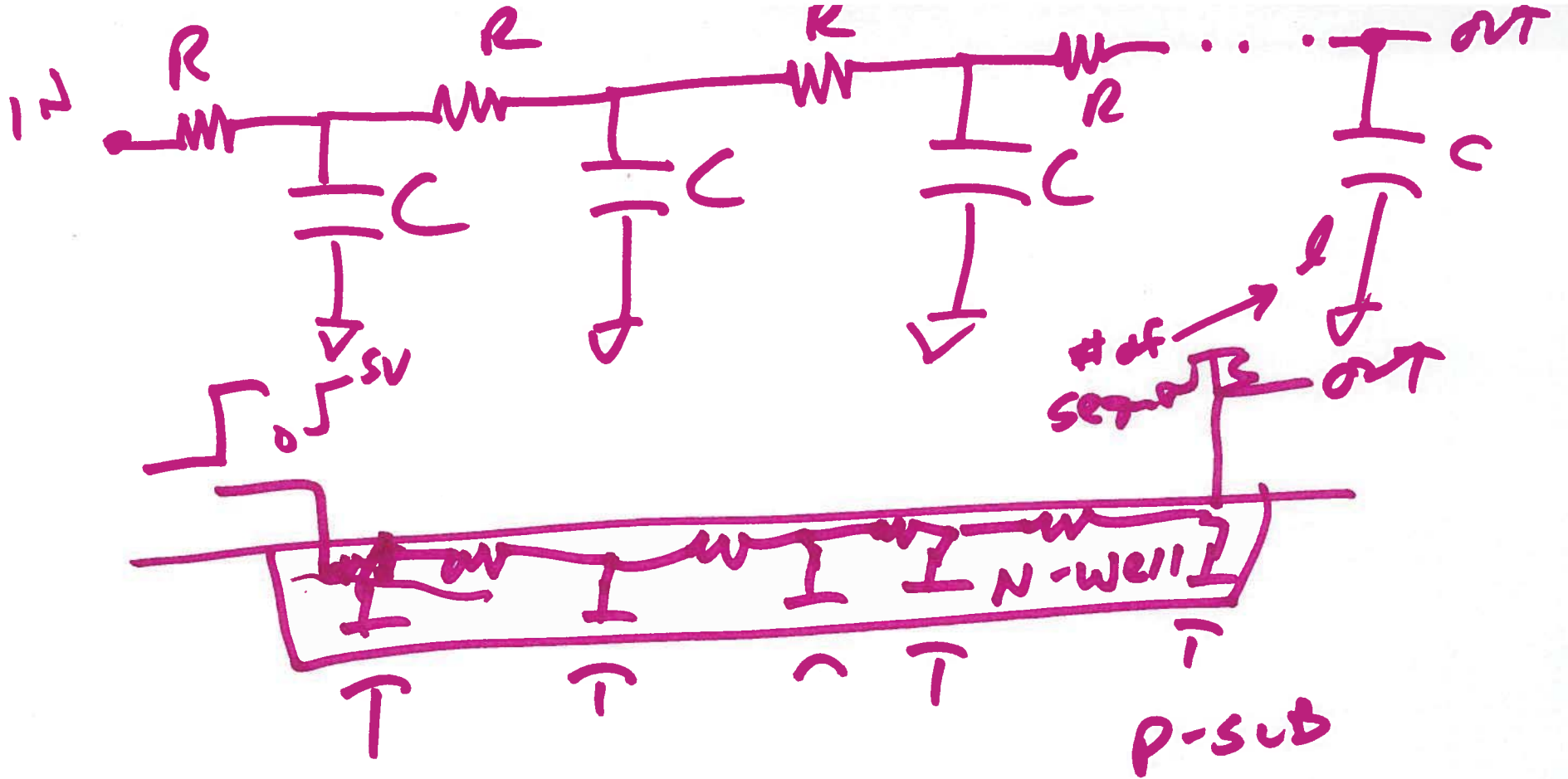

$$\begin{aligned}
 t_w &= 0.7RC + 0.72RC + 0.73RC + 0.74R \\
 &+ 0.72RC + 0.73RC + 0.74R \\
 &= 0.7RC \cdot \left(\frac{2+1}{2} \right) \approx 0.7RC \frac{2^2 + 4 + \dots}{2} \\
 &= 0.7RC(1+2+3+\dots+n) \\
 &\approx 0.7RC \frac{n^2}{2} \\
 &\approx 0.35RCn^2
 \end{aligned}$$

CMOSedu.com

$\approx 0.35RCn^2$

7)

