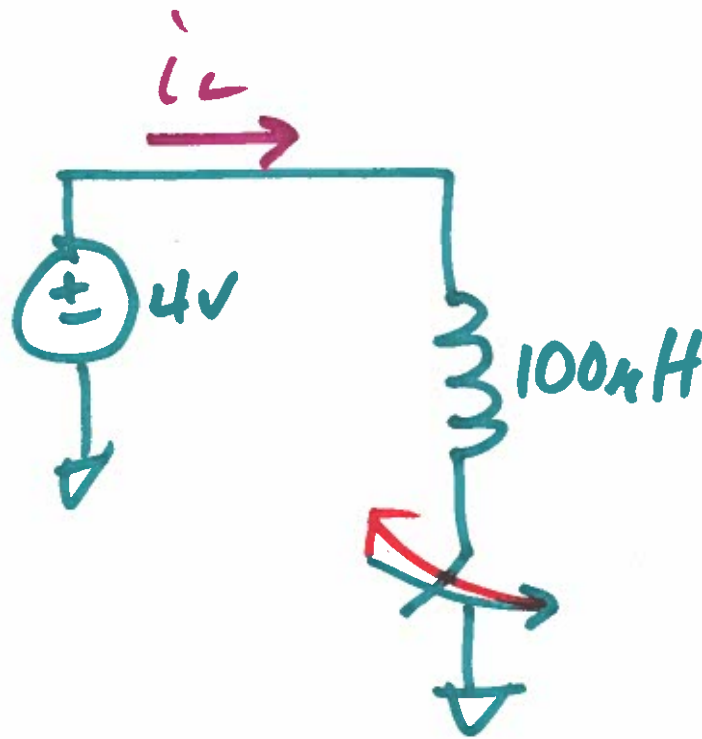



# EE421 / ECG 621 Digital IC Design

OCT. 16, 2019

## Lecture 14




$$+ V_L = 4$$
$$-$$

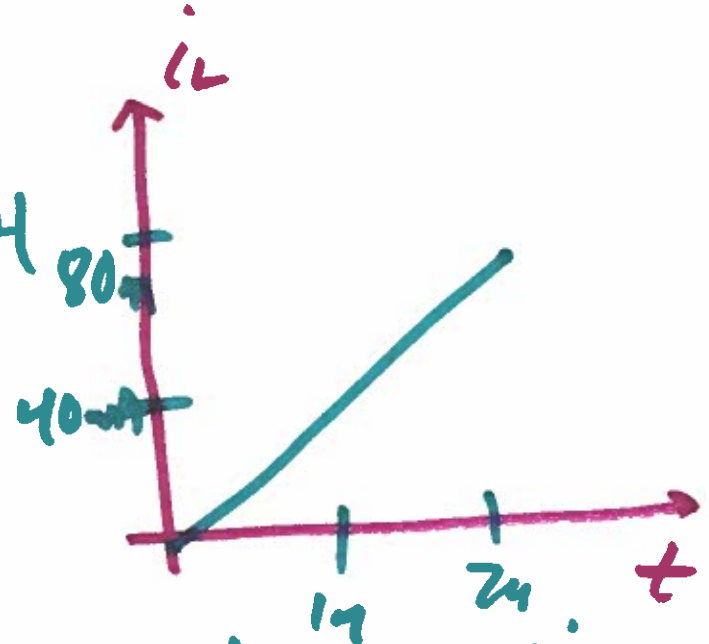



$$V = L \cdot \frac{di}{dt}$$
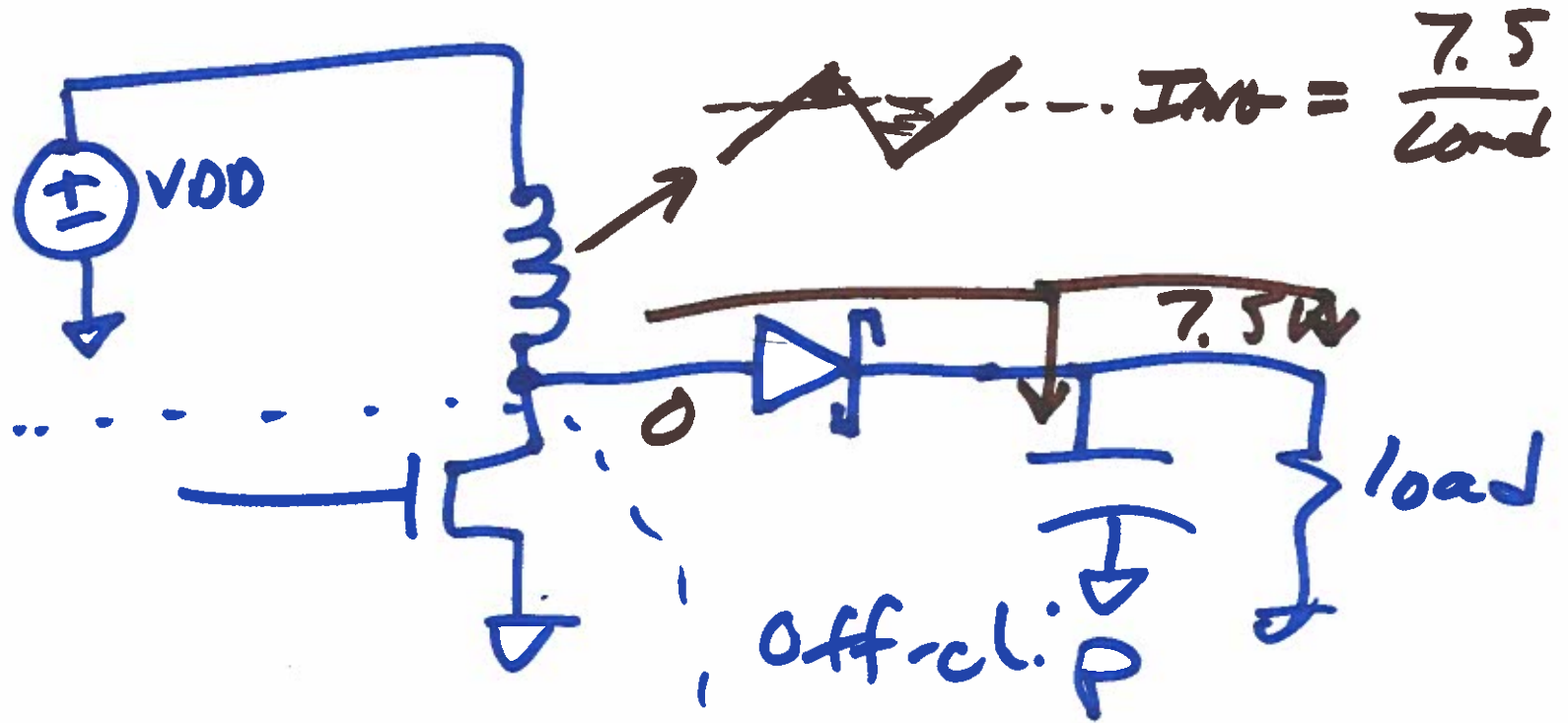
$$\rightarrow \frac{4}{100\mu\text{H}} = \frac{di}{dt} = \frac{40\mu\text{A}}{1\text{S}}$$



Boost converter

2)

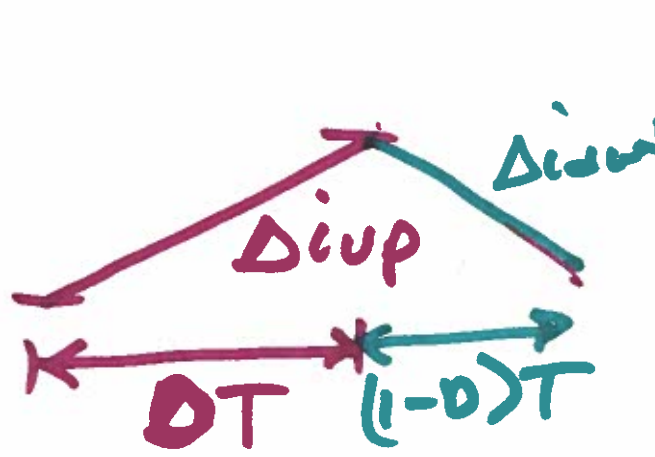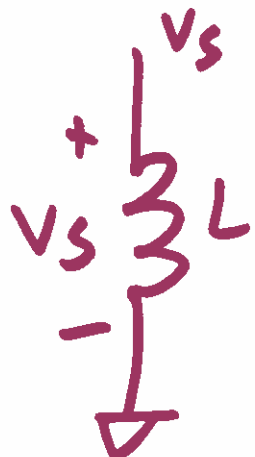

$$V = L \cdot \frac{di}{dt}$$


$$\frac{V_s}{L} = \frac{\Delta i_{Lp}}{D \cdot T}$$

$$T = \frac{1}{f}$$



$$\frac{V_s - V_{out}}{L} = \frac{\Delta i_{Lw}}{(1-D)T}$$

D = duty cycle

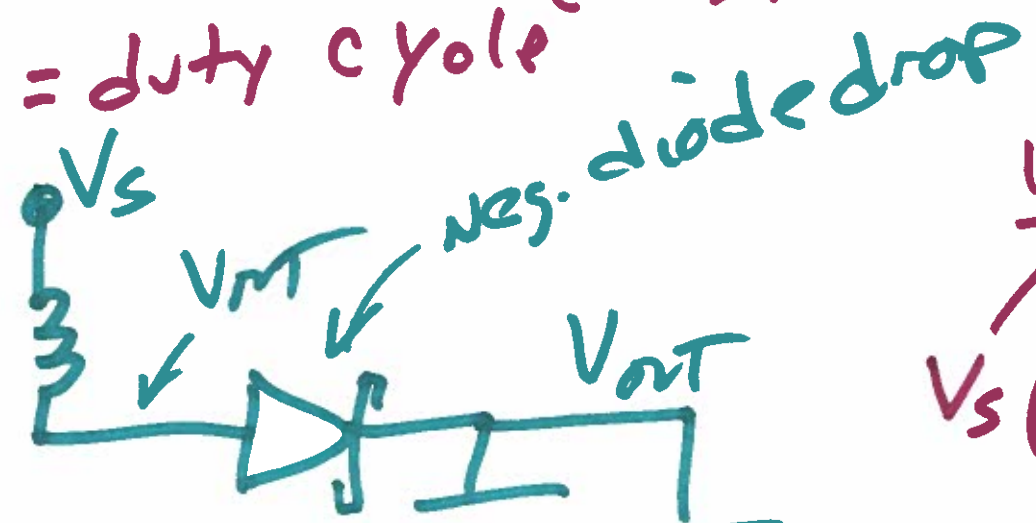

$$\frac{V_s}{f} \cdot D = \left( \frac{V_s - V_{out}}{L} \cdot (1-D) \cdot T \right)$$


$$V_s \left( \frac{D}{L} \right)$$

3)

$$\cancel{V_S} D = V_S + \cancel{V_S} D + V_{OUT} - D V_{OUT}$$



$$V_S = V_{OUT} (1 - D)$$

$$V_{OUT} = \frac{V_S}{1 - D}$$


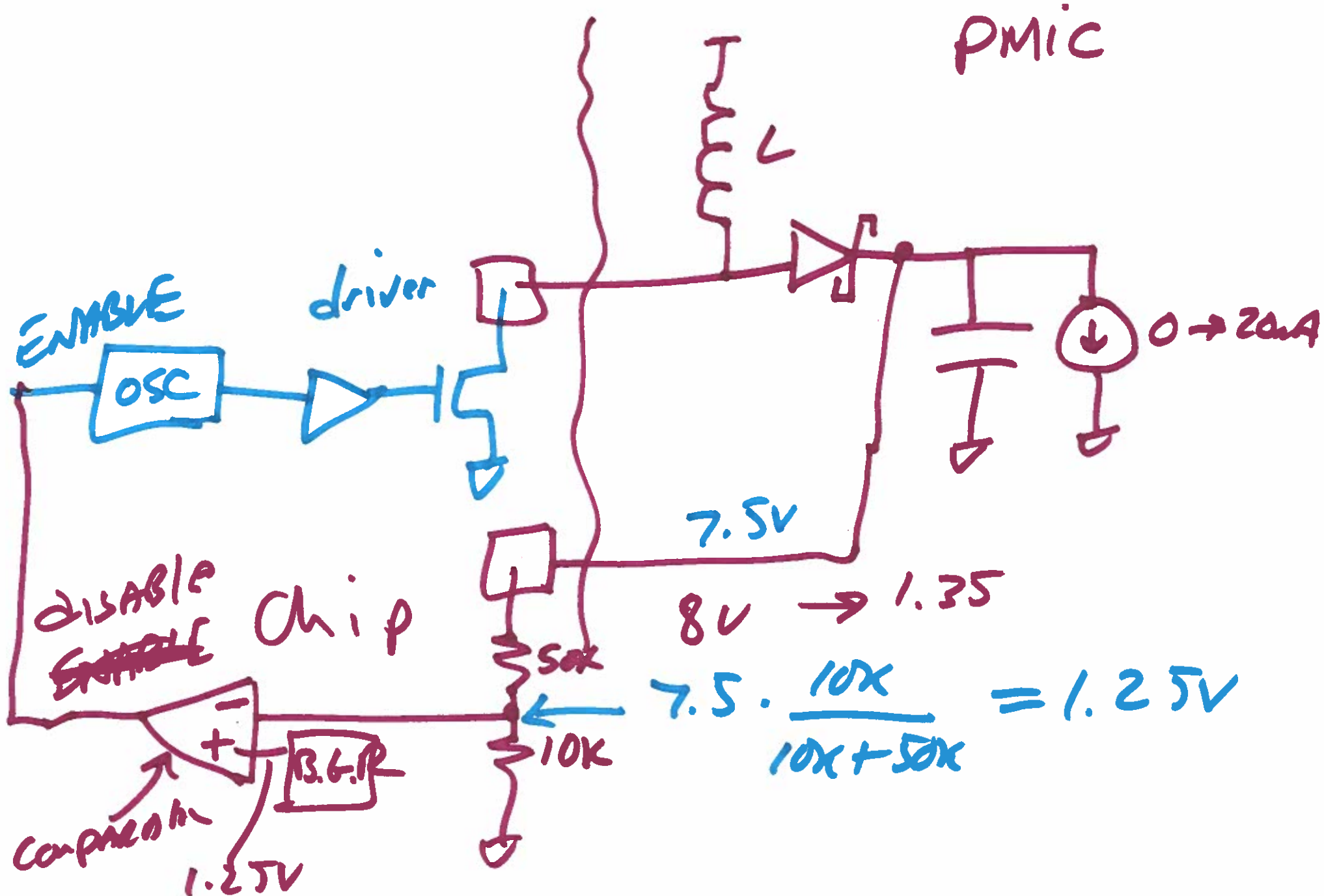


5)



# Ring oscillator

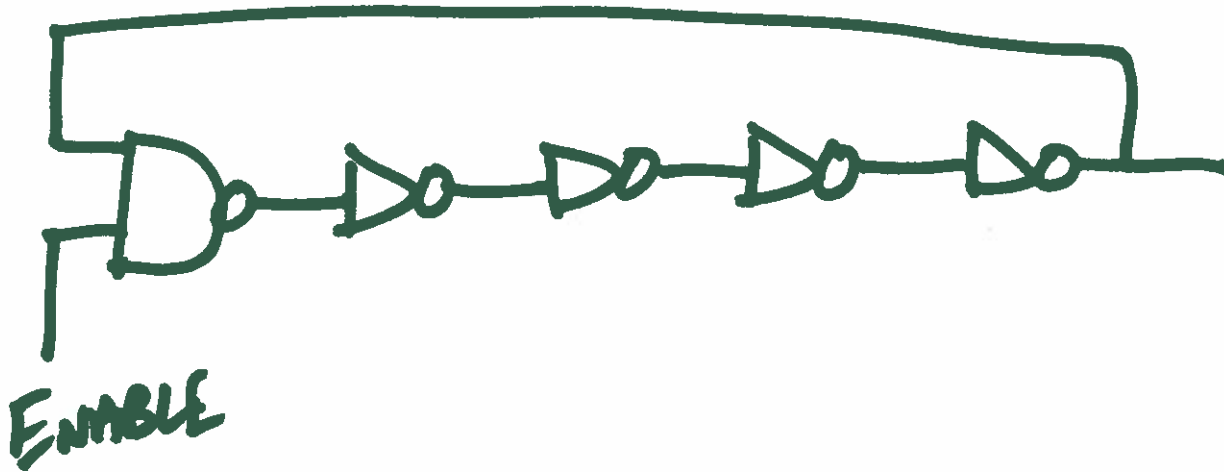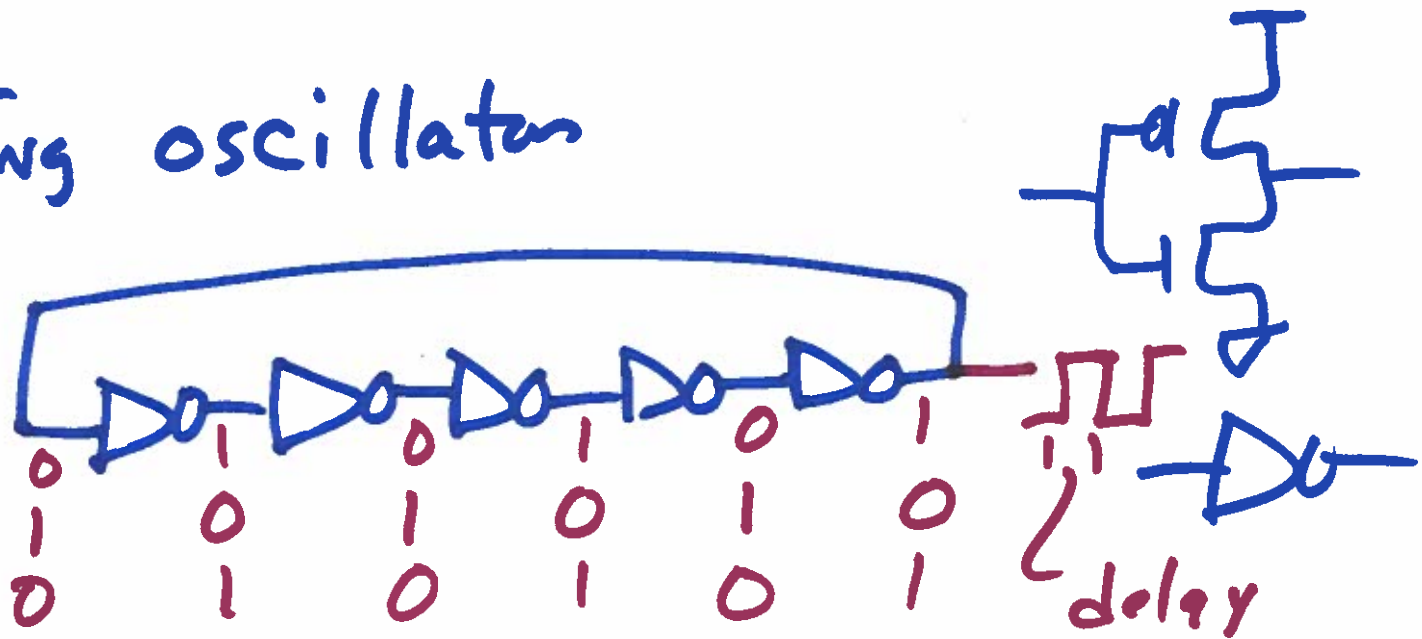

b)

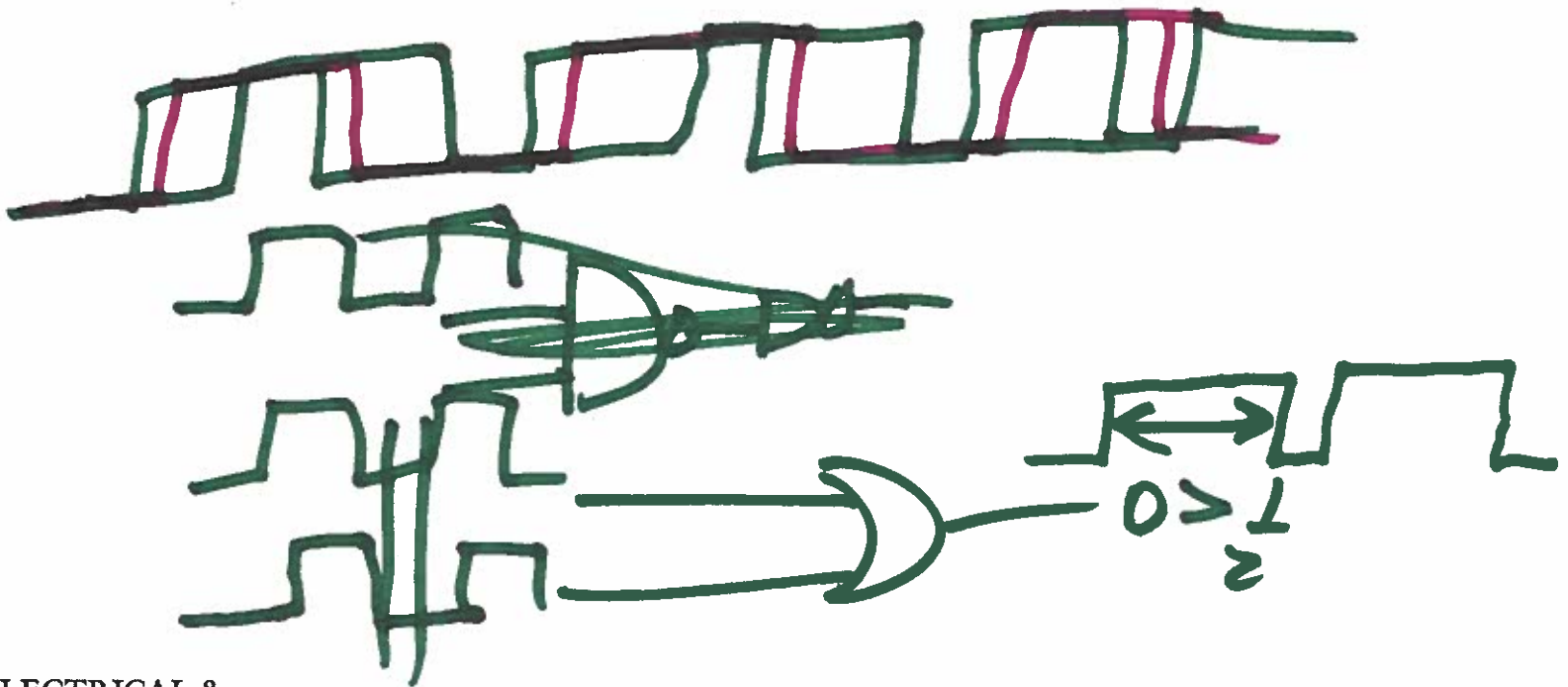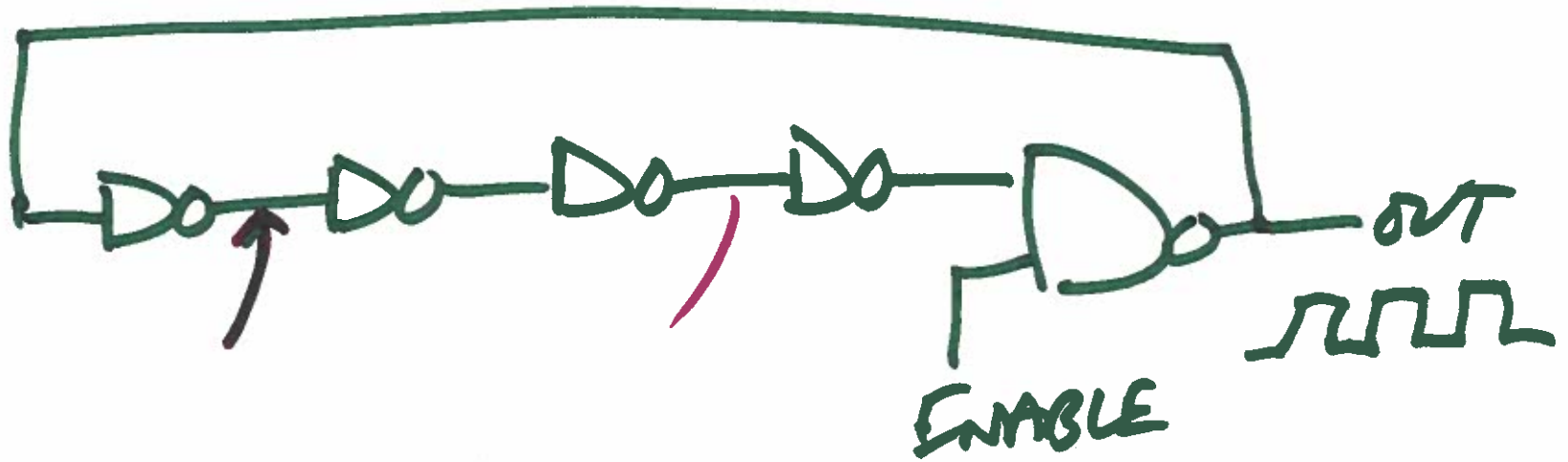

7)

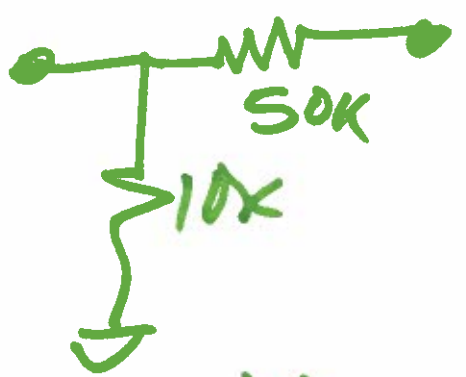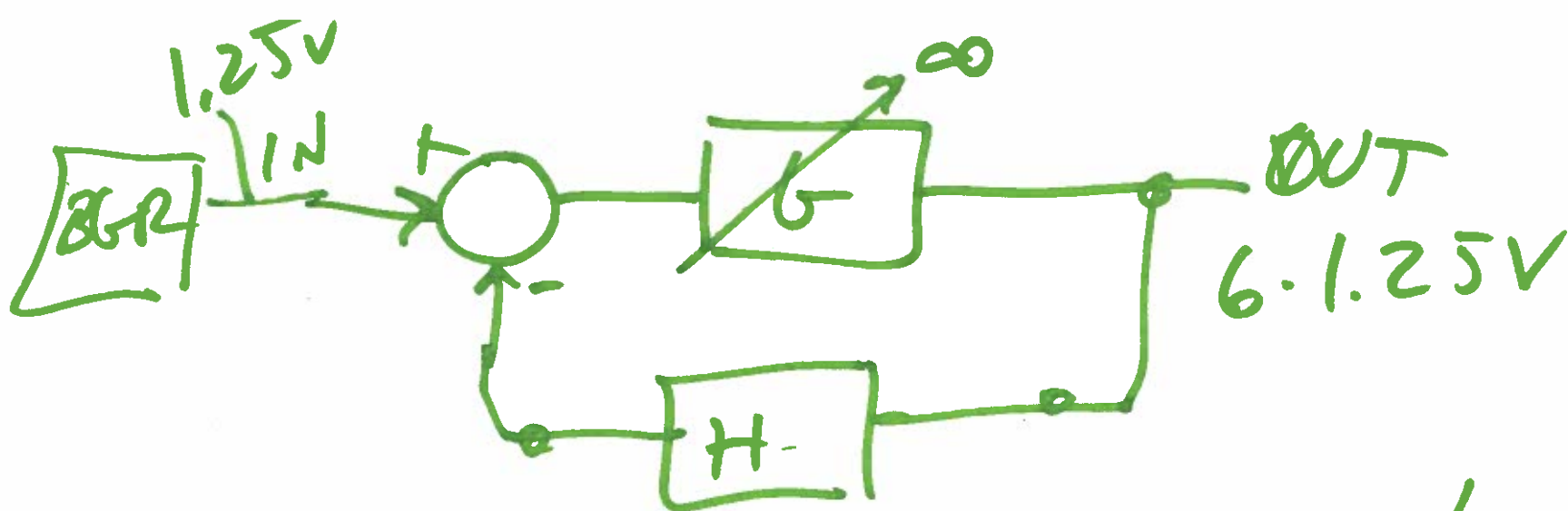

$$H = \frac{1}{6}$$

$$\begin{aligned} \frac{OUT}{IN} &= \frac{G}{1 + GH} \\ &= \frac{1}{\frac{1}{G} + H} \\ G \rightarrow \infty \\ &\approx \frac{1}{H} \\ &= 6 \end{aligned}$$

8)