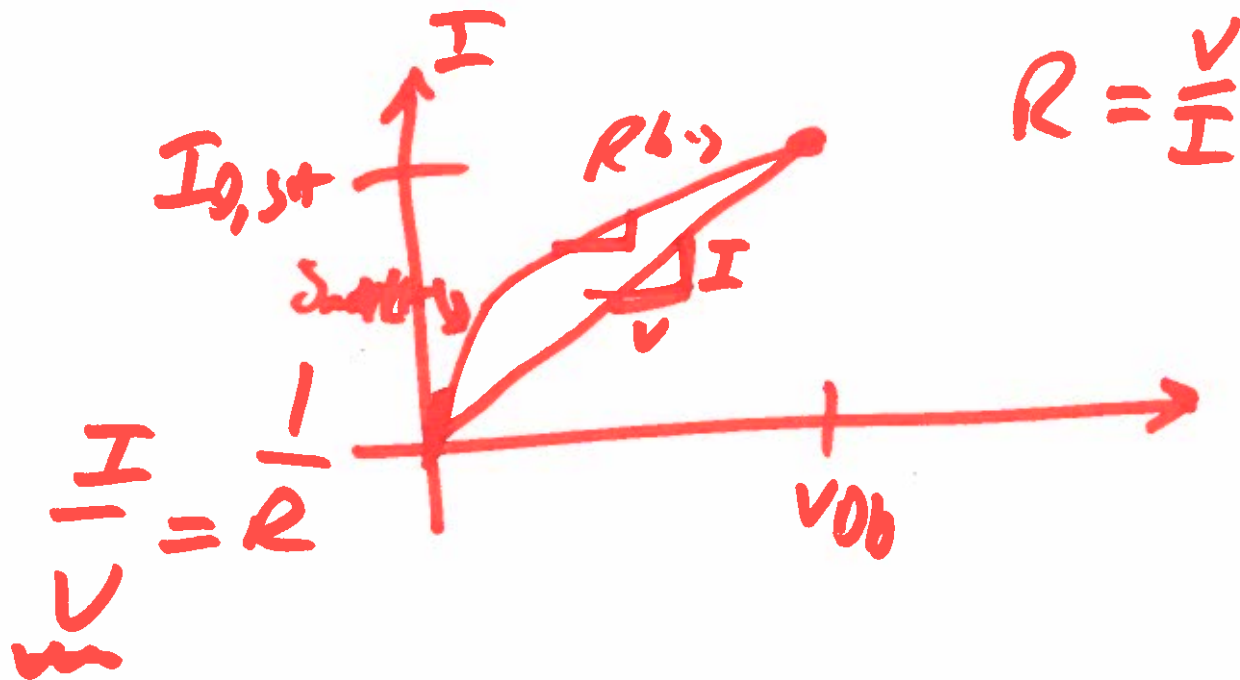


EE421 / ECG 621

Digital IC Design


Lecture 20

Nov. 6, 2019





Complex CMOS logic

$$z = AB + C$$

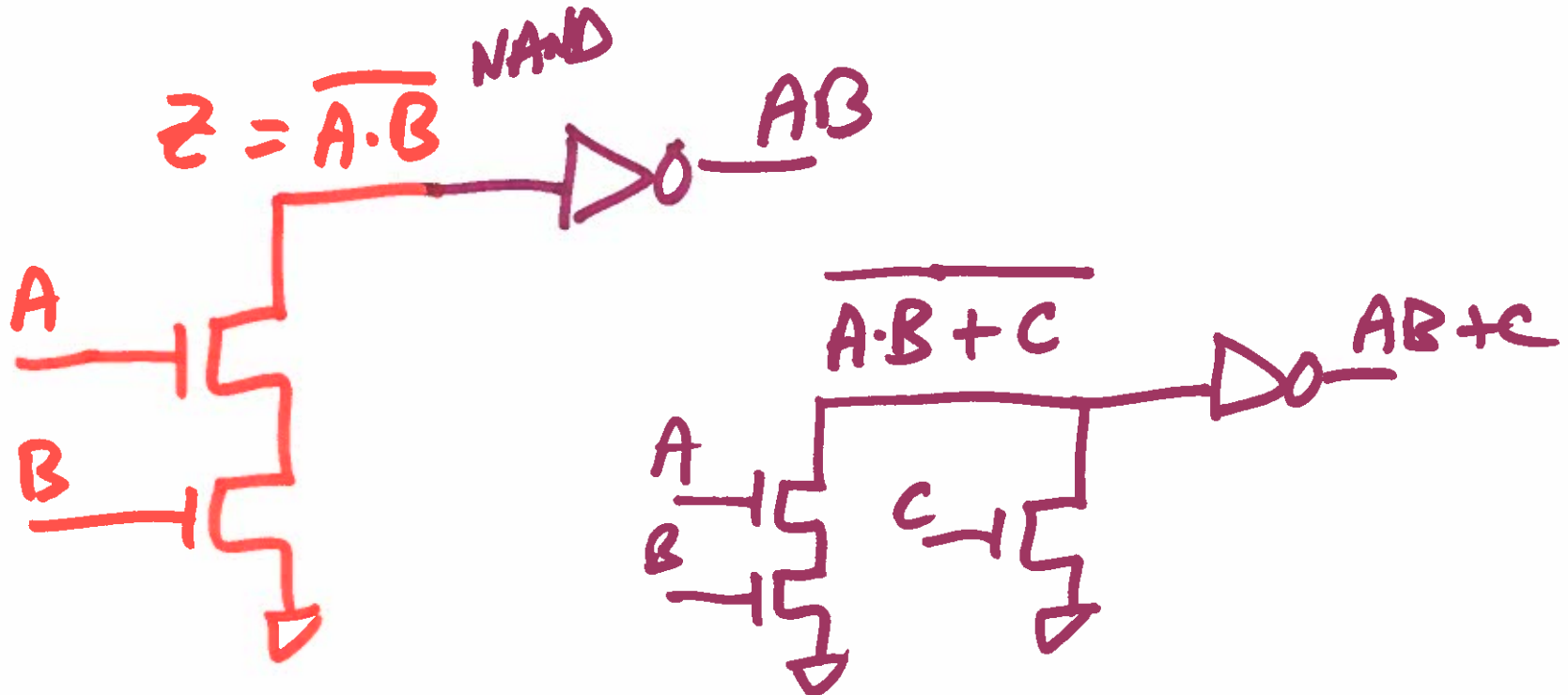


NAND

A	B	$A \text{ NAND } B$	$A \text{ AND } B$
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

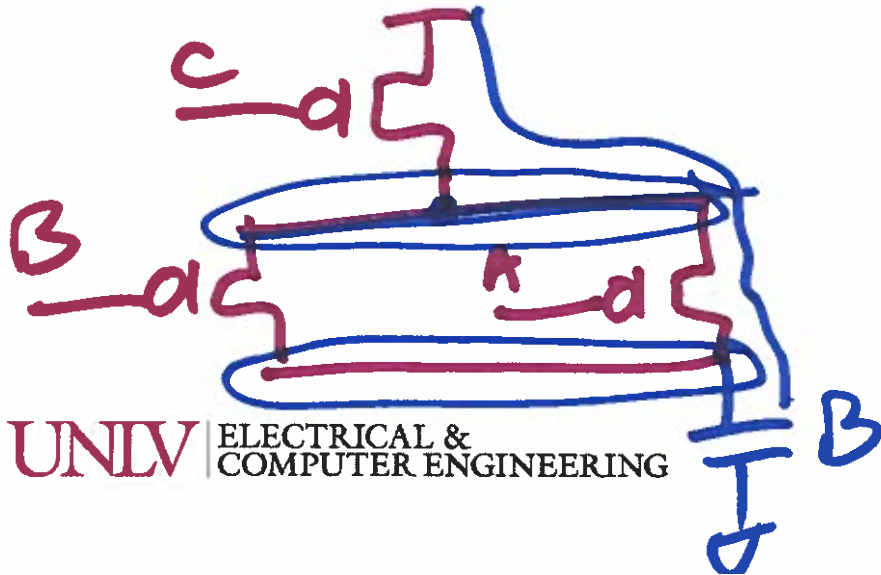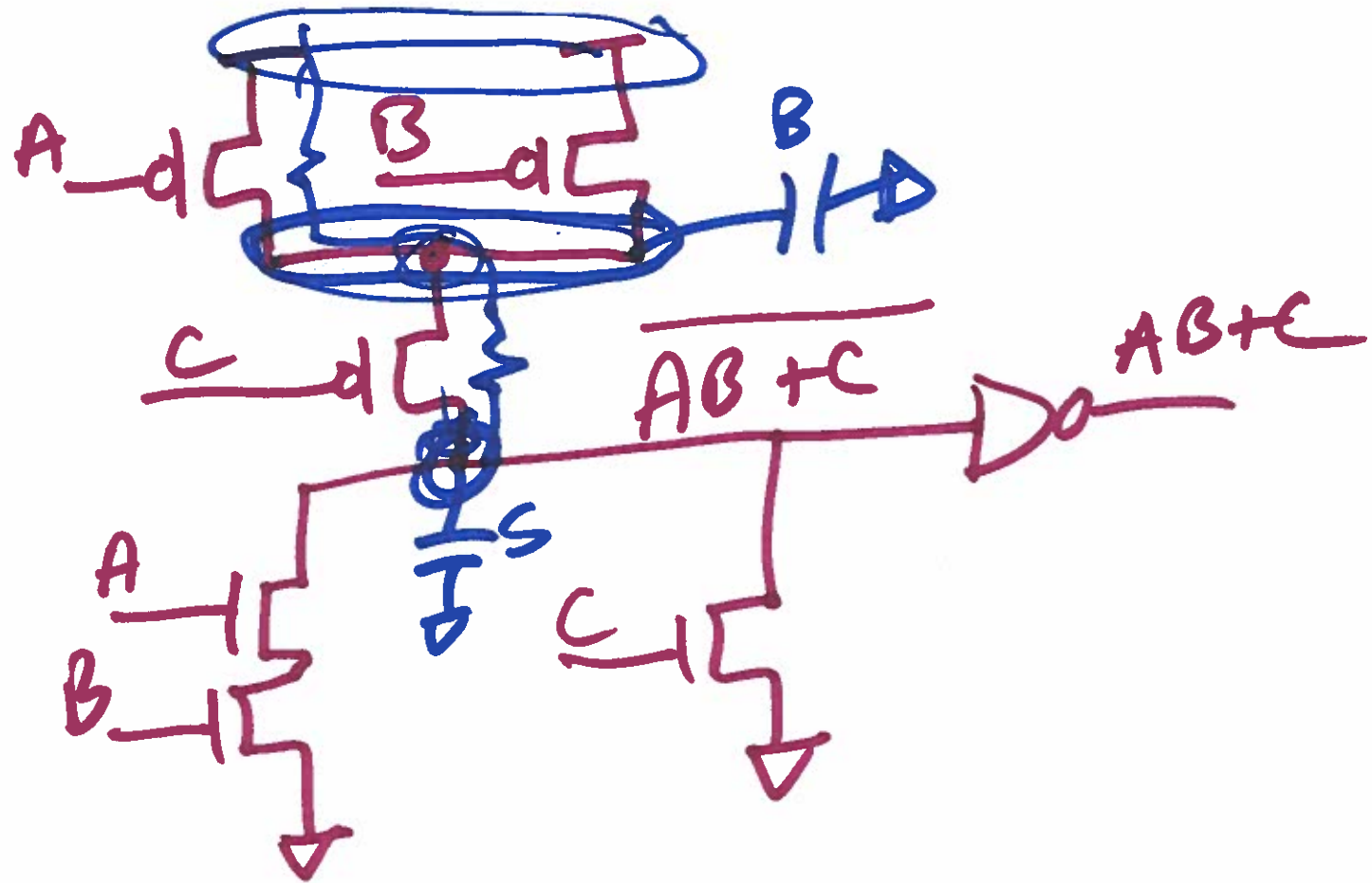

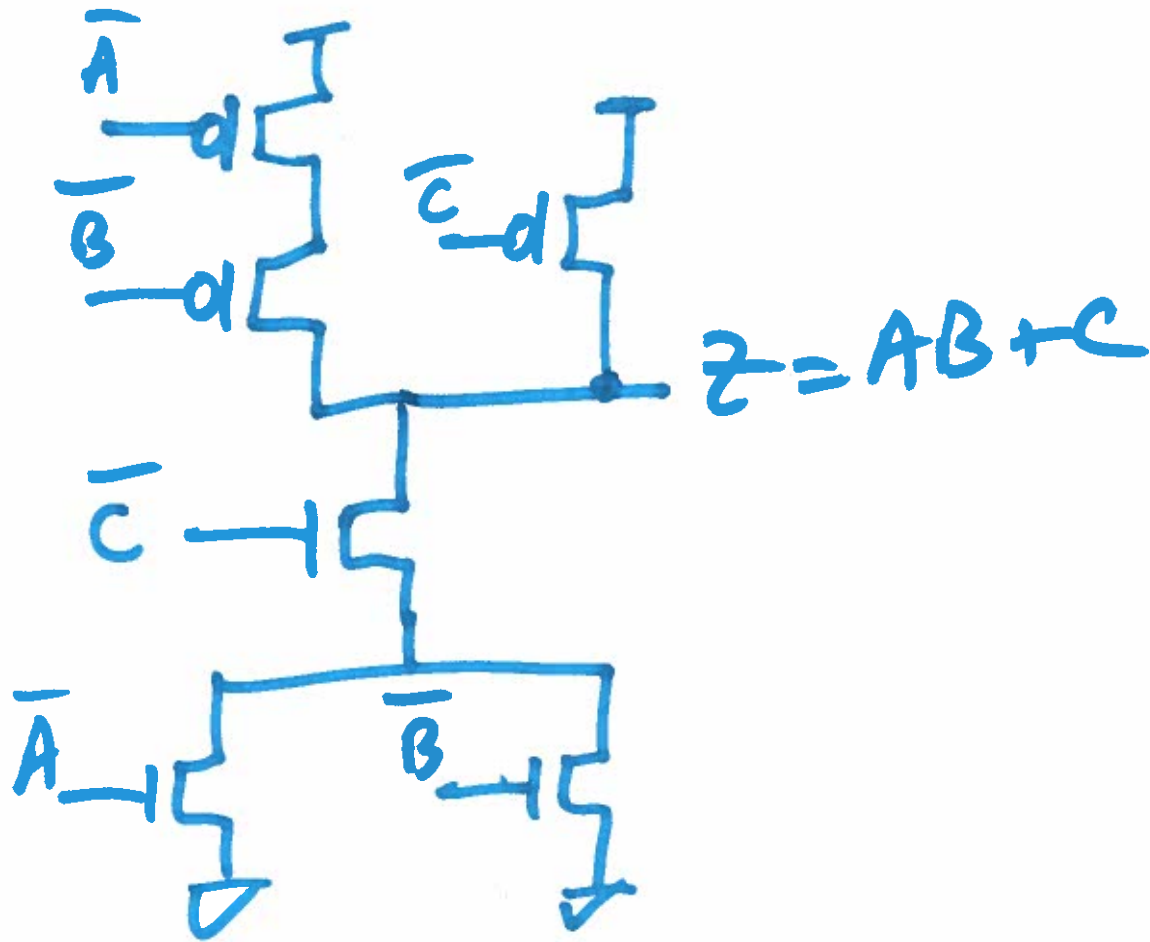
$$z = AB + C = \overline{(\overline{A+B}) \cdot \overline{C}}$$




$$z = \bar{A}B + A\bar{B}$$

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

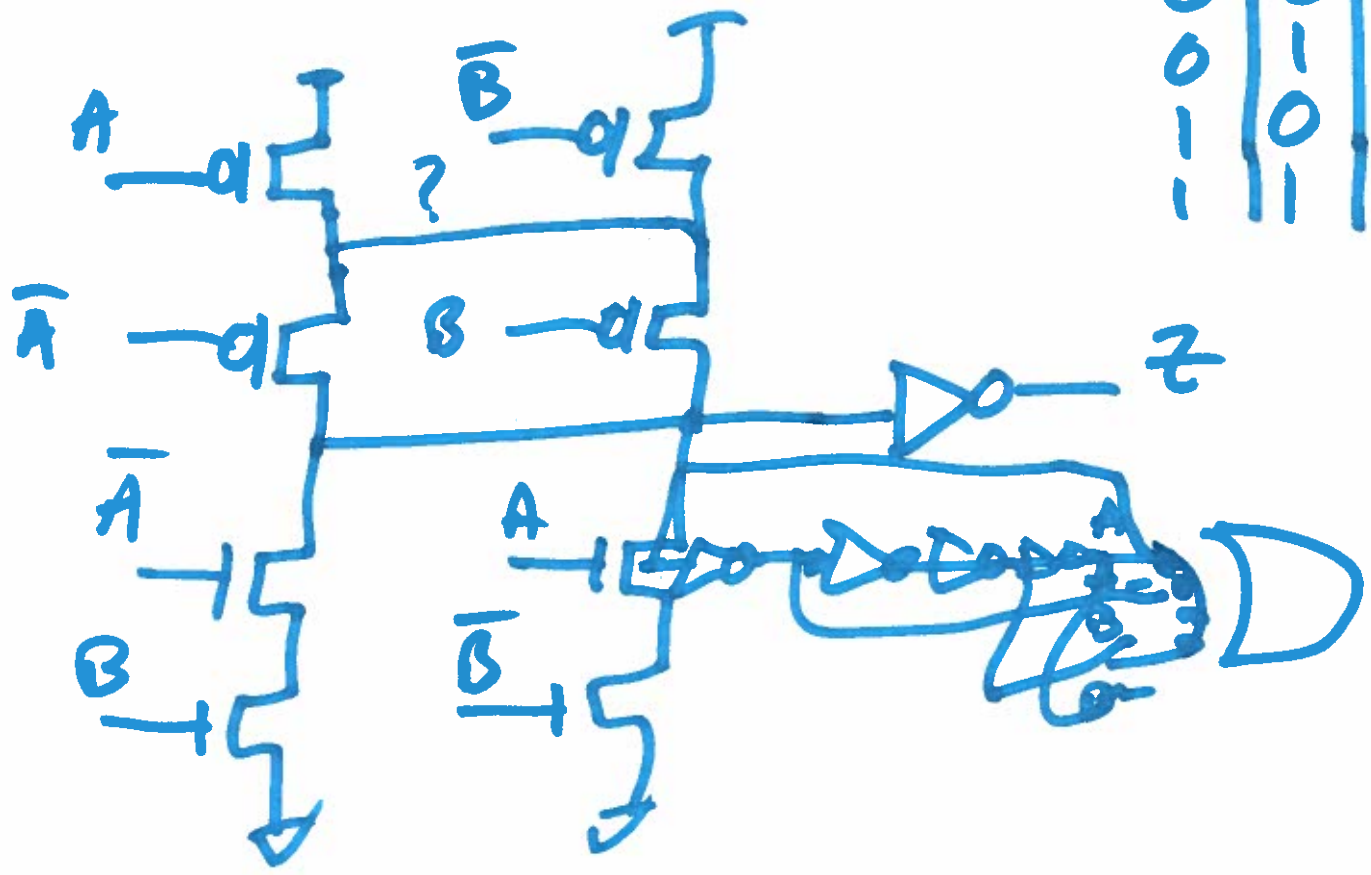

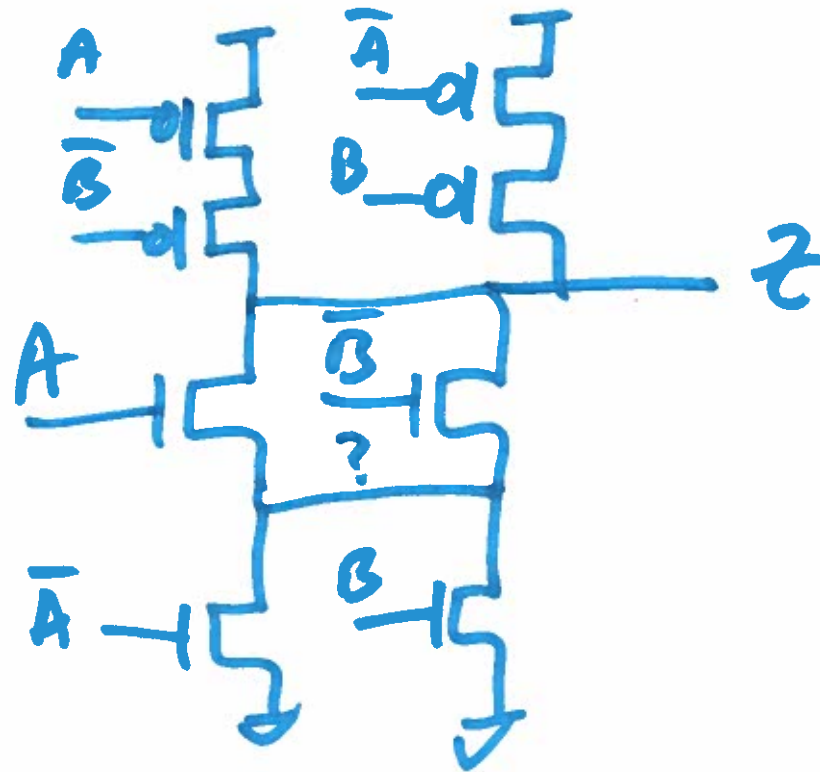
4)

$$z = \bar{A}B + A\bar{B} = \overline{(A+B)(\bar{A}+\bar{B})}$$





$$z = \bar{A}BC + CD + \bar{A}BCA$$

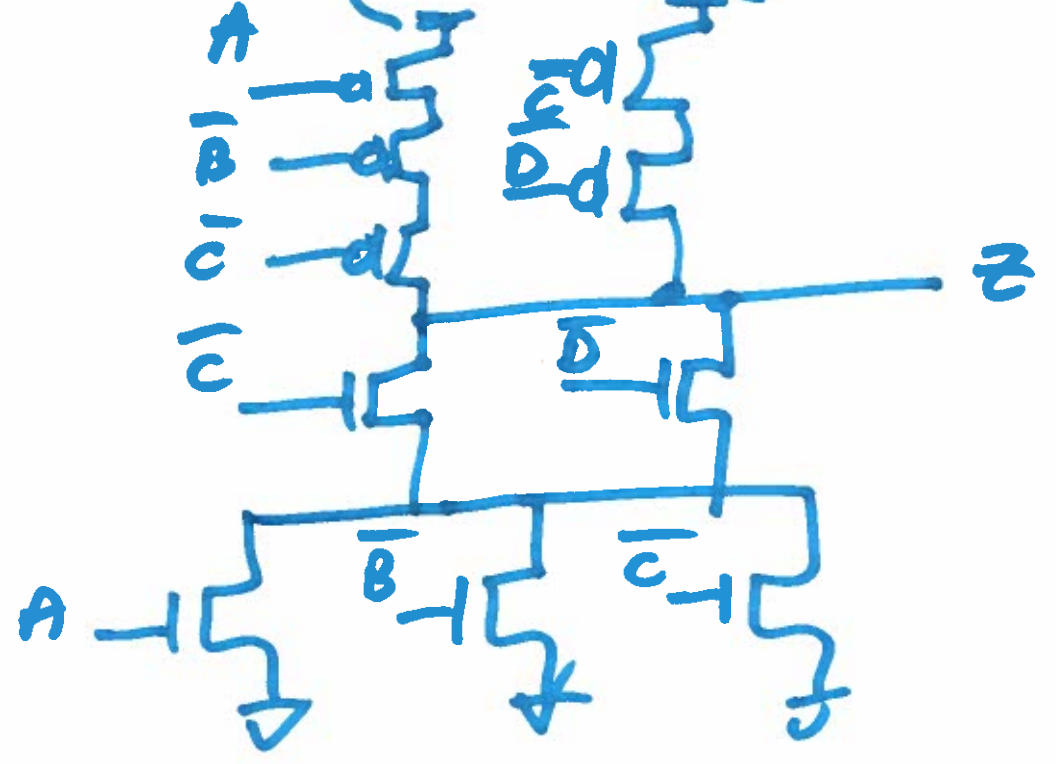
$$= (A + \bar{B} + \bar{C})(\bar{C} + D)$$



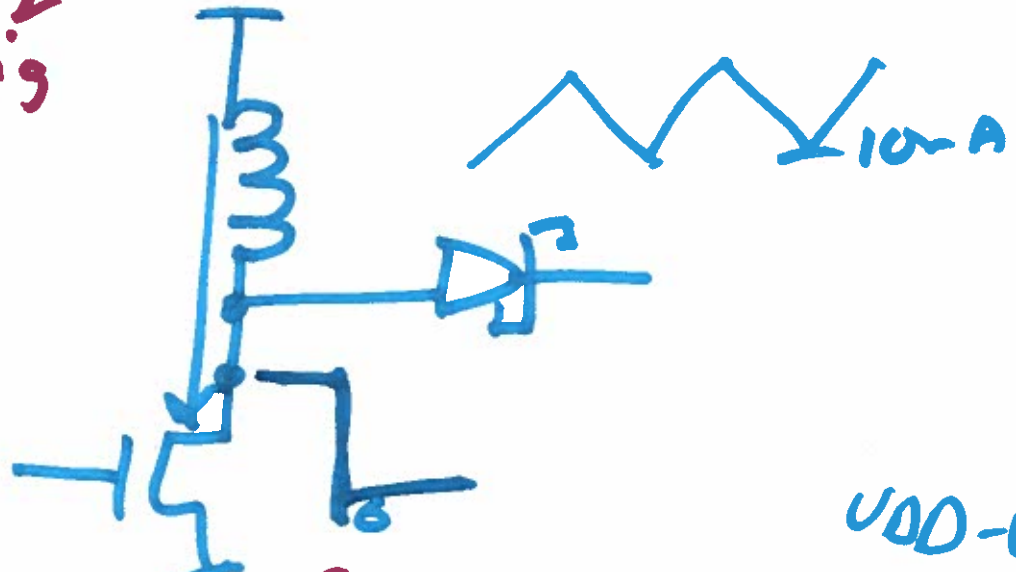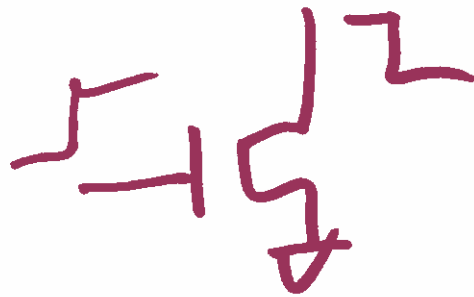
$$\frac{l(l+1)}{2} \approx \frac{l^2}{2} \quad \text{big}$$


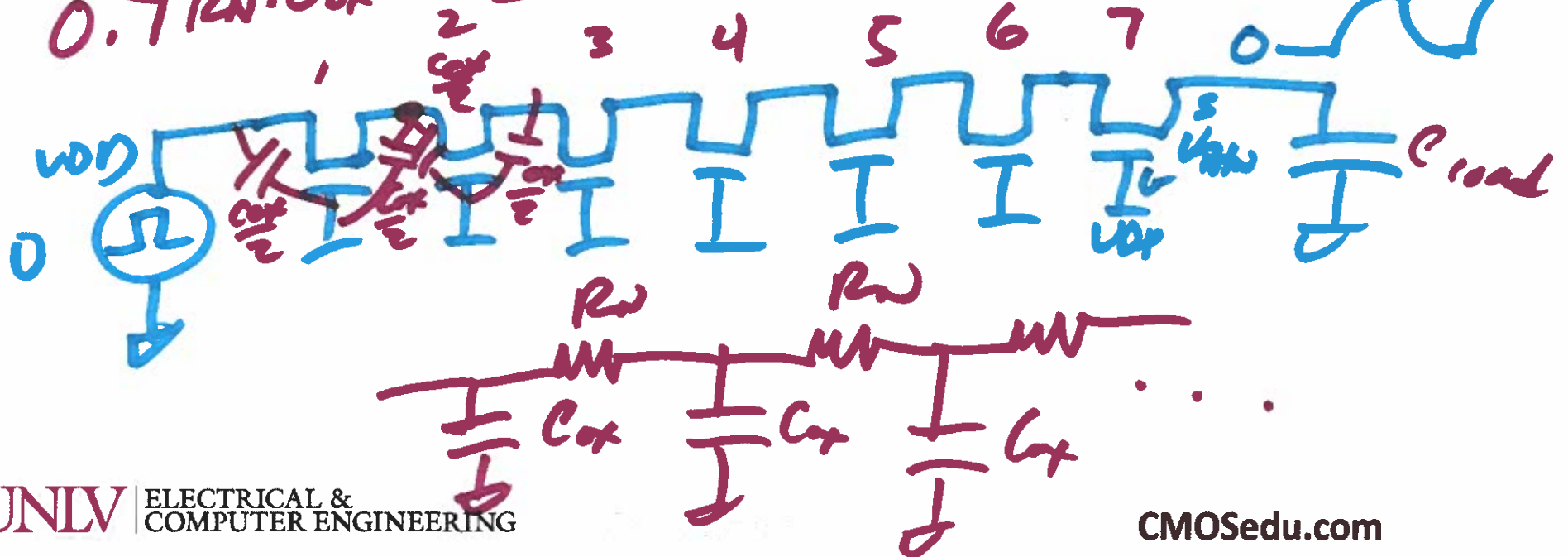
$$t_{PHL} = t_{PLH} = 0.7 R_N \cdot C_{ox} \cdot \frac{7(7+1)}{2} + 7 R_N \cdot C_{load}$$



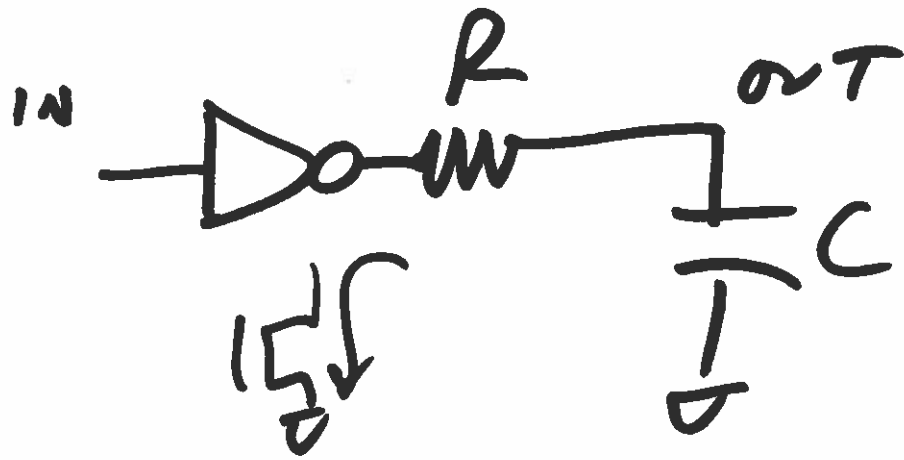

$$t_{PHL} = 0.7(R + R_w) \cdot C + R_w \cdot (C_{cp} + C_{cn})$$

$$t_{PLH} = 0.7(R + R_p) \cdot C + R_p \cdot (C_{cp} + C_{cn})$$

$$C_{cn} = C_{ox}' \cdot W_N L_N$$

$$C_{cp} = C_{ox}' \cdot W_p L_p$$