
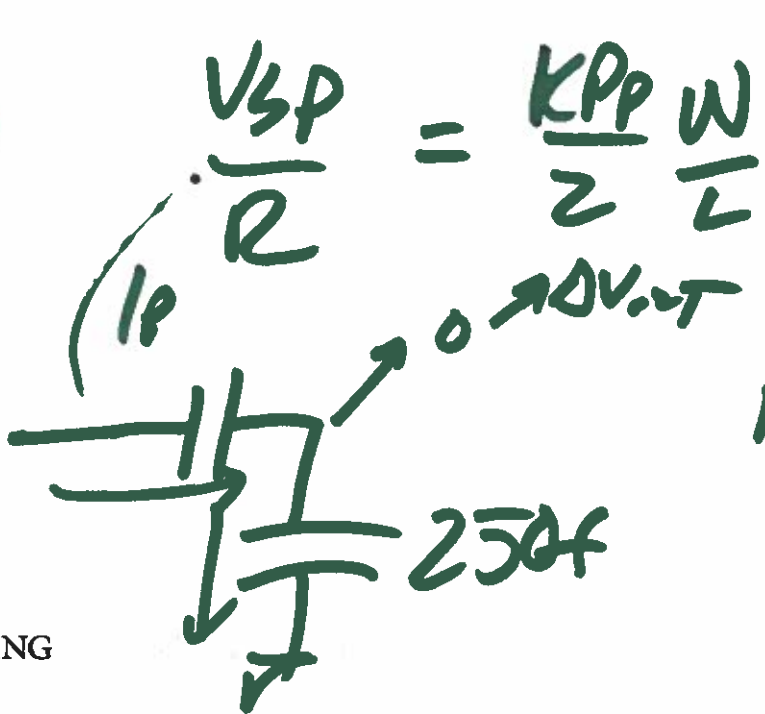


EE 421 / ECG 621

Digital IC Design


Dec. 4, 2019

Lecture 27

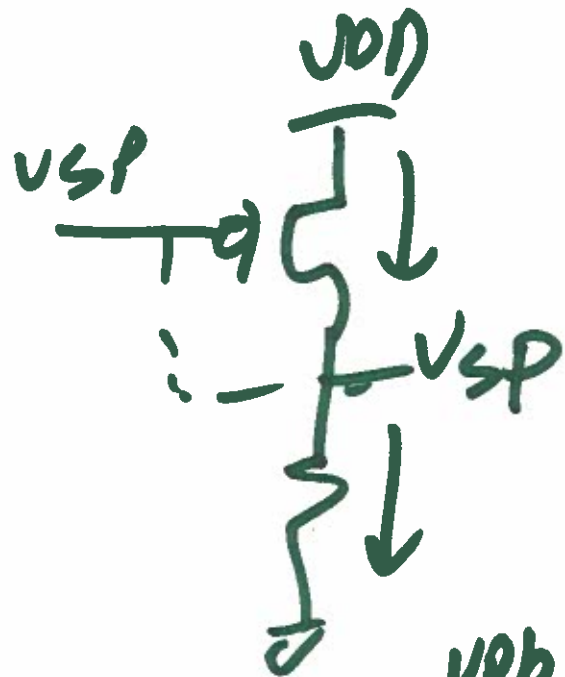

$$\frac{V_{SP}}{R} = \frac{K_{PP} W}{2 L} (V_{DD} - V_{SP} - V_{THP})^2$$
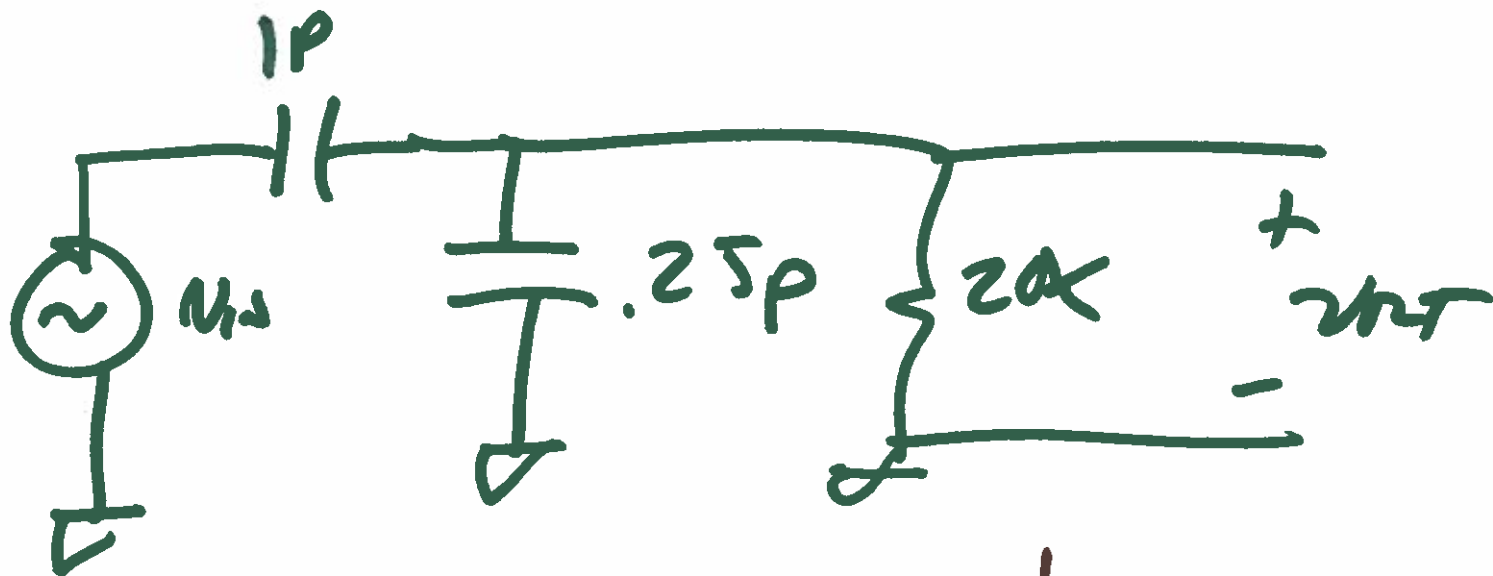
$$I_D \cdot (5 - \Delta V_{out}) = \Delta V_{out} \cdot 230fF$$



$$V_{out} = V_{in} \cdot \frac{20k \cdot \frac{1}{j \cdot 2\pi f \cdot 250f}}{20k + \frac{1}{j \cdot 2\pi f \cdot 250f}}$$

---


$$\left( \right) + \frac{1}{j \cdot 2\pi f \cdot 1pF}$$

$$\frac{1}{2} =$$

$$\frac{20K}{20K \cdot j \cdot 2\pi f \cdot 250pF + 1}$$

$$= \frac{20K}{1 + j 31.4N \cdot f}$$

$$\frac{1}{j \cdot 2\pi f \cdot 1pF} = \frac{j(-15.96)}{f}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{2} = \left( \frac{20K}{1 + j 31.4Nf} + j \left( \frac{-15.96}{f} \right) \right)$$

$$\frac{1}{2} = \left| \frac{20k}{20k + j\left(\frac{-15.96}{f}\right) + 500} \right|$$

$$\left| 20.5k + j\left(\frac{15.96}{f}\right) \right| = 40k$$

$$\sqrt{(20.5)^2 + \left(\frac{15.96}{f}\right)^2} = 40k$$

$$\left(\frac{15.96}{f}\right)^2 = 3.8$$


$$f = 8.156 \pm 12$$

$$CV = Q$$

$$100\mu\text{A} \cdot 100\text{ps} = Q$$

$$I_{\text{avg}} = \frac{Q}{10\text{ns}}$$

100ps

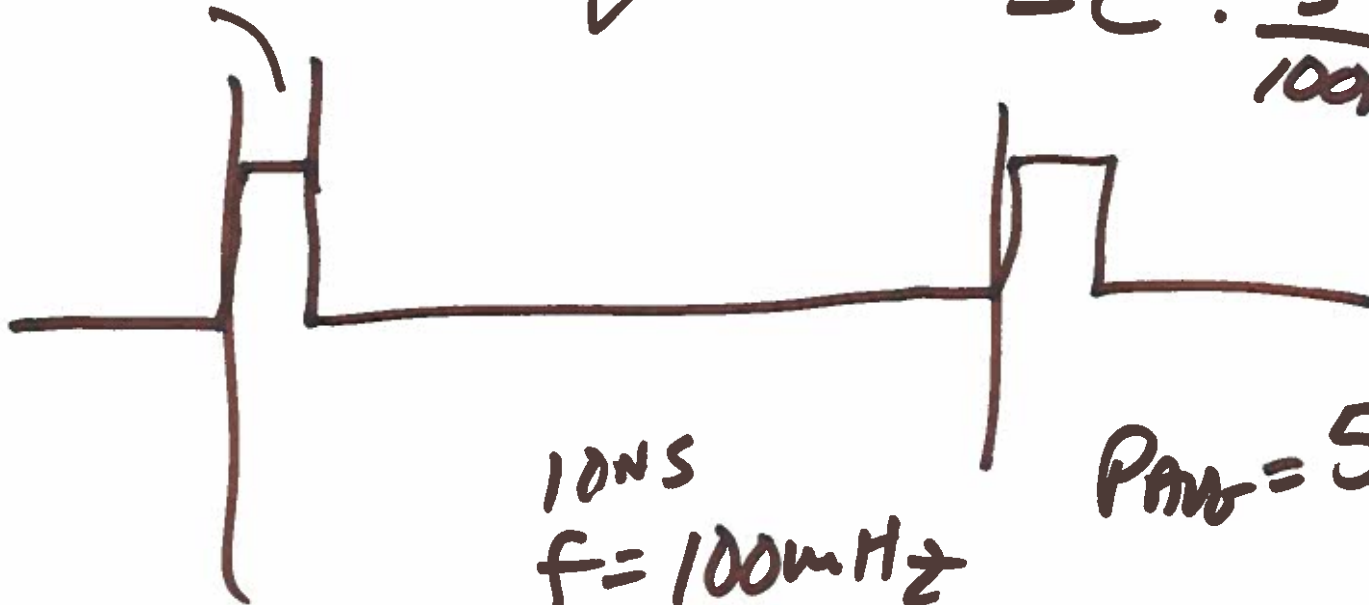


$$I = C \frac{dV}{dt}$$

$$100\mu\text{A} = C \cdot \frac{5}{100\text{ps}}$$

10ns  
 $f = 100\text{MHz}$
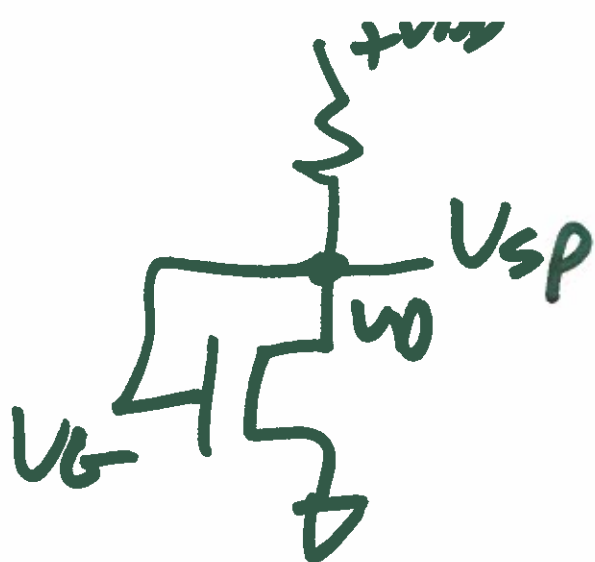
$$P_{\text{avg}} = 5\text{V} \cdot \frac{100\mu\text{A} \cdot 100\text{ps}}{10\text{ns}}$$



$$V_{GS} \geq V_{THN}$$

$$V_{DS} \geq V_{GS} - V_{THN}$$

$$V_{D-ys} \geq V_G - V_S - V_{THN}$$

$$V_D \geq V_G - V_{THN}$$

$$0 \geq -V_{THN}$$

YES ALWAYS

