 


# EE 421 / ECG 621



## Digital IC Design
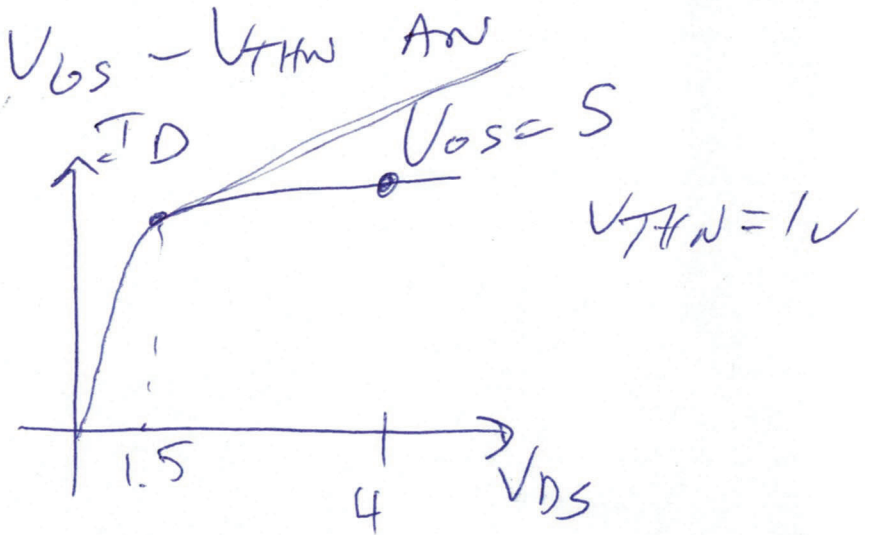 
### Lecture 13

OCT. 7, 2020



Why is  $V_{DS,SAT} = V_{GS} - V_{THN}$  an overestimate?





Practice Midterm Exam – EE 421 Digital Electronics and ECG 621 Digital IC Design  
 Fall – University of Nevada, Las Vegas

NAME: \_\_\_\_\_

Open book, closed notes.

Show your work for credit. When possible place boxes around your answers.

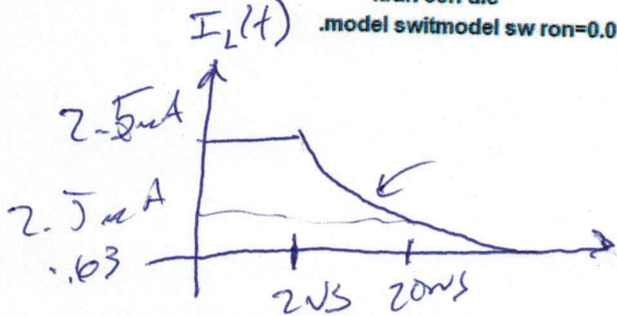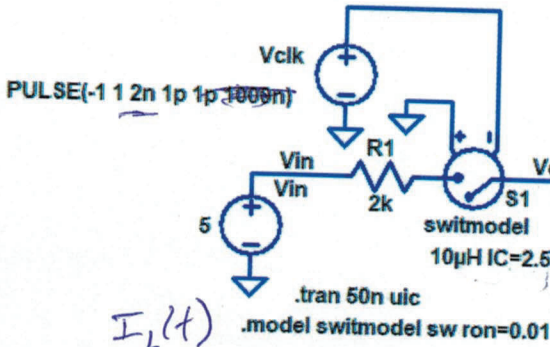
1. Plot the current through the inductor in the following circuit. (10 points)



$$\tau = \frac{L}{R} = \frac{10\mu}{1k} = 10\text{ns}$$

$$I_L(t) = 2.5\mu A e^{-t/\tau}$$

$$t \geq 2\text{ns}$$

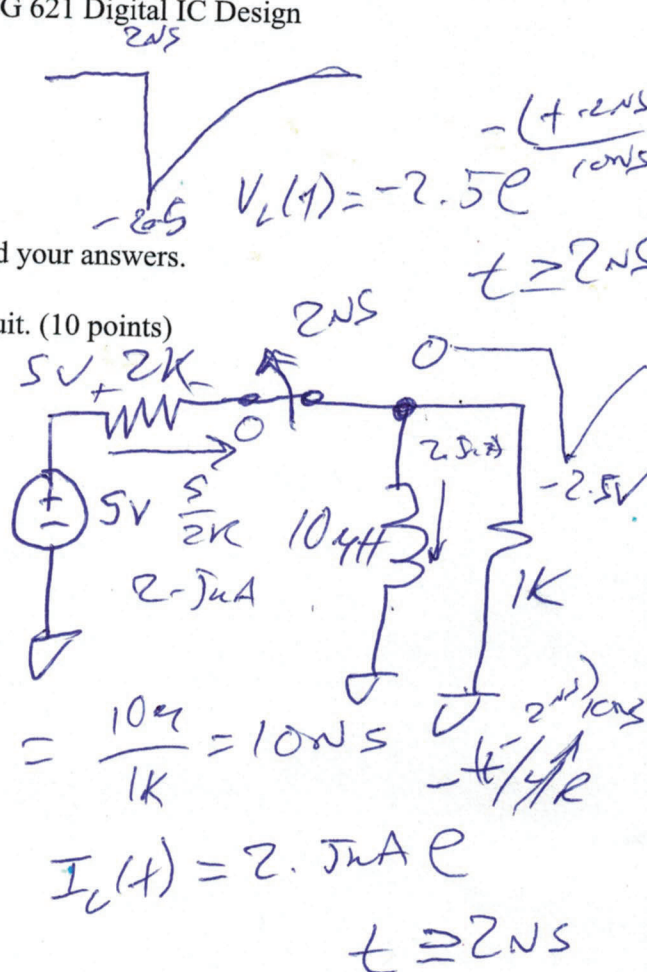

2. What key binding is used to descend and edit a cell in Cadence? (5 points)


shift - x

3. Estimate the delay through an n-well resistor having a sheet resistance of 1kohm/square and a zero-bias depletion capacitance of 100 fF/um<sup>2</sup>. Assume the resistor is 100 um long and 2 um wide. (5 points)


$$t_d = 0.35 \cdot \underbrace{1k \cdot \frac{100}{2}}_{R_{TOT}} \cdot \underbrace{\frac{100 \text{ fF}}{\text{um}^2} \cdot (100 \text{ um} \times 2 \text{ um})}_{C_{TOT}}$$

2)

 4. Explain in your own words why depletion capacitance of a pn junction decreases with increasing reverse bias. Use a cross-sectional view of a pn junction showing the depletion region's width in your explanation. Also show a plot of the depletion capacitance against reverse bias. Do not use equations in your explanation. (15 points)



 
depletion region (depleted of free carriers, holes move to p leaving behind  $\ominus$  charge causing n-side to have  $\oplus$  charge)



Attract electrons, which in direction shown which cause  $w \rightarrow$

$C \downarrow$

 5. Work problem 3.5 on page 80. (10 points)




CONTACT  $R = 10 \Omega$

contact resistance  
=  $5 \Omega$

3)



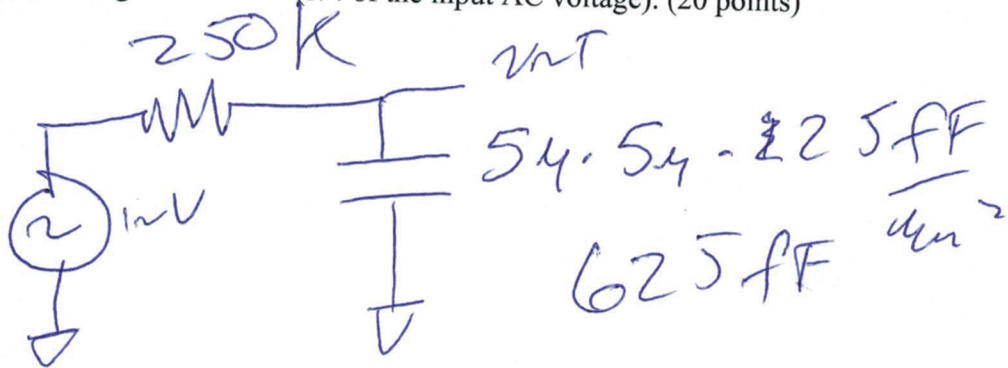6. For problem 6.1 on page 162 determine the frequency when the AC component of the output voltage is 0.75 mV (3/4 of the input AC voltage). (20 points)



$$0.75 = 1 \cdot \frac{1}{j \cdot 2\pi f \cdot 625 \text{ f}}$$

$$\frac{1}{j \cdot 2\pi f \cdot 625 \text{ f}} + 250 \text{ k}$$

$$0.75 = \frac{1}{1 + j \cdot 2\pi f \cdot 625 \text{ f} \cdot 250 \text{ k}}$$

$$.5625 = \frac{1}{1 + (f \cdot 981 \text{ n})^2} \sqrt{1 + (f \cdot 981 \text{ n})^2}$$

$$.5625 (f \cdot 981 \text{ n})^2 = 0.4375$$



$$f^2 (981 \text{ n})^2 = 0.777$$

$$f \cdot 981 \text{ n} = .88$$

$$f = 899 \text{ MHz}$$

4)

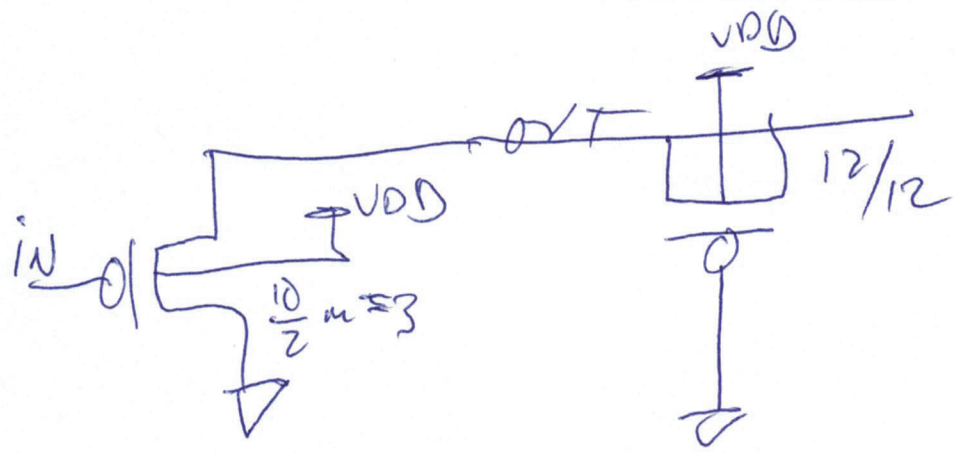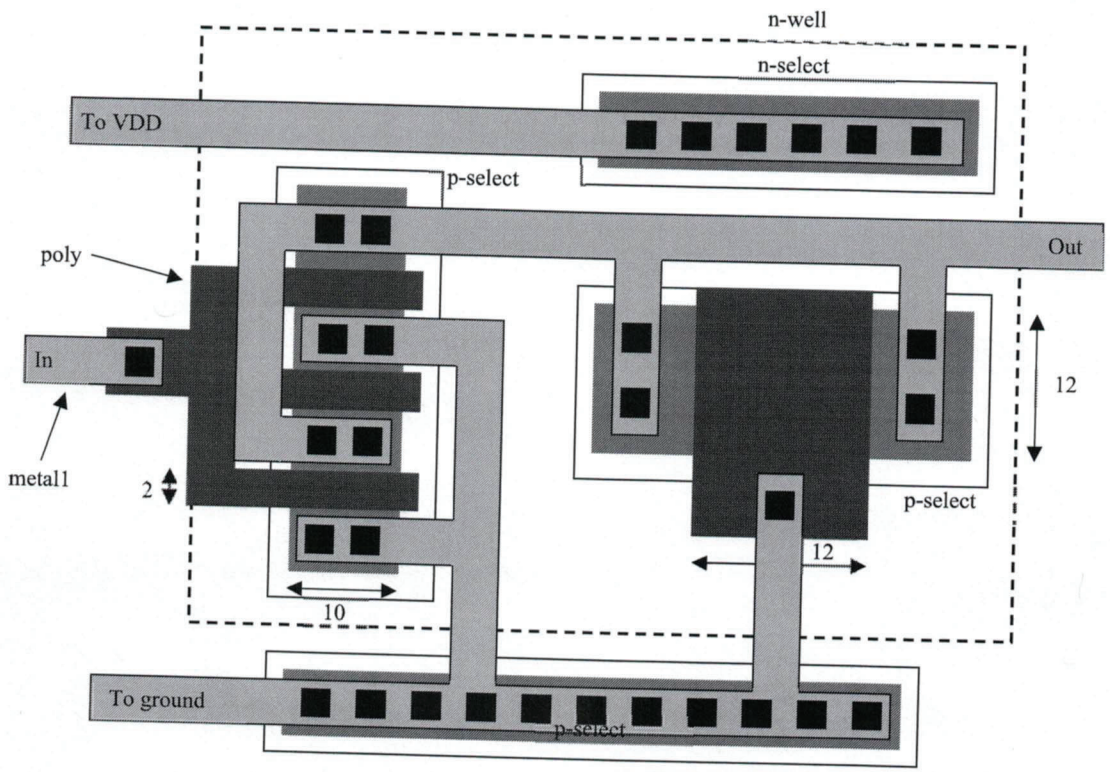
7. Sketch the corresponding schematic for the following layout. Make sure the body connections of the MOSFETs are clearly seen in your schematic. (15 points)



5)

8. Sketch the layout of a 30k poly2 resistor in the C5 process using the hires layer assuming the sheet resistance is 1k/square. Make sure to label each of the layers in your layout. Sketch the cross-sectional view of your layout. Explain what the hires layer does during the fabrication process. (20 points)

hi-res blocks poly2 from being doped

 

b)