

$$\frac{C \cdot A}{t} = C \cdot E \cdot F \cdot 421 / E \cdot L \cdot G \cdot 621$$


mbit<sub>cell</sub>

# Digital IC Design


ASIC


NOV. 25, 2020

## Lecture 25

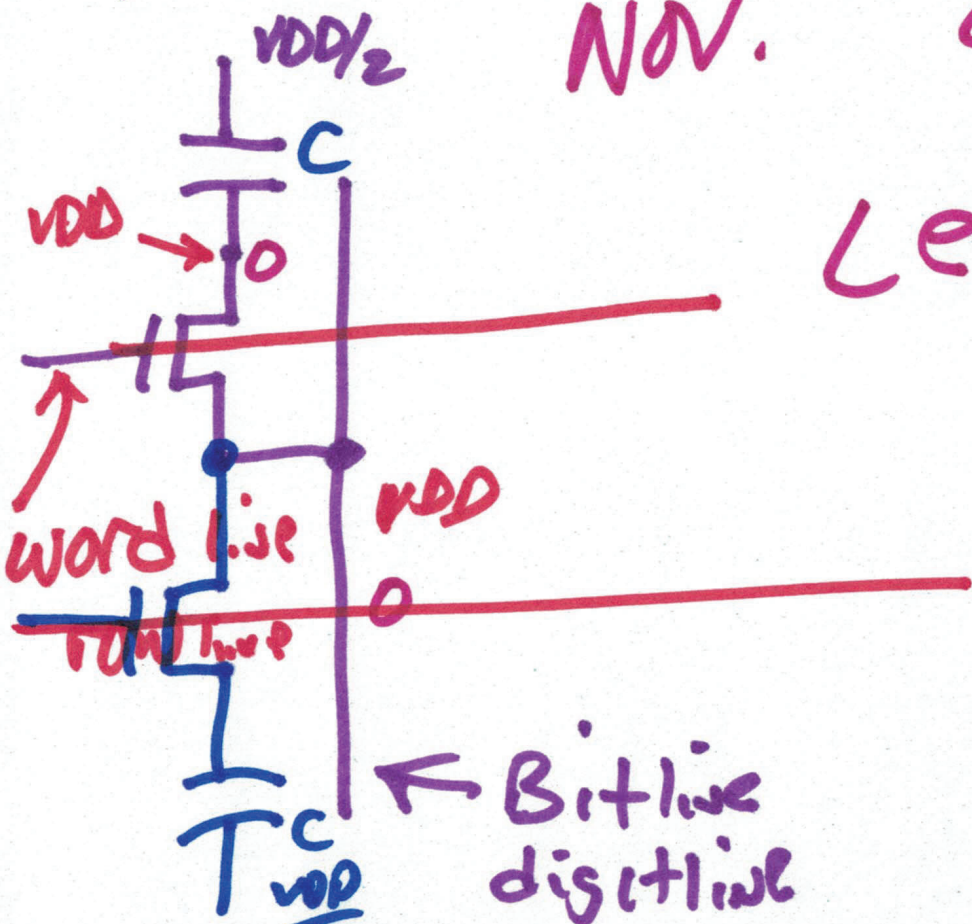

Bit line  
digit line

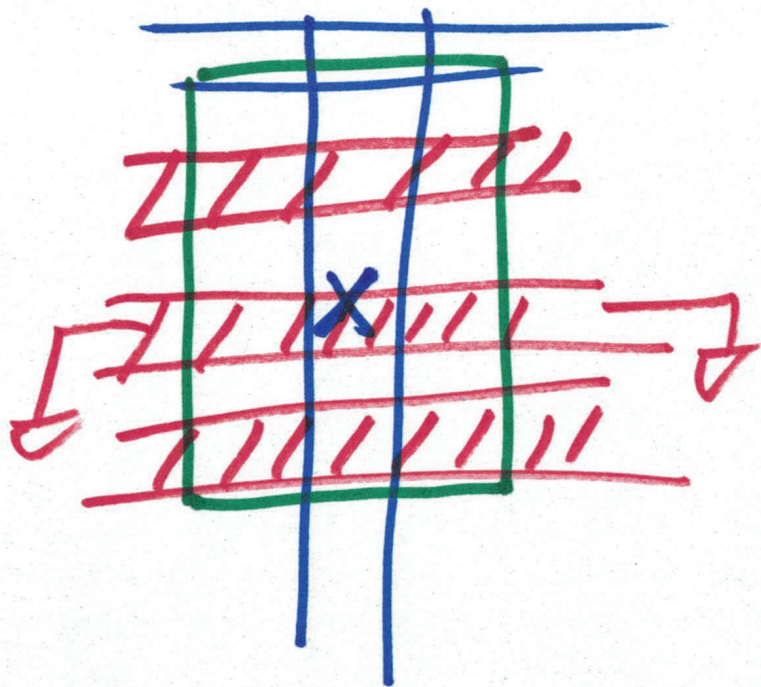


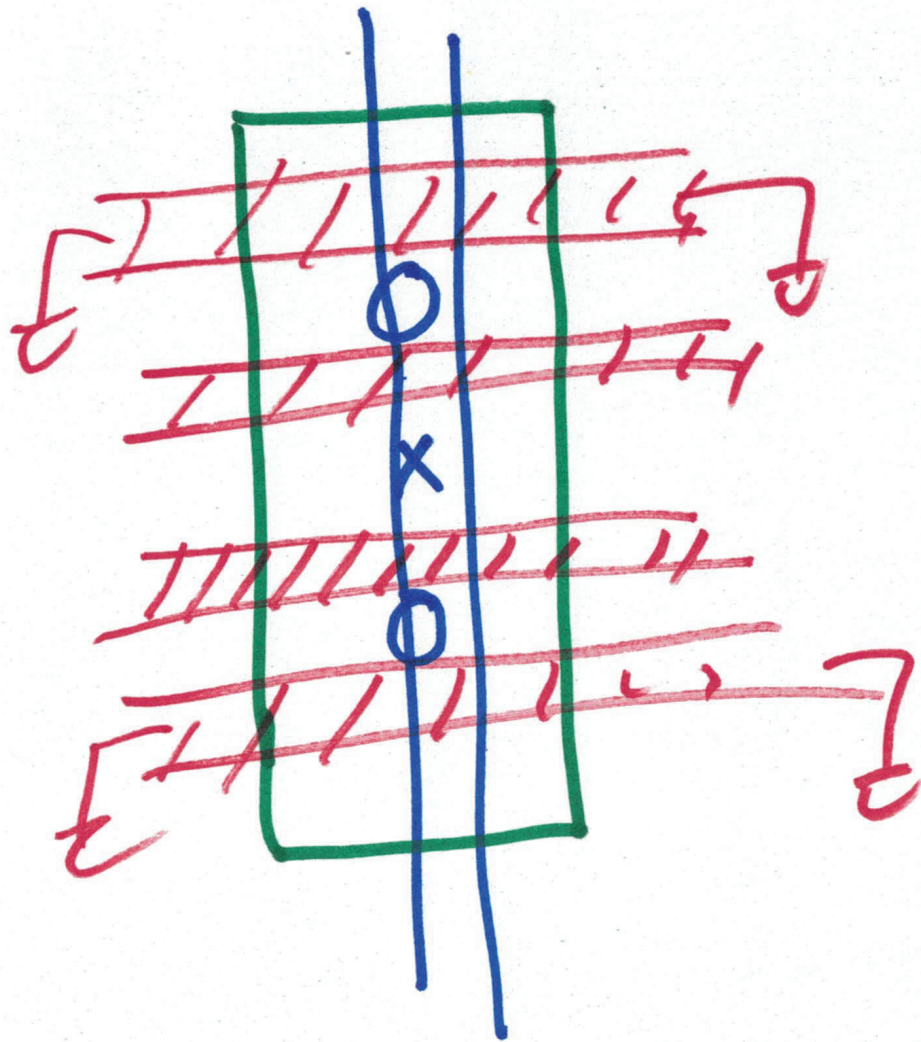

256 x 256  
64k bits

4Gb

2)

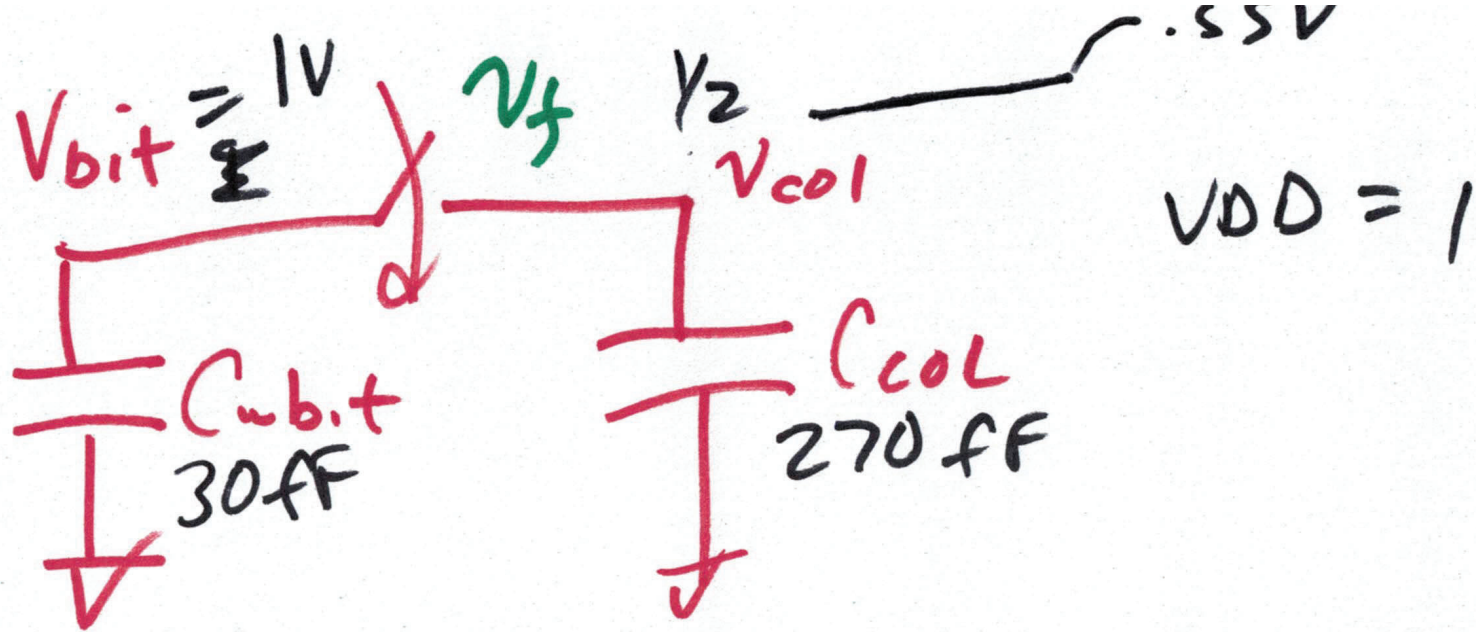



$$V_{bit} \cdot C_{bit} + V_{col} \cdot C_{col} = V_f \cdot (C_{bit} + C_{col})$$

$$V_f = \frac{V_{bit} \cdot C_{bit} + V_{col} \cdot C_{col}}{C_{bit} + C_{col}}$$



$$0.55 = \frac{1 \cdot 30 fF + \frac{1}{2} \cdot 270 fF}{30 fF + 270 fF}$$

$$V_f = \frac{165}{300} = 0.55$$


3)

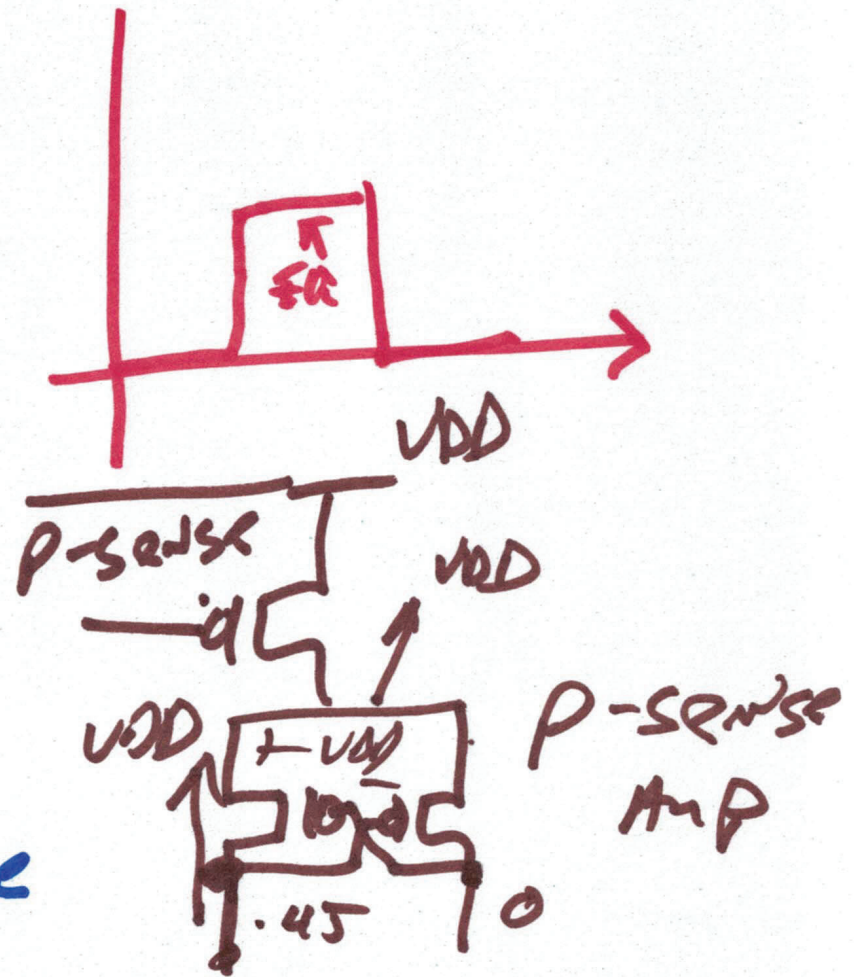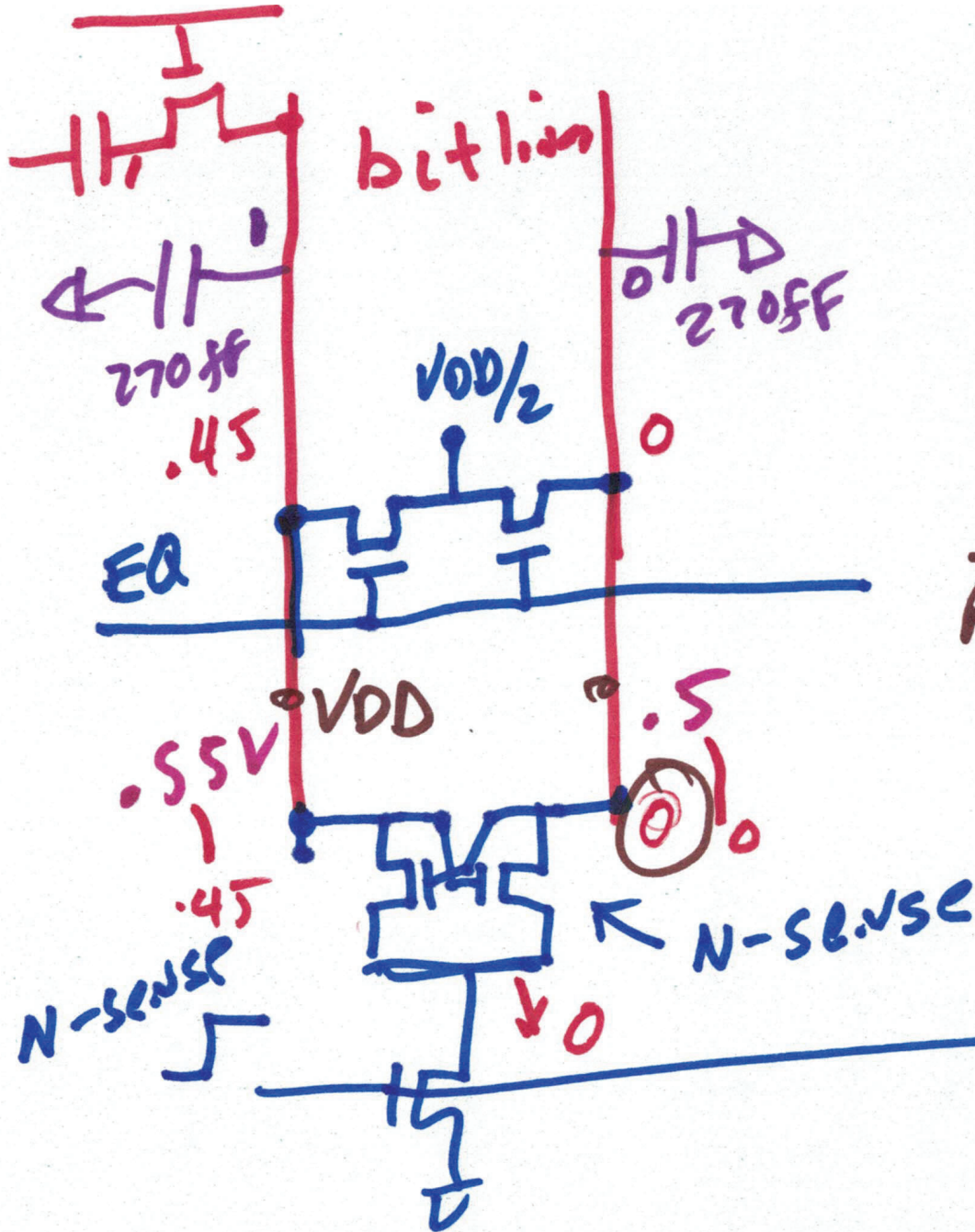

4)

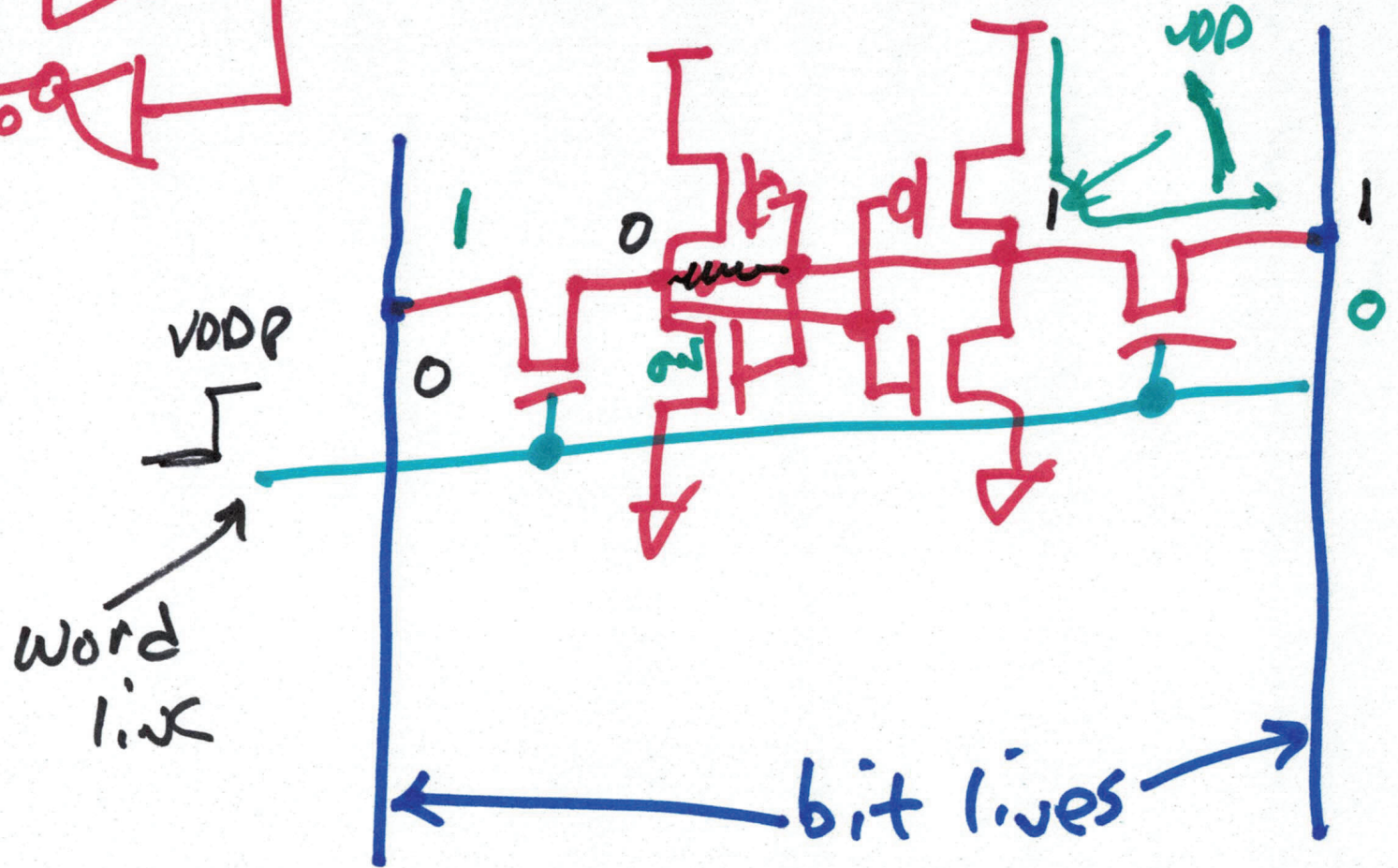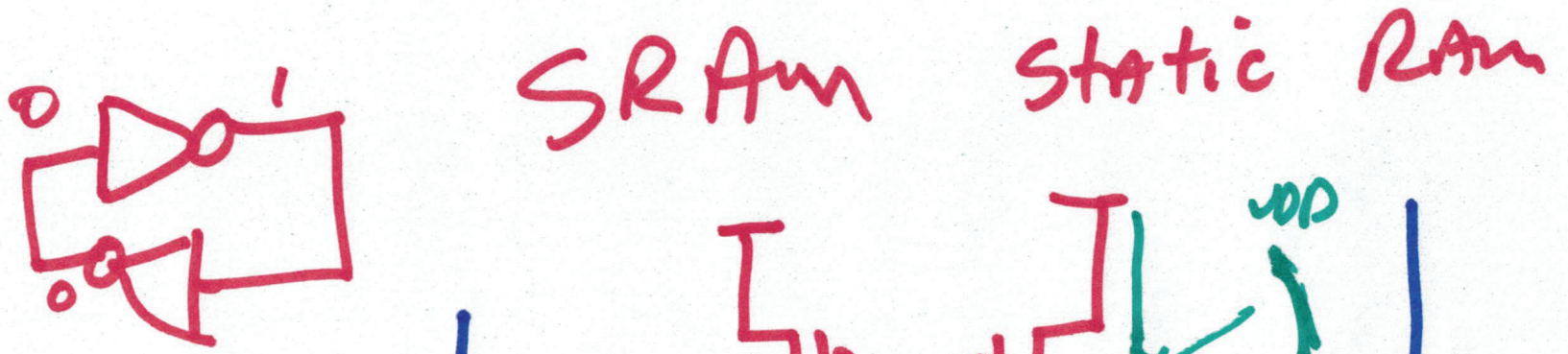


6T SRAM

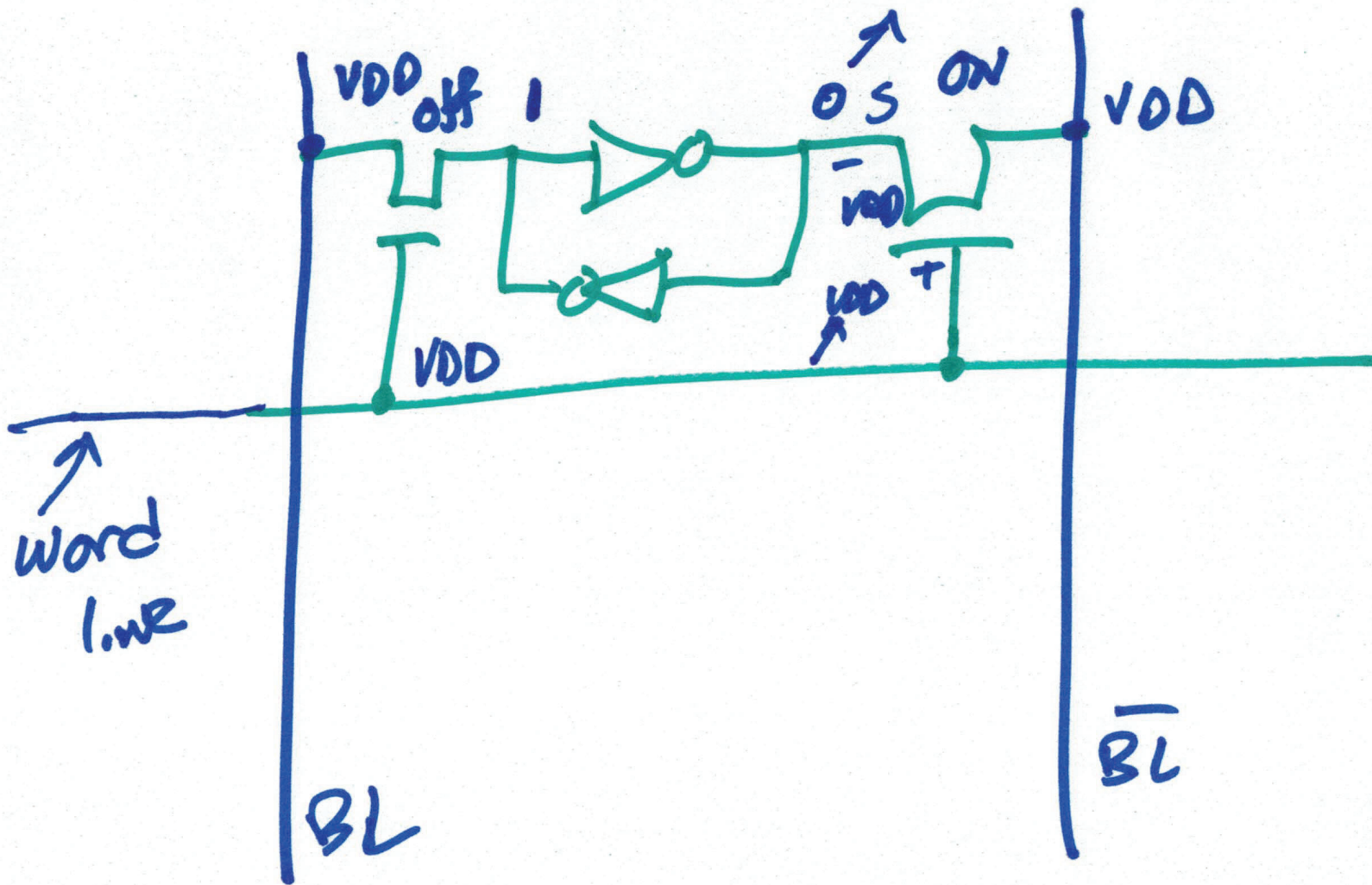

6)

# Chalcogenides

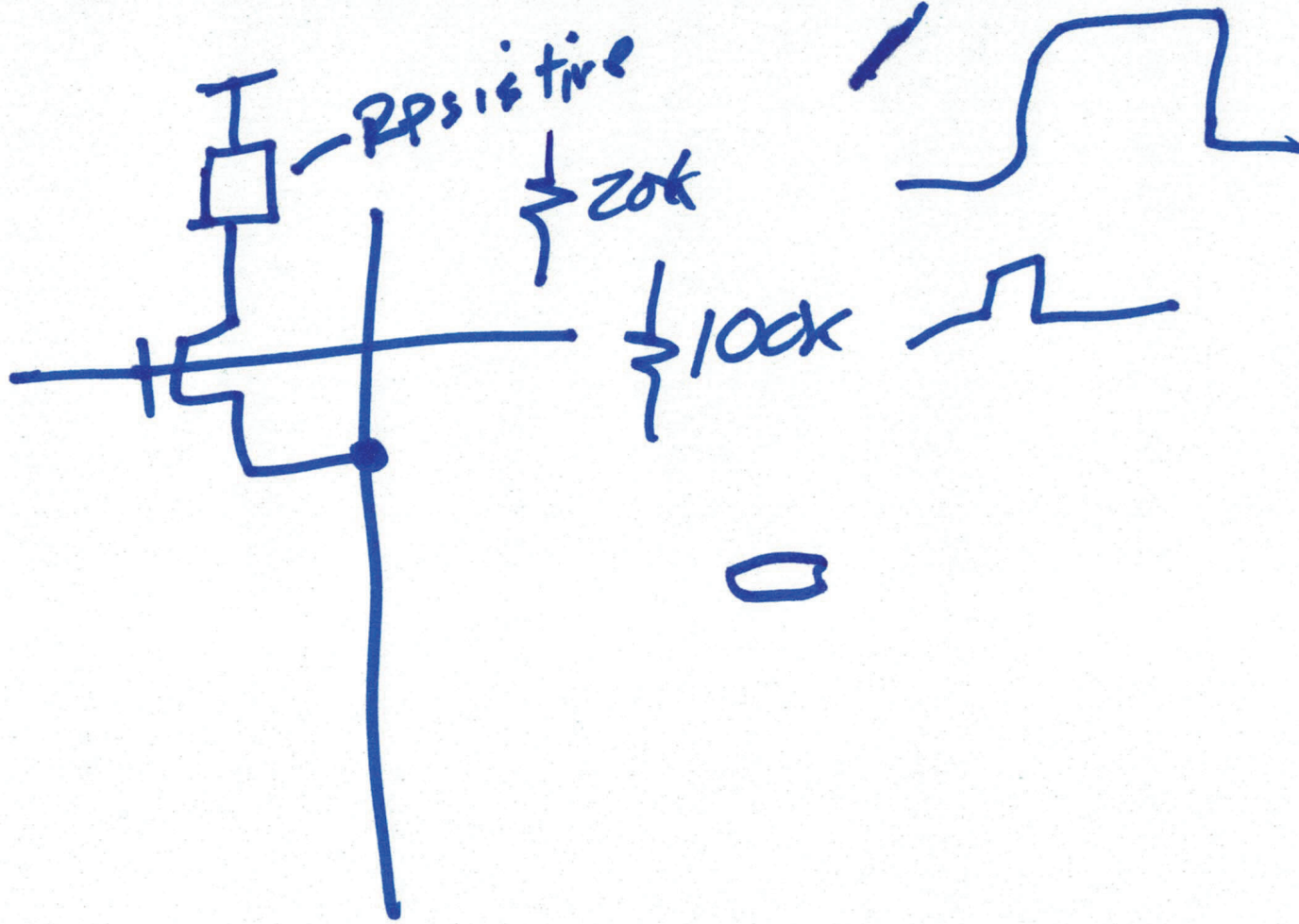

1)