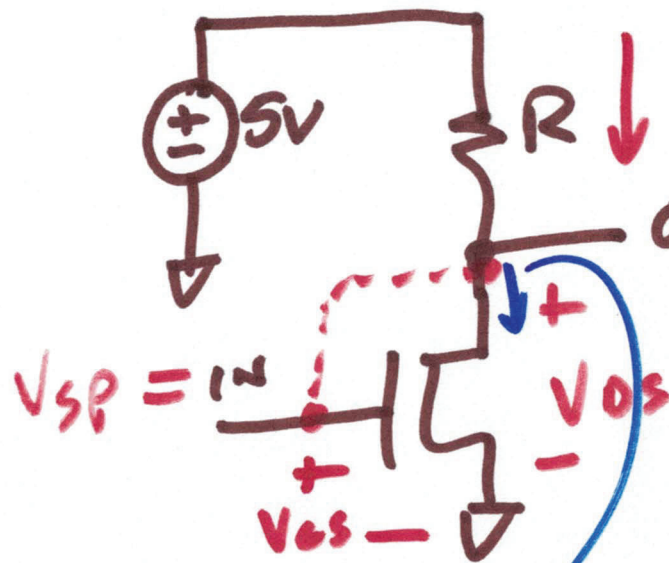


EE 421 / ELG 621

Digital IC Design

Lecture 17

OCT. 25, 2021



$$\frac{5 - V_{SP}}{R} = \frac{K_{PN} W_N}{2 L_N} (V_{SP} - V_{TN})^2$$

OUT = V<sub>SP</sub>

$$V_{OS} \geq V_{GS} - V_{TN} \text{ (for saturation)}$$

$$0 \geq -V_{TN}$$

$\frac{K_{PN} W_N}{2 L_N}$ . Always in saturation  
 $I_D \neq 0, V_{OS} > V_{TN}$

$$\frac{V_{DD} - V_{SP}}{R} = \frac{K_P \mu_{WN}}{2 L_N} (V_{SP} - V_{THN})^2$$

$$(V_{SP} - V_{THN})^2 = \frac{(V_{DD} - V_{SP}) \cdot 2L_N}{R K_P \mu_{WN}}$$

$$V_{SP}^2 - 2V_{SP}V_{THN} + V_{THN}^2 = X (V_{DD} - V_{SP})$$


$$X = \frac{2L_N}{R K_P \mu_{WN}}$$

$$V_{SP}^2 - V_{SP} (2V_{THN} + X) + V_{THN}^2 - X V_{DD} = 0$$

2)

$$K_{PN} = 120 \mu A$$

$$V_{TH} = 0.8$$

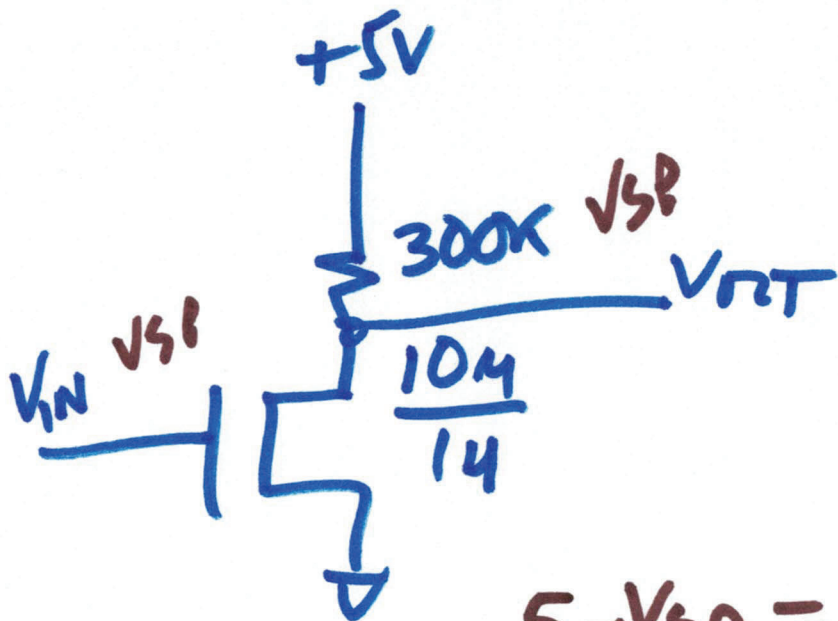

$$\frac{5 - V_{SP}}{300k} = \frac{120 \mu A \cdot 10}{2} \cdot (V_{SP} - 0.8)^2$$

$$5 - V_{SP} = 300k \cdot 600 \mu A (V_{SP}^2 - 1.6V_{SP} + 0.64)$$

$$5 - V_{SP} = 180 \cdot V_{SP}^2 - 288V_{SP} + 115.2$$

$$0 = 180 \cdot V_{SP}^2 - 287V_{SP} + 110.2$$

$$V_{SP}^2 - 1.594 + 0.612 = 0$$

3)


$$V_{SP} = \frac{1.594 \pm \sqrt{(1.594)^2 - 4(.612)'}}$$

$$= \frac{1.594 \pm \sqrt{\cancel{.304^2}}}{2}$$

$$V_{SP} = \frac{1.594 \pm .304}{2} =$$

$$\boxed{V_{SP} = .949} \text{ or } .645$$

4)

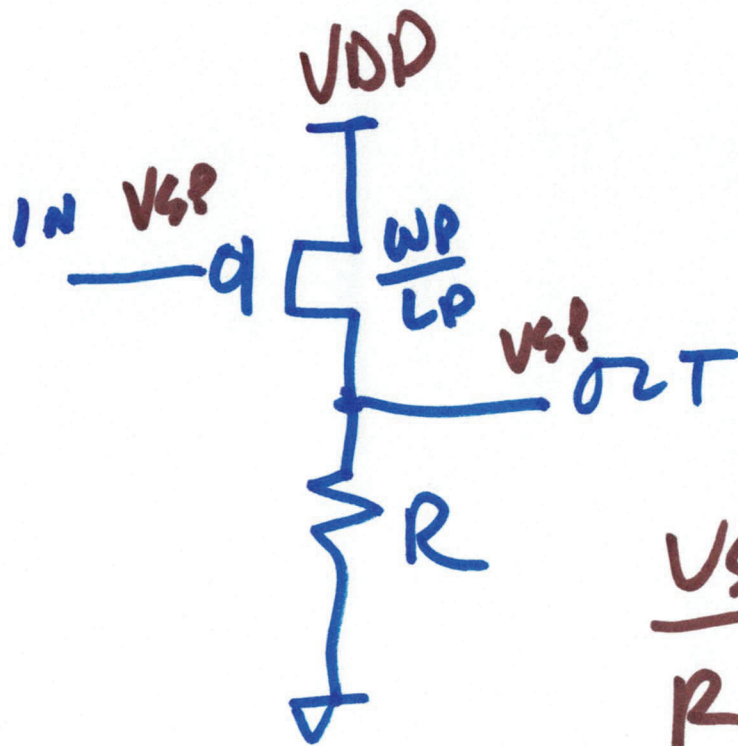


$$\frac{V_{SP}}{R} = \frac{K_{PP}}{2} \frac{W_P}{L_P} (V_{SG} - V_{THP})^2$$

$$\frac{V_{SP}}{R} = \frac{K_{PP}}{2} \frac{W_P}{L_P} (V_{DD} - V_{SP} - V_{THP})^2$$

# CMOS Inverter

switching point  $V_{SP}$

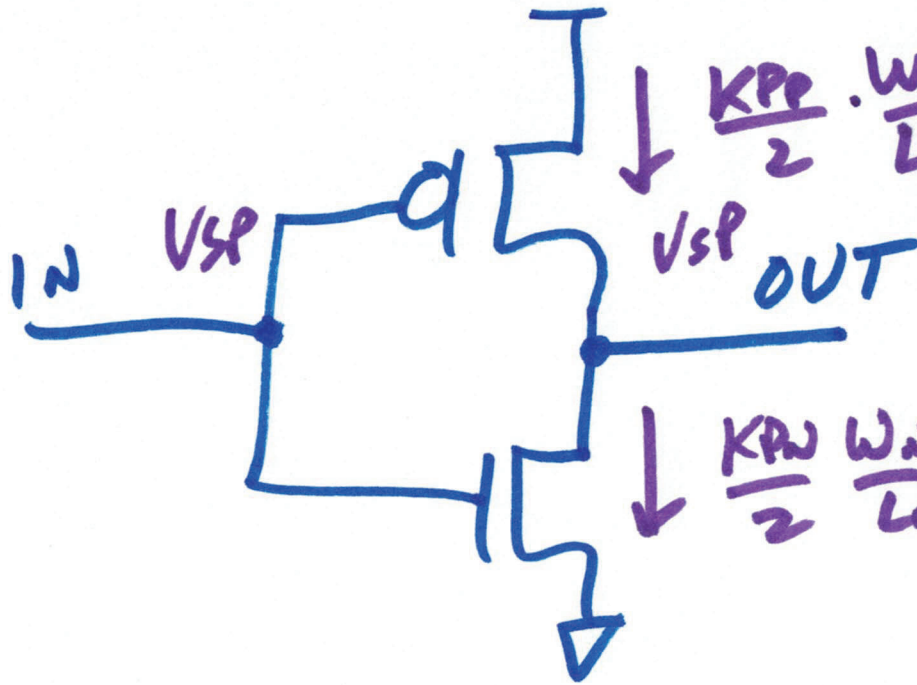

$$\downarrow \frac{K_{PP}}{2} \cdot \frac{W_P}{L_P} \cdot (V_{DD} - V_{SP} - V_{THP})^2$$

$$\downarrow \frac{K_{PN}}{2} \cdot \frac{W_N}{L_N} \cdot (V_{SP} - V_{THN})^2$$

$$\sqrt{\frac{K_{PP}}{2} \cdot \frac{W_P}{L_P} \cdot (V_{DD} - V_{SP} - V_{THP})^2} = \sqrt{\frac{K_{PN}}{2} \cdot \frac{W_N}{L_N} \cdot (V_{SP} - V_{THN})^2}$$

6)

$$x = \sqrt{\frac{\frac{K_{PP} W_P}{2 L_P}}{\frac{K_{DN} W_N}{2 L_N}}} = \sqrt{\frac{\beta_P}{\beta_N}}, \quad \beta_N = K_{PN} \cdot \frac{W_N}{L_N}$$

$$x(V_{DD} - V_{SP} - V_{THP}) = V_{SP} - V_{THN}$$




$$V_{THN} + x(V_{DD} - V_{THP}) = V_{SP}(1 + x)$$

$$V_{SP} = \frac{V_{THN} + \cancel{x(V_{DD} - V_{THP})} x(V_{DD} - V_{THP})}{1 + x}$$


$$V_{SP} = \frac{V_{THN} + \sqrt{\frac{\beta_P}{\beta_N}} (V_{DD} - V_{THP})}{1 + \sqrt{\frac{\beta_P}{\beta_N}}}$$

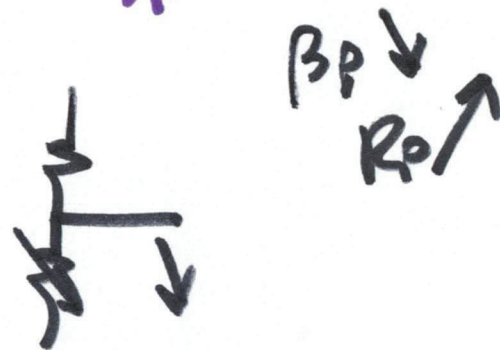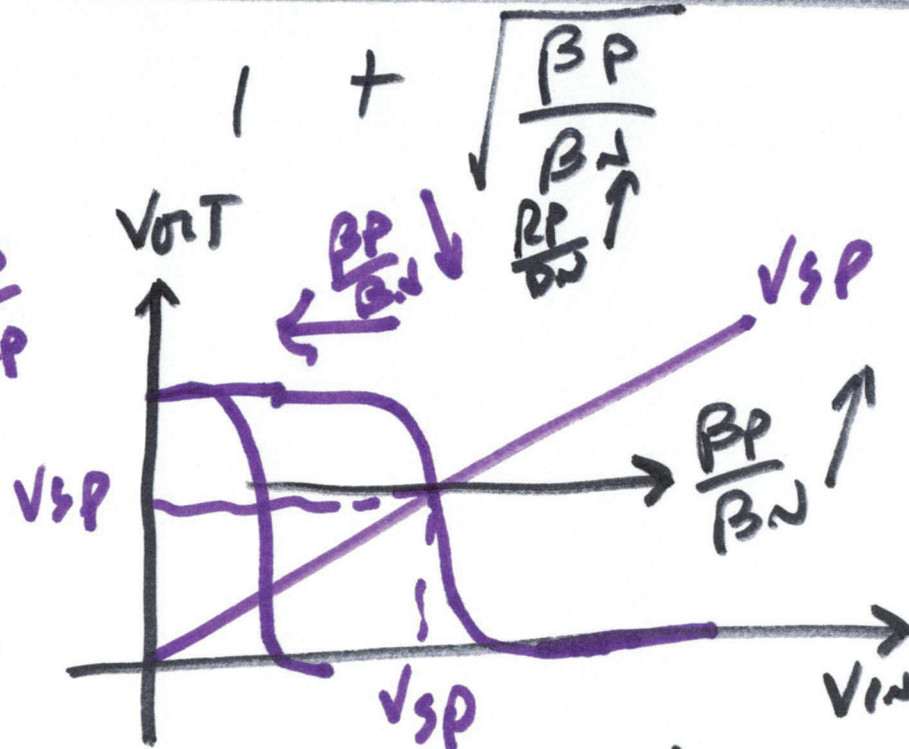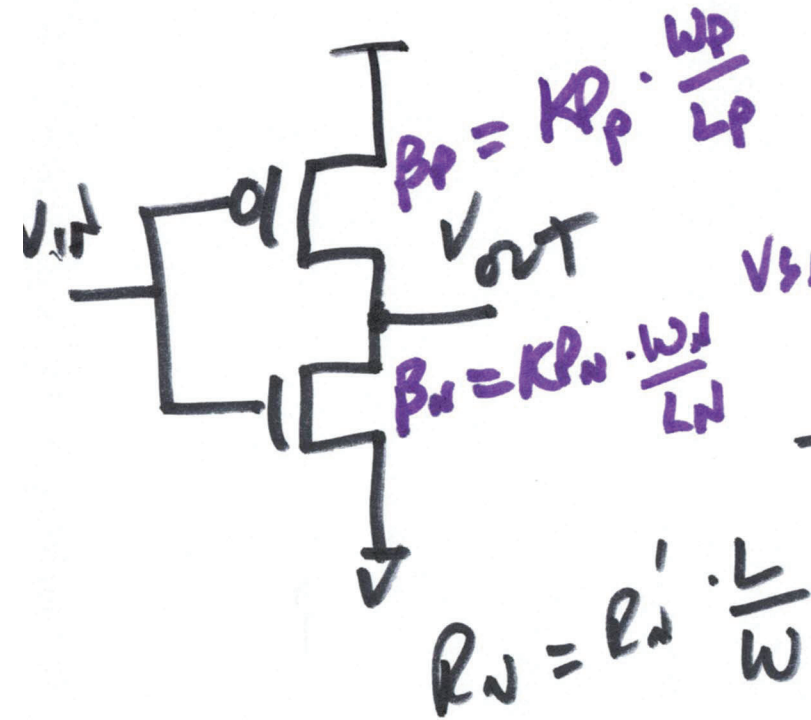1)


$$V_{SP} = \frac{V_{THN} + \sqrt{\frac{\beta_P}{\beta_N}} (V_{DD} - V_{THP})}{1 + \sqrt{\frac{\beta_P}{\beta_N}}}$$






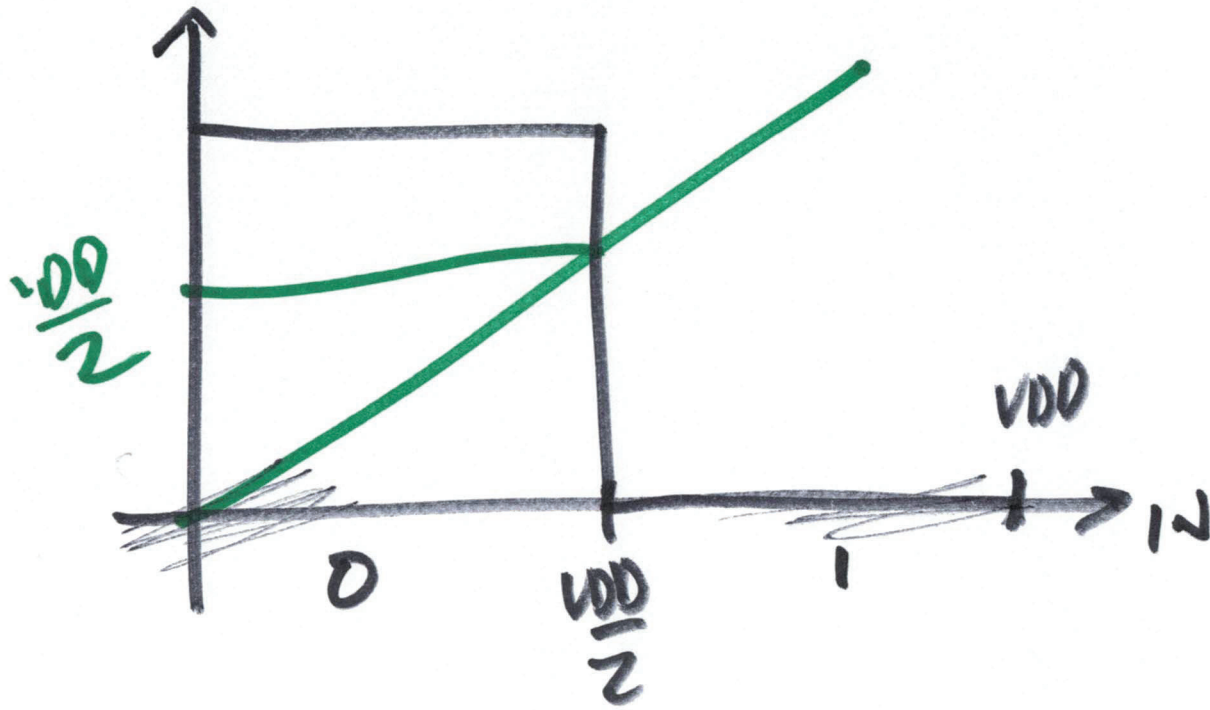


9)

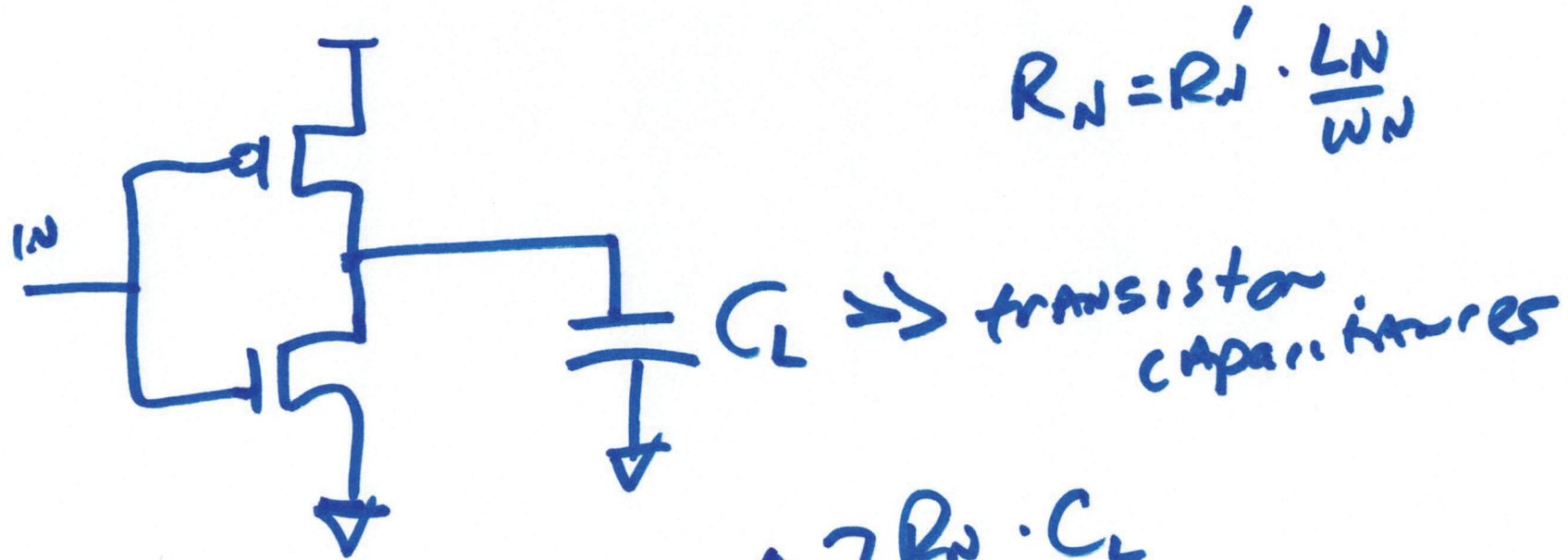

$$R_N = R_i' \cdot \frac{L_N}{W_N}$$

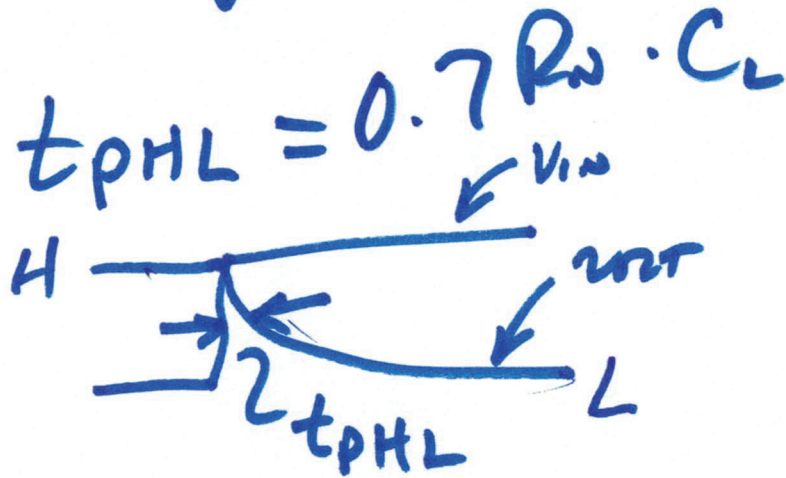



$$t_{PLH} = 0.7 R_P \cdot C_L$$

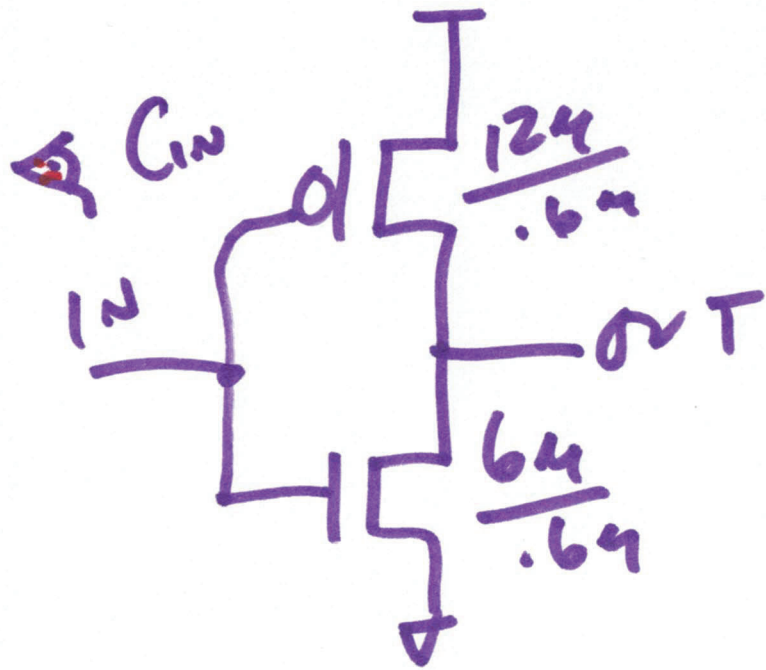

$$\begin{aligned}
 C_{in} &= C_{inn} + C_{inp} \\
 &= \frac{3}{2} C_{oxN} + \frac{3}{2} C_{oxP} \\
 &= \frac{3}{2} \cdot \frac{2.5 \text{ fF}}{4 \mu\text{m}^2} \cdot 6 \mu\text{m} \cdot 6 \mu\text{m} + \\
 &\quad \frac{3}{2} \cdot \frac{2.5 \text{ fF}}{4 \mu\text{m}^2} \cdot 12 \mu\text{m} \cdot 6 \mu\text{m} \\
 &= \frac{3}{2} \cdot 2.5 \text{ fF} (3.6 + 7.2)
 \end{aligned}$$

$$C_{in} = 40.5 \text{ fF}$$

11)

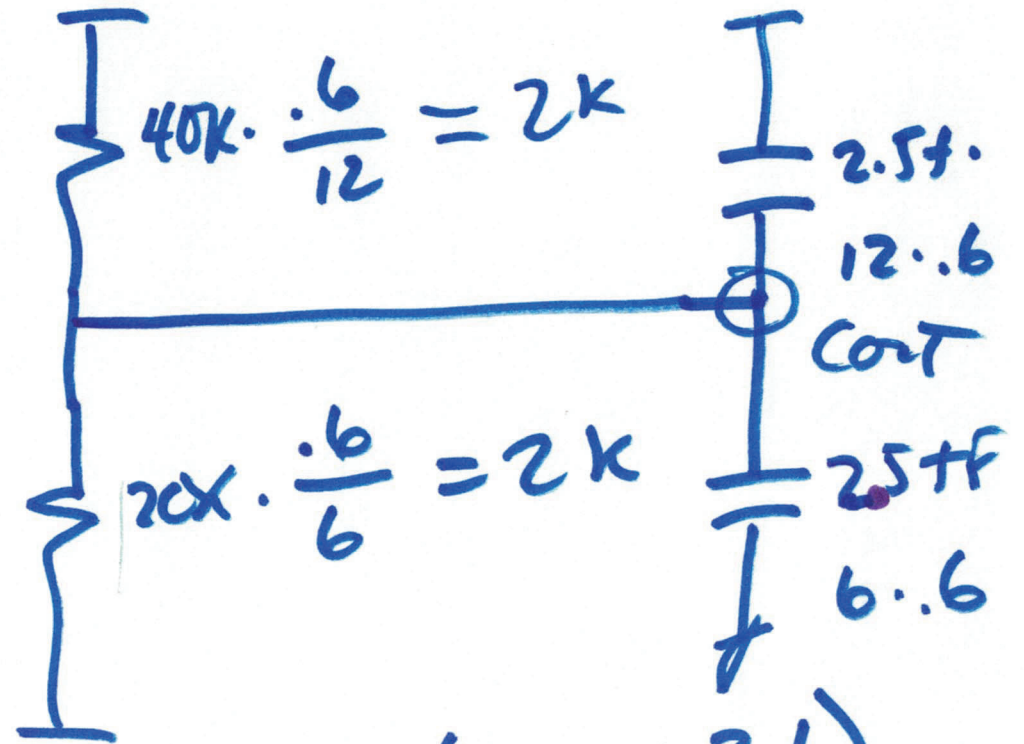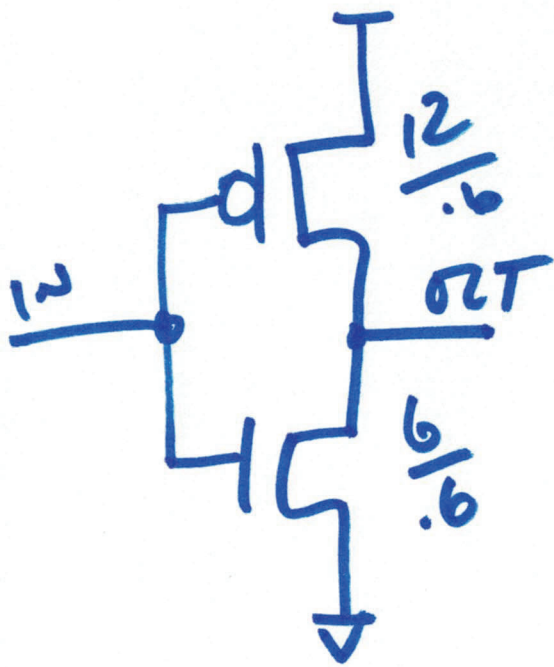


$$C_{out} = 2.5 \text{ fF} (7.2 + 3.6)$$

$$= 27 \text{ fF}$$

$$t_{PLH} = 0.7 R_p \cdot C_{out}$$

$$t_{PHL} = 0.7 R_n \cdot C_{out}$$

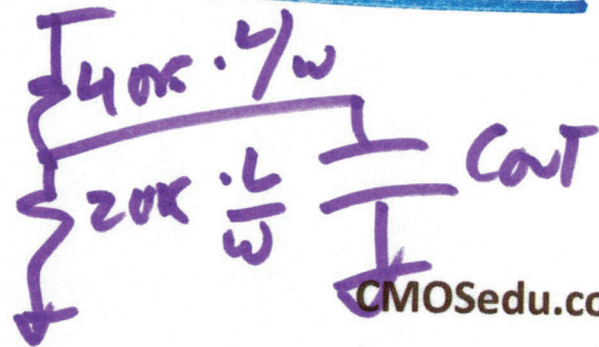

(2)

