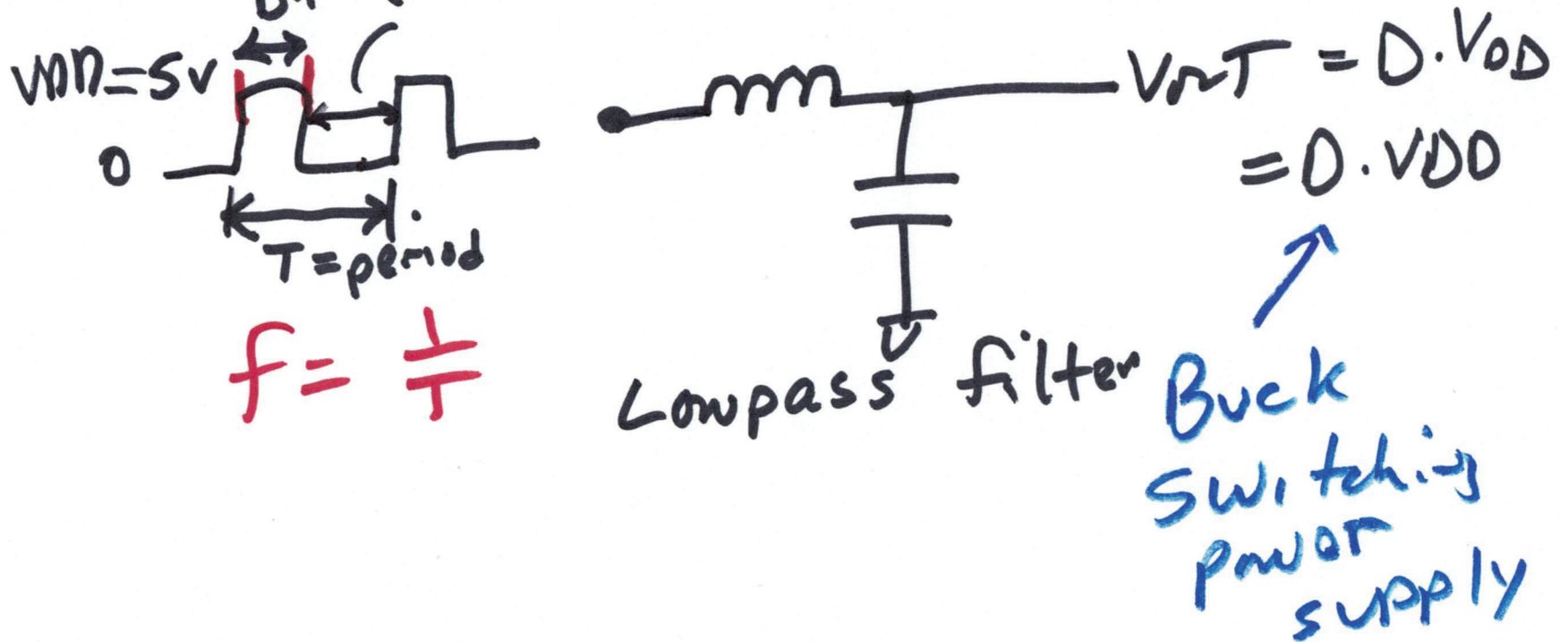



EE 421 / ECG 621

Digital IC Design

October 18, 2023

Lecture 14



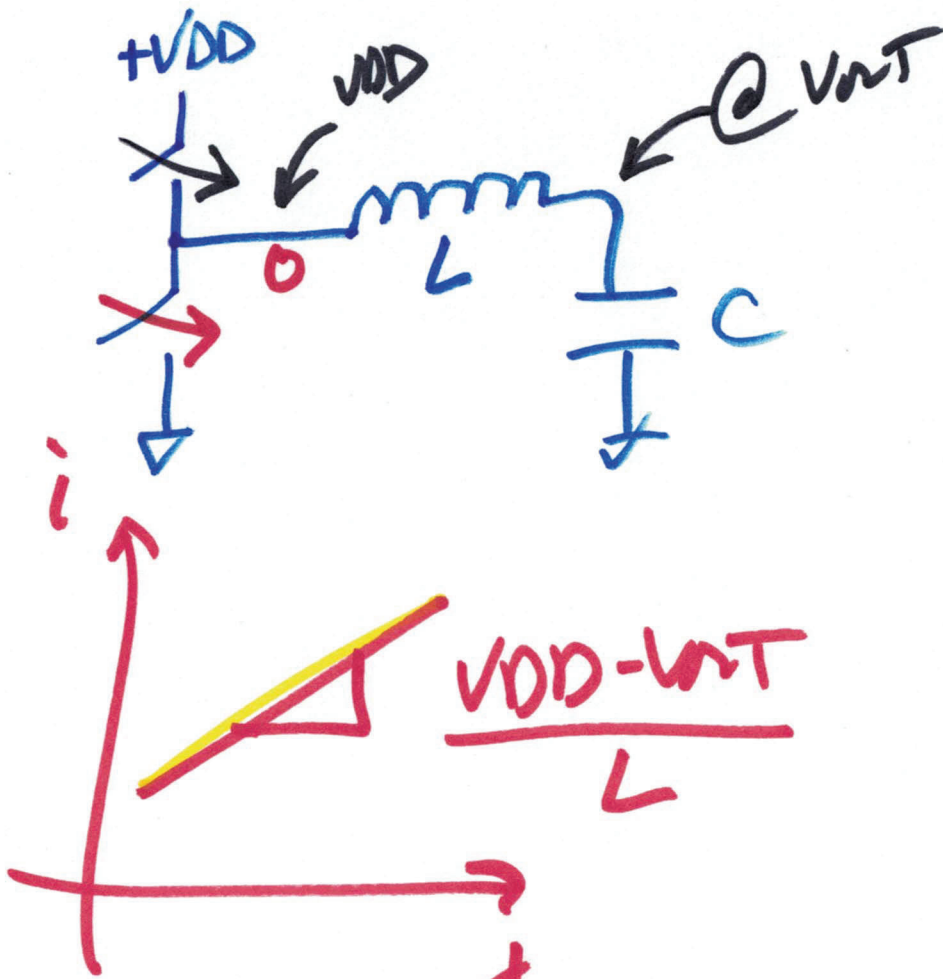

$$V = L \cdot \frac{di}{dt}$$

$$V_{DD} - V_{out} = L \cdot \frac{di}{dt}$$

$$\frac{V_{DD} - V_{out}}{L} = \frac{di}{dt}$$

$$i(t) = \text{ramp}$$

$$0 - V_{out} = L \cdot \frac{\Delta i}{\Delta t}$$


$$(1-D)T \frac{\Delta i}{\Delta t} = \frac{-V_{out}}{L}$$

$$V_{DD} - V_{out} = L \cdot \frac{\Delta i}{\Delta t}$$

$$\Delta i = \frac{V_{DD} - V_{out}}{L} \cdot \Delta t$$

$$\Delta i = (1-D)T \left(\frac{-V_{out}}{L} \right) = \frac{V_{DD} - V_{out} \cdot DT}{L}$$

2)

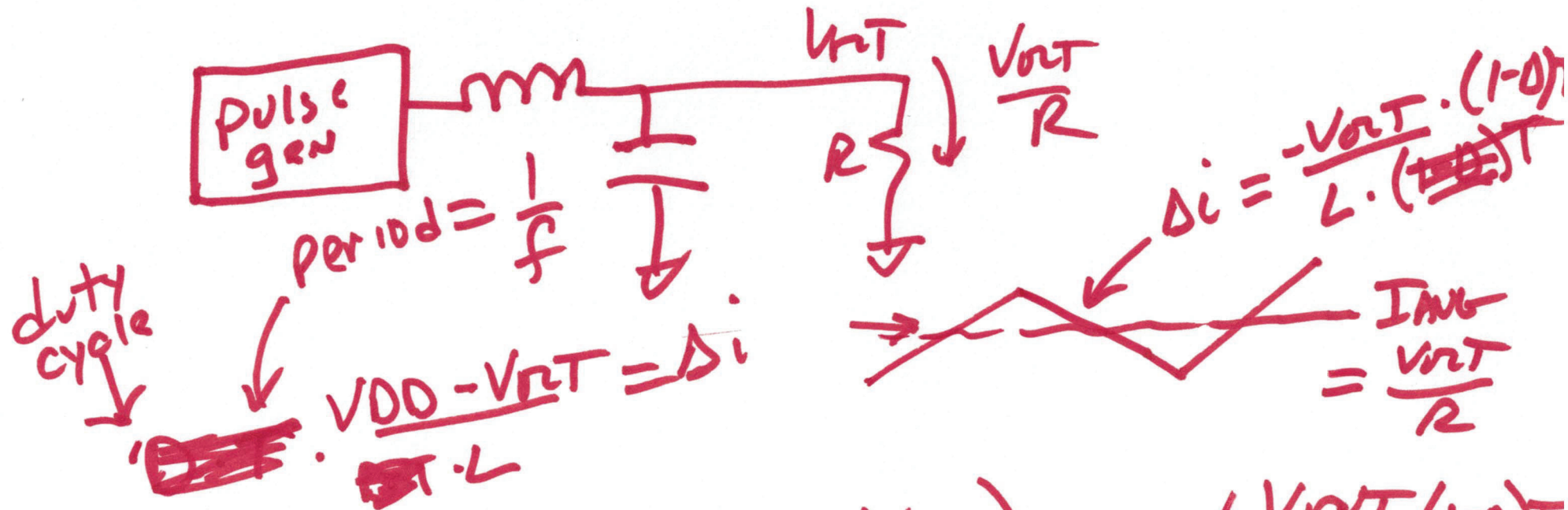


D.T

$$D \cdot T \cdot \frac{(V_{DD} - V_{RT})}{L} = \frac{+V_{RT} \cdot (1-D)T}{L}$$

$$D \cdot T \cdot V_{DD} - \cancel{D \cdot T \cdot V_{RT}} = +V_{RT} \cdot (1-D)T - \cancel{+V_{RT} \cdot D \cdot T}$$

$$D V_{DD} = V_{RT}$$

3)

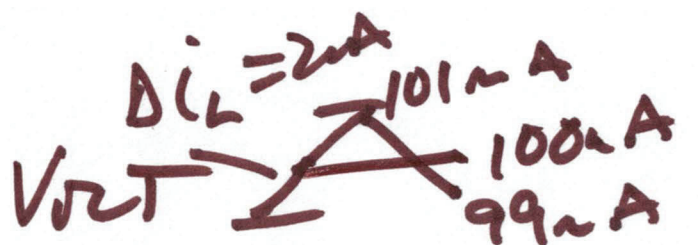

↑ Assump $V_{VT} = \text{CONST}$


$V = L \frac{di}{dt}$
 $\text{CONST} \frac{V}{L} = \frac{di}{dt}$

Voltage across inductor = CONSTANT = $V_{DD} - V_{VT}$

$$\frac{V_{DD} - V_{VT}}{L} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{D \cdot T}$$

$$\Delta i_L = \frac{D \cdot T}{L} (V_{DD} - V_{VT})$$

4)

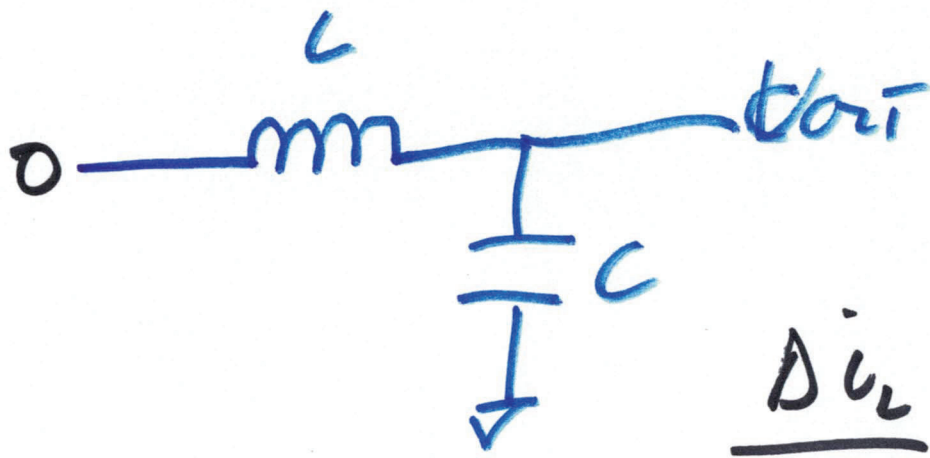


$$\frac{\Delta i_L}{(1-D)T} = \frac{0 - v_{out}}{L}$$


$$\Delta i_L = \frac{-v_{out} \cdot (1-D)T}{L}$$


$$\frac{DT}{K} (V_{DD} - v_{out}) = \frac{v_{out}}{R} (1-D)T$$

$$DV_{DD} - Dv_{out} = v_{out} - Dv_{out}$$

$$D \cdot V_{DD} = v_{out}$$

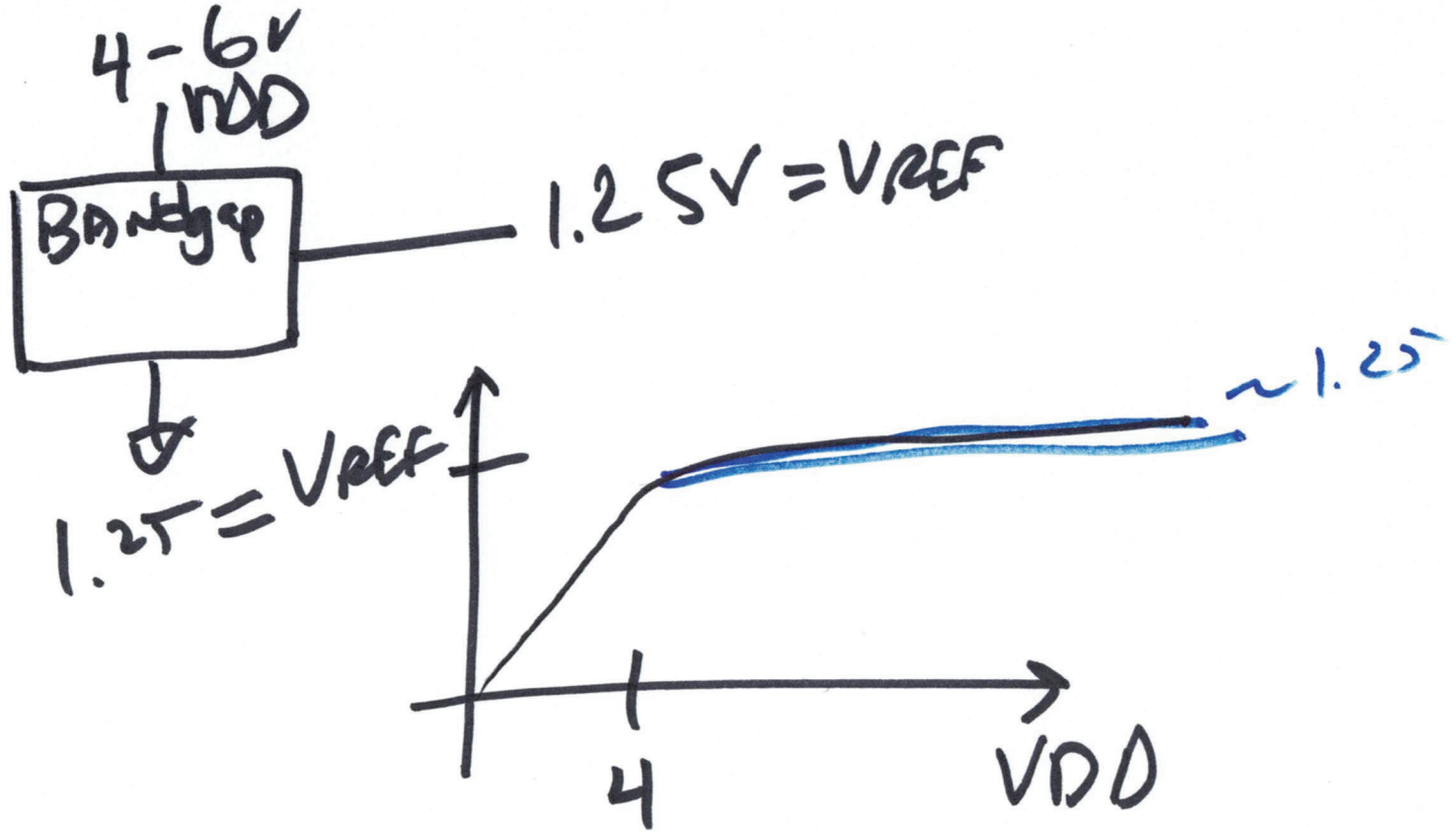


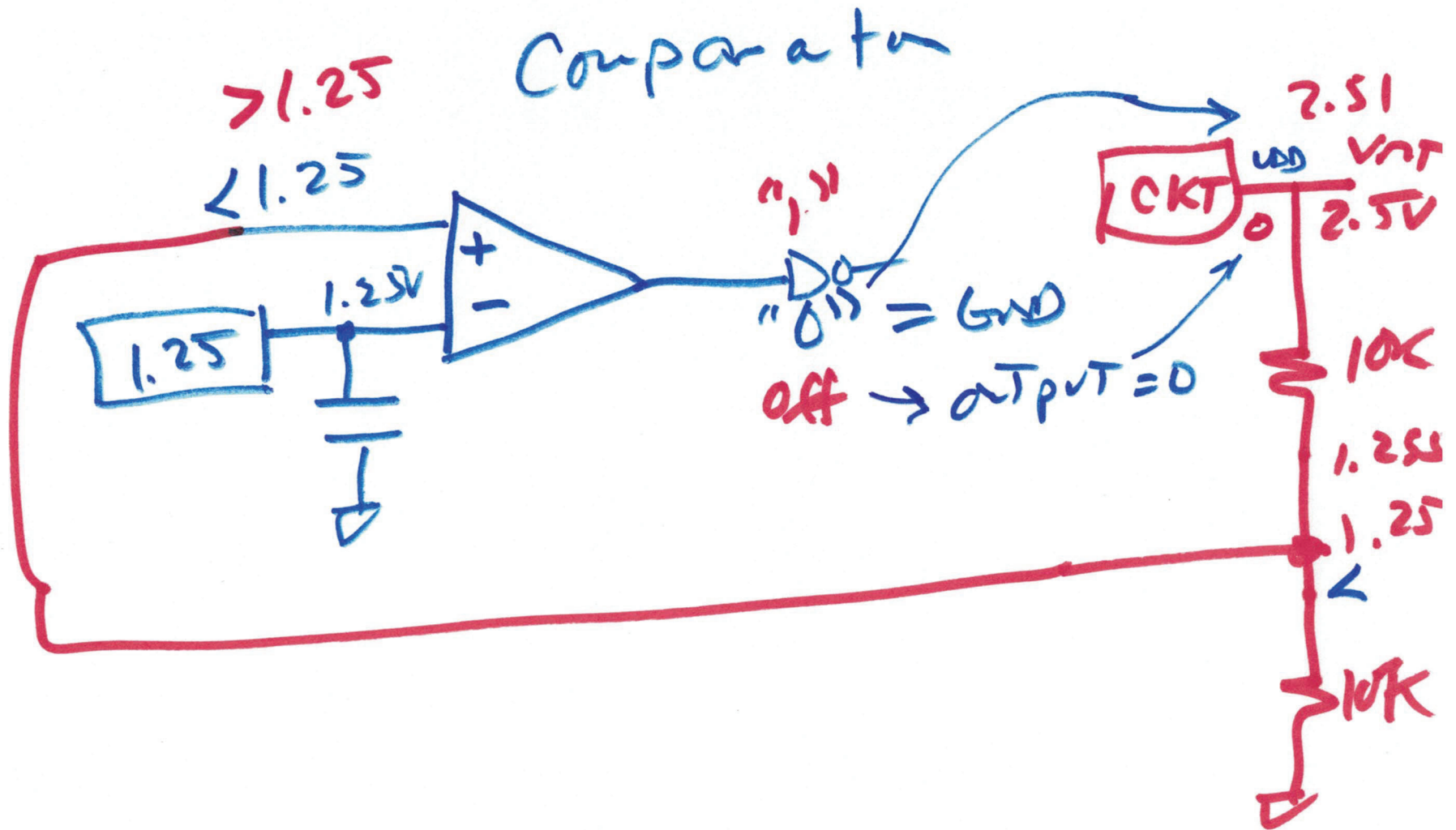


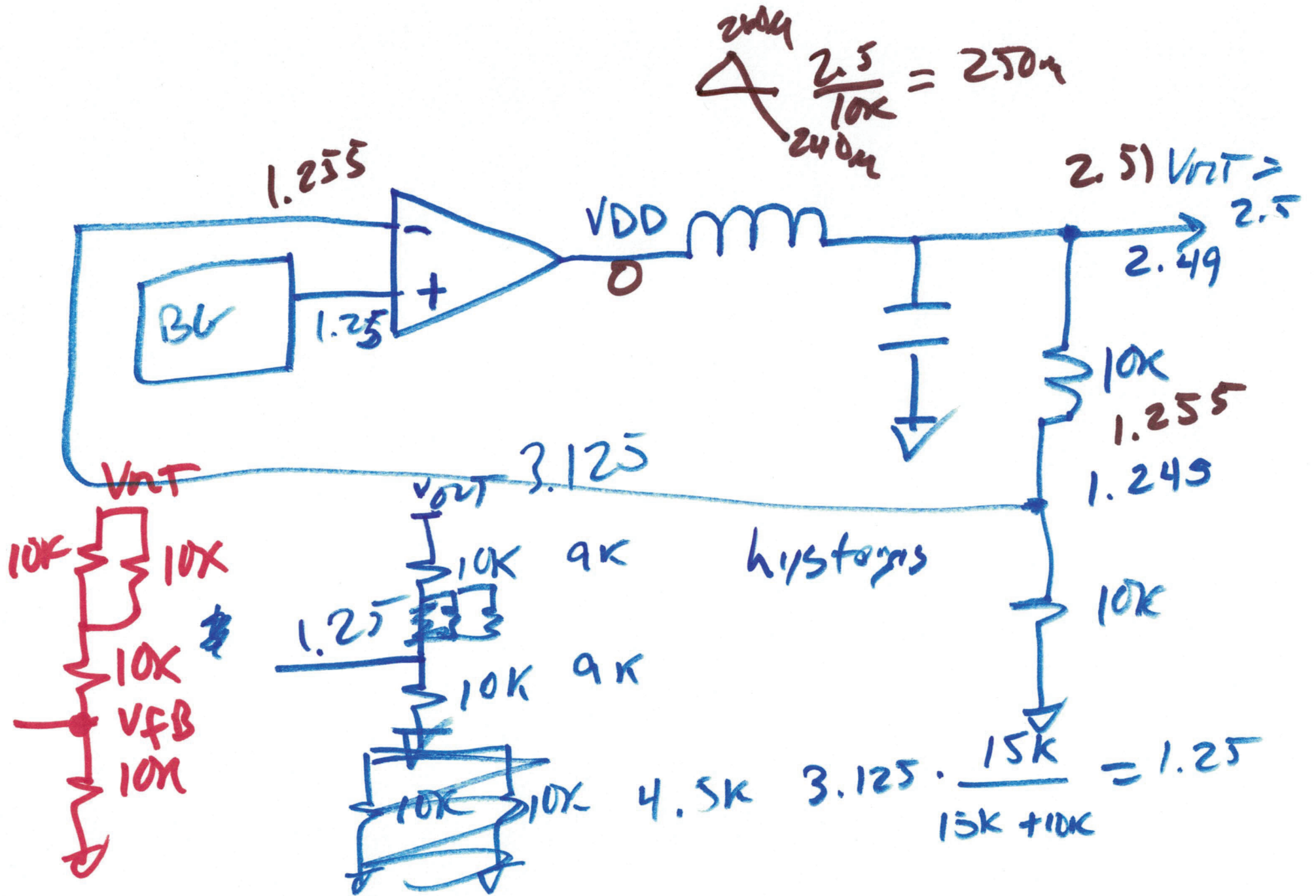


$$f = \frac{1}{T}$$
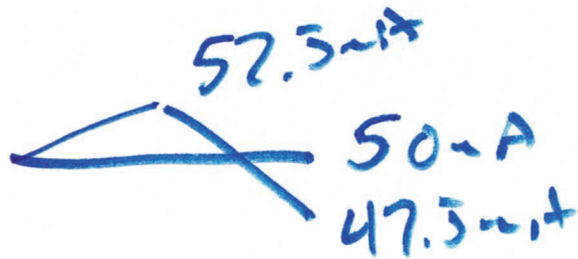
$$\Delta i = D \cdot T \frac{(V_{DD} - V_{th})}{L}$$



$$D = \frac{3.125}{5}$$

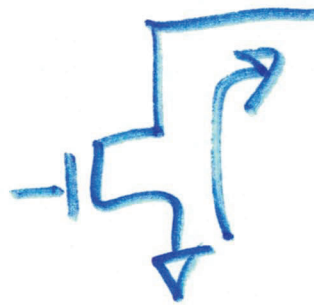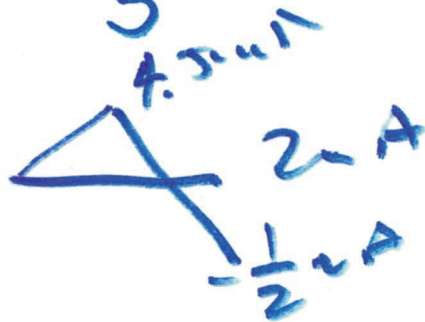

$$L = \frac{D \cdot (V_{DD} - V_{th})}{\Delta i \cdot f}$$

$$L = \frac{\frac{V_{th}}{V_{DD}} \cdot (V_{DD} - V_{th})}{5 \text{ mA} \cdot f}$$

$$\frac{P_L}{P_{supply}} = \epsilon_{eff}$$

$V_{DD} = V_{INT}$
↓
4.5
5.5

$$D = \frac{V_{OHI}}{4.5} = 0.7?$$

