




EE 421 / ECG 621

Digital IC Design


October 23, 2023

Lecture 15


$$K_P = \mu_n \cdot C_{ox}$$

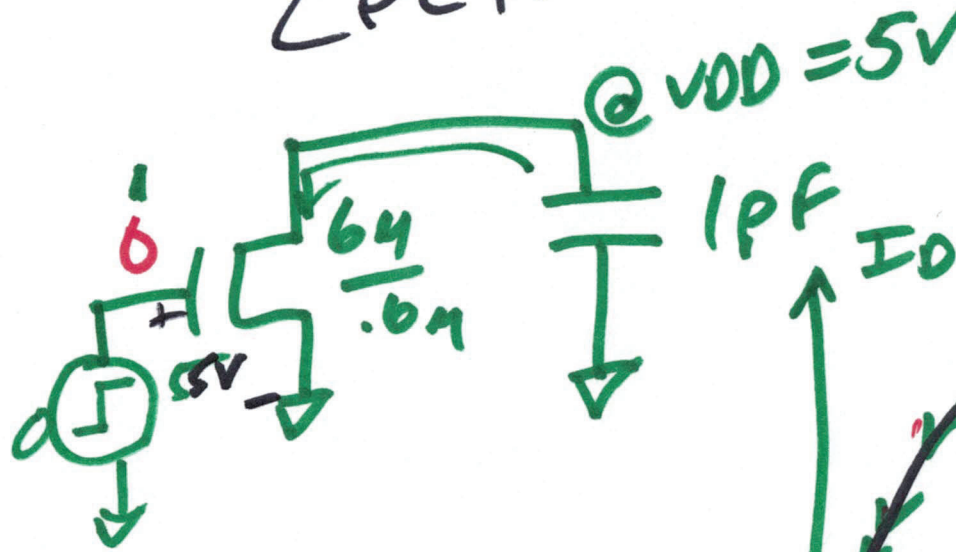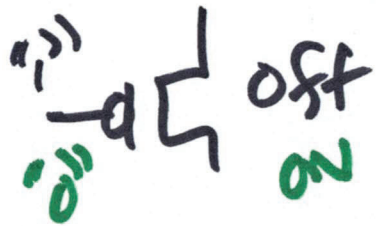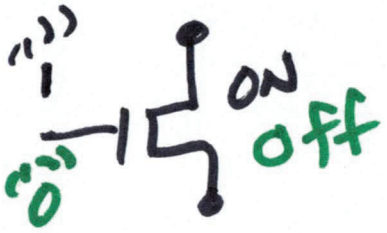
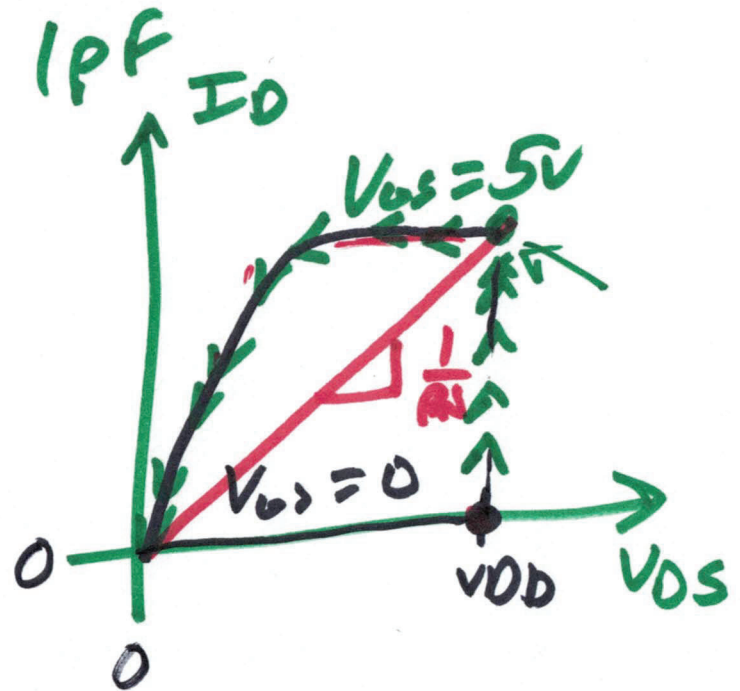
$$R_n = \frac{V_{DD}}{\frac{K_P}{2} \cdot \frac{W}{L} (V_{DD} - V_{thn})^2}$$



1)

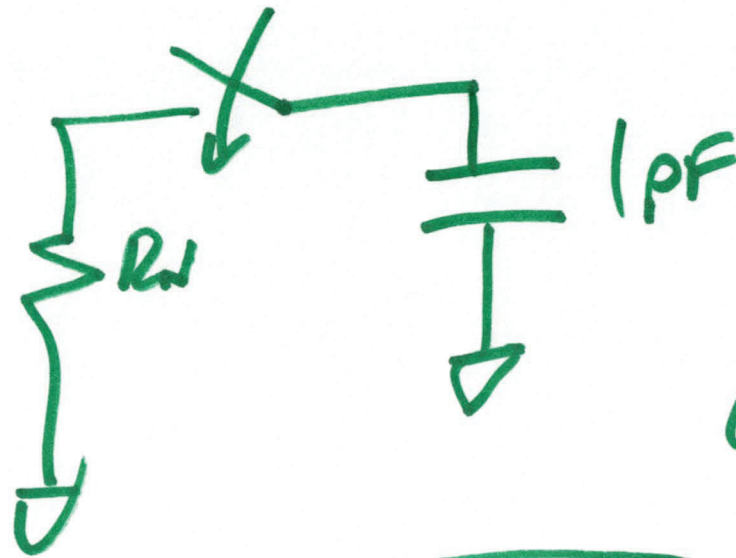

$$0.7R_w \cdot 1\text{pF}$$

$$R_w = R_w' \cdot \frac{L}{W}$$

$$C_{ox} = C_{ox}' \cdot L \cdot W$$

$$R_p = R_p' \cdot \frac{L}{W}$$

$$R_N = \frac{5}{2.5 \mu A} = 2K = R_N' \cdot \frac{L}{W} = R_N' \cdot \frac{0.6}{6}$$


$$R_N' = 20K$$

Switch closed


$$V_{GS} > \frac{V_{DD}}{2}$$

Switch open

$$V_{GS} < \frac{V_{DD}}{2}$$

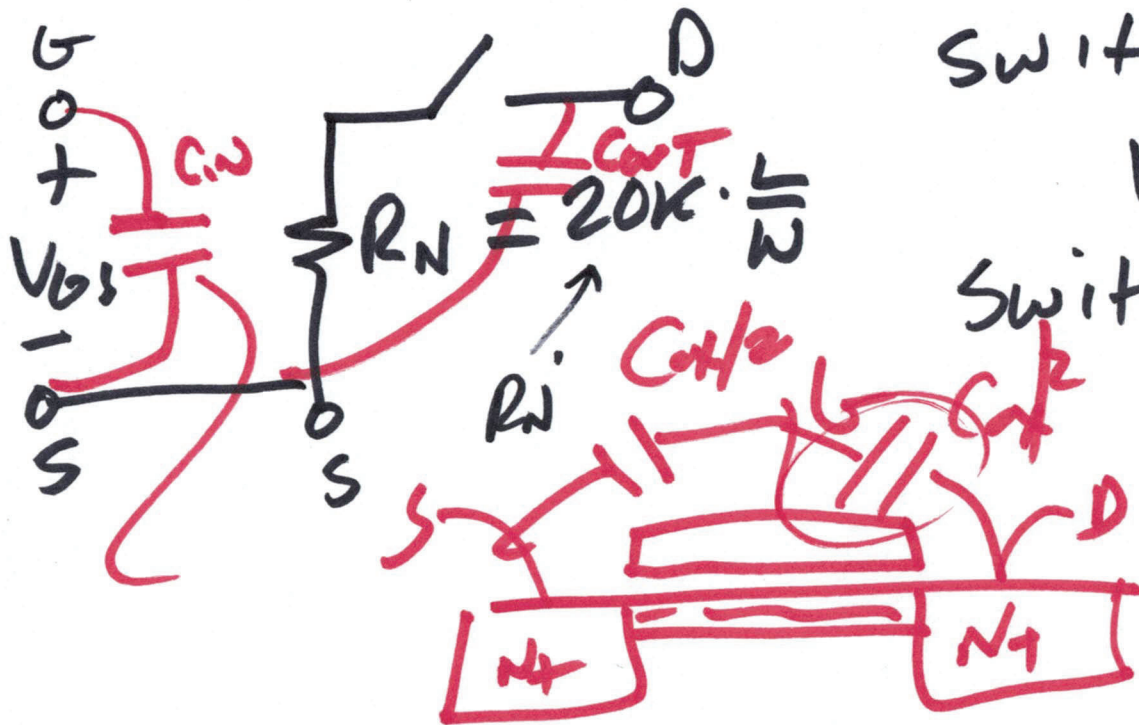

$$Cv = Q$$

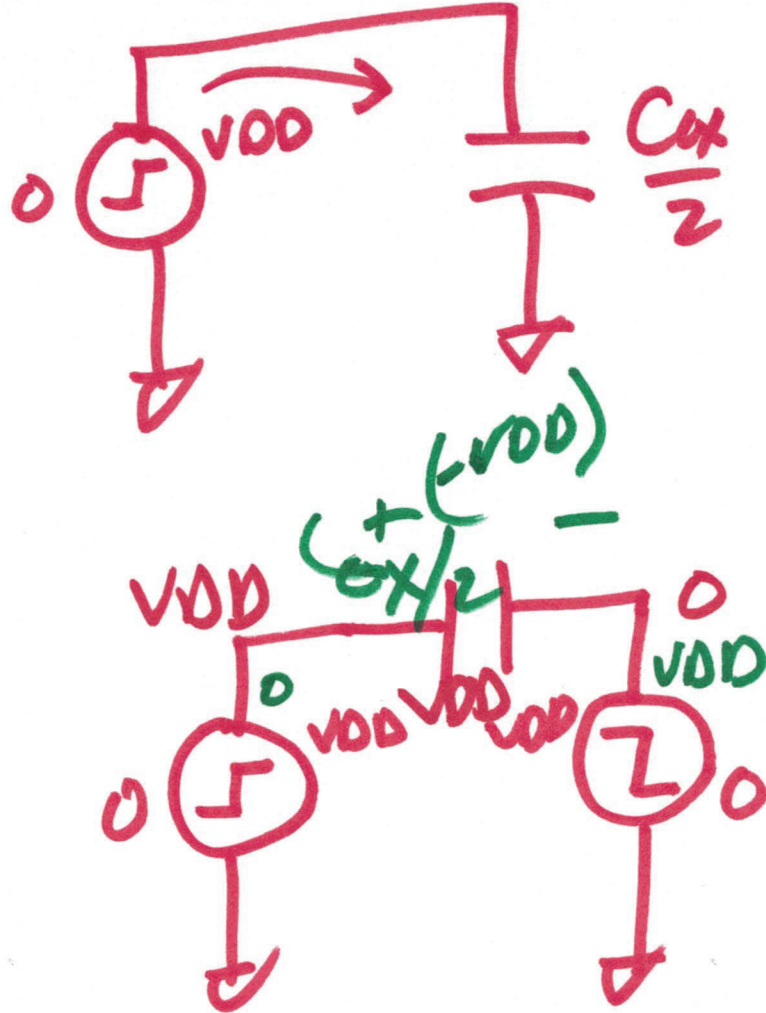

$$\frac{C_{ox}}{2} \cdot V_{DD} = Q$$


$$Q_i = -V_{DD} \cdot \frac{C_{ox}}{2}$$

$$Q_f = V_{DD} \cdot \frac{C_{ox}}{2}$$


$$2V_{DD} \cdot \frac{C_{ox}}{2}$$

$$V_{DD} \cdot C_{ox}$$




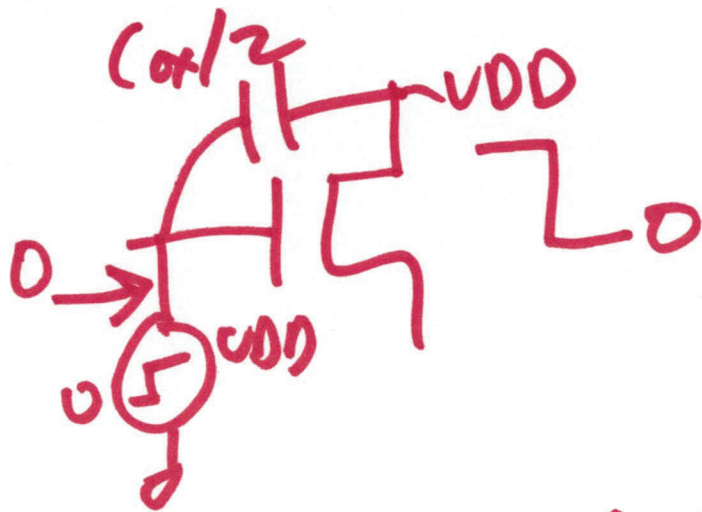




$$Q = V_{DD} \cdot C_{ox}$$

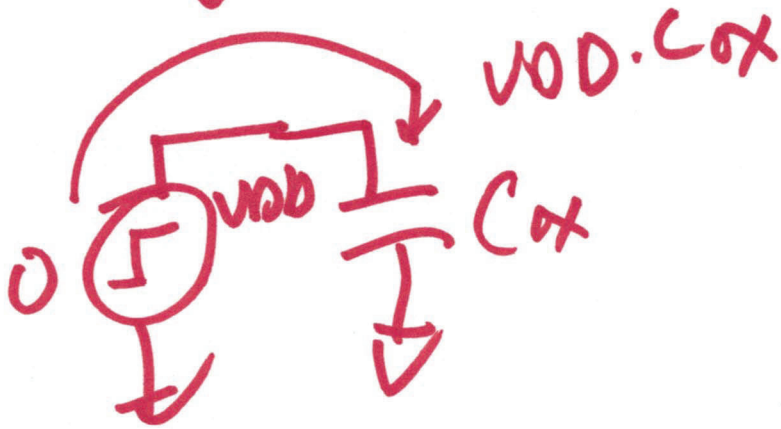

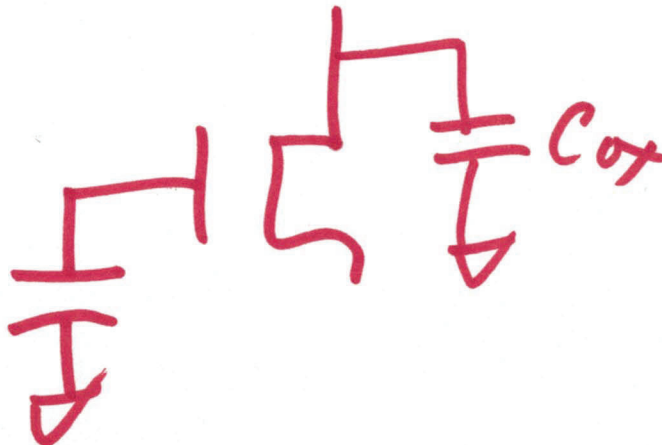
$$\frac{3}{2} C_{ox} \cdot C_{ox} + \frac{C_{ox}}{2}$$




5)

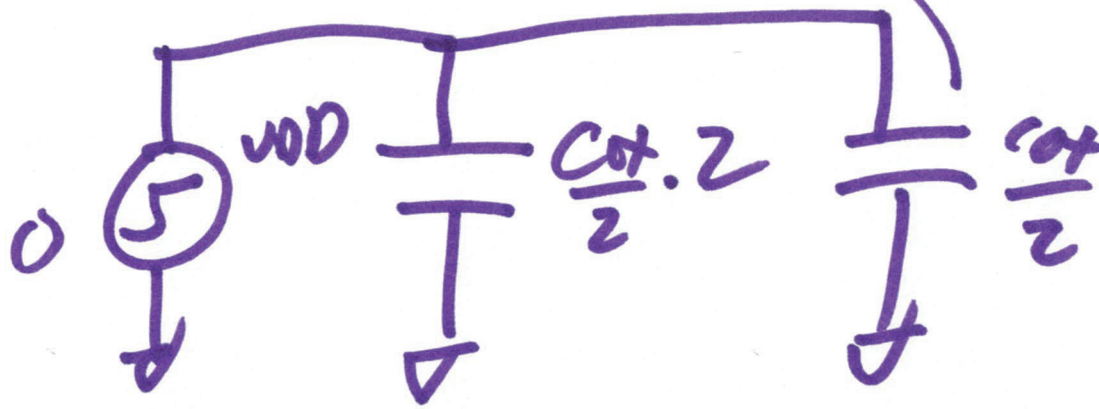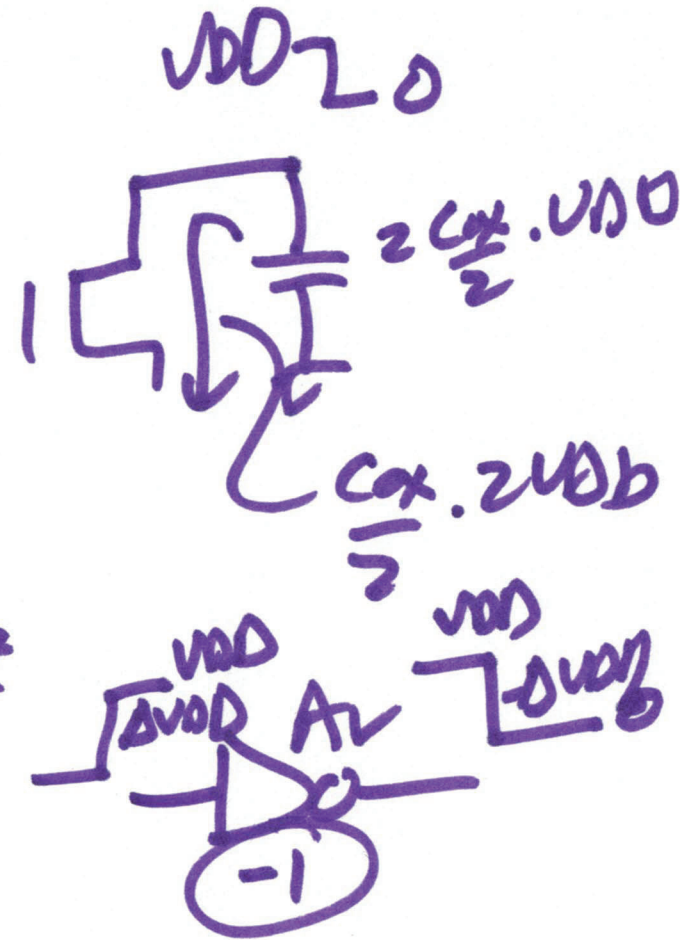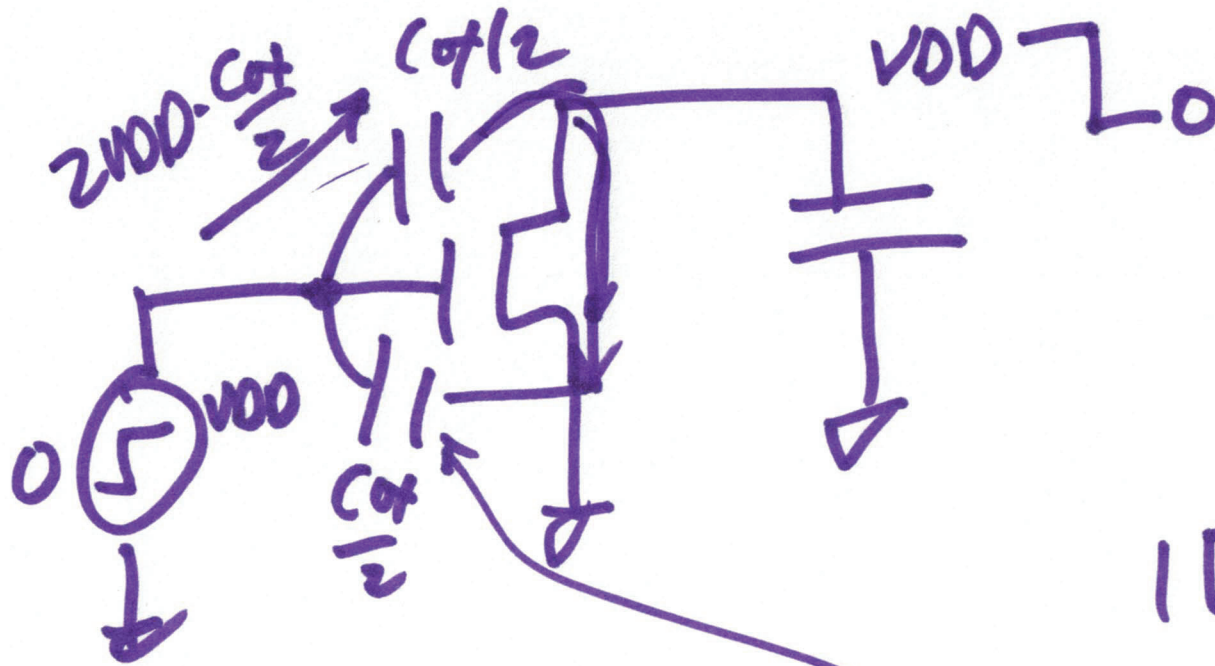

# Digital Model

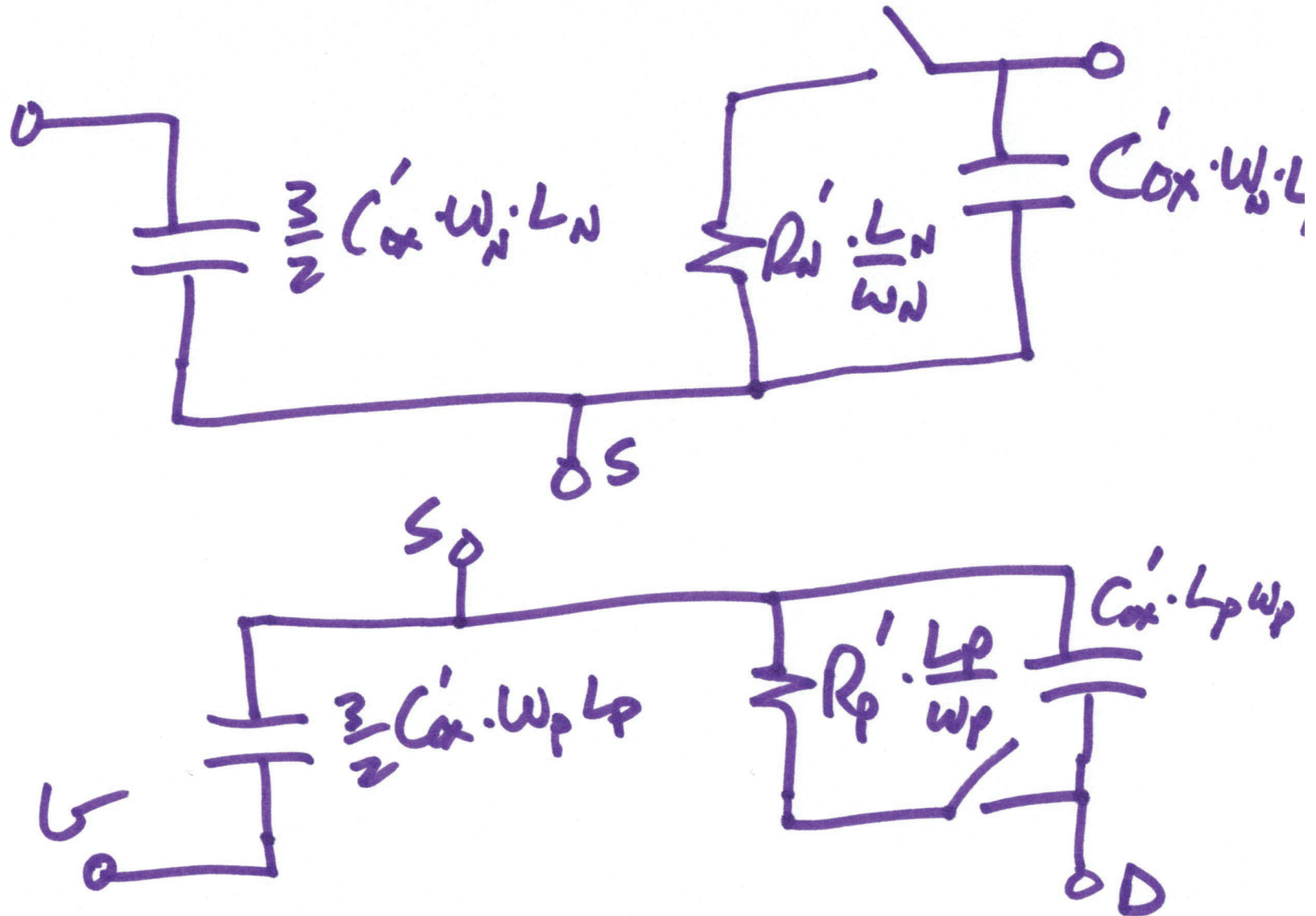

$$\frac{v_{in}}{j\omega C(1+|A|)}$$

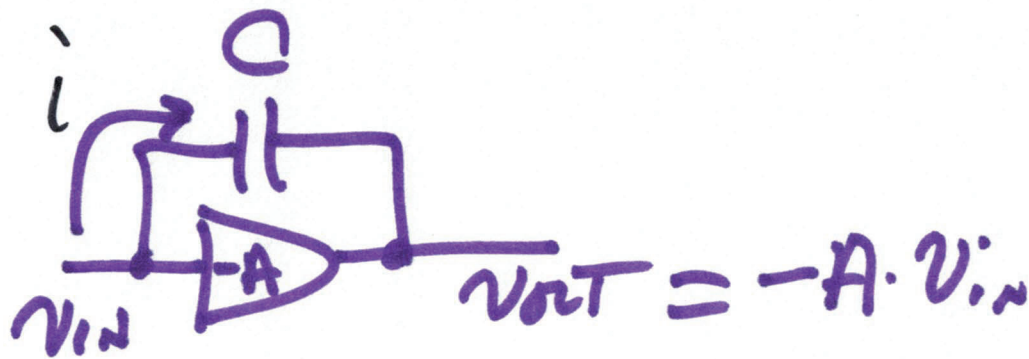

~~$$i = v_{in} - (-A \cdot v_{out}) = \frac{(v_{out} - v_{out})}{-A}$$~~

$$i = \frac{v_{in} - (-A \cdot v_{out})}{\frac{1}{j\omega C(1+|A|)}} = \frac{v_{out} - v_{out}}{\frac{1}{j\omega C(1+|A|)}}$$



~~$$C(1+|A|) \cdot \frac{v_{in}(1+|A|)}{j\omega C(1+|A|)} = \frac{v_{in}(1+|A|)}{j\omega C(1+|A|)}$$~~

$$\frac{v_{in}}{j\omega C(1+|A|)} = \frac{v_{out}}{j\omega C(1+|A|)}$$

$$C(1+|A|)$$

8)



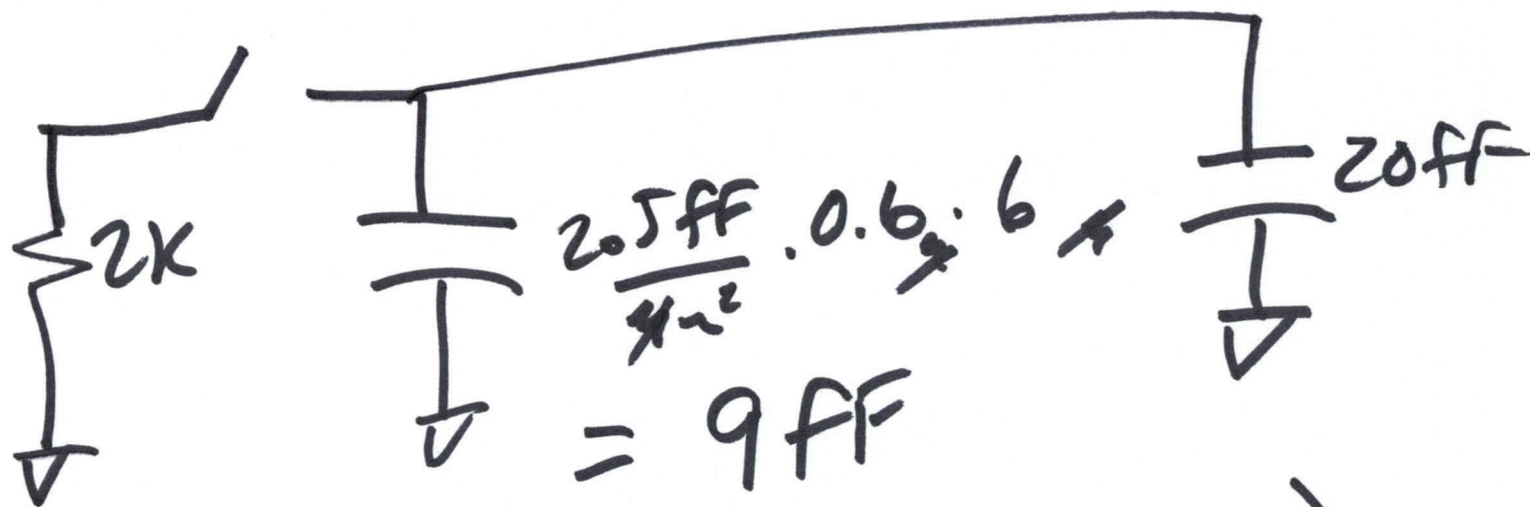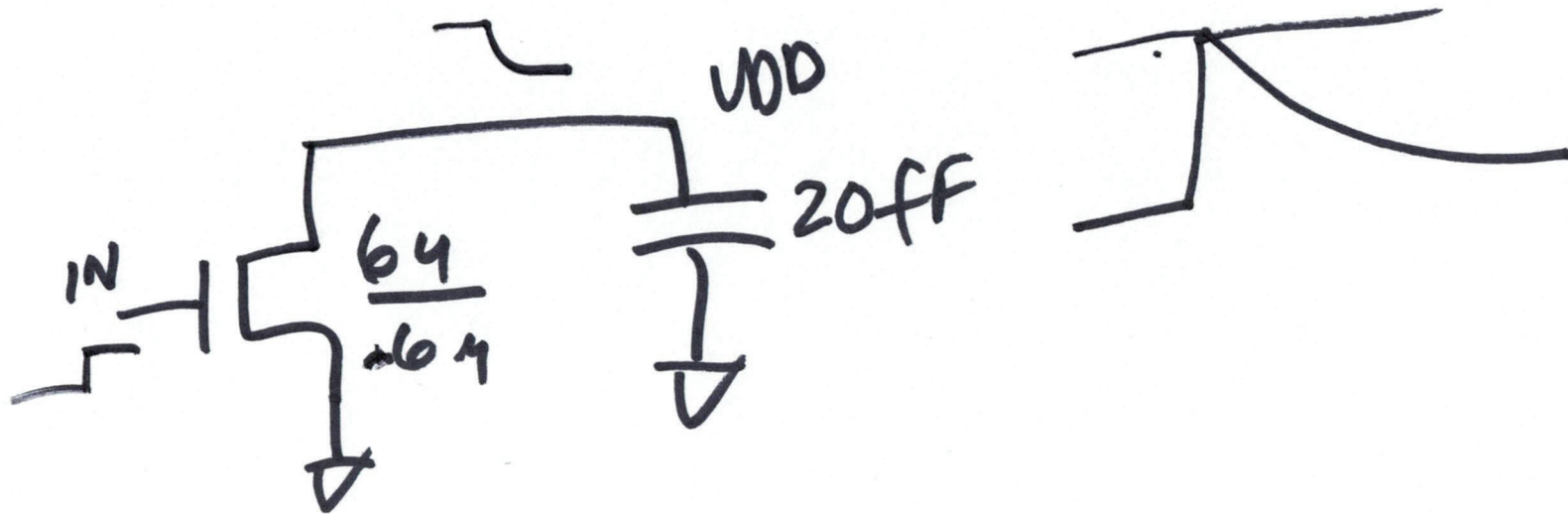

$$t_d = 0.7 \cdot 2k (9 \text{ fF} + 20 \text{ fF})$$

$$t_d = 40 \text{ ps}$$