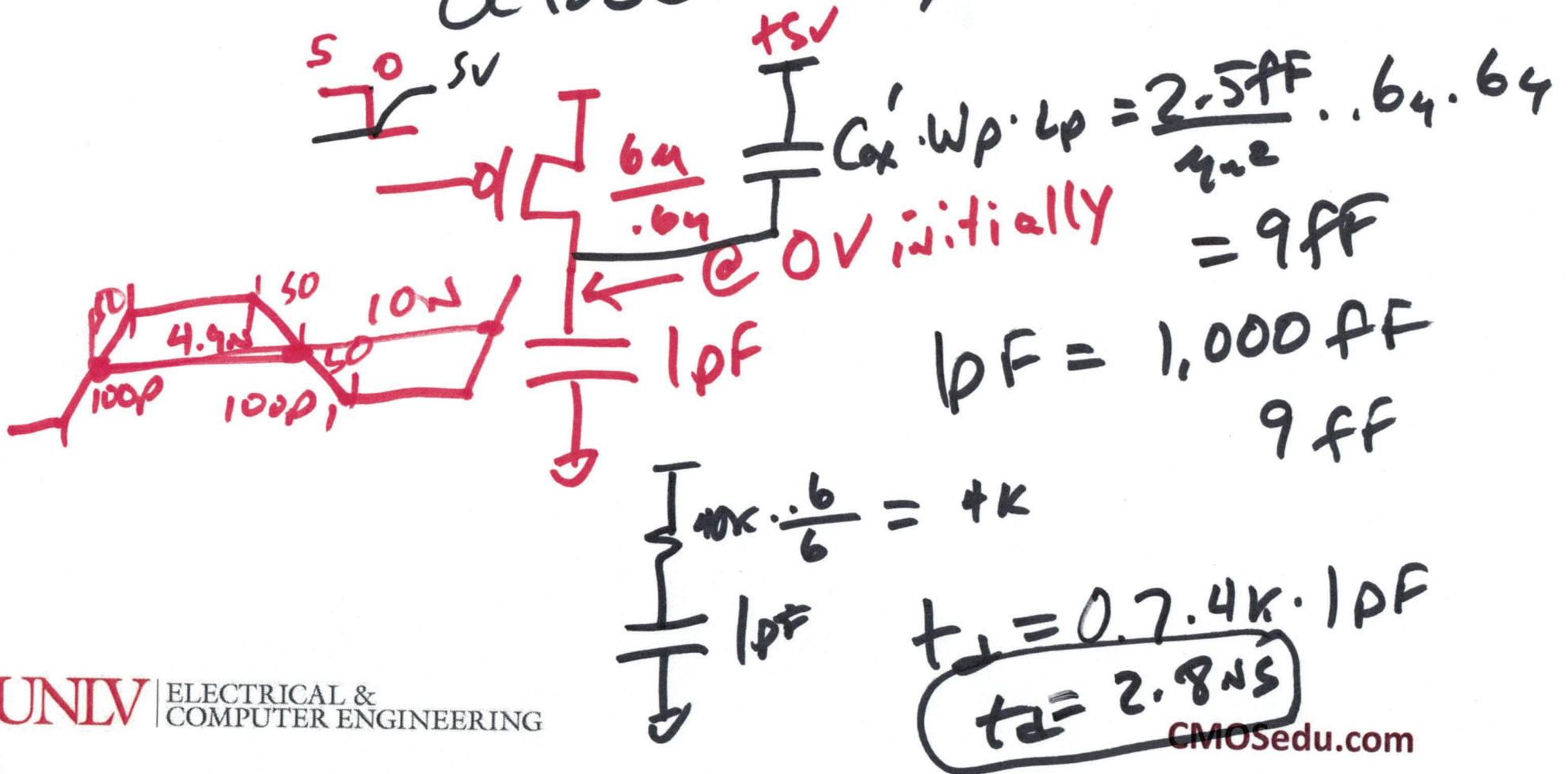


EE 421 / ECG 621

Digital IC Design


Lecture 17

October 30, 2023



$K_{PN} = \mu_{n1} C_{ox}$

$V_{SP} = \text{Switching Point}$

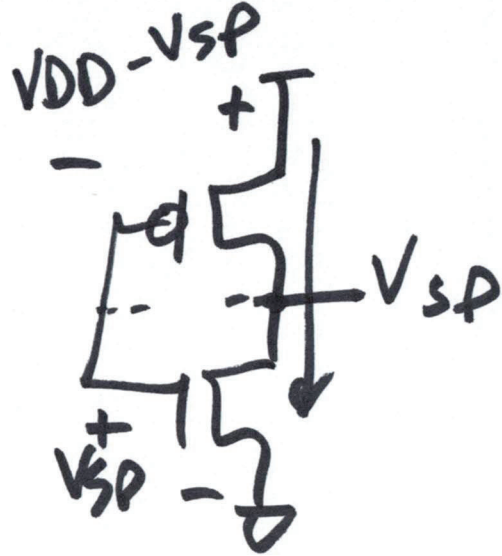

$$\frac{K_{PN}}{2} \frac{W_N}{L_N} (V_{SP} - V_{THN})^2 =$$

$$\frac{K_{PP}}{2} \frac{W_P}{L_P} (V_{DD} - V_{SP} - V_{THP})^2$$

$$\sqrt{\frac{\beta_N}{2}} (V_{SP} - V_{THN}) =$$


$$\sqrt{\frac{\beta_P}{2}} (V_{DD} - V_{SP} - V_{THP})$$

$$V_{SP} \left(\sqrt{\frac{\beta_N}{2}} + \sqrt{\frac{\beta_P}{2}} \right) = \sqrt{\frac{\beta_N}{2}} V_{THN}$$

$$+ \sqrt{\frac{\beta_P}{2}} (V_{DD} - V_{THP})$$

$$\beta_N = K_{PN} \cdot \frac{W_N}{L_N}$$
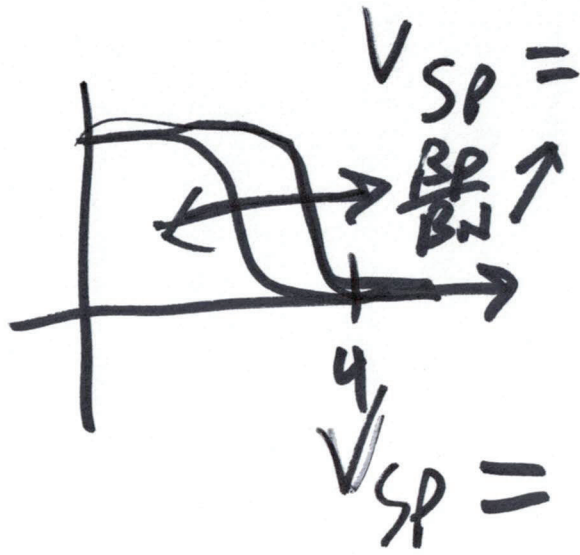
$$\beta_P = K_{PP} \cdot \frac{W_P}{L_P}$$






$$\frac{\sqrt{\frac{\beta_n}{2}} V_{THN} + \sqrt{\frac{\beta_p}{2}} (V_{DD} - V_{THP})}{\sqrt{\frac{\beta_n}{2}} + \sqrt{\frac{\beta_p}{2}}}$$



$$\frac{V_{THN} + \sqrt{\frac{\beta_p}{\beta_n}} (V_{DD} - V_{THP})}{1 + \sqrt{\frac{\beta_p}{\beta_n}}}$$

$\beta_p \Rightarrow \beta_n$
 $V_{SP} \approx V_{DD} - V_{THP}$

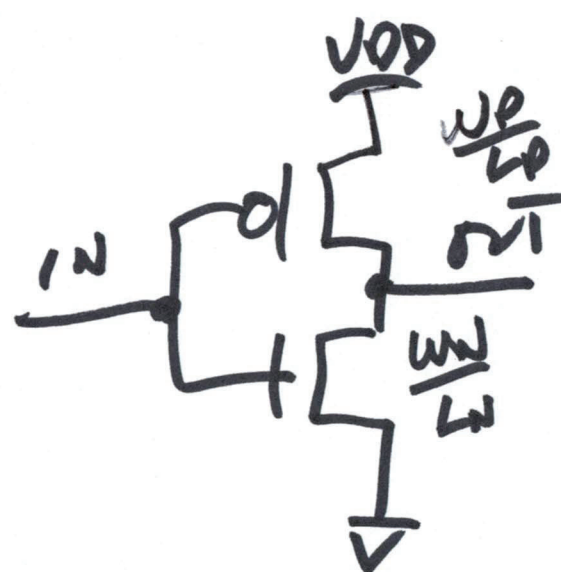$\beta_p = \frac{W_p}{L_p} \cdot K_{PP}$
 $= \frac{W_p}{L_p} \cdot \mu_p \cdot C_{ox}$
 $\beta_n \Rightarrow \beta_p$
 $V_{SP} \Rightarrow V_{THN}$




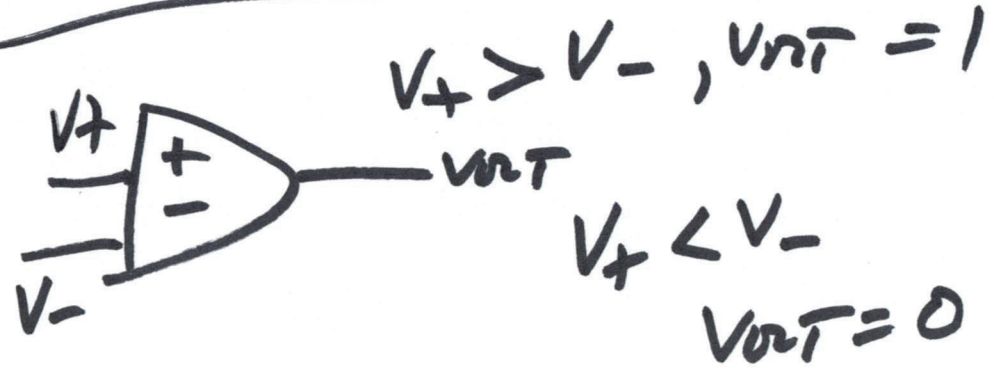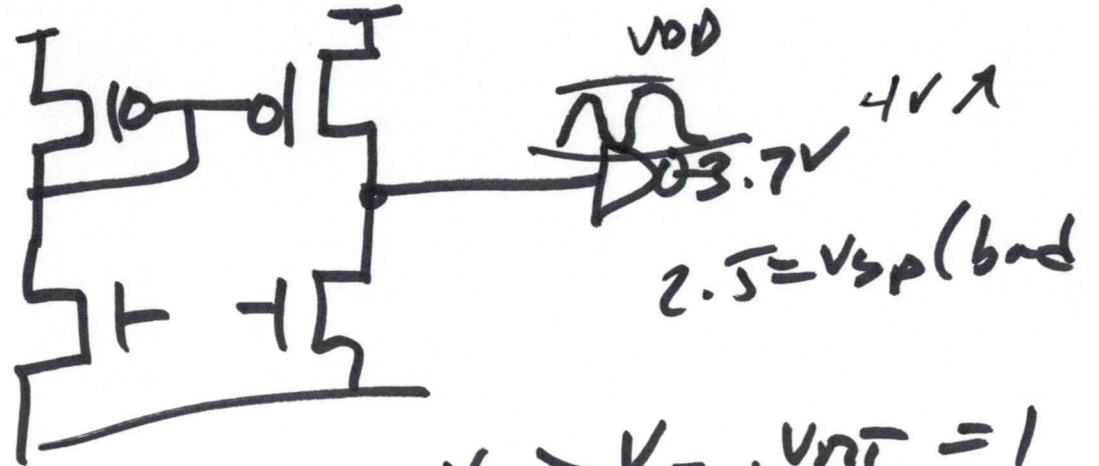

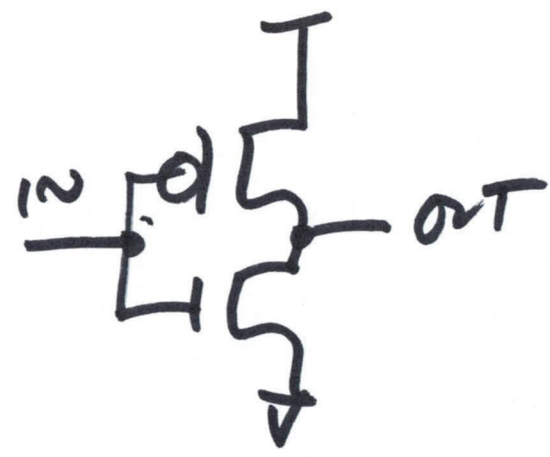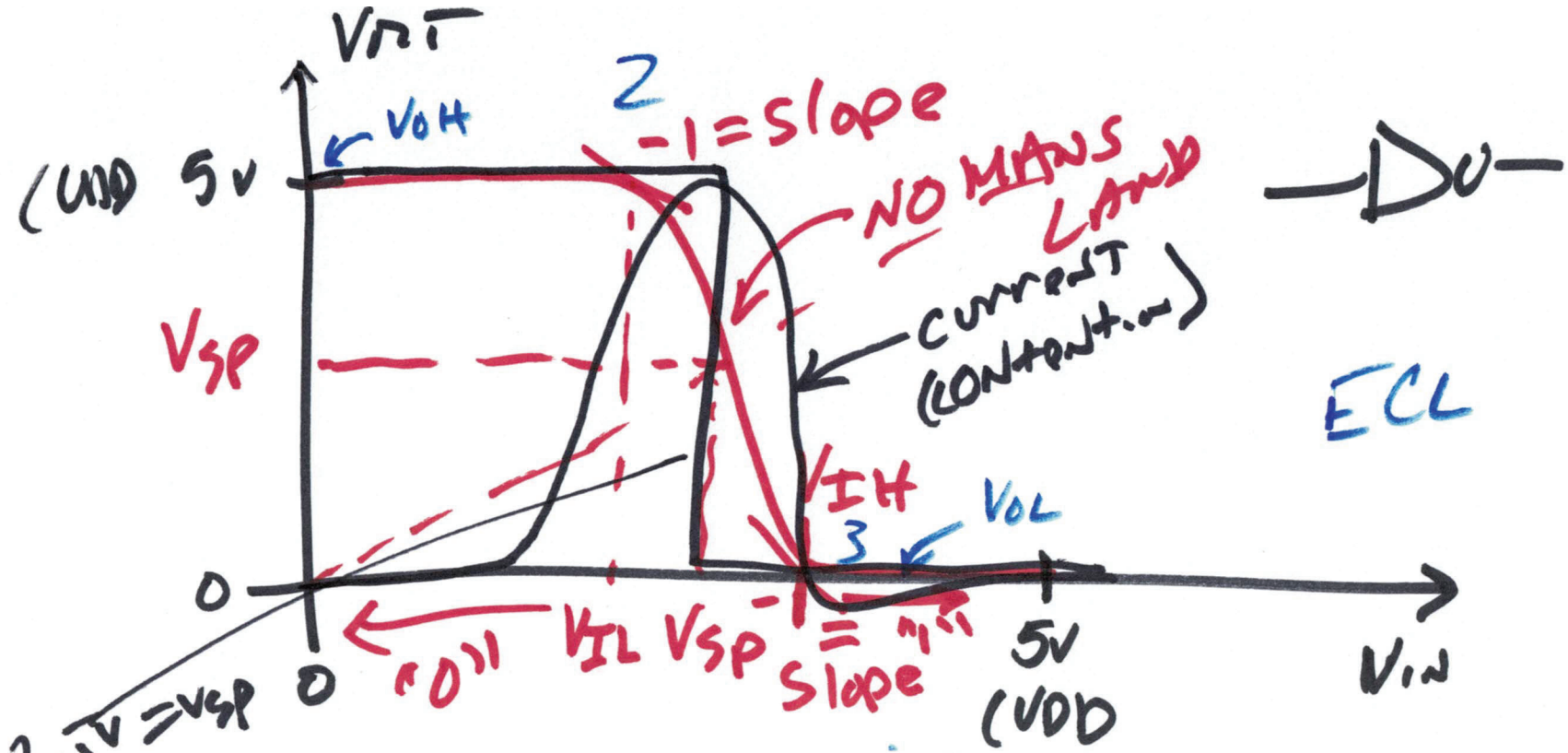

Noise Margin
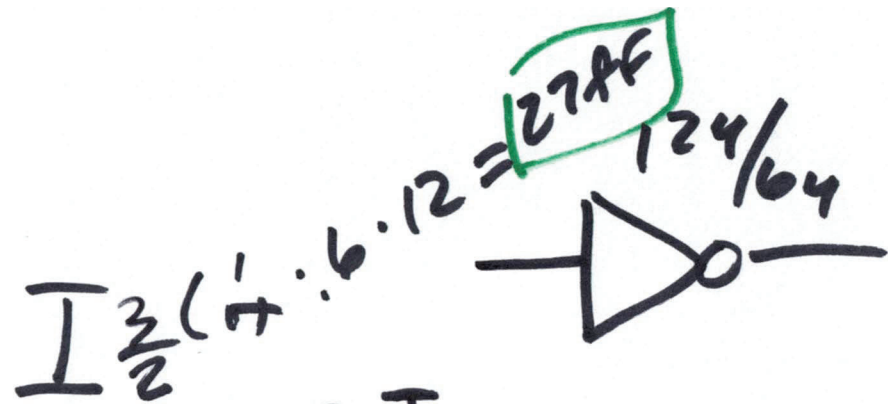
$$\begin{aligned}
 NMH &= V_{OH} - V_{IH} \\
 NMH &= 5 - 3 = 2V \\
 NML &= V_{IL} - V_{OL} \\
 NML &= 2 - 0 = 2
 \end{aligned}$$





$$R_n = R_p = 20k \cdot \frac{6}{6} = 40k \cdot \frac{6}{12} = 2k$$

$C_{ox} \cdot L_p \cdot W_p = \frac{2.5 \text{ fF}}{\mu\text{m}^2} \cdot 6 \cdot 124 = 18 \text{ fF}$

$C_{ox} \cdot L_n \cdot W_n = \frac{2.5 \text{ fF}}{\mu\text{m}^2} \cdot 64 \cdot 64 = 9 \text{ fF}$

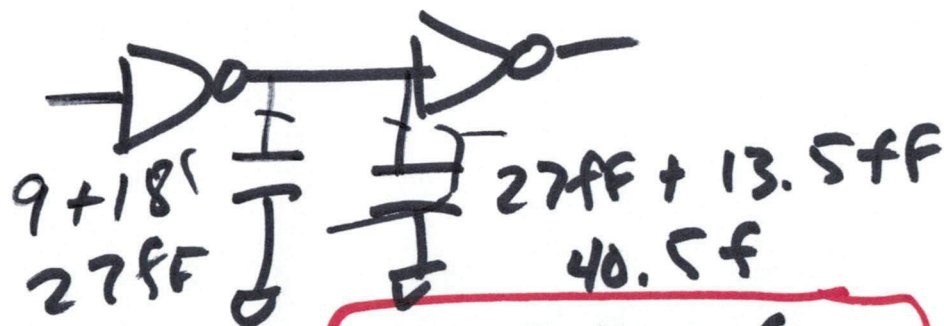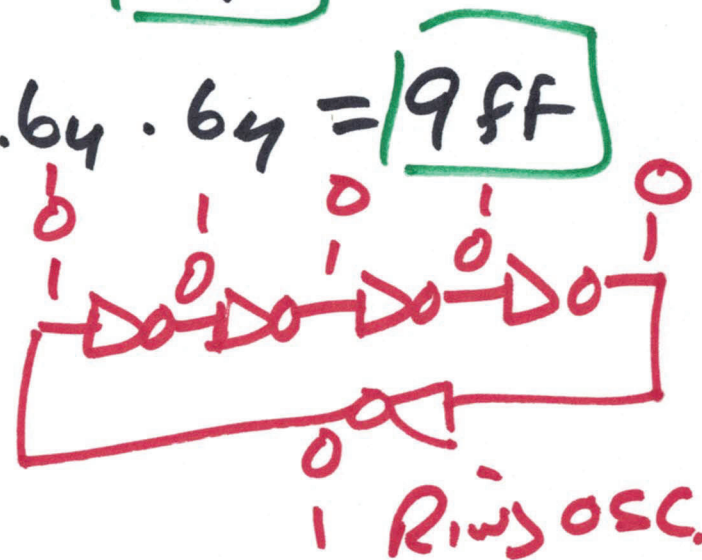$\frac{3}{2} C_{ox} \cdot L_n \cdot W_n = 13.5 \text{ fF}$



$67.5 \text{ fF} = C_{PT}$

6)