


EE 421 / ECE 621


Digital IC Design

NOVEMBER 6, 2023

Lecture 19


$$V_{out} = D \cdot V_{DD}$$

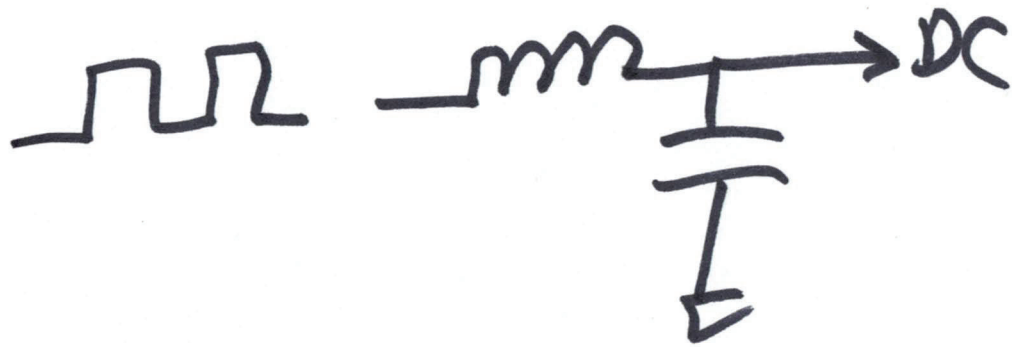

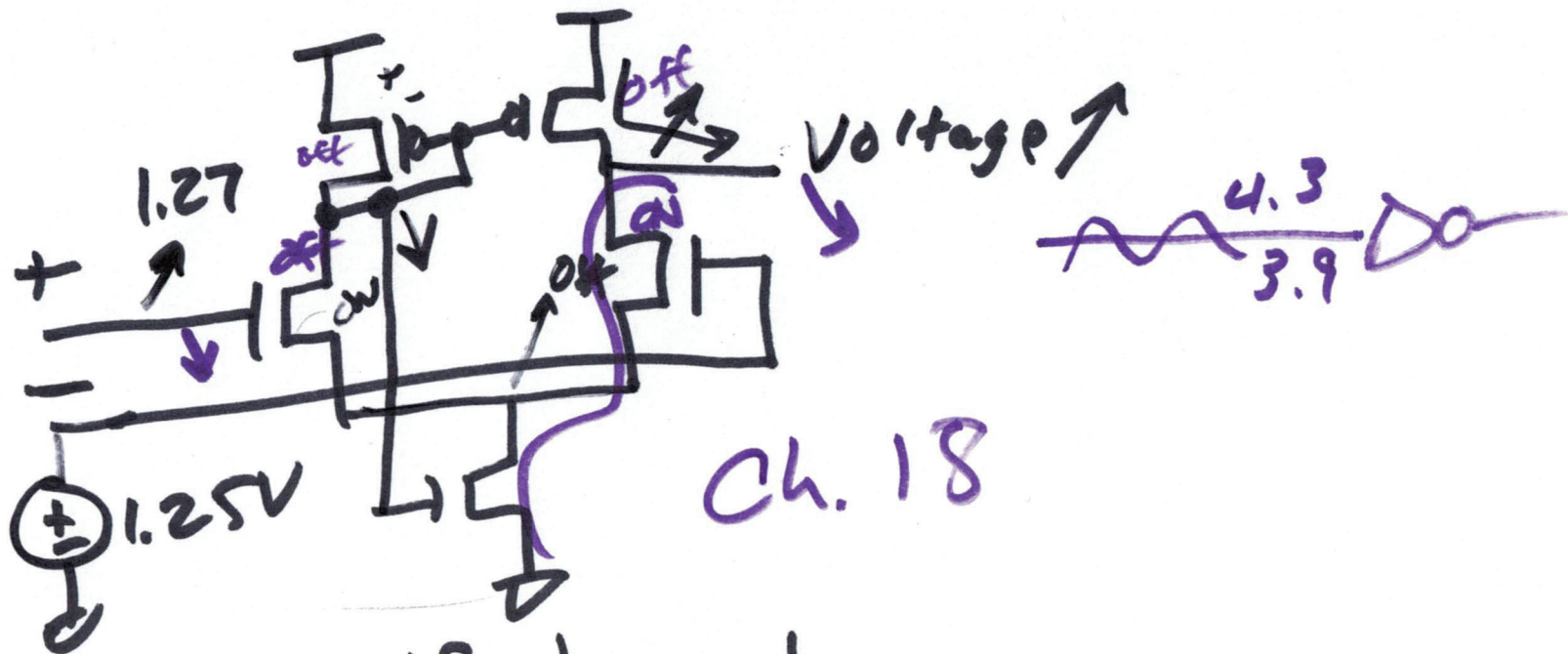

Self-biased  
diff-AMP

Ch. 18

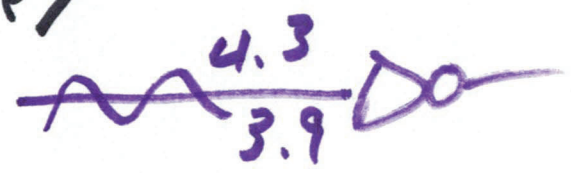

2)