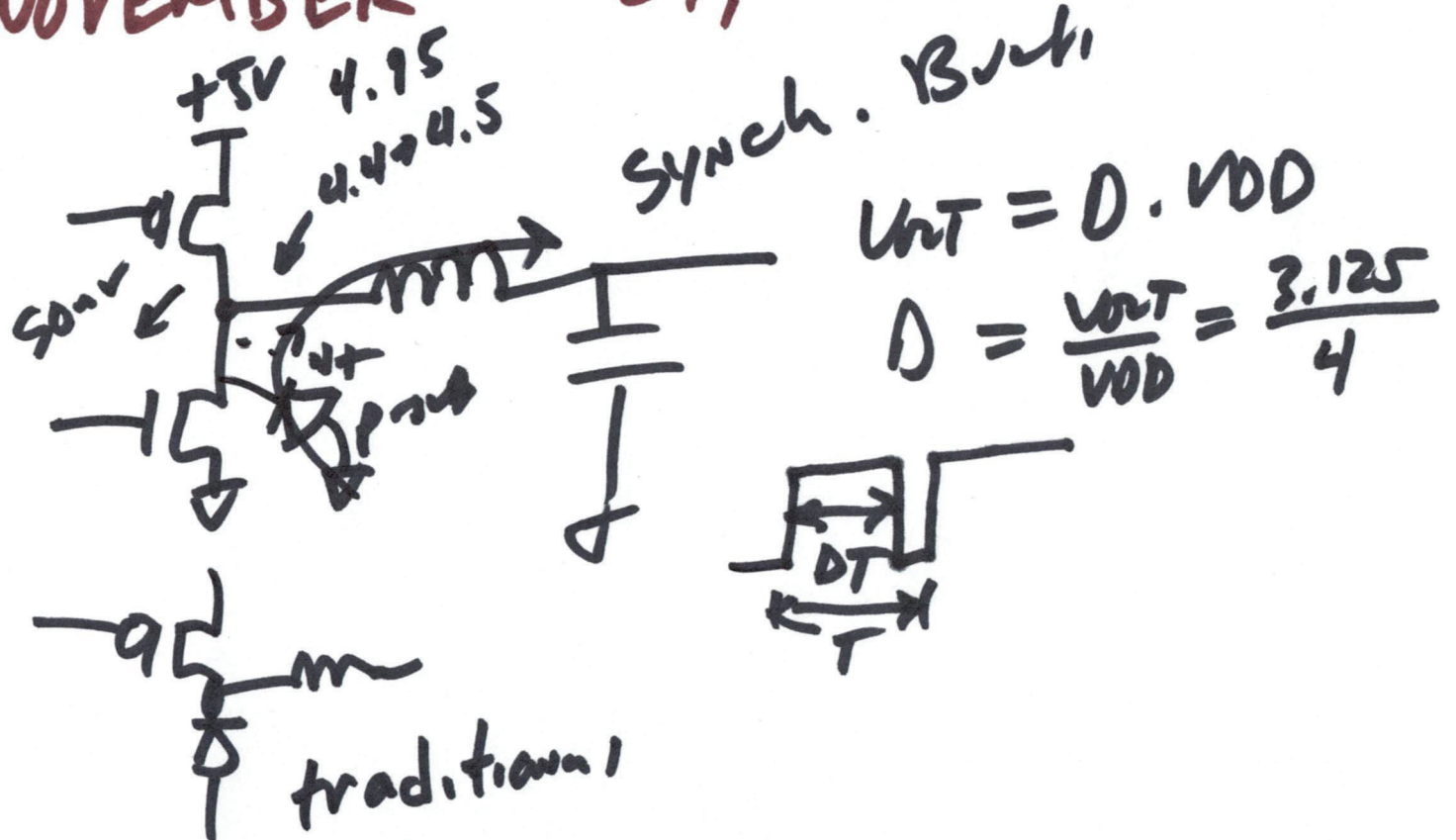




EE 421 / ECG 621

# Digital IC Design

## Lecture 24

NOVEMBER 27, 2023



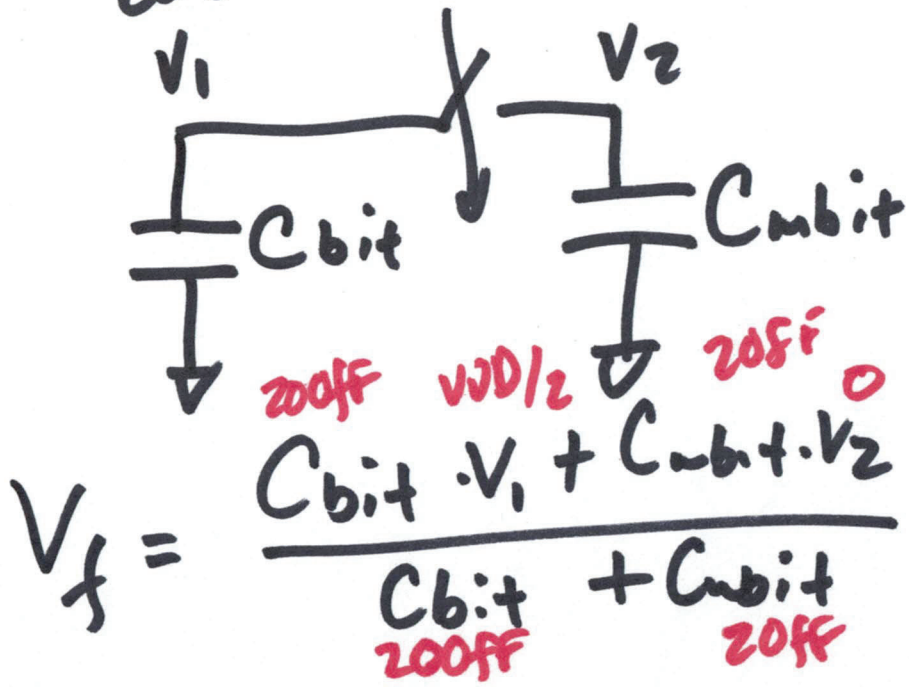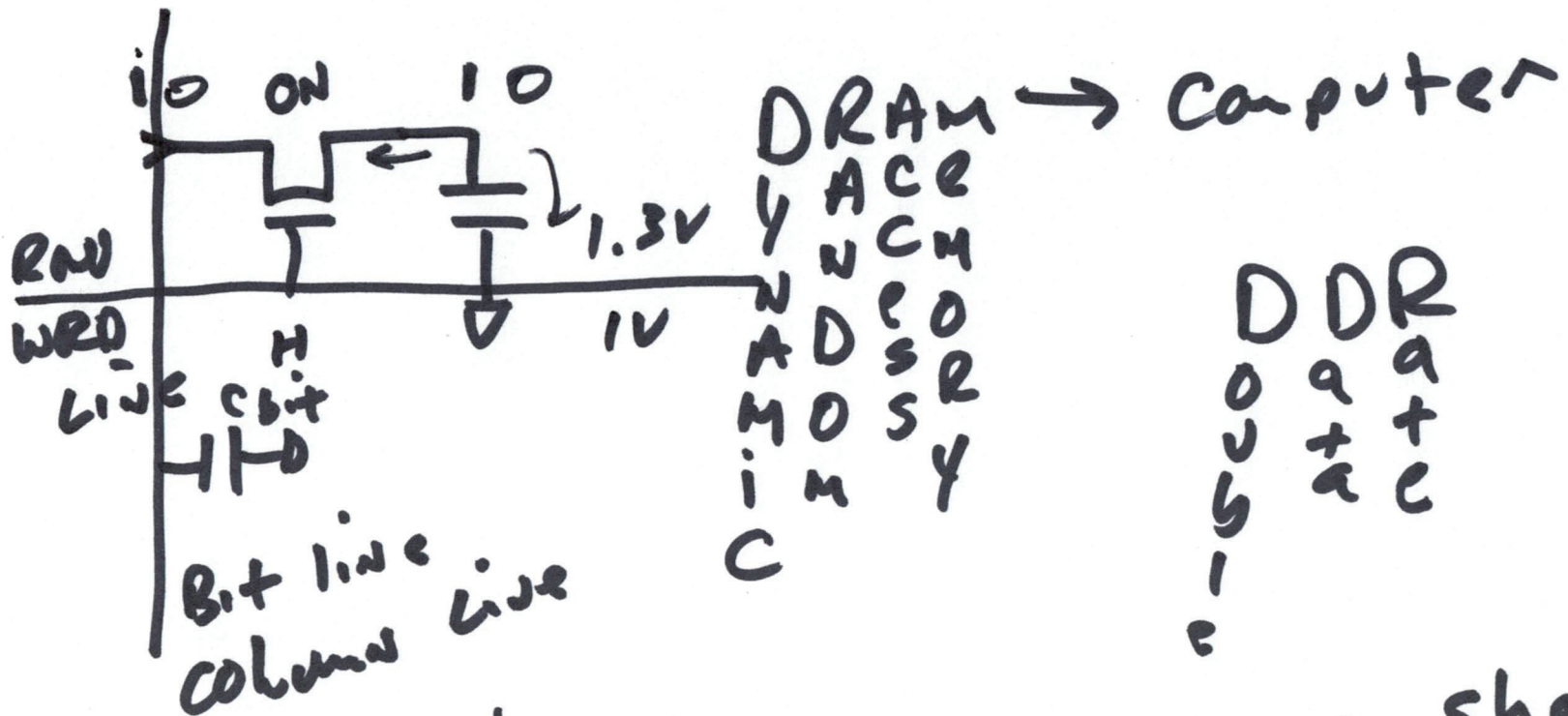


Charge sharing

$$CV = Q$$


$$C_{bit} \cdot V_1 + C_{bit} \cdot V_2 = V_f (C_{bit} + C_{bit})$$

$$V_f = \frac{C_{bit} \cdot V_1 + C_{bit} \cdot V_2}{C_{bit} + C_{bit}}$$

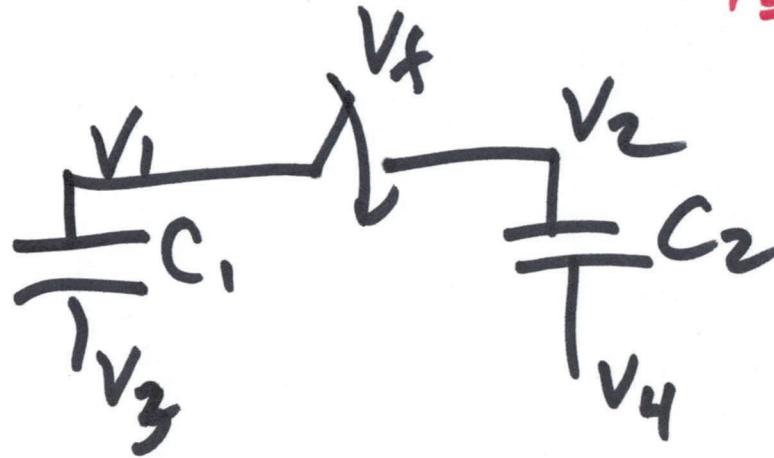$\frac{200}{220} \cdot \frac{VDD}{2}$   
 $\downarrow \frac{1}{2} V$   
 $\frac{1}{2}$   $\uparrow$   $46 \mu V$   
 $454 \mu V$


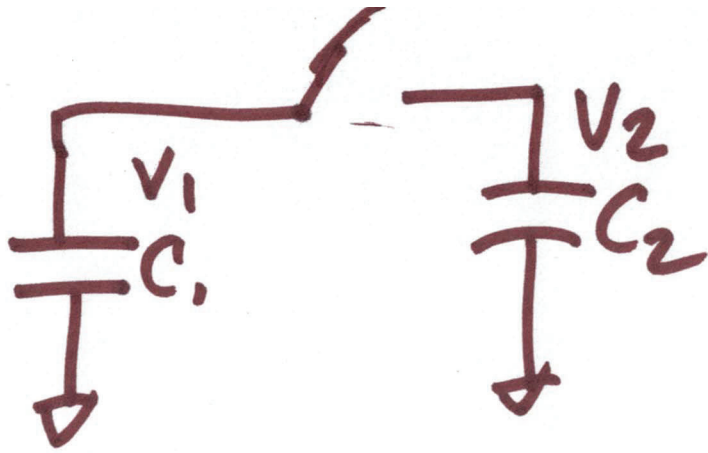
$$C_1(V_1 - V_3) + C_2(V_2 - V_4) = C_1(V_f - V_3) + C_2(V_f - V_4)$$



$$\Sigma = \frac{1}{2} C V^2$$

$$\frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 = \frac{1}{2} (C_1 + C_2) \cdot \left( \frac{V_1 C_1 + V_2 C_2}{C_1 + C_2} \right)^2$$

$$V_f = \frac{V_1 C_1 + V_2 C_2}{C_1 + C_2}$$

$$= \frac{1}{2} \frac{(V_1 C_1 + V_2 C_2)^2}{C_1 + C_2}$$

