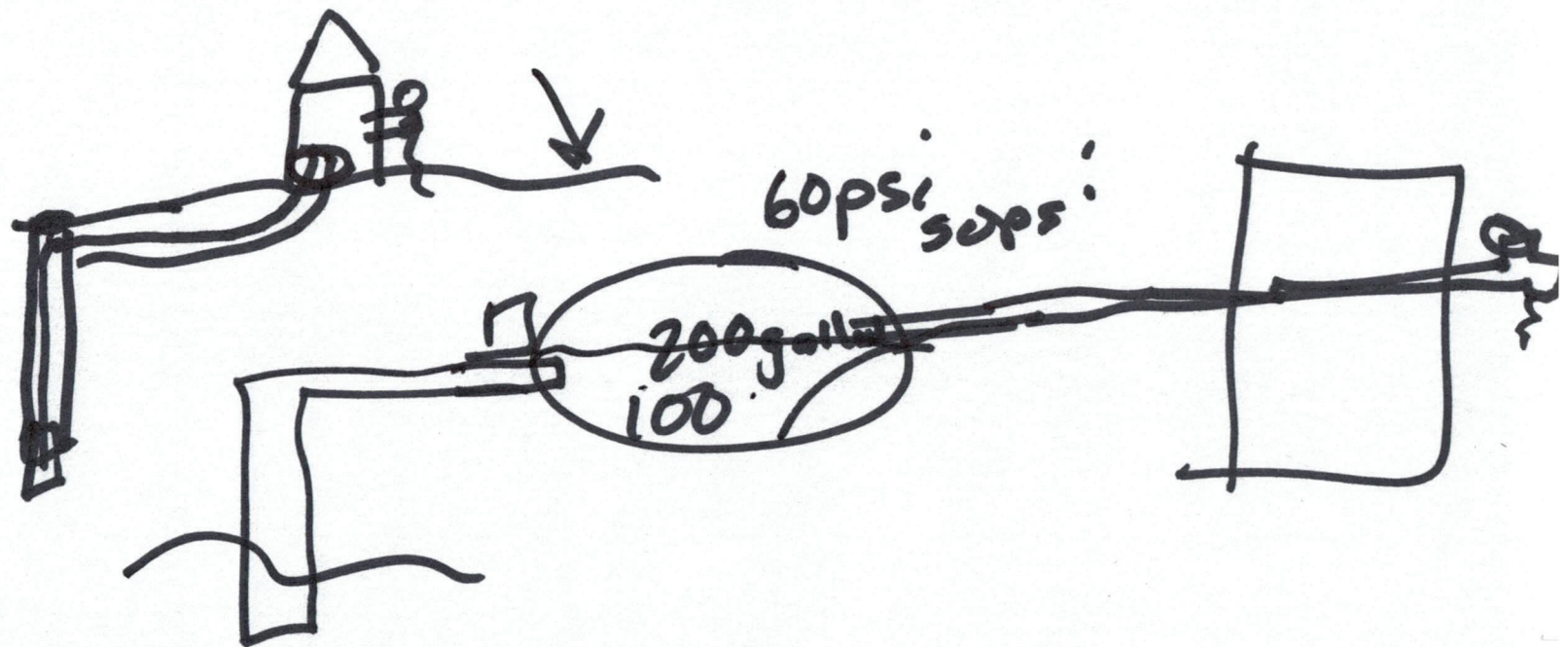



EE 421/ECG 621

Digital IC Design


September 18, 2023

Lecture 6




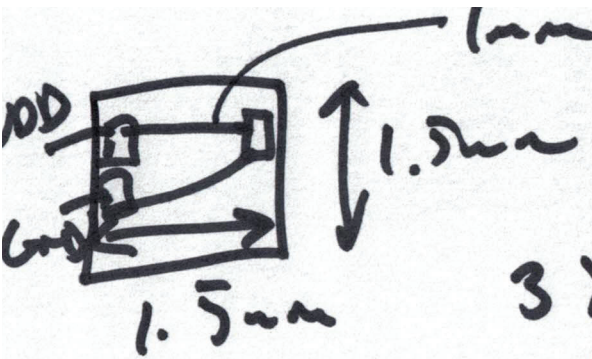

PDN
 POWER NETWORK
 REVIEW

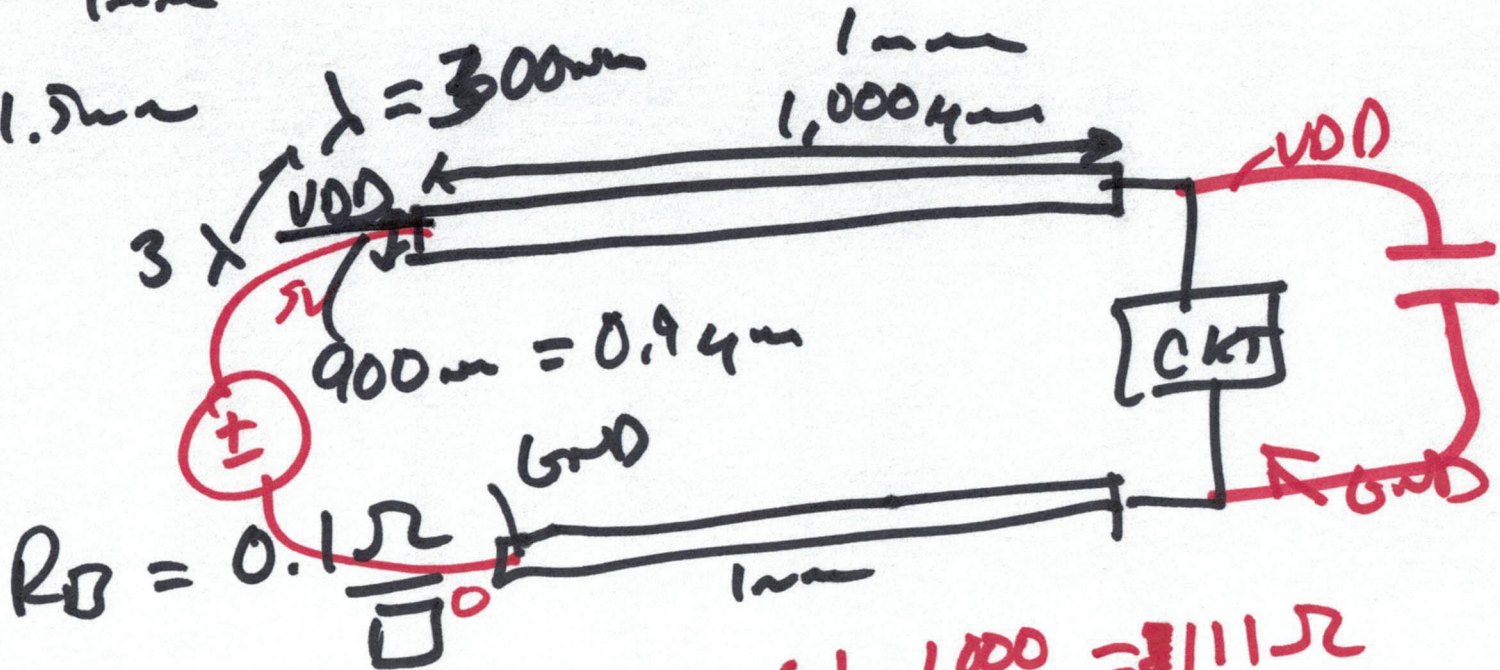

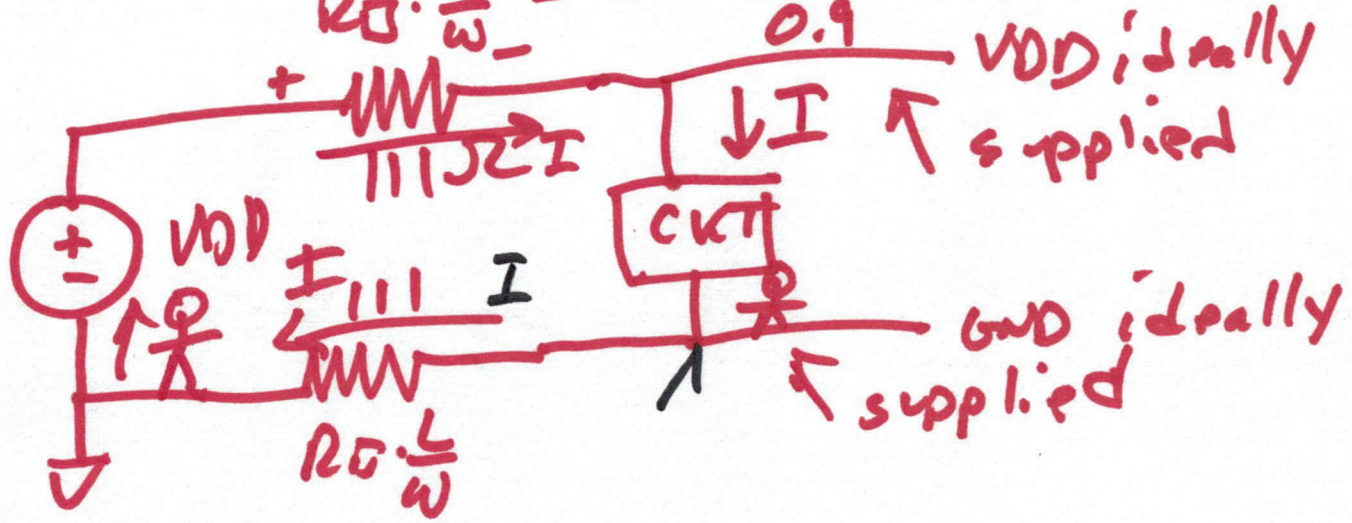
$$R_0 \cdot \frac{L}{w} = 0.1 \cdot \frac{1,000}{0.9} = 111 \Omega$$



$$+V_{DD} - I \cdot R_D \cdot \frac{L}{W} = V_{DD} |_{\text{supplied}}$$

$$R_D \cdot \frac{L}{W} \cdot I = GND |_{\text{supplied}}$$

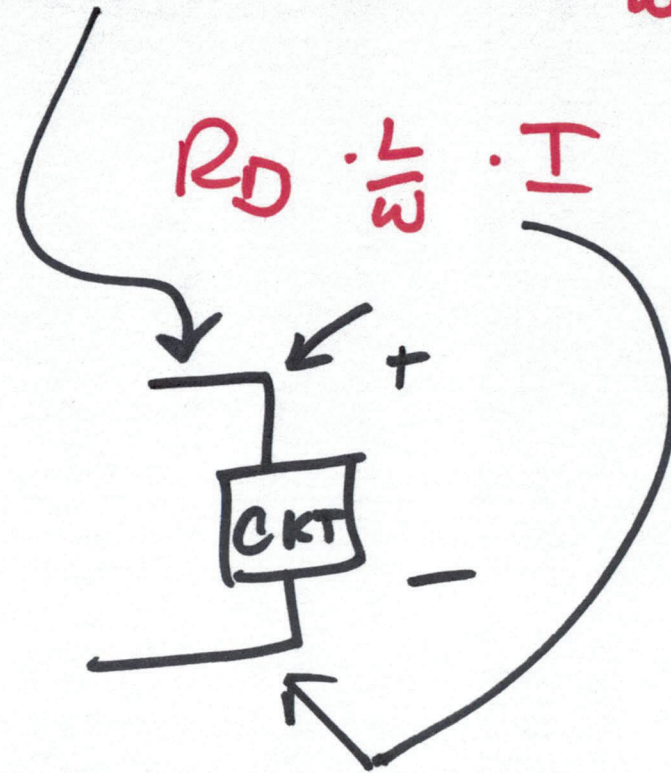

$$V_{DD} - I R_D \frac{L}{W} - R_D \frac{L}{W} \cdot I$$

Voltage across CKT



$$= V_{DD} - 2I \cdot R_D \cdot \frac{L}{W}$$

3)

I/O 1 Gbit/s


$$Cv = Q$$

$$I = C \frac{dV}{dt}$$

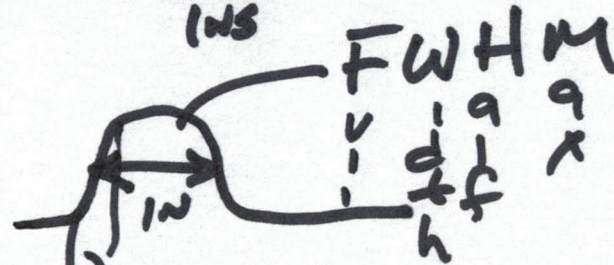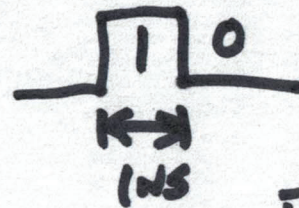


100ps = rise time

$$I = C \frac{dV}{dt}$$

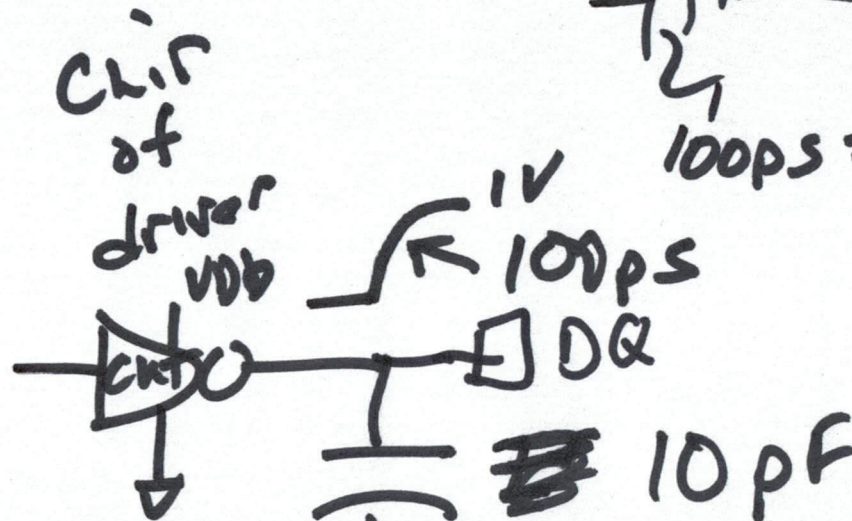


$$= 10\text{pF} \cdot \frac{1\text{V}}{100\text{ps}}$$
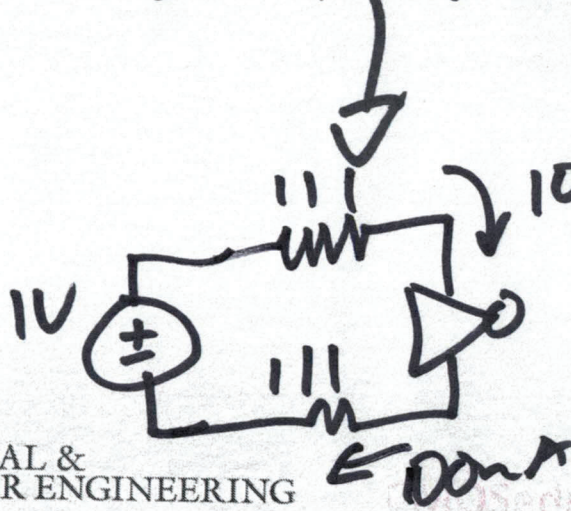
$$= \frac{1\text{V} \cdot 10^{-12}\text{F}}{10^{-10}\text{s}} = 100\text{ nA}$$



4)

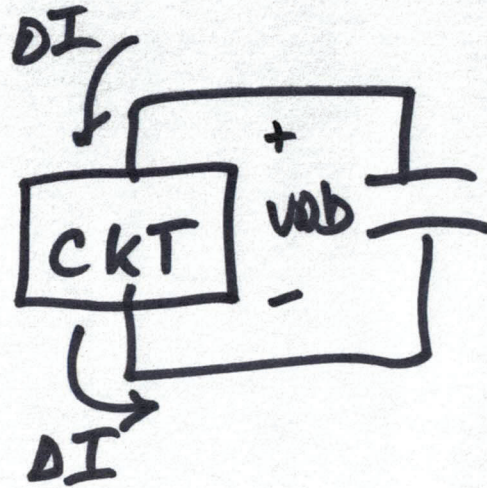

$$\Delta I = C \frac{\Delta V_{DD}}{\Delta t}$$

$$\Delta V_{DD} = \frac{\Delta I \cdot \Delta t}{C}$$

$\Delta V_{DD} \rightarrow \Delta I_{DD}$

