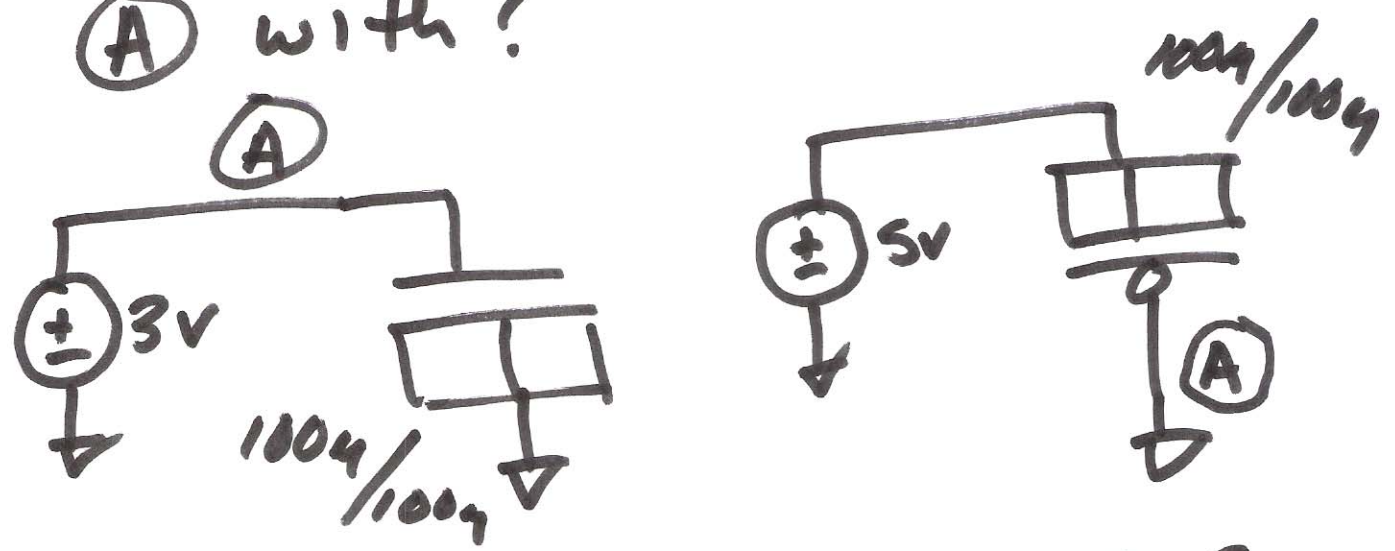


H.W. #1 EE 422, ECG 622

Use the long channel MOSFETS from the book. Verify hand calcs with simulations.

1) What is the capacitance each MOSFET loads node (A) with?



2) Show the rise time across C can be calculated using $2.2RC$.

