
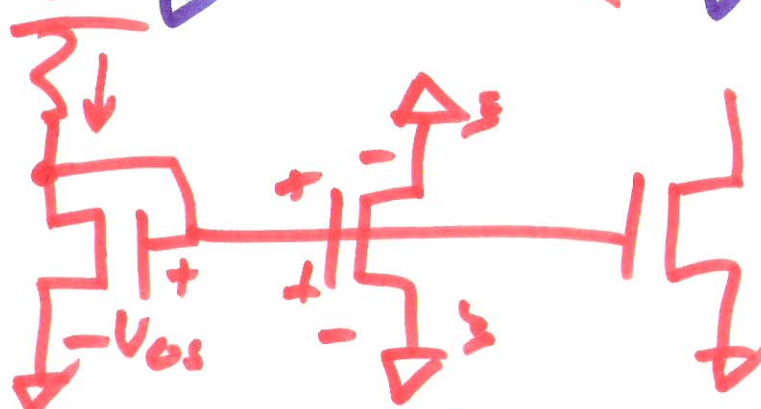


EE 422 / ECG 622



Analog IC Design


Lecture 10 2/25/13

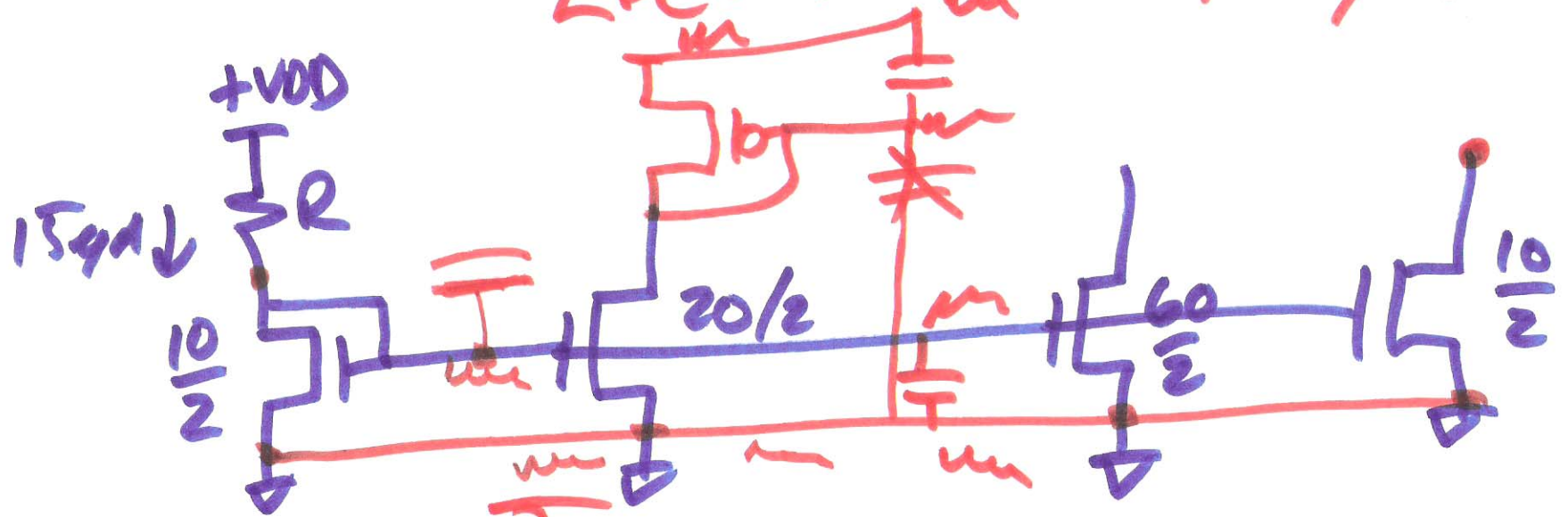

$$C_{ox} \cdot W \cdot L$$
$$\frac{E_{ox}}{t_{ox}}$$


1)

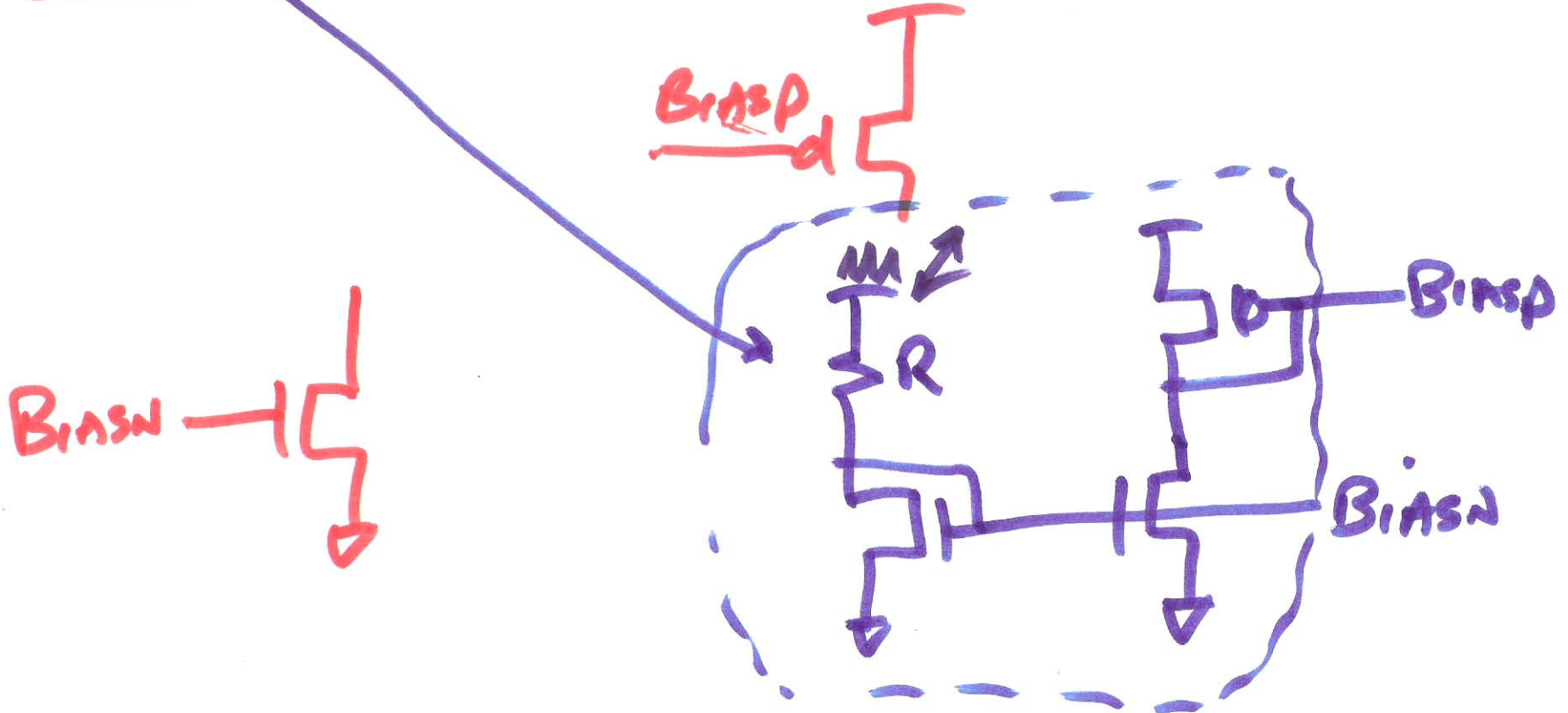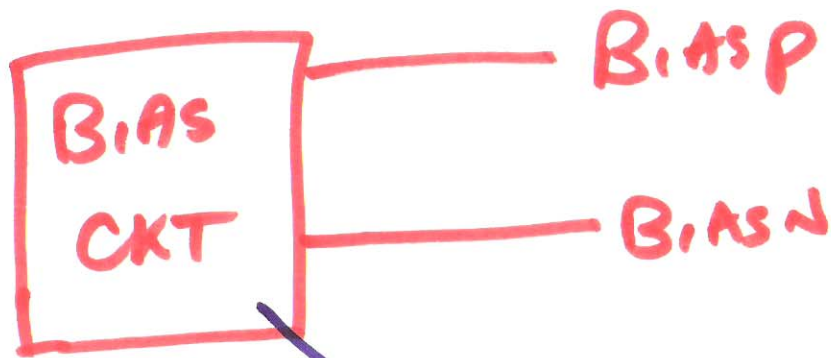

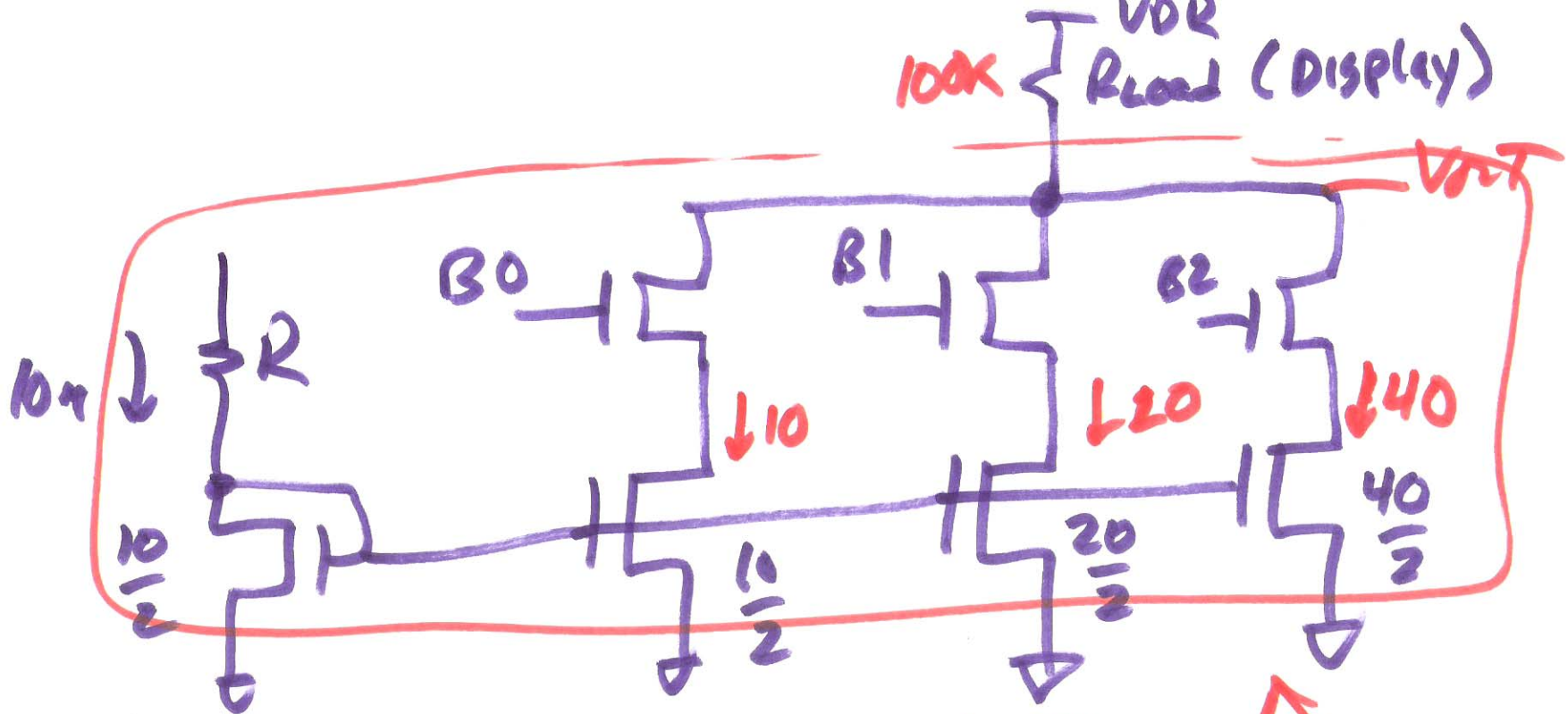

B0	B1	B2	V _{out}	I
0	0	0	5V	0
1	0	0	4V	10 μ
0	1	0	3V	20 μ

Digital to Analog Converter (DAC)

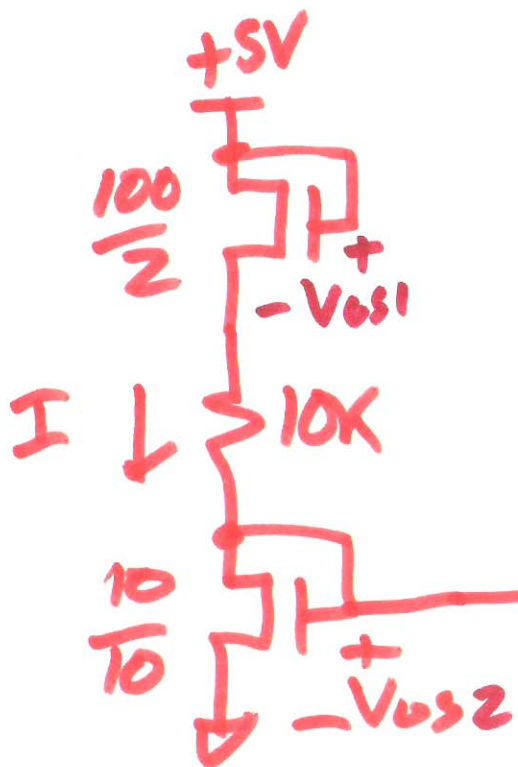

$$5 - V_{GS1} - I \cdot 10K - V_{GS2} = 0$$

$$I = \frac{\beta_1}{2} (V_{GS1} - V_{THN})^2 =$$

$$\frac{\beta_2}{2} (V_{GS2} - V_{THN})^2$$


$$V_{GS} = \sqrt{\frac{2I}{\beta_1}} + V_{THN}$$

$I = ?$ $V_{GS2} = ?$


$$5 - \sqrt{\frac{2I}{\mu A/V \cdot \frac{100}{2}}} - V_{THN} - I \cdot 100K - \sqrt{\frac{2I}{\mu A/V \cdot \frac{10}{10}}} - V_{THN} = 0$$

$$(a + b\sqrt{x} + cx)^2 - \sqrt{\frac{2I}{\mu A/V}} \left(\sqrt{\frac{2}{100}} + \sqrt{\frac{10}{10}} \right) - I \cdot 10K = 0$$

let $x = \sqrt{I}$

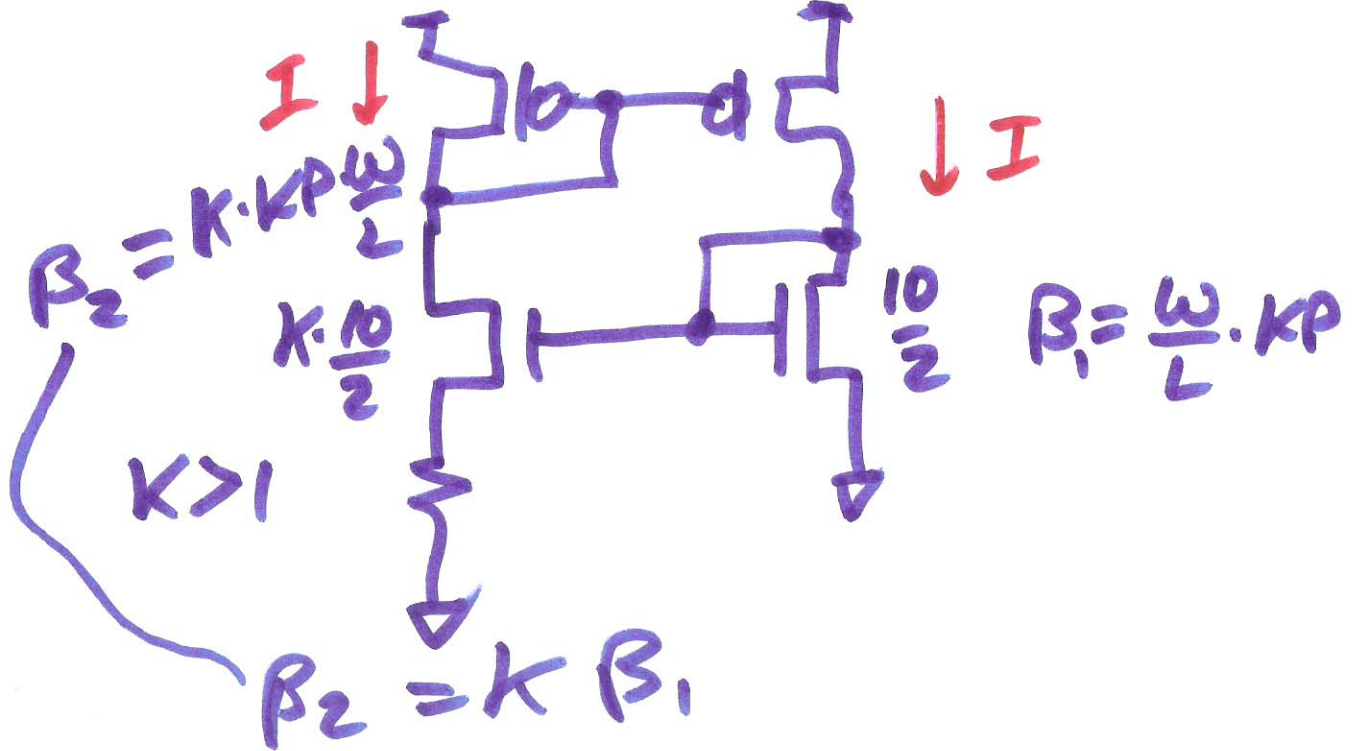


Beta is multiplied up!

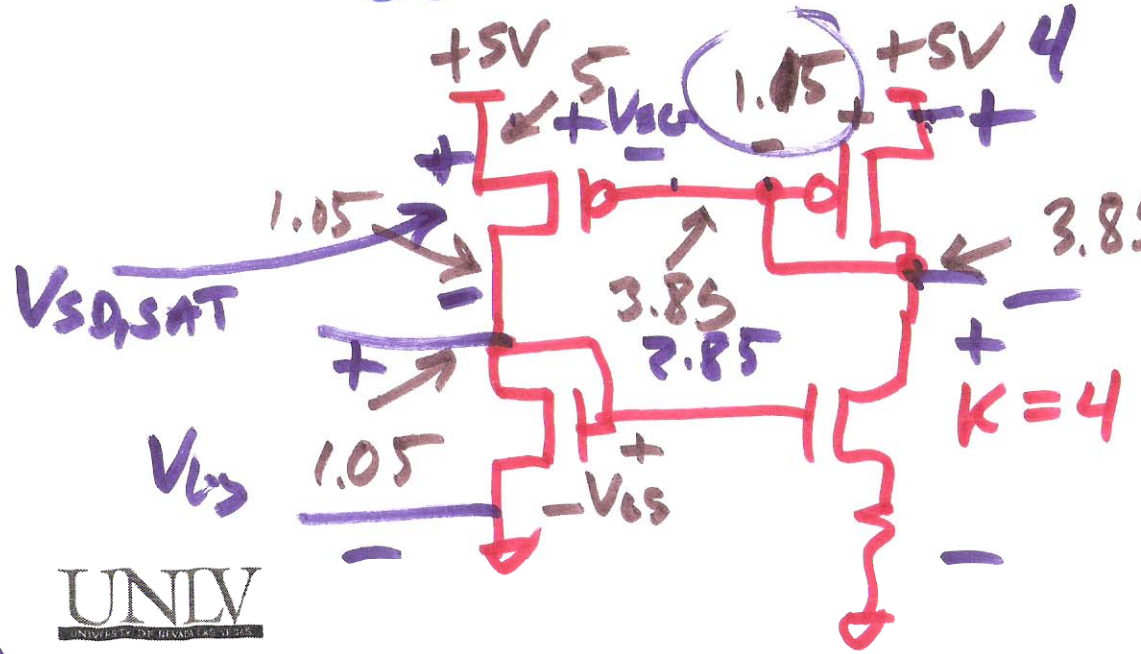

$V_{DD,MIN} = ?$
 $\geq V_{DS,SAT} + V_{GG}$

$V_{DD,MIN} \geq V_{GG} + V_{DS,SAT}$

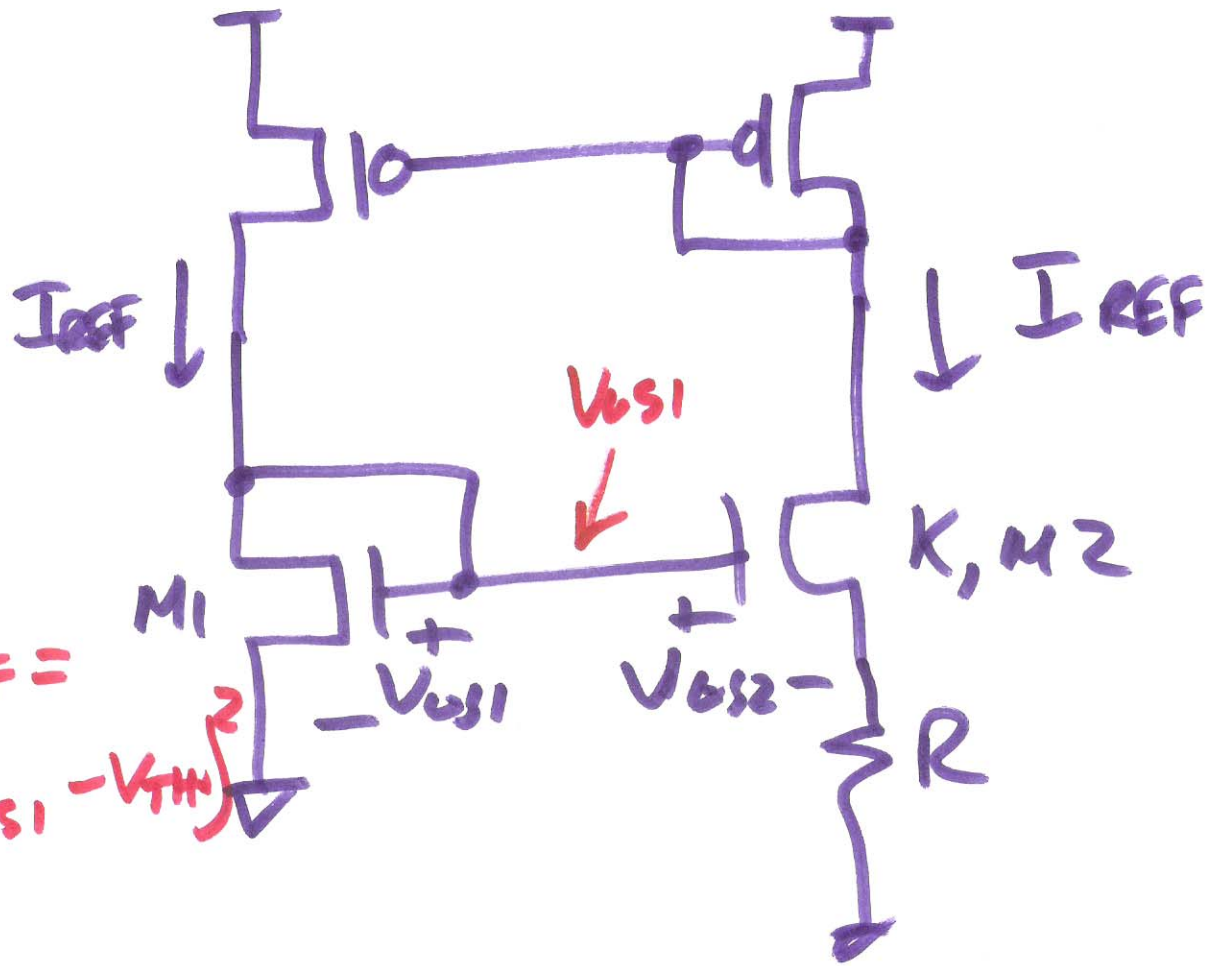

$$I_{REF} = \frac{\beta_1}{2} (V_{GS1} - V_{TH})^2$$

$$V_{GS1} = V_{GS2} + I_{REF} \cdot R$$

$$\approx \sqrt{\frac{2 I_{REF}}{\beta_1}} + V_{TH} = \sqrt{\frac{2 I_{REF}}{K \cdot \beta_1}} + V_{TH} + I_{REF} R$$

$$-I_{REF} \cdot R + \sqrt{\frac{2I_{REF}}{\beta_1}} \left(1 - \frac{1}{\sqrt{K}}\right) = 0$$

$$\sqrt{I_{REF}} \cdot R = \sqrt{\frac{2}{\beta_1}} \left(-\frac{1}{\sqrt{K}} + 1\right)$$

$$I_{REF} = \frac{2}{\beta_1 \cdot R^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

$$\frac{1}{g_m} = \frac{1}{150 \mu A} = R$$

$R = 6.5k$

$$K = 4$$

$$K = 4$$

$$R = \frac{1}{g_m}$$

$$I_{REF} = \frac{1}{2\beta_1 \cdot R^2}$$

$$\frac{1}{R} = \sqrt{2\beta_1 I_{REF}} = g_m$$