


Lecture II

EE 422 ECG 622

March 1, 2013


$$V_{GS} = V_{DS,SAT} + V_{THN}$$

$$V_{DS,SAT} = V_{GS} - V_{THN}$$

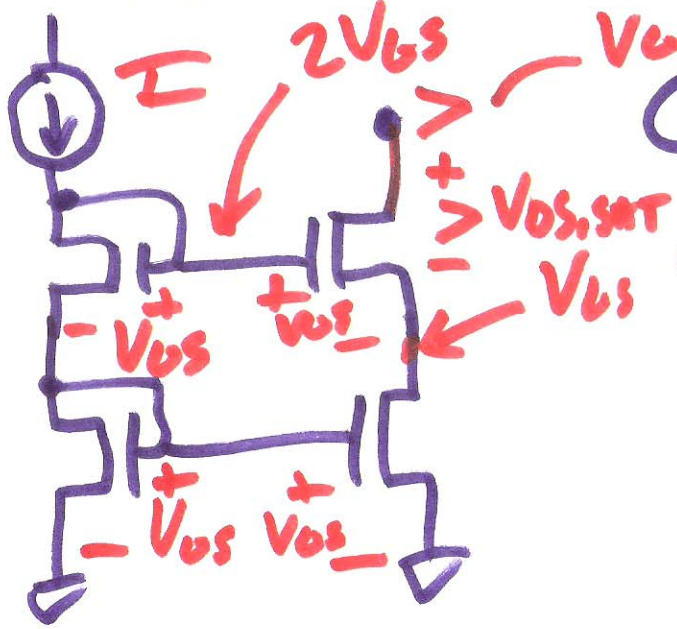


$V_{GS} + V_{DS,SAT}$
CASCODE

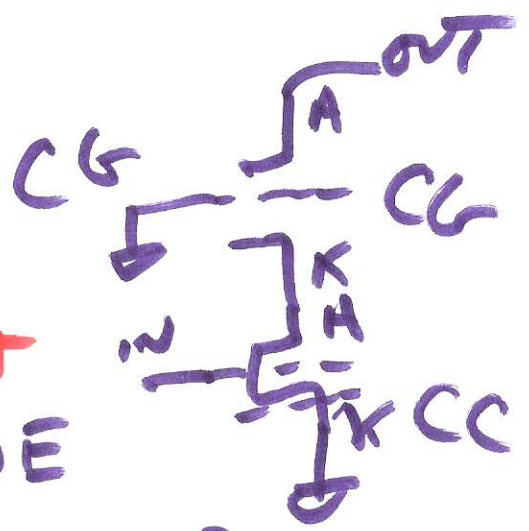cascode of
Common-gate
AND
Common-cathode



1)

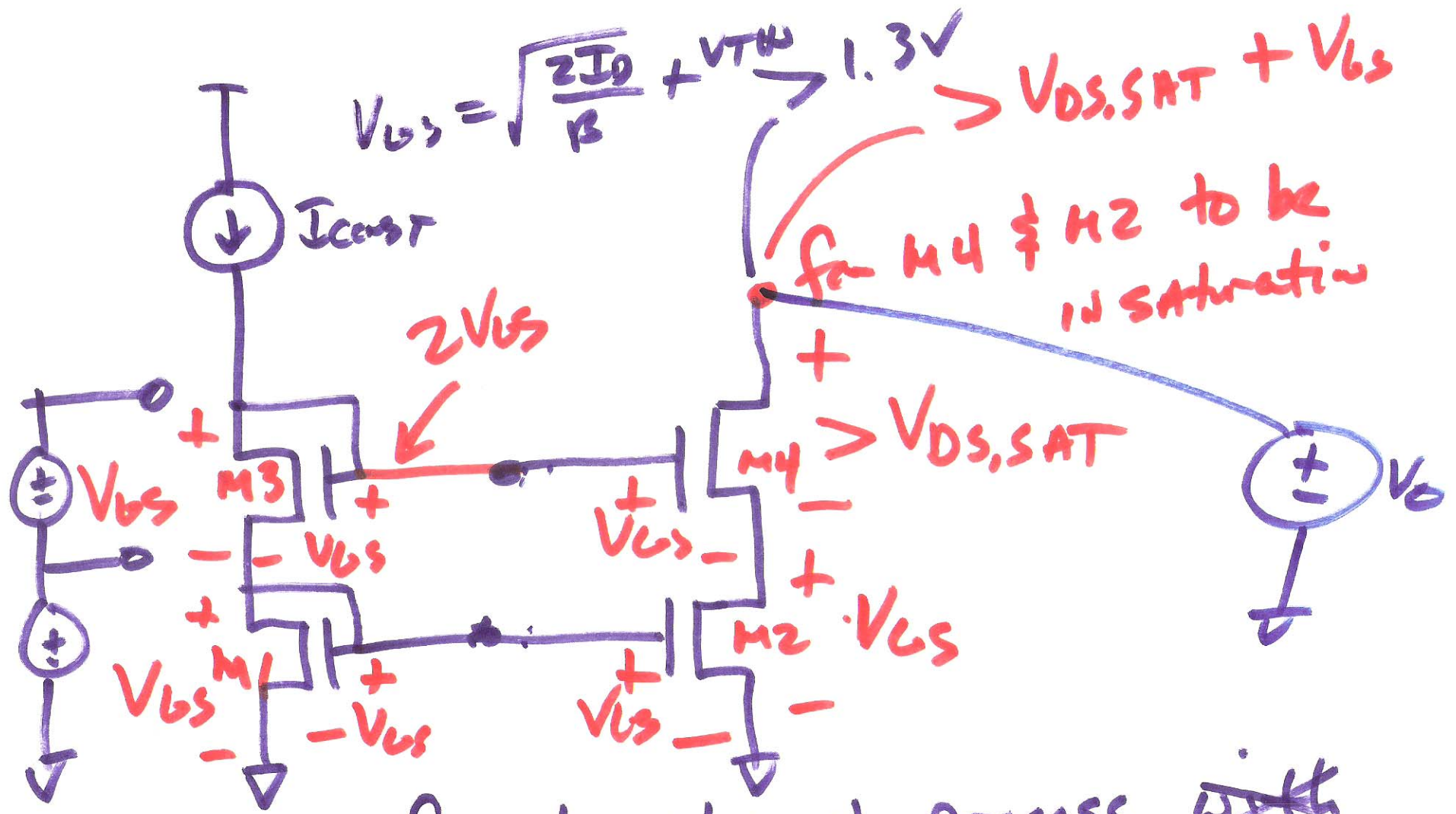


for long channel process ~~with~~
 use TABLE 9.1

$V_{GS} = 1.05$ $V_{THU} = 0.8$
 $V_{DS,SAT} = .25$

2)

START-UP CKT

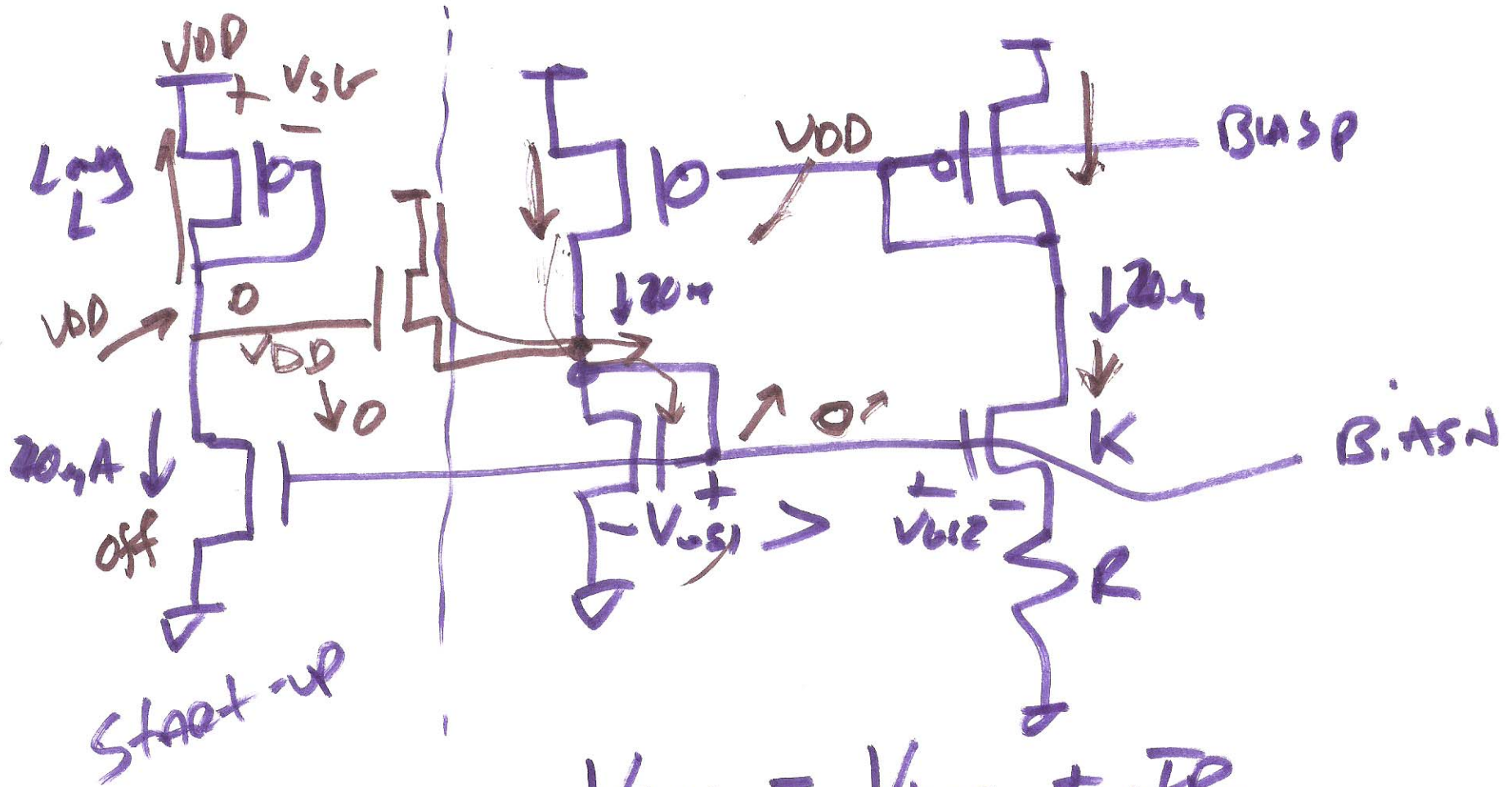

$$V_{S1} = V_{S2} + IR$$

$$V_{S1} = \sqrt{\frac{2I}{\beta}} + V_{TH}$$


$$V_{S2} = \sqrt{\frac{2I}{\beta \cdot K}} + V_{TH}$$

$$\frac{v_A}{v_f} = \frac{1}{1 + K R S^{-1}}$$

$$\frac{v_f}{v_T} = \frac{1/g_{m1}}{R + 1/g_{m2}}$$

$$g_{m1} K = g_{m2}$$
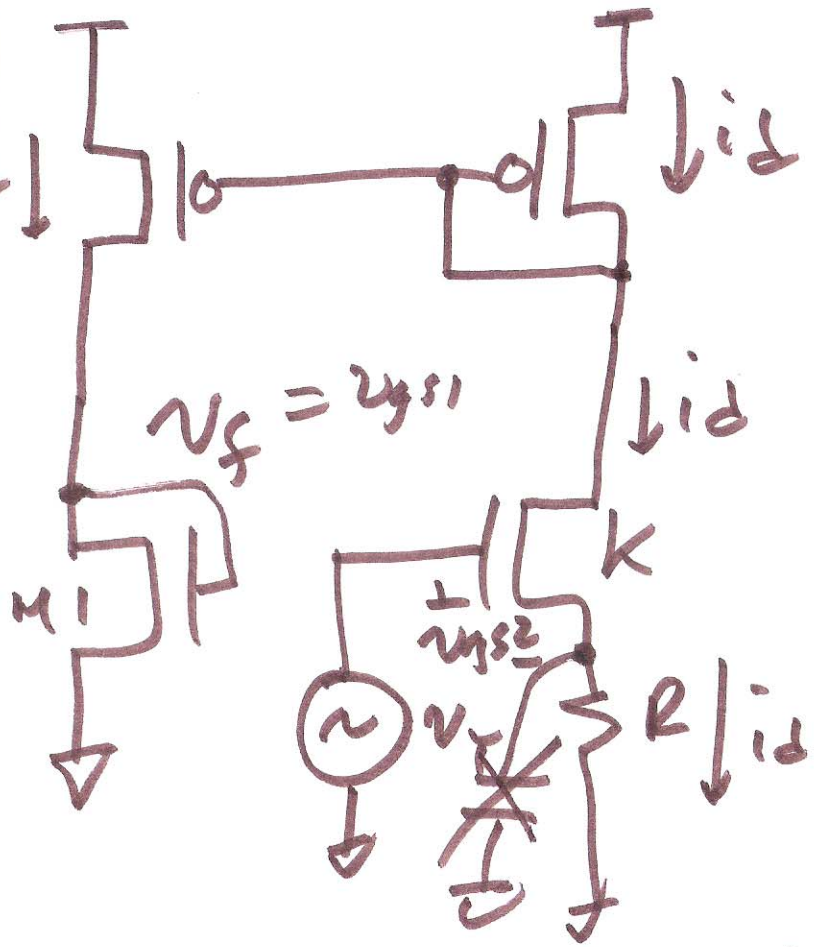
$$i_d = \frac{v_T}{\frac{1}{g_{m2}} + R}$$



$$g_m = \beta \cdot (V_{GS} - V_{TH}) = \sqrt{2\beta I_D}$$

$$g_m v_{gs} = i_d$$

$$\frac{i_d}{v_f} = g_{m1}$$


$$v_f = \frac{i_d}{g_{m1}}$$

$$v_T = v_{gs2} + i_d \cdot R = i_d \left(\frac{1}{g_{m2}} + R \right)$$

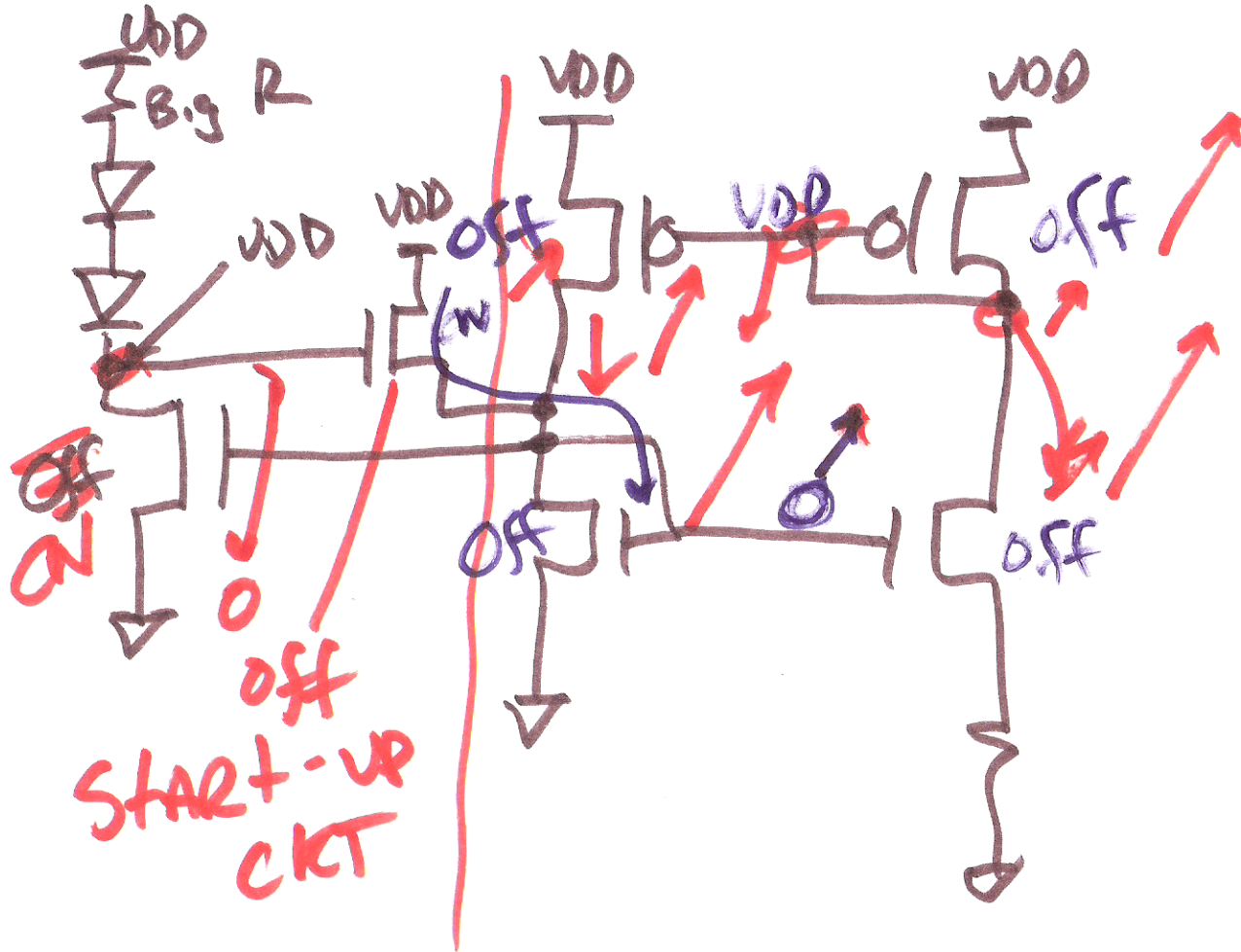4)

$$\begin{aligned}
 \frac{v_f}{v_T} &= \frac{1}{g_{m1} \cdot R + \frac{g_{m1}}{g_{m2}}} \\
 &= \frac{1}{g_{m1} \cdot R + \frac{1}{k}} \\
 &= \frac{1}{1 + k g_{m2} \cdot R} < 1
 \end{aligned}$$

$$\begin{aligned}
 R &\rightarrow 0 \\
 \frac{v_f}{v_T} &\rightarrow 1
 \end{aligned}$$




6)



Wide-swing operation

~~NO~~
 $2V_{DS,SAT} + V_{THN} = V_{GS} + V_{DS,SAT}$

$> 2V_{DS,SAT}$

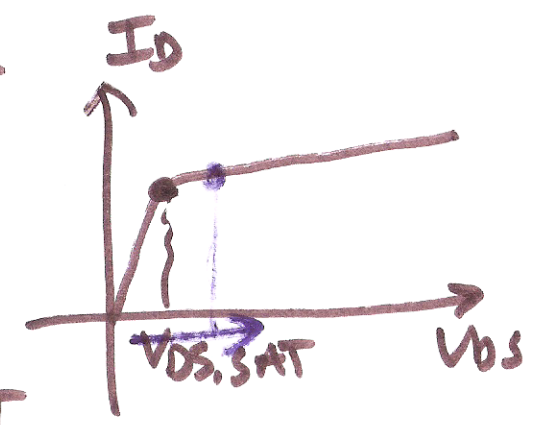
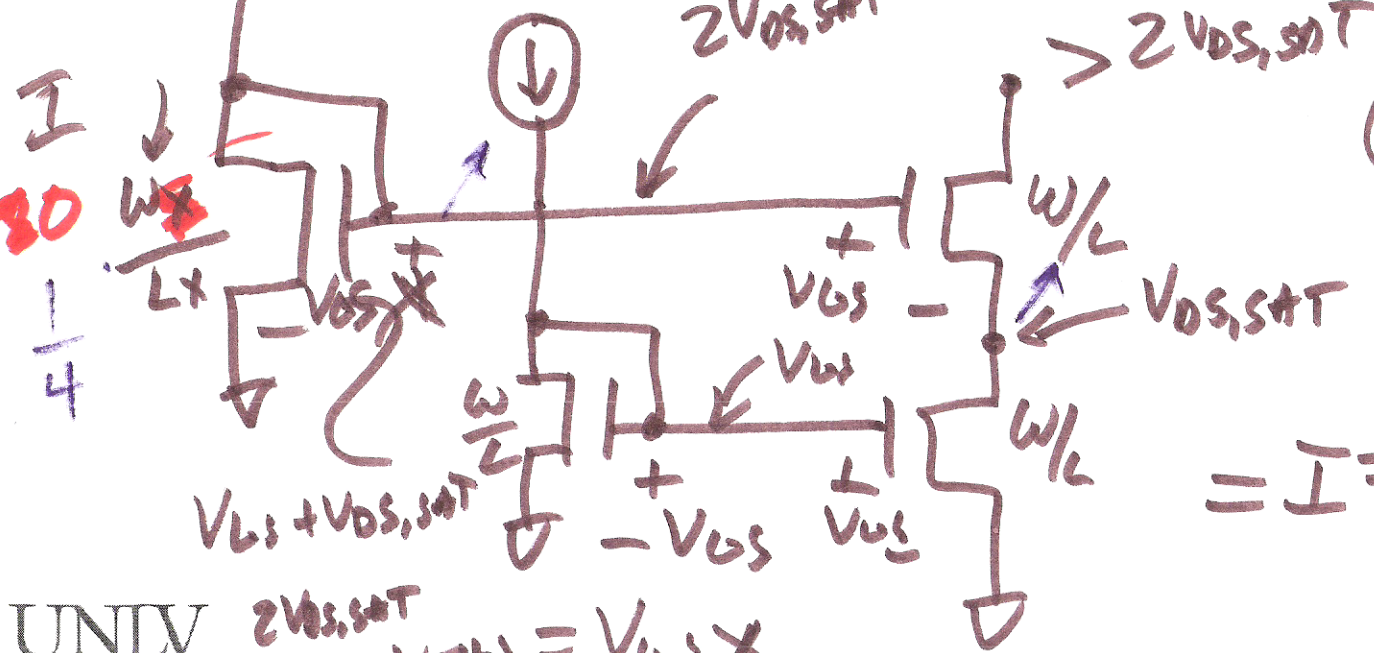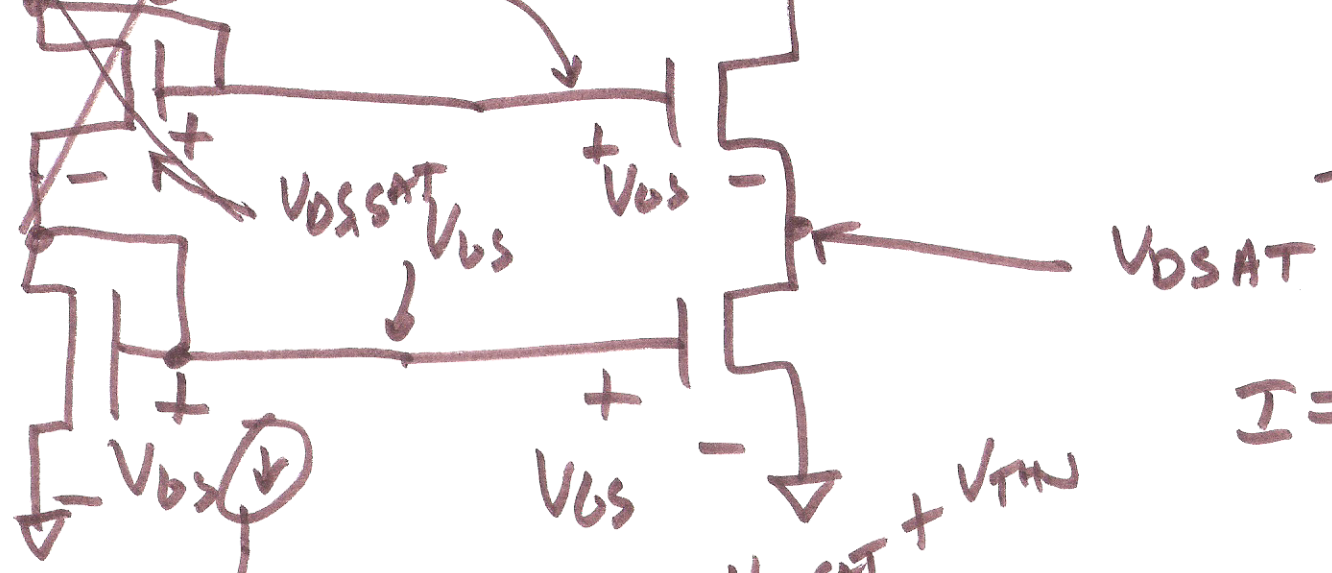
$$I = \frac{K_{PN}}{2} \cdot \frac{W_x}{L_x} (V_{GS} - V_{THN})^2$$





$$(V_{GS} - (2V_{DS,SAT} + V_{THN}))^2$$

$$= I = \frac{K_{PN}}{2} \cdot \frac{W_x}{L_x} 4 (V_{DS,SAT})^2$$

$2V_{DS,SAT} + V_{THN} = V_{GS} - V_{DS,SAT}$

7)

DC Bias Voltages

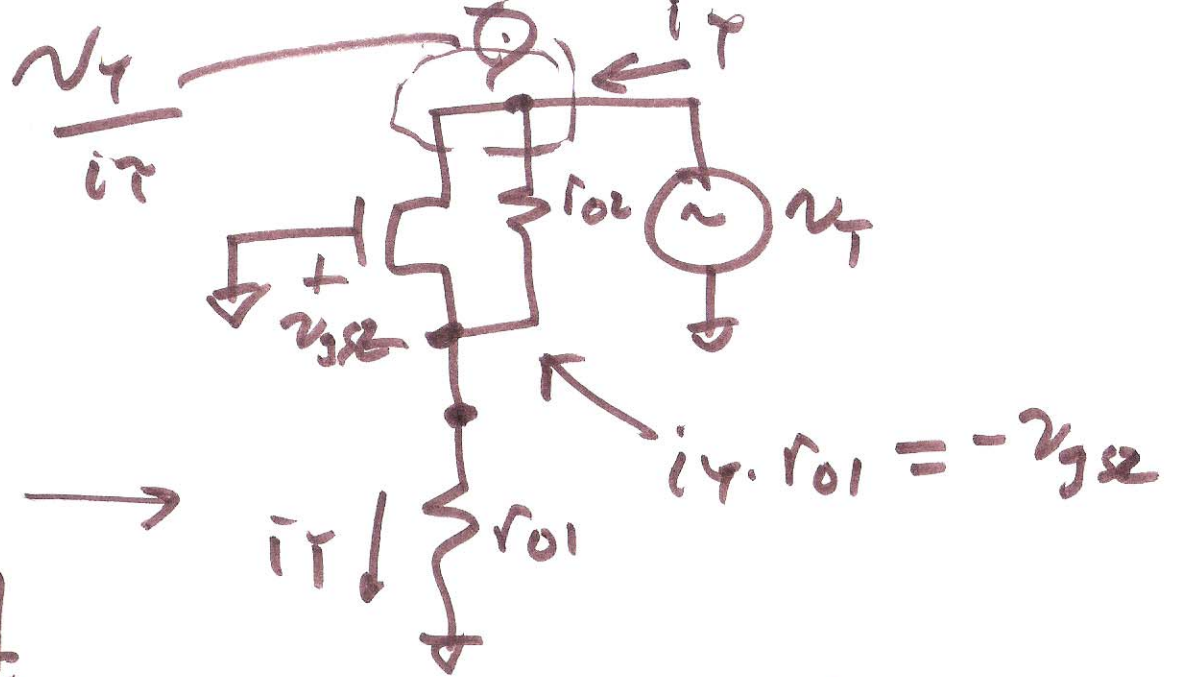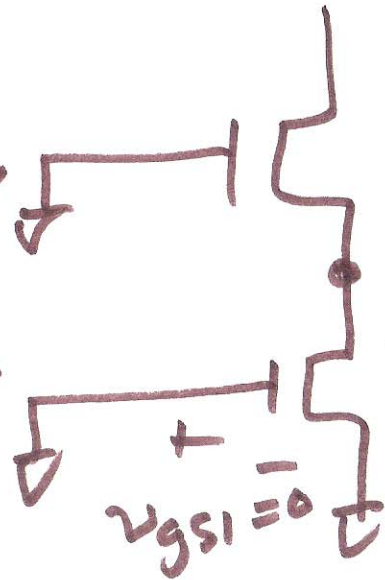

$$i_T = g_{m2} v_{gs2} + \frac{v_T - i_T \cdot r_{o1}}{r_{o2}}$$

$$i_T = g_{m2} (-i_T \cdot r_{o1}) + \frac{v_T}{r_{o2}} - i_T \cdot \frac{r_{o1}}{r_{o2}}$$

$$i_T \left(1 + g_{m2} r_{o1} + \frac{r_{o1}}{r_{o2}} \right) = \frac{v_T}{r_{o2}}$$

8)

$$\frac{v_T}{l_T} = r_{o2}(1 + g_m r_{o1}) + r_{o1}$$

EXACT = $r_{o2} + r_{o1} + \underbrace{g_m r_{o2} r_{o1}}$

ROCAS = $\frac{v_T}{l_T} \approx \frac{g_m r_{o2}}{r_{o1}} r_{o1}^2$ Approx.

$r_{o1} = r_{o2}$

9)