

EE 422 / ECG 622


Analog IC Design

Lecture 14, 3/15/13


AC=0



$i_d = v_{sg} \cdot g_{mP}$

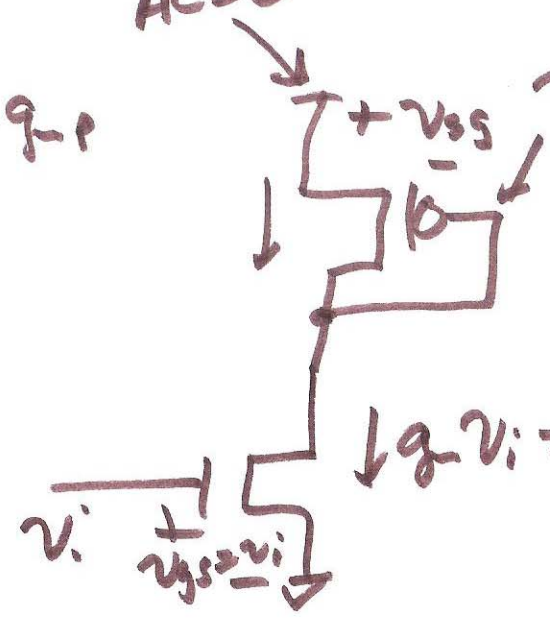$v_o = -v_{sg} = -\frac{i_d}{g_{mP}} \Rightarrow g_{mN} v_i = -g_{mP} v_o$


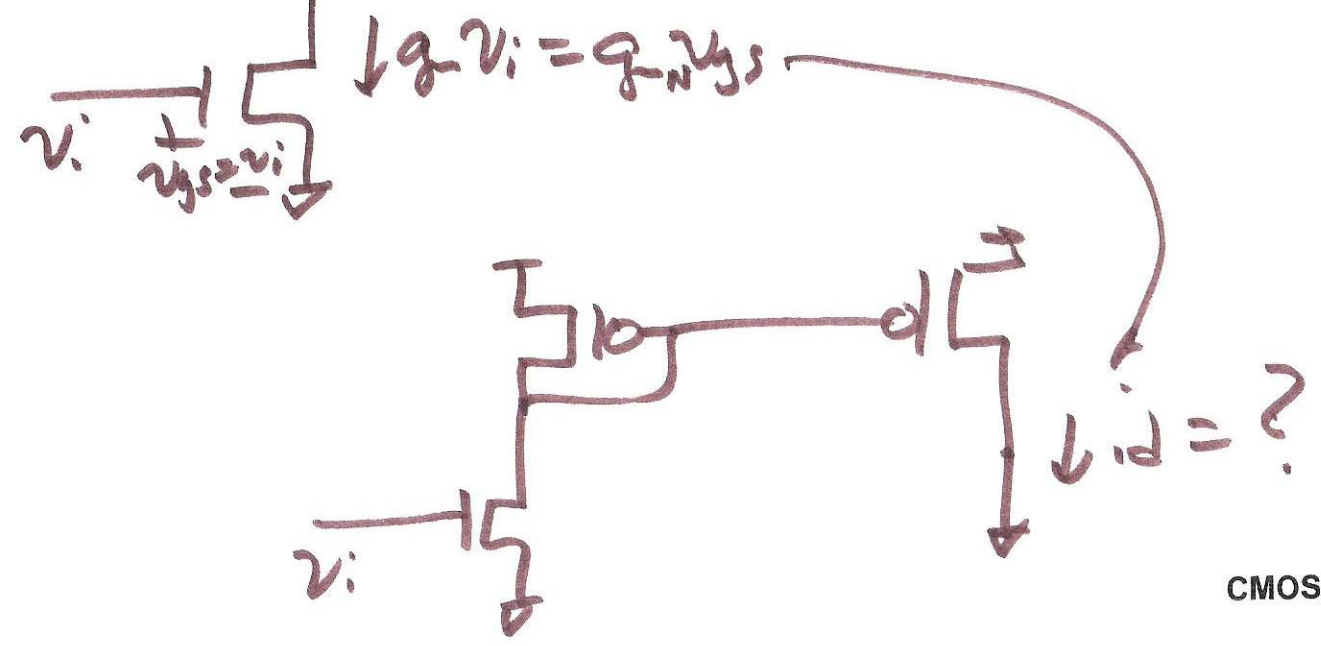
$$\frac{v_o}{v_i} = -\frac{g_{mN}}{g_{mP}}$$



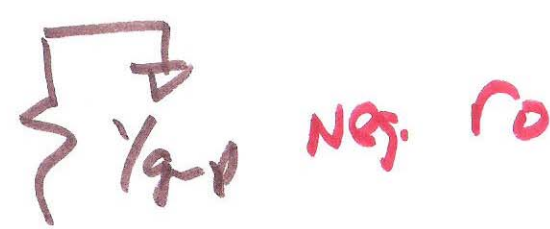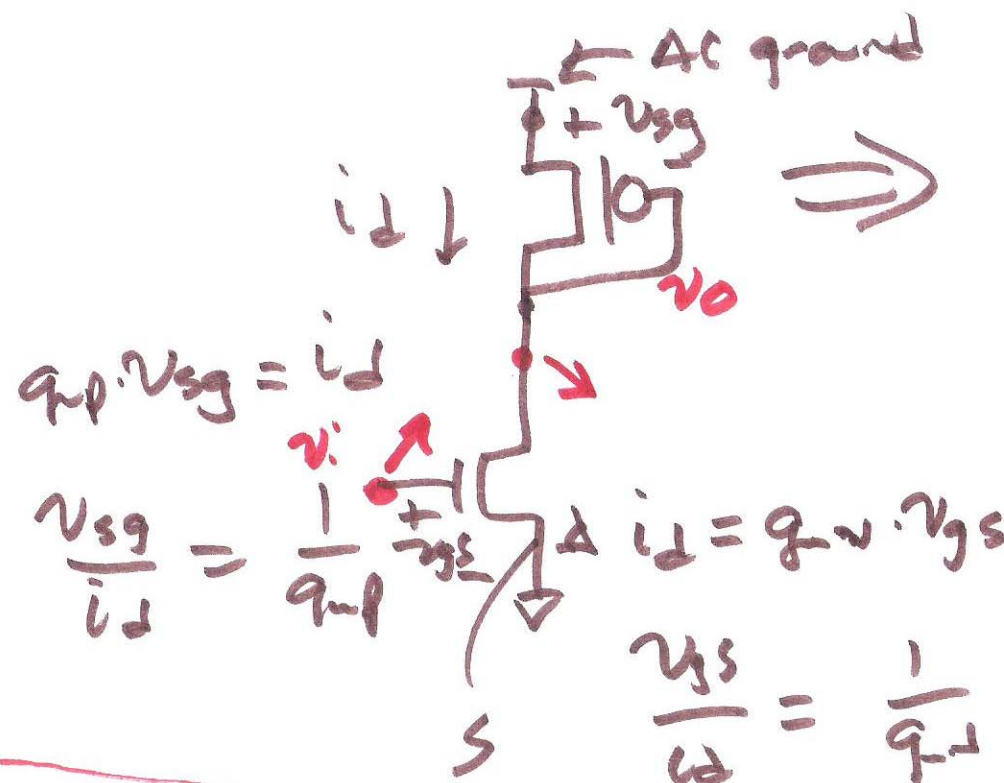

$$g_{mP} \cdot v_{sg} = i_d$$

$$\frac{v_{sg}}{i_d} = \frac{1}{g_{mP}}$$

$$i_d = g_{mN} \cdot v_{gs}$$


$$\frac{v_{gs}}{i_d} = \frac{1}{g_{mN}}$$

$$\text{gain} = - \frac{1/g_{mP}}{1/g_{mN}}$$

$$= - \frac{g_{mN}}{g_{mP}}$$

resistance in drain


resistance in source

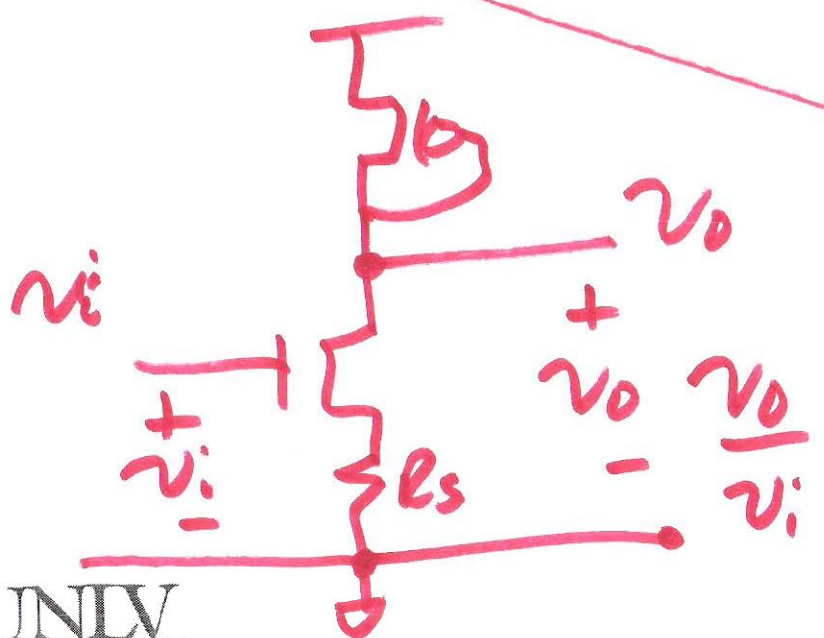

$$\frac{v_o}{v_i} = - \frac{1/g_{mP}}{1/g_{mN} + R_s}$$

~~$1/g_{mN}$~~

Common-source Amplifier

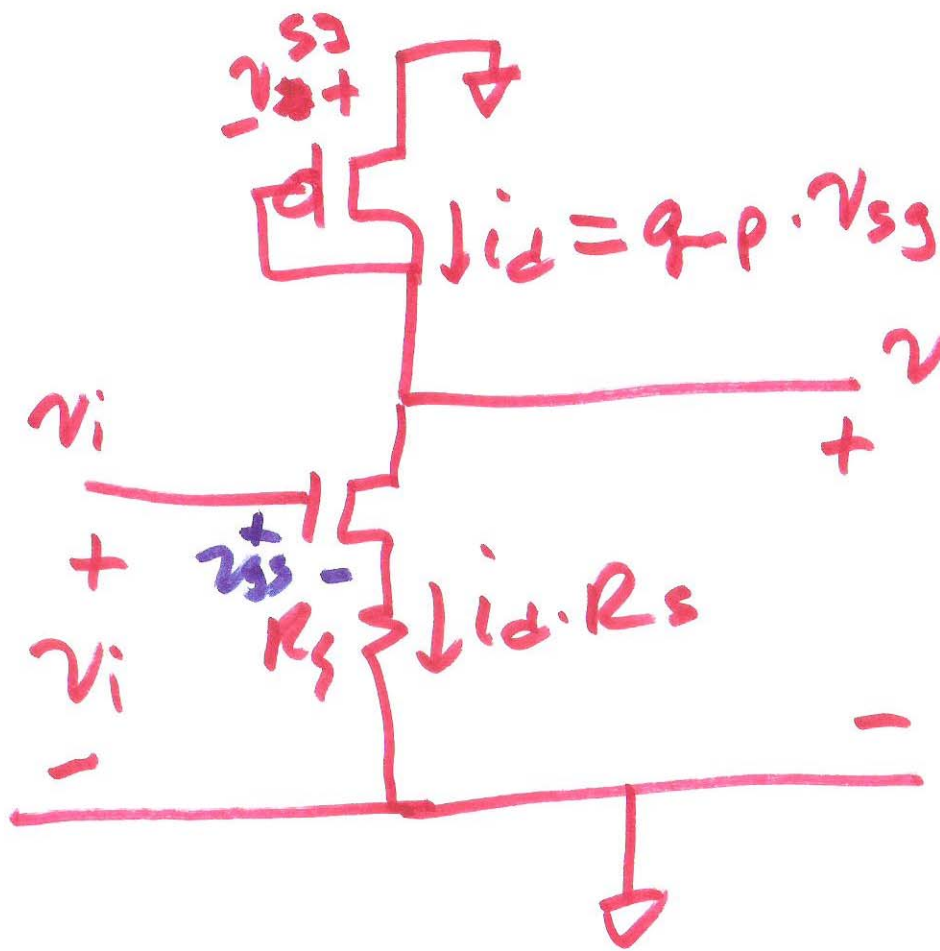

$$v_{gs} = \frac{i_d}{g_m}$$

$$v_{out} = -v_{gs} = -\frac{i_d}{g_m}$$

$$v_i = v_{gs} + i_d \cdot R_s$$

$$= \frac{i_d}{g_m} + i_d \cdot R_s$$


$$v_i = i_d \left(\frac{1}{g_m} + R_s \right)$$

$$-\frac{i_d}{g_m}$$

$$\frac{v_{out}}{v_i} =$$

$$\frac{-i_d/g_m}{i_d \left(\frac{1}{g_m} + R_s \right)}$$

3)

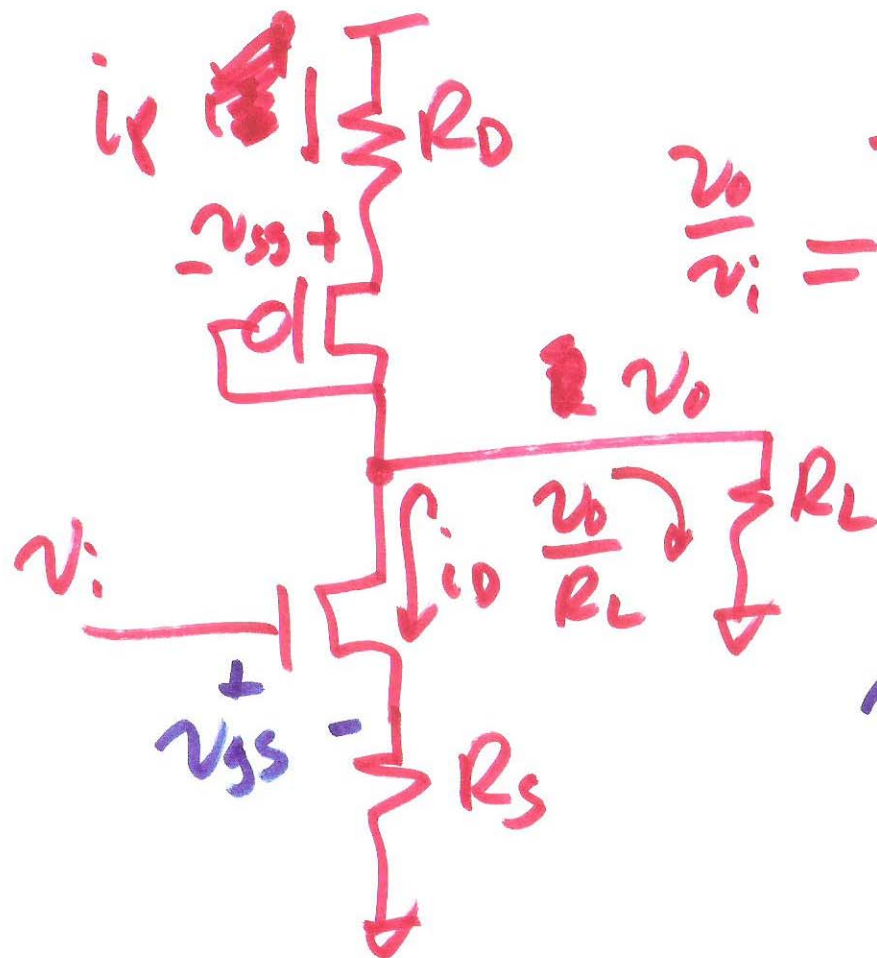

$$\frac{v_o}{v_i} = \frac{-(R_o + 1/g_{mP}) \parallel R_L}{R_s + 1/g_{mN}}$$

$$v_i = v_{gs} + i_d \cdot R_s$$

$$= i_d \left(\frac{1}{g_{mN}} + R_s \right)$$

$$i_d = i_p - \frac{v_o}{R_L}$$

$$v_o = -v_{sg} - i_p \cdot R_o$$

$$= -i_p \left(\frac{1}{g_{mP}} + R_o \right)$$


$$i_p = \frac{-v_o}{1/g_{mP} + R_o}$$

$$v_i = i_d \cdot (1/g_{mN} + R_S)$$

$$i_d = -v_o \left(\frac{1}{R_L} + \frac{1}{1/g_{mP} + R_D} \right)$$

$$v_i = \frac{-v_o (1/g_{mN} + R_S)}{R_L \parallel (1/g_{mP} + R_D)}$$
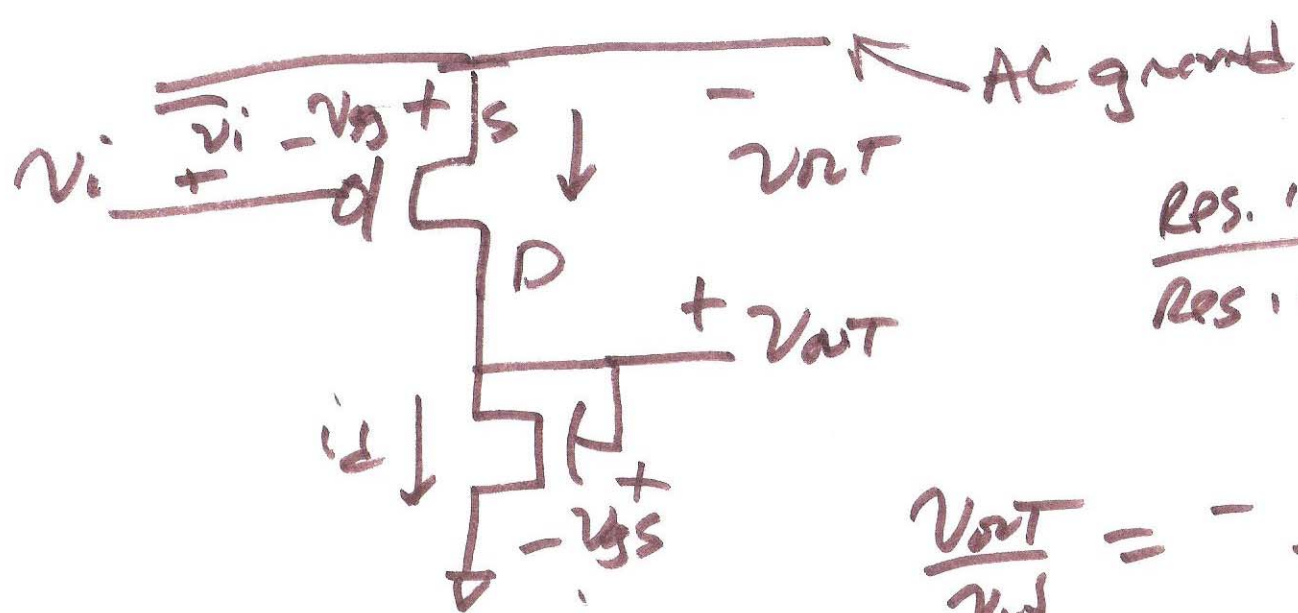
$$\frac{v_o}{v_i} = \frac{-R_L \parallel (1/g_{mP} + R_D)}{1/g_{mN} + R_S}$$



$\frac{R_{PS. \text{ IN DRAIN}}}{R_{ES. \text{ IN SOURCE}}}$

$$\frac{v_{OUT}}{v_{iN}} = - \frac{1/g_{mN}}{1/g_{mP}}$$

$$v_{OUT} = v_{GS} = \frac{i_d}{g_{mN}}$$

$$v_i = -v_{SG} = -\frac{i_d}{g_{mP}}$$


$$= -\frac{g_{mP}}{g_{mN}}$$

$$\frac{v_{OUT}}{v_i} = \frac{i_d/g_{mN}}{-i_d/g_{mP}} = -\frac{g_{mP}}{g_{mN}}$$


6)



Common-Drain or source follower

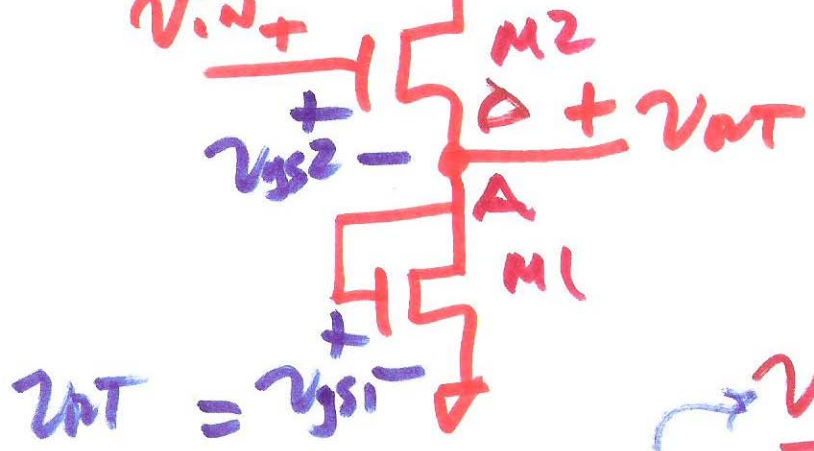

$Z_{in} = v_{gs1}$

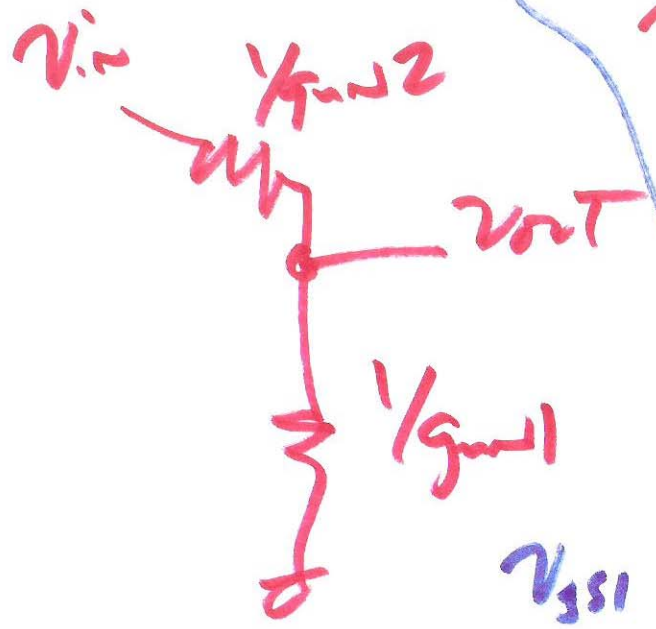

$$\frac{v_{out}}{v_{in}} = \frac{1/g_{m2}}{1/g_{m1} + 1/g_{m2}}$$


$$v_{in} = v_{gs2} + v_{gs1}$$

$$= \frac{i_d}{g_{m2}} + \frac{i_d}{g_{m1}}$$

$$v_{gs1} = v_{out} = \frac{i_d}{g_{m1}}$$

Common-Drain



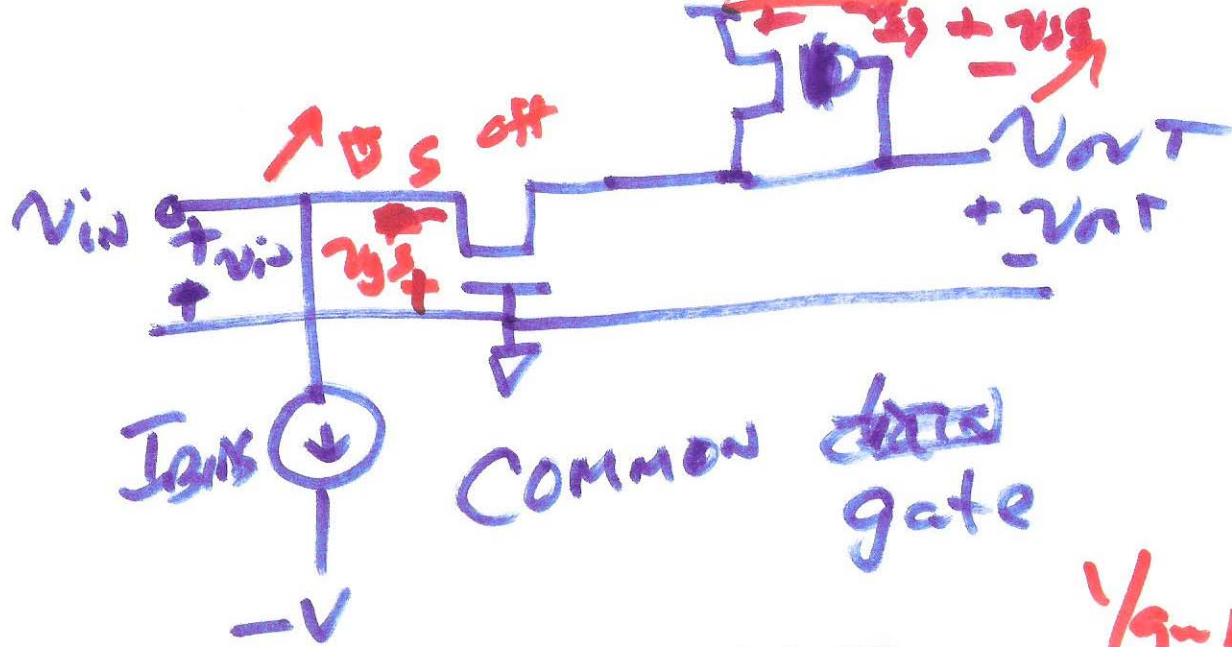


$$\frac{v_{out}}{v_{id}} = \frac{1/g_{m,p}}{1/g_{m,n}}$$

$$v_{in} = -v_{gs} = -\frac{i_d}{g_{m,n}}$$

$$v_{out} = -v_{sg} = -\frac{i_d}{g_{m,p}}$$
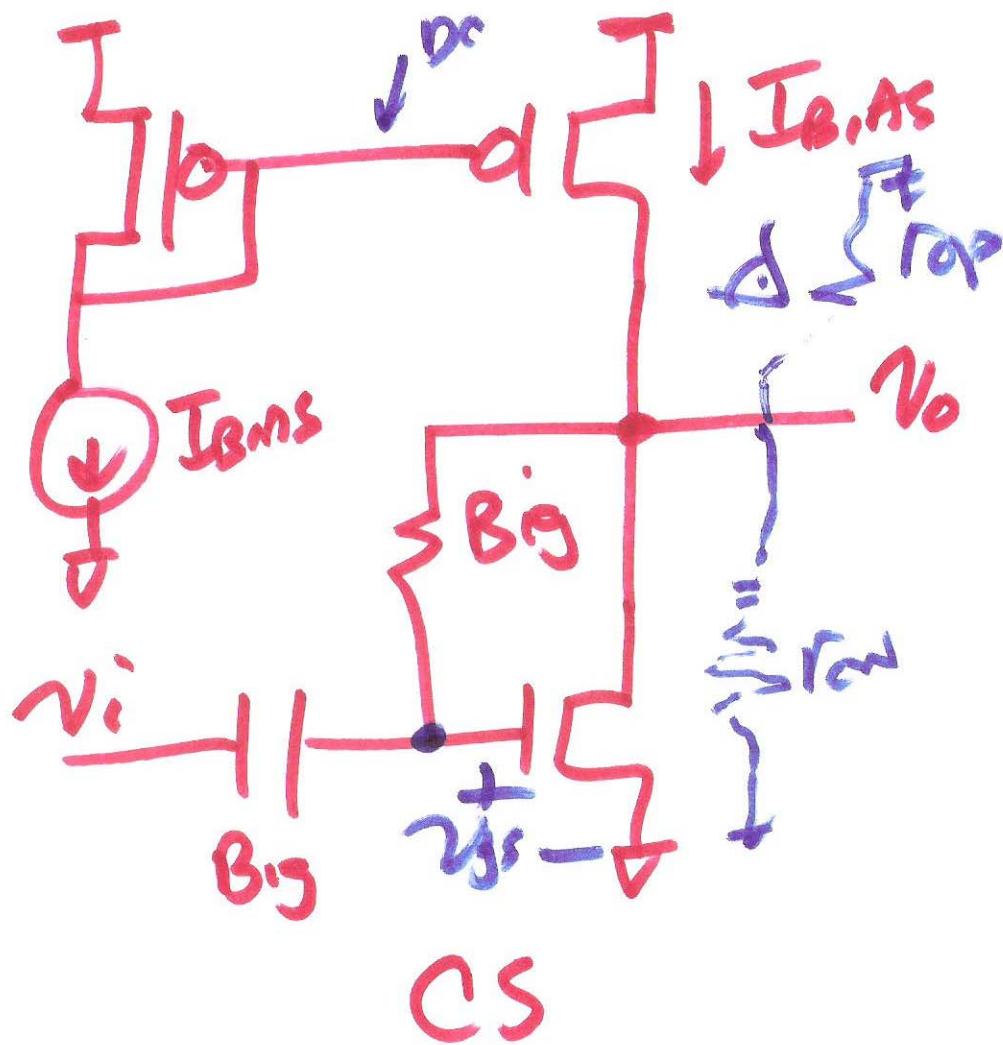
$$\frac{v_{out}}{v_{in}} = \frac{-i_d/g_{m,p}}{-i_d/g_{m,n}} = \frac{1/g_{m,p}}{1/g_{m,n}}$$




$$\frac{v_{out}}{v_{in}} = \frac{-r_{op} || r_{on}}{1/g_{m,n}}$$


$$= -g_{m,n} (r_{on} || r_{op})$$

o

9)

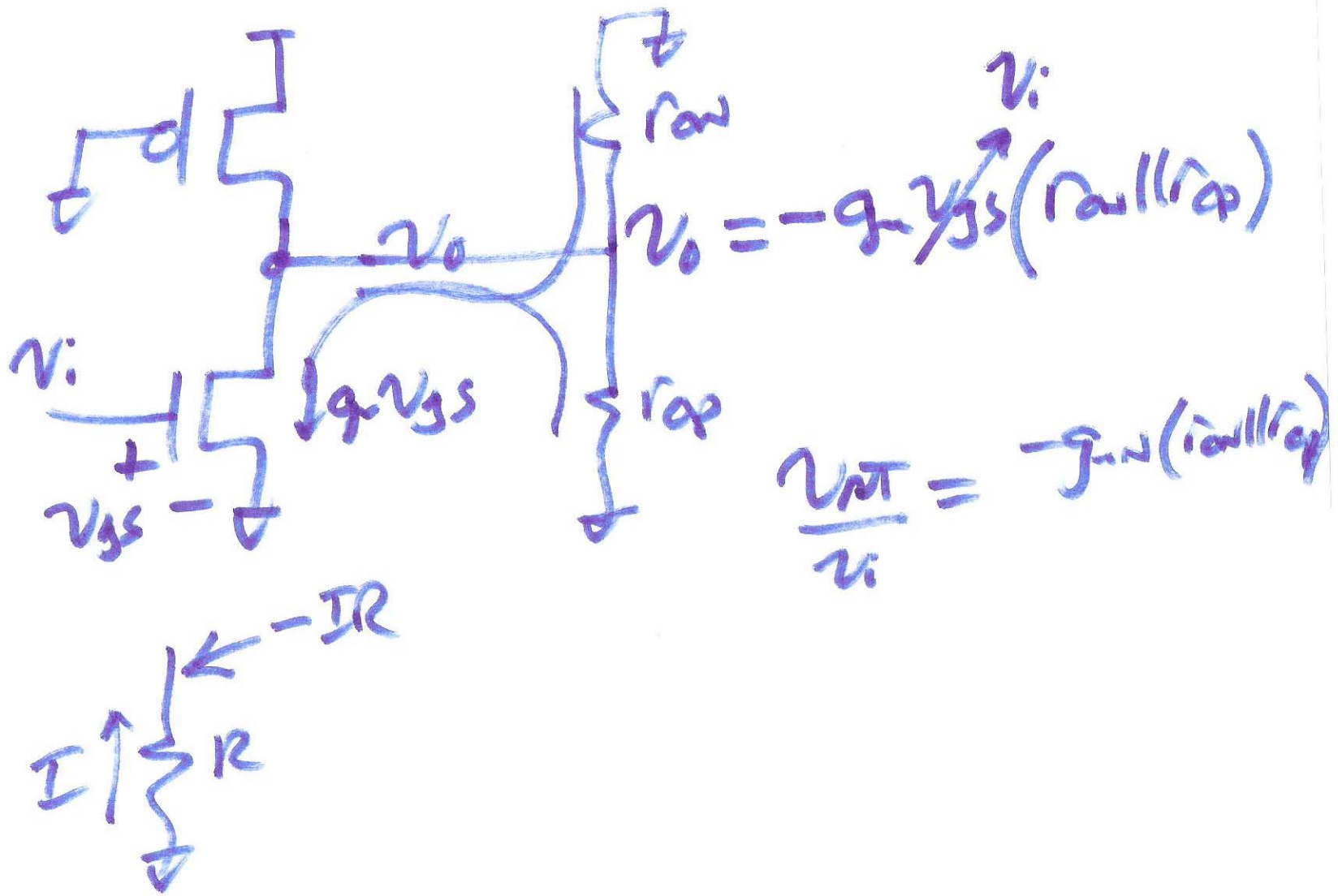


Miller Effect

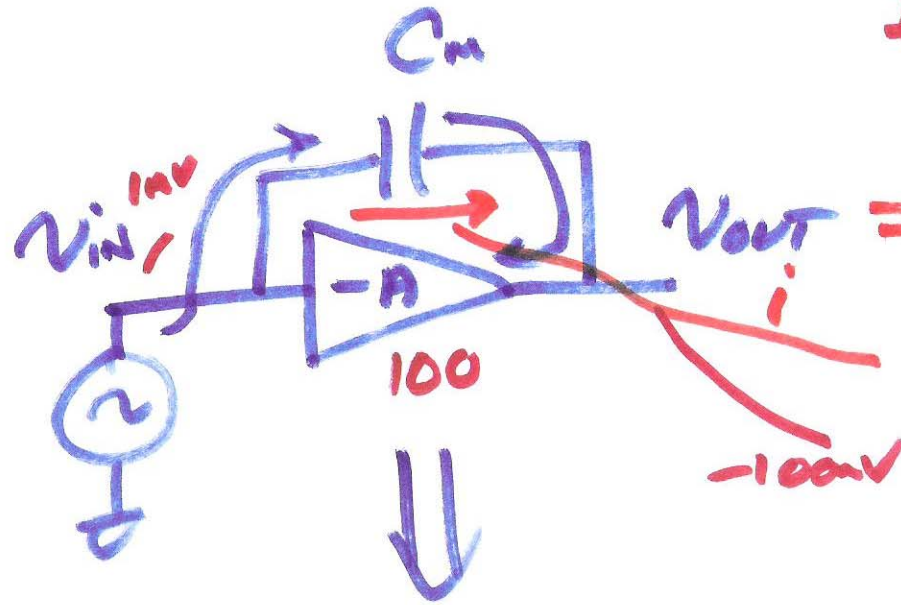

$$I = C \frac{dV}{dt}$$

$$V_{out} = \frac{-A \cdot V_{in}}{V_{in} - V_{out}}$$

$$\frac{1}{j\omega C_m}$$

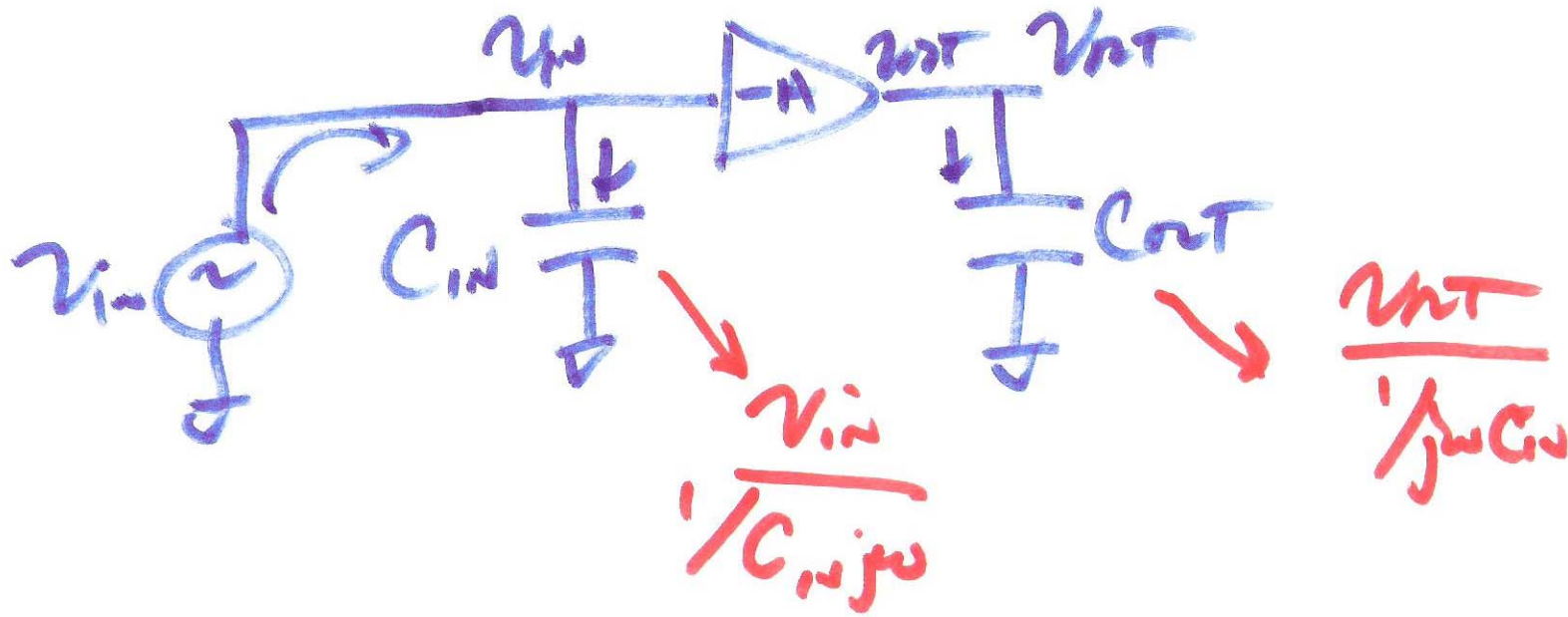

11)

$$v_{in} \cdot C_{in} \cdot j\omega = j\omega C_m (v_{in} - v_{out})$$


$$v_{in} C_{in} = C_m (v_{in} - (-A \cdot v_{in}))$$

$$v_{in} C_{in} = C_m (|A| + 1) v_{in}$$


$$C_{in} = C_m (1 + |A|)$$

$$C_{out} = \frac{C_m}{1 + |A|}$$

12)

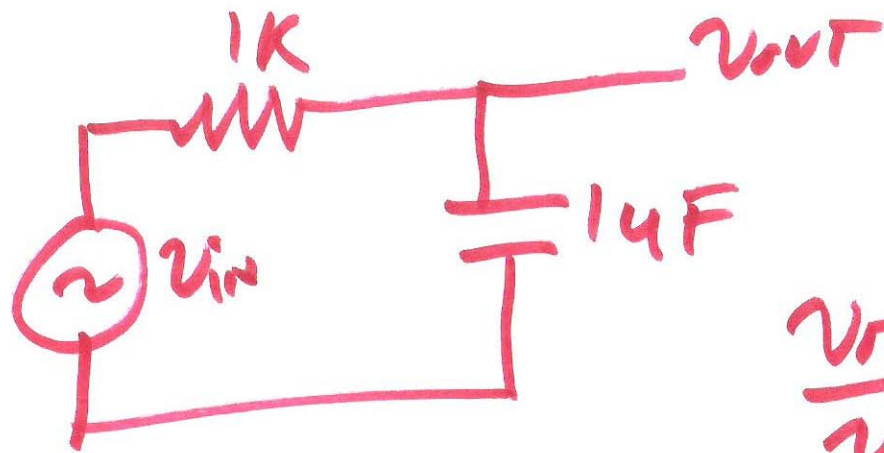


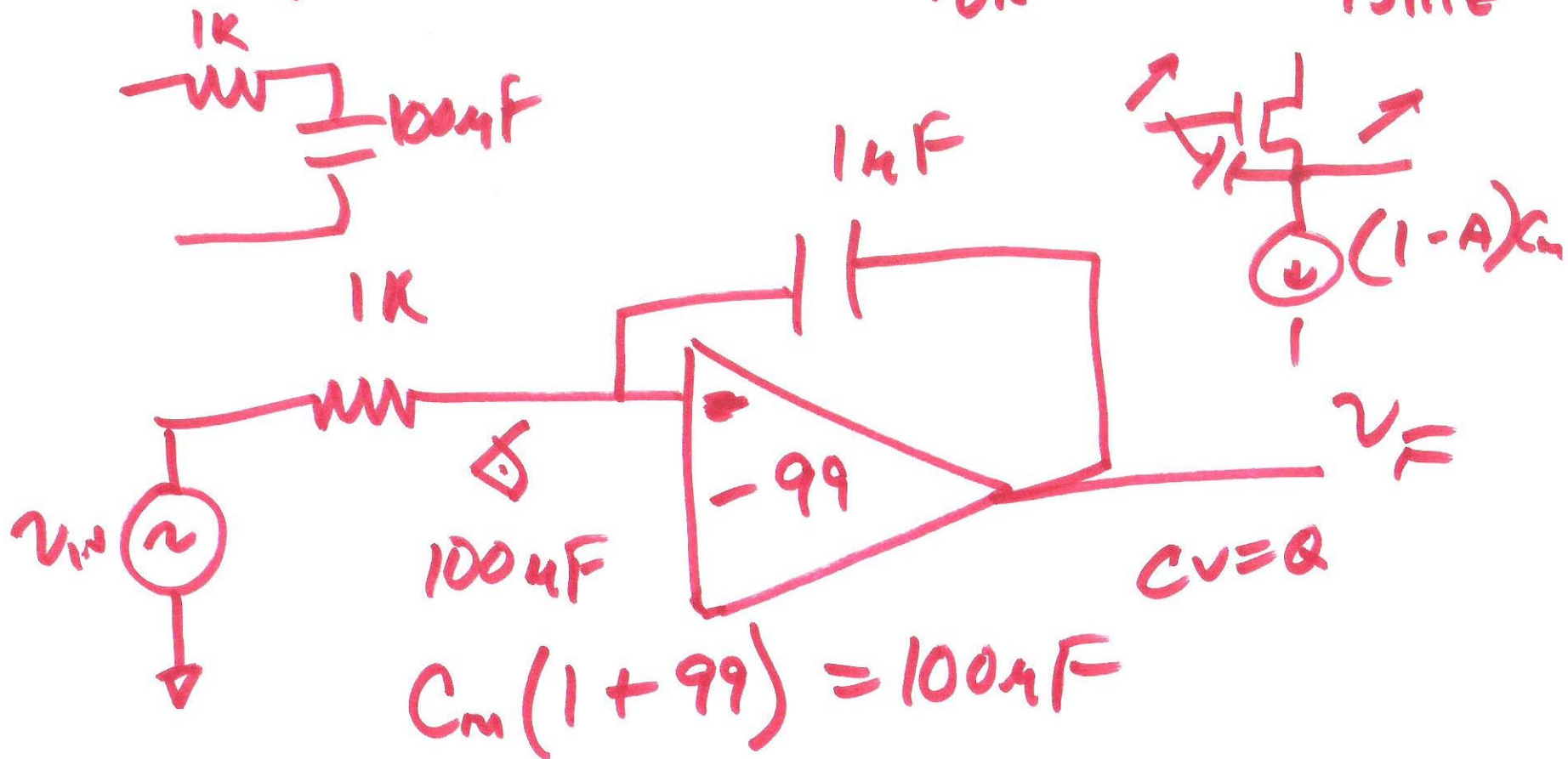
$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + j \frac{f}{1.59 \text{ MHz}}}$$



$$C_m (1 + 99) = 100 \mu\text{F}$$

$$1.59 \text{ MHz}$$

13)

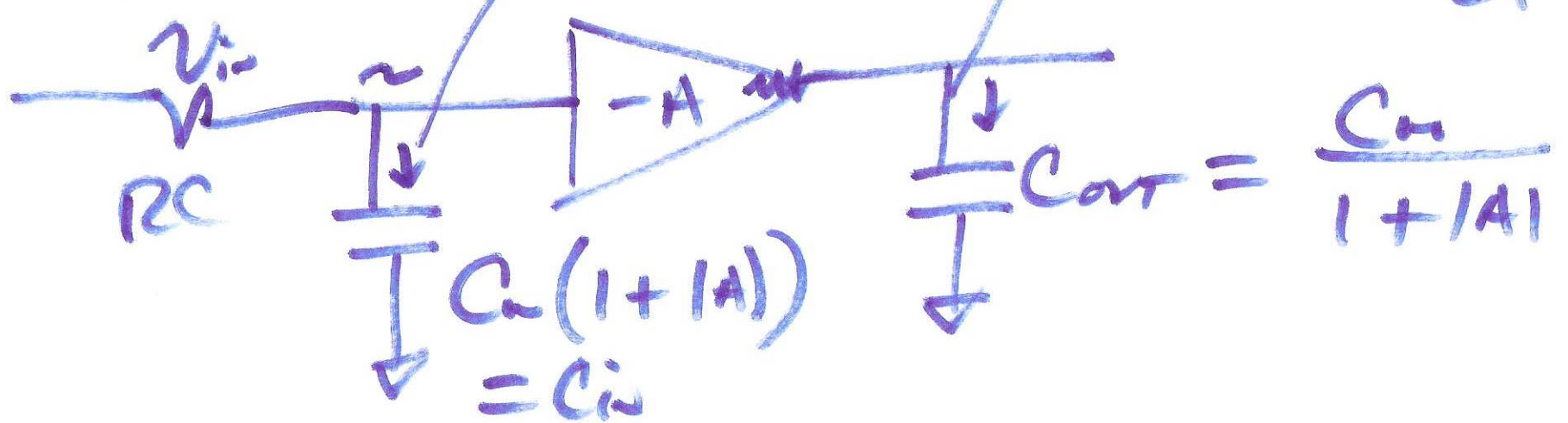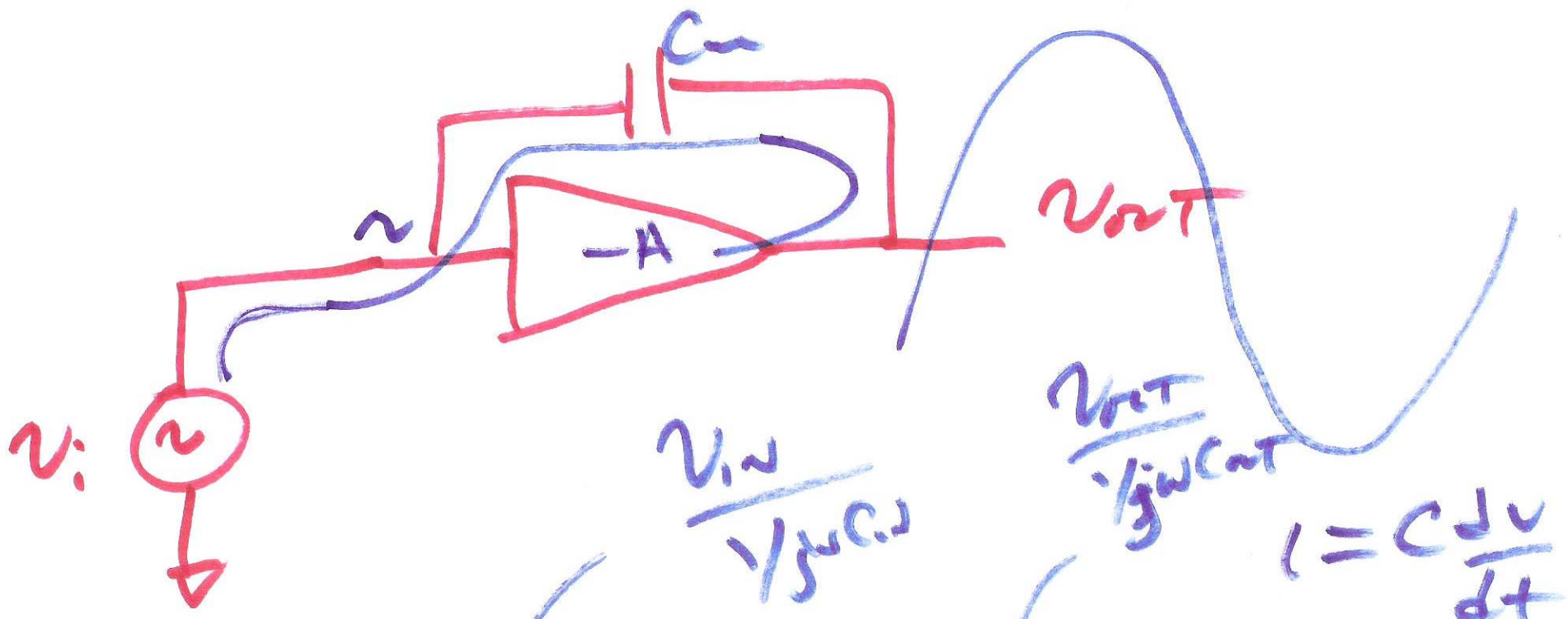

14)