



Lecture 15 EE 422 / ECG 622

March 18, 2013

$C_{GD} \propto W$
M/F

MOSFET CAPACITANCES


→ SATURATION ←

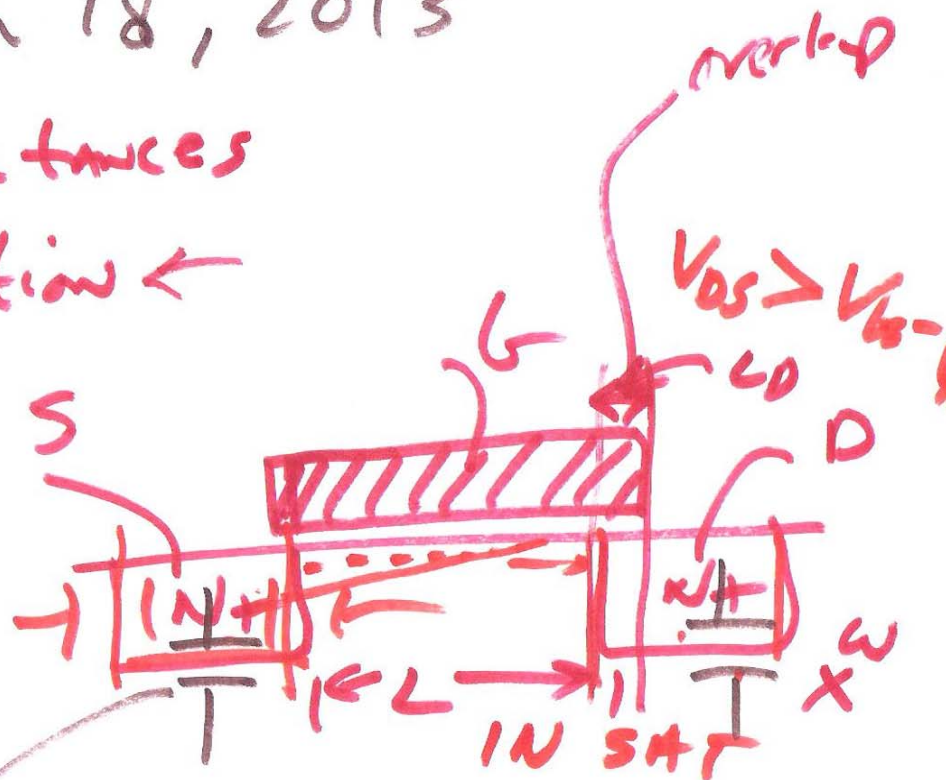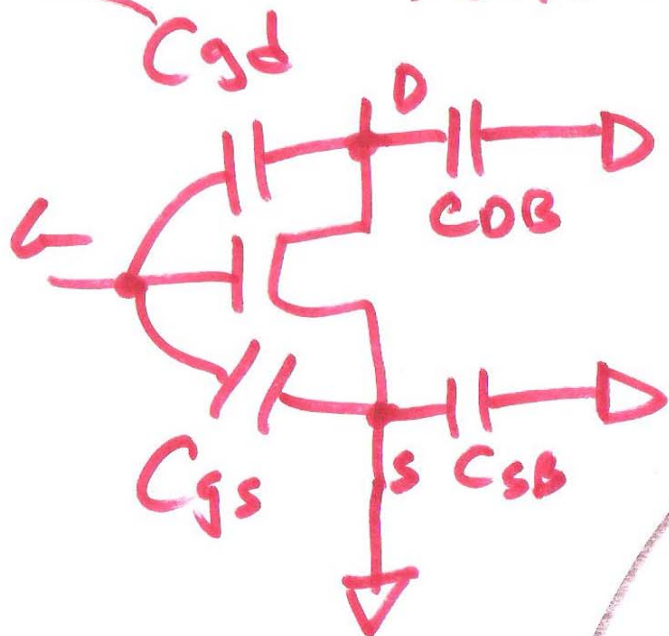

$$C_{GS} = \frac{2}{3} C_{ox}' \cdot W \cdot L$$




depletion capacitances!

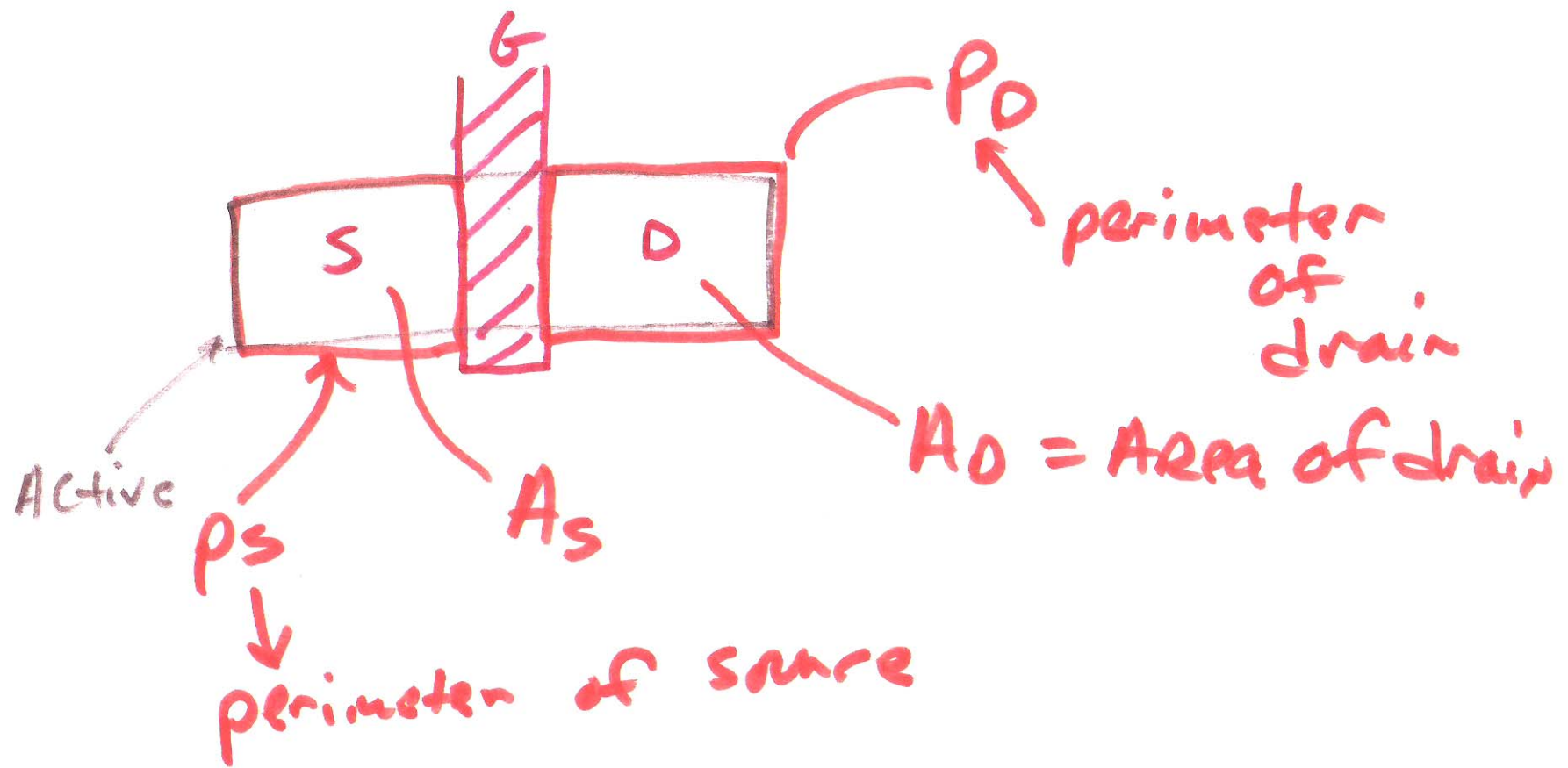
$$\parallel \frac{\epsilon_{ox}}{t_{ox}}$$



$$C_{DB} = C_{DB \text{ AREA}} + C_{DB \text{ sidewall}}$$

$$= \frac{C_j \cdot A_D}{\left(1 + \frac{|V_{DB}|}{p_b}\right)^{M_j}} + \frac{C_{jsw} \cdot P_D}{\left(1 + \frac{|V_{DB}|}{p_{bsw}}\right)^{M_{jsw}}}$$

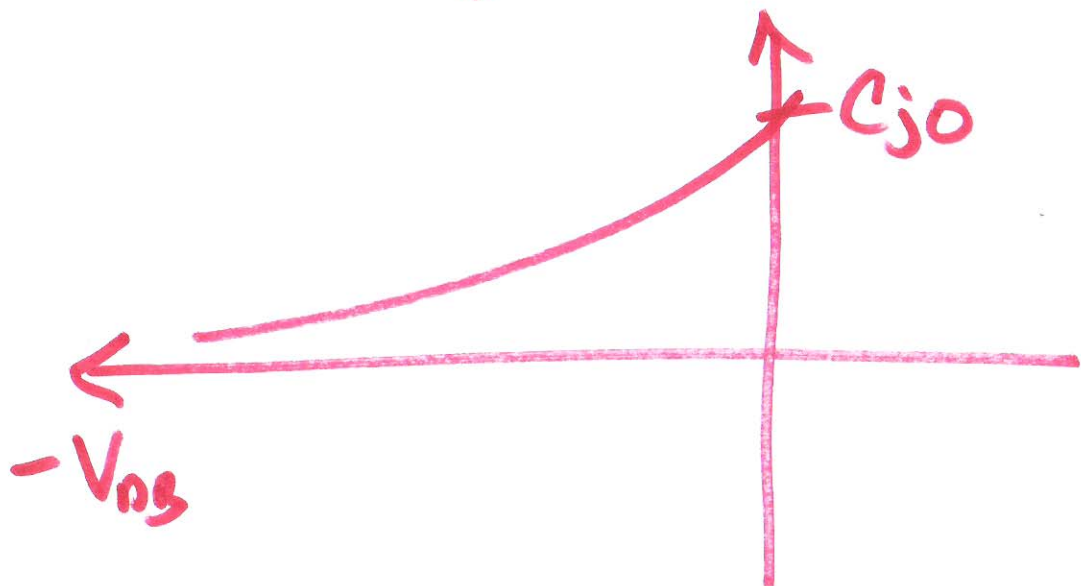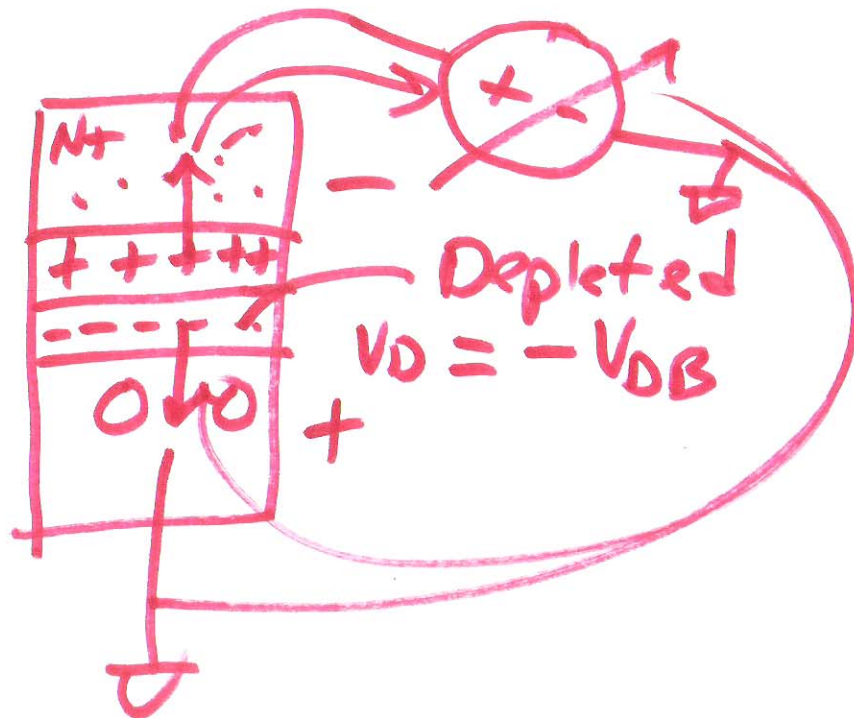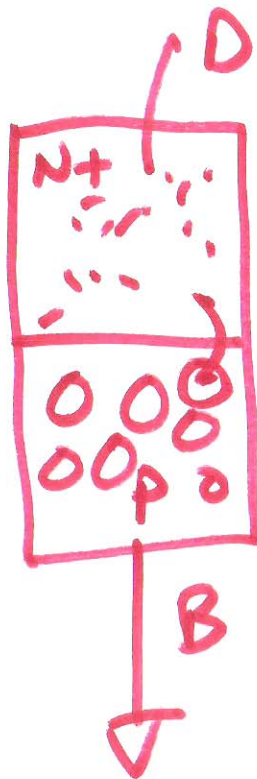

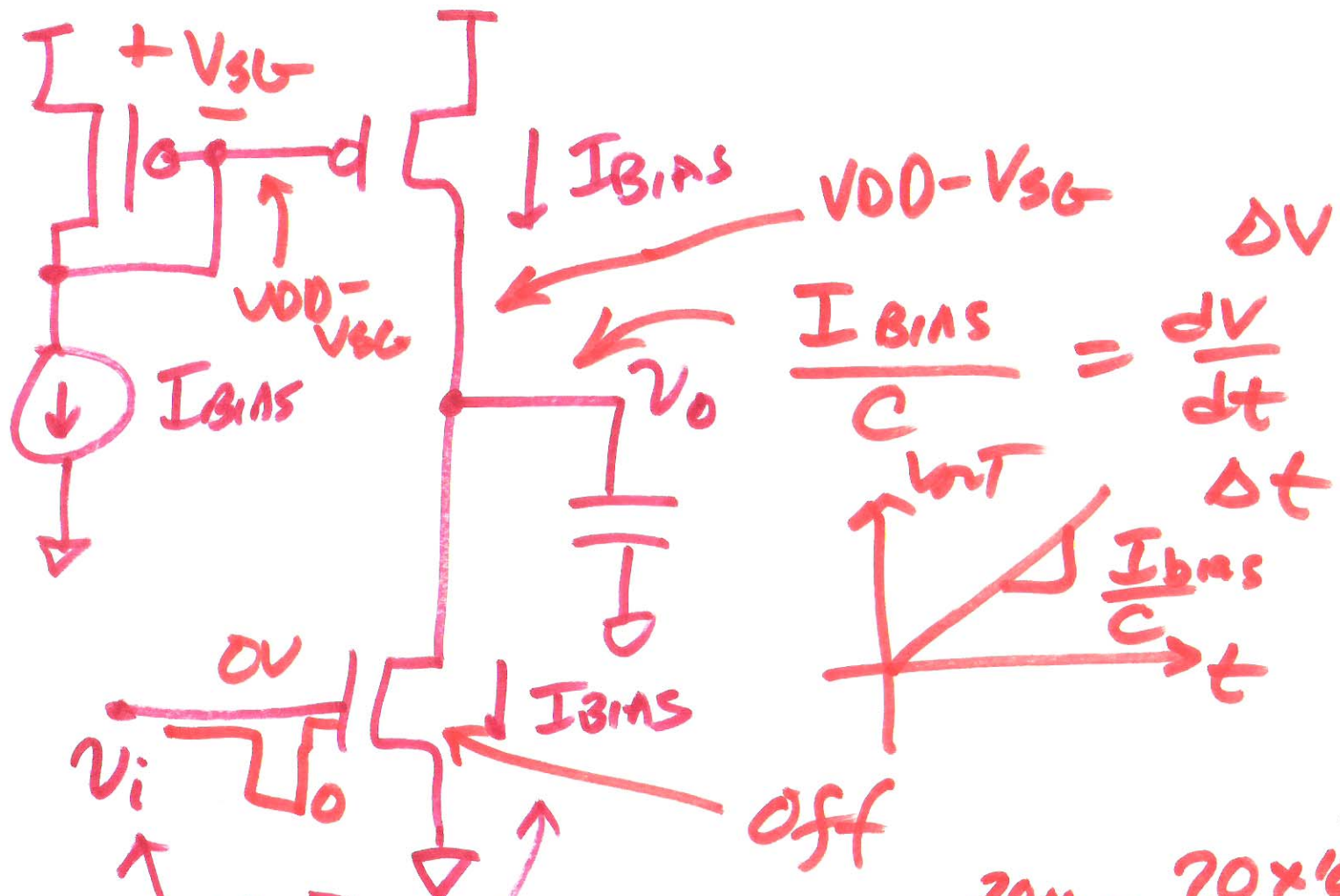

$$\frac{I_{BIAS}}{C} = \frac{dV}{dt}$$


$$\tau = \frac{C}{I_{BIAS}}$$

Slew-rate limitations


constant current charging a CAP!

$$\frac{20\mu A}{1p} = \frac{20 \times 10^{-6}}{1 \times 10^{-12}}$$

$$\frac{20V}{4s} = \frac{0.02V}{ns}$$

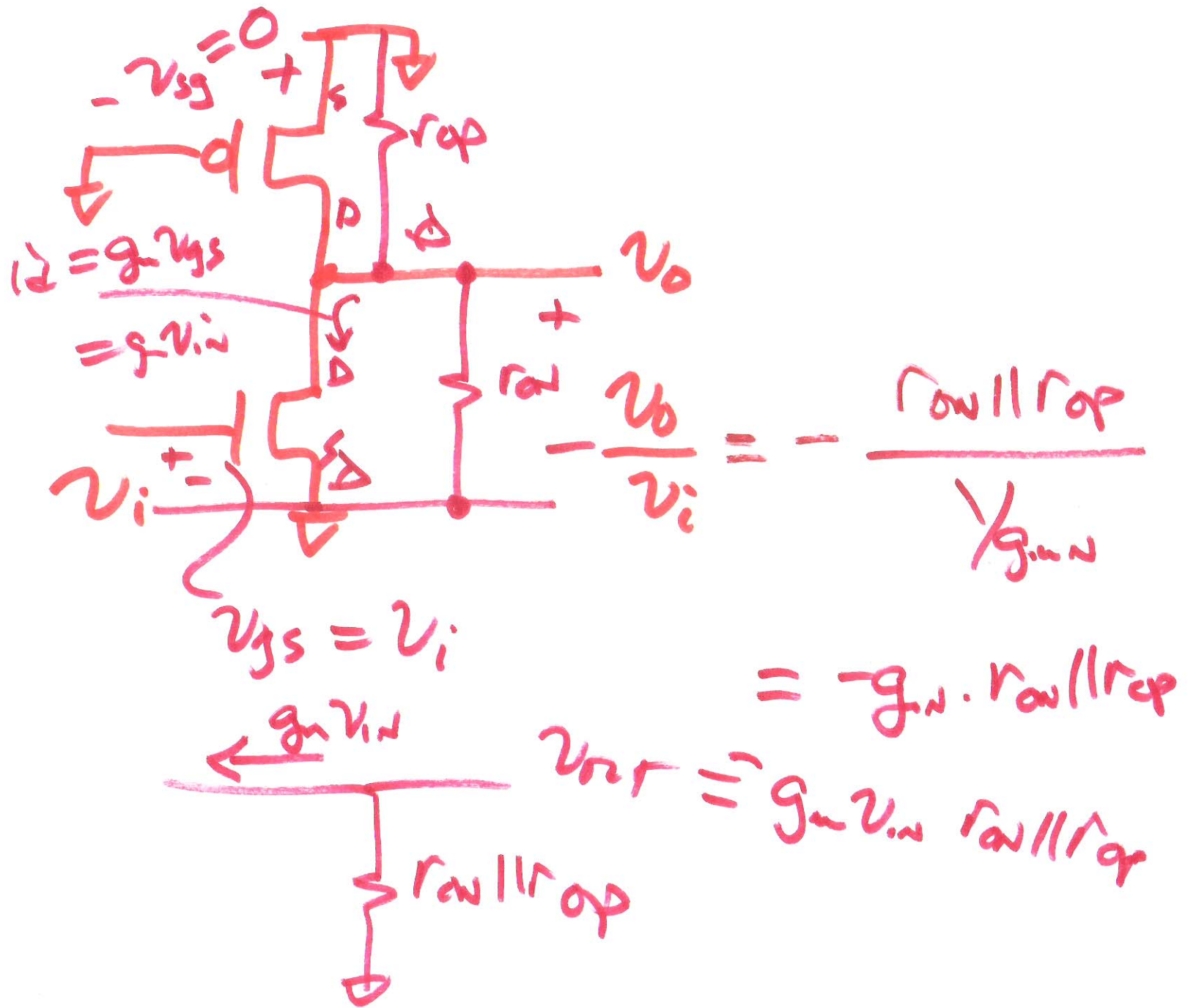

5)


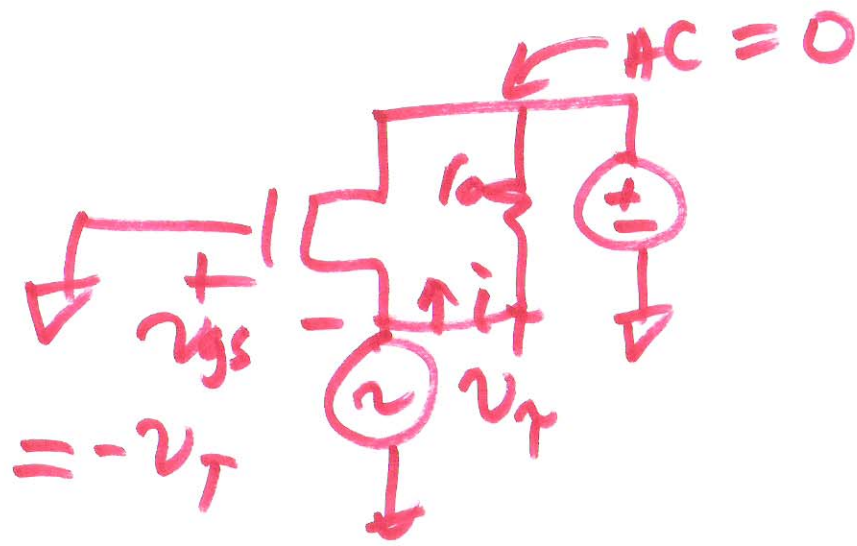


$$i_d = g_m \cdot v_{gs}$$


$$-i_T = g_m \cdot -v_T$$

$$\frac{v_T}{i_T} = \frac{1}{g_m}$$
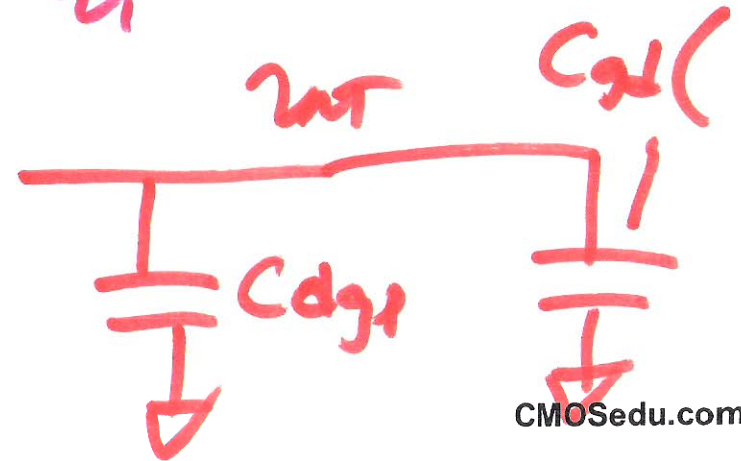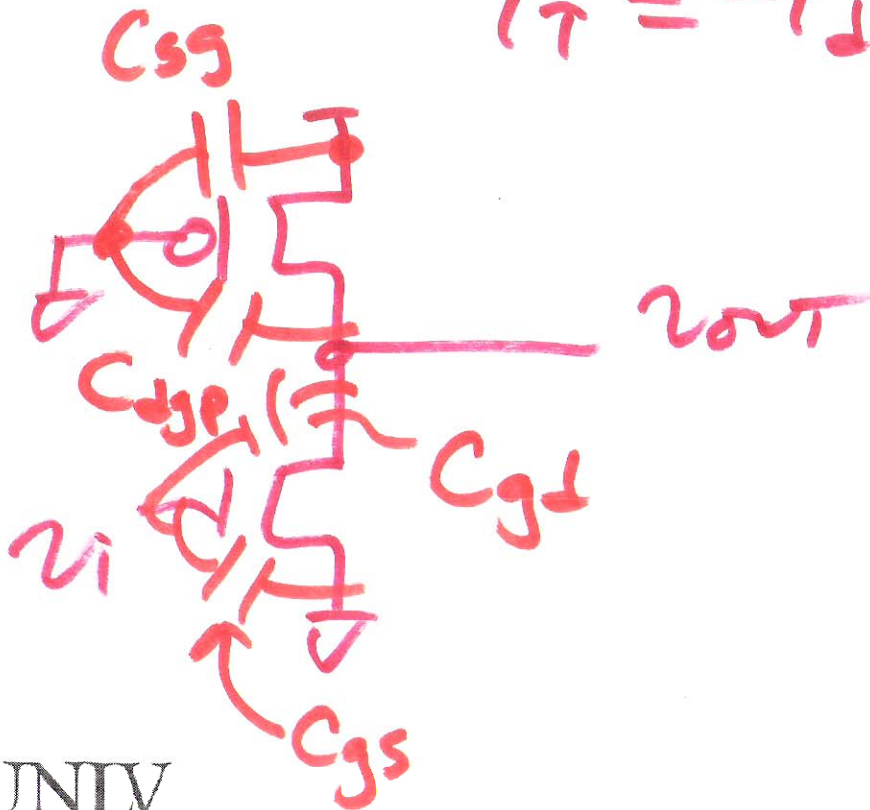
$$\frac{v_{out}}{v_i} = -g_m r_{out} r_{op}$$






6)

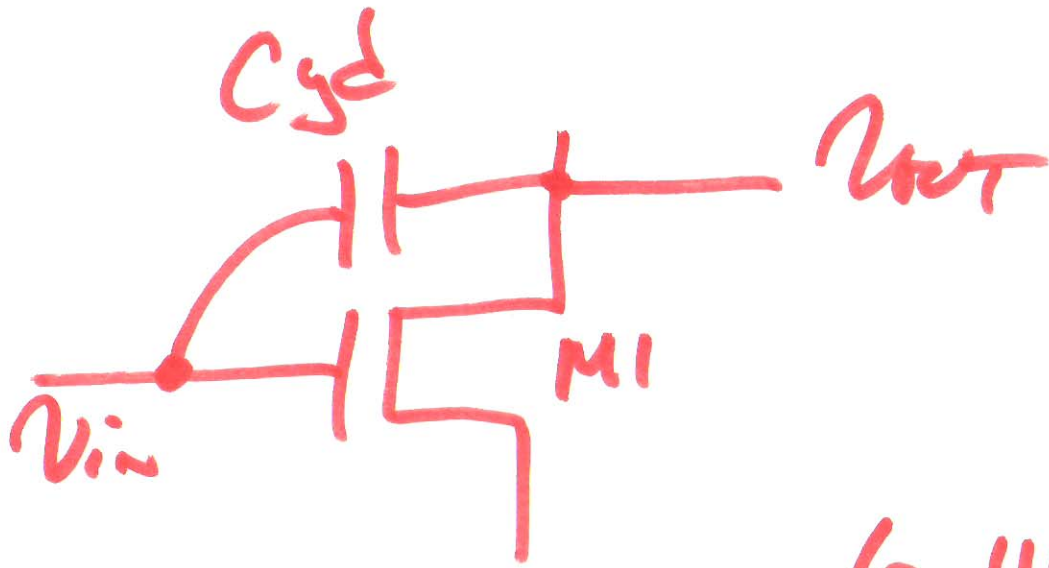

$$A = -g_m (r_{o1} \parallel r_{op}) C_{in} \left(1 + \frac{1}{|A|} \right)$$

$\downarrow \mu C_{gd}$

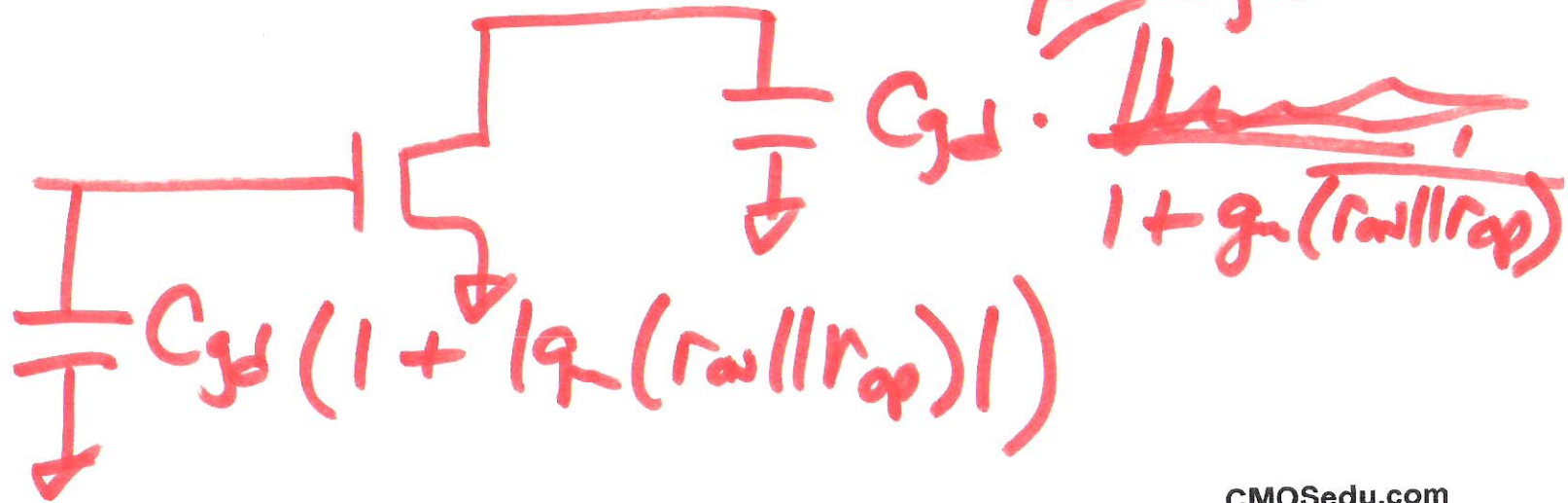

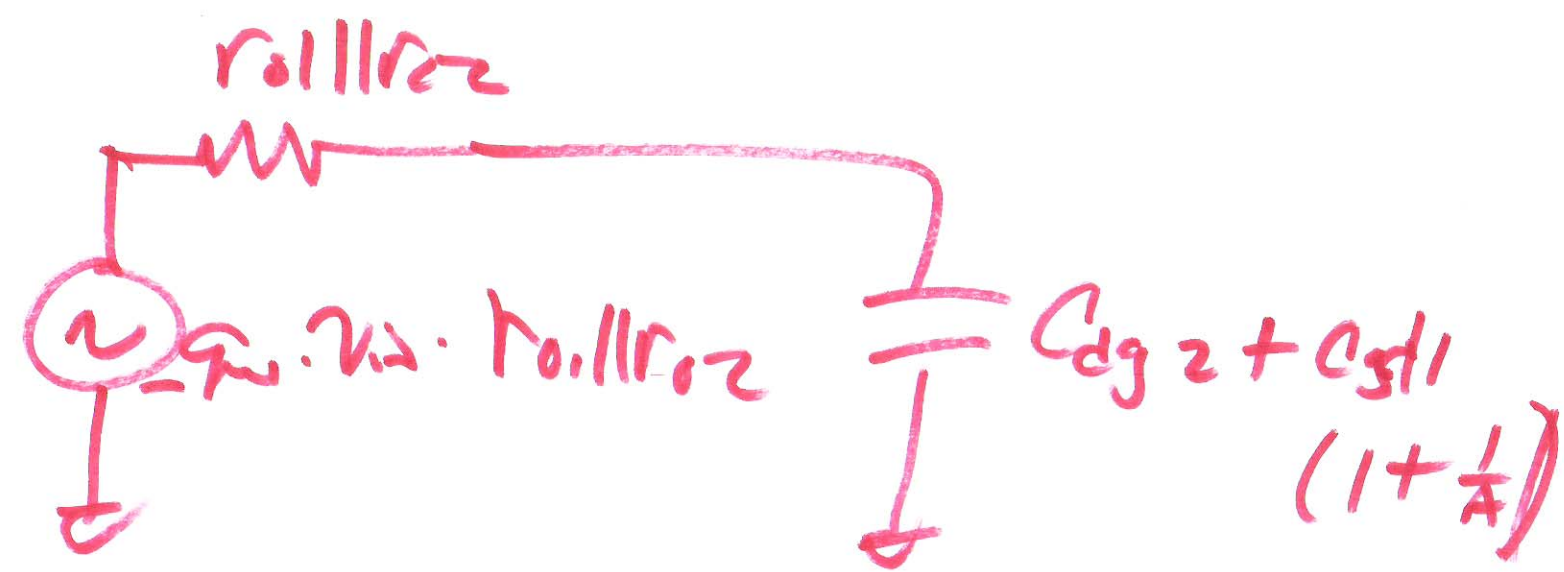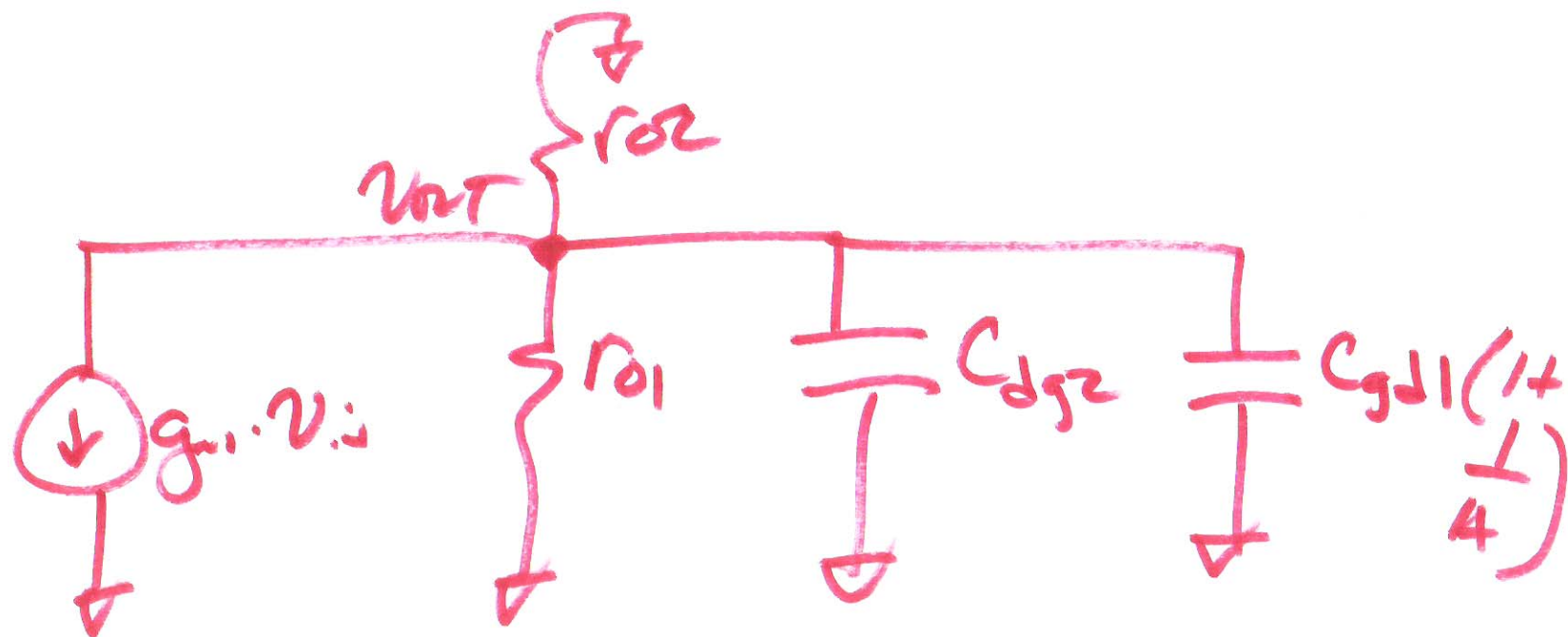

8)