
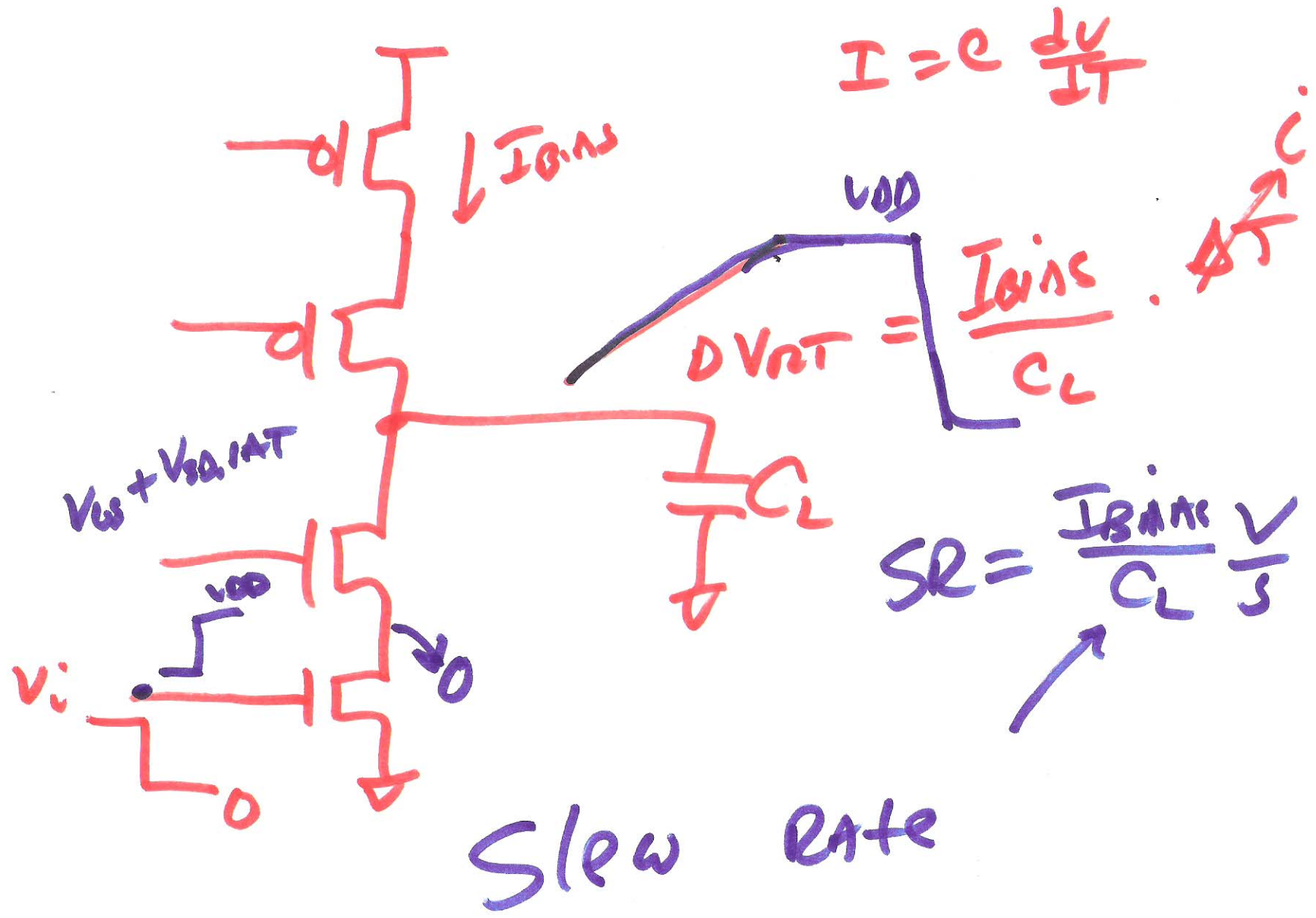


2)

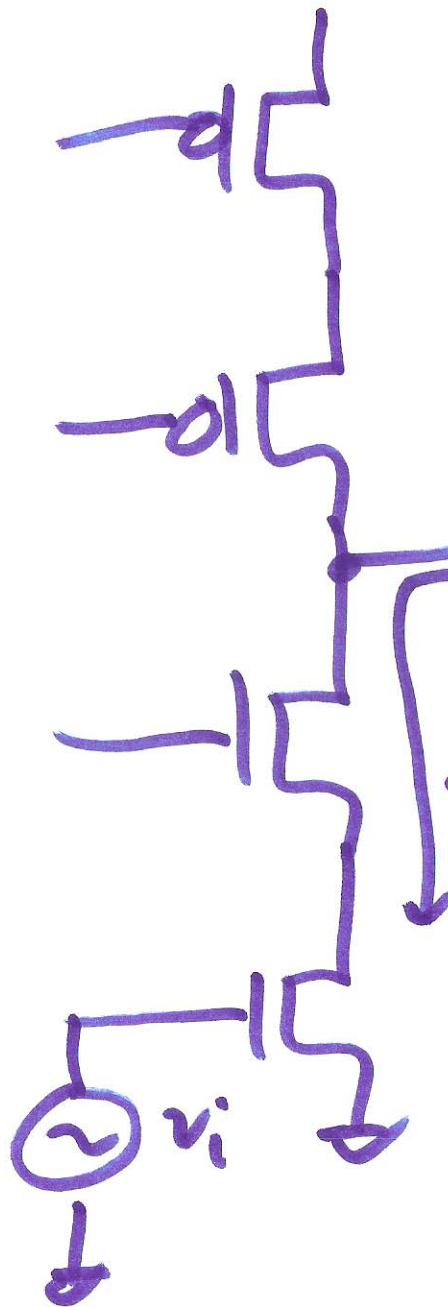

3)



$$f_{un} = \frac{150 \mu A}{2\pi \cdot 10 pF} = 2.5 \text{ MHz}$$

$$v_{out} = -g_m v_i \cdot \frac{1}{j\omega C_L}$$

$\frac{1}{6.28 \cdot 6.5 \text{ K} \cdot 10 pF}$   
 $\frac{1}{6.28 \cdot 65 n}$

$$\left| \frac{v_{out}}{v_i} \right| = \frac{g_m}{\omega \cdot C_L} = 2.5 n$$


$g_m = \frac{1}{400 n}$

When  $\left( \frac{v_{out}}{v_i} \right) = 1, f = f_{un}$


$$f_{un} = \frac{g_m}{2\pi \cdot C_L}$$

4)

# Short-channel

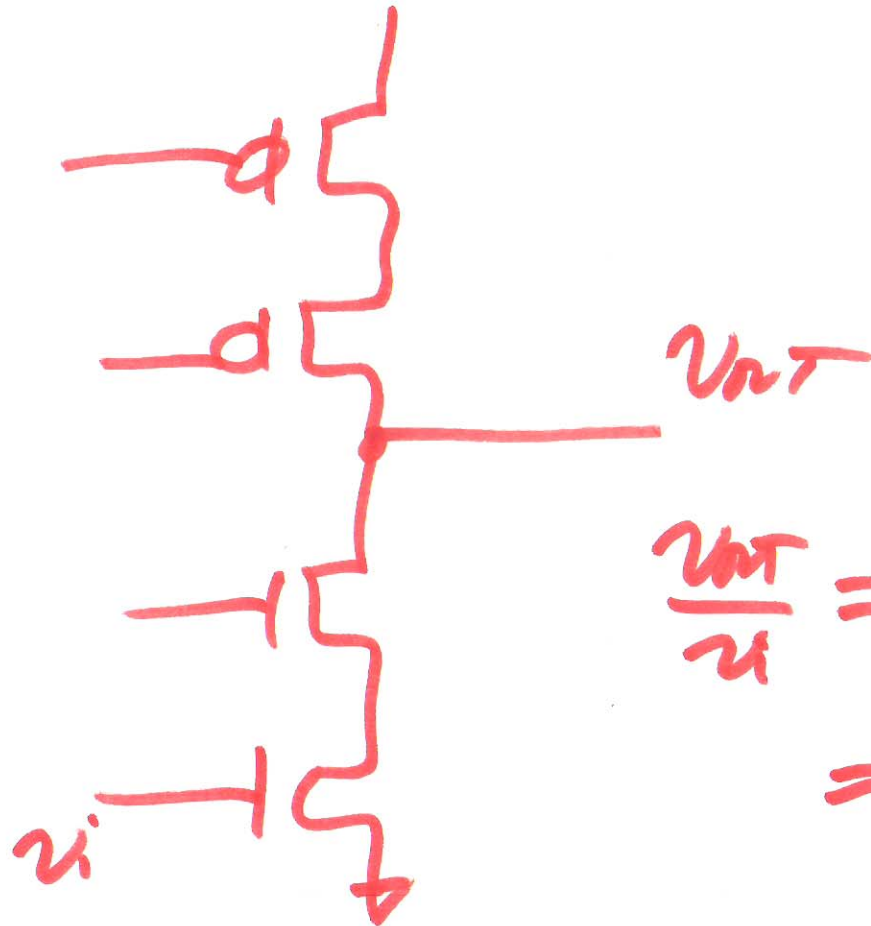
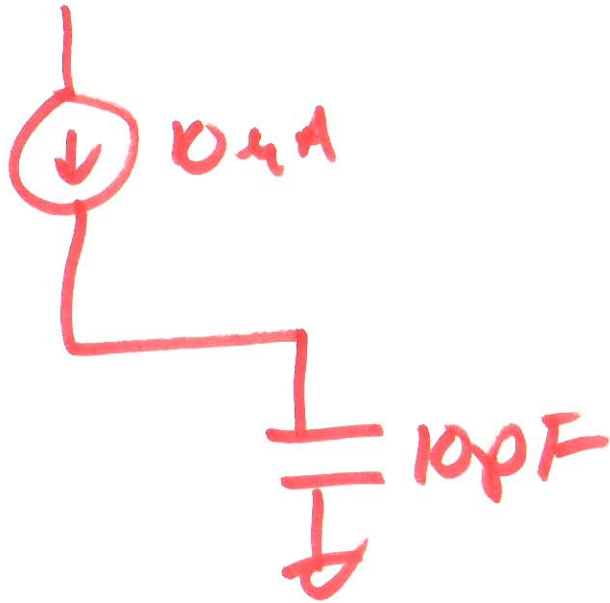
$$\begin{aligned} \frac{v_{out}}{v_i} &= -g_m R_{oens} // R_{oensp} \\ &= -1.50 \frac{\mu A}{V} \cdot 16.6 // 4.2 \text{ ME} \\ &\approx -500 \end{aligned}$$




$$\begin{aligned}
 SR &= \frac{I}{C} = \frac{10 \text{ nA}}{10 \text{ pF}} \\
 &= \frac{1 \text{ V}}{4 \text{ s}} \\
 &= \frac{10^6}{\text{s}} \\
 &= \frac{1 \text{ MEG-V}}{\text{s}}
 \end{aligned}$$

100 nV →

$$\frac{1 \text{ V}}{1 \text{ ns}} = \frac{100 \text{ nV}}{100 \text{ ns}}$$

6)



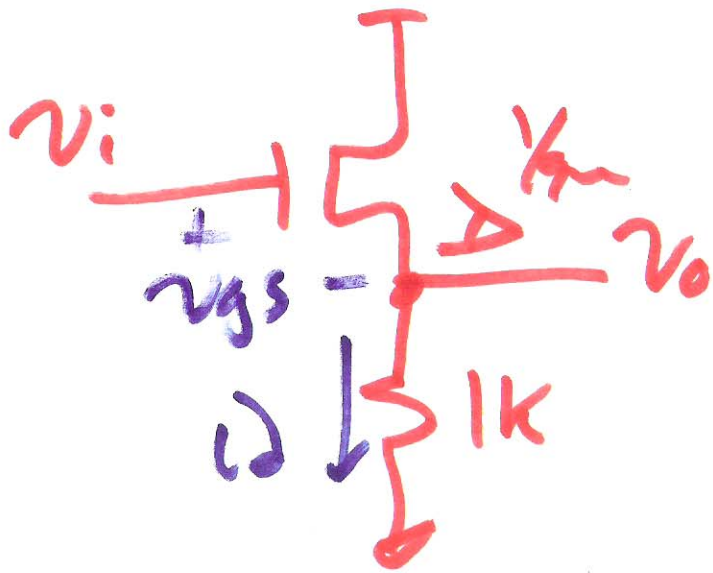


$$v_{gs} = v_i - v_o$$

$$v_o = 1k \cdot i_d$$

$$i_d = g_m v_{gs} = g_m (v_i - v_o)$$

$$v_o = 1k \cdot g_m (v_i - v_o)$$
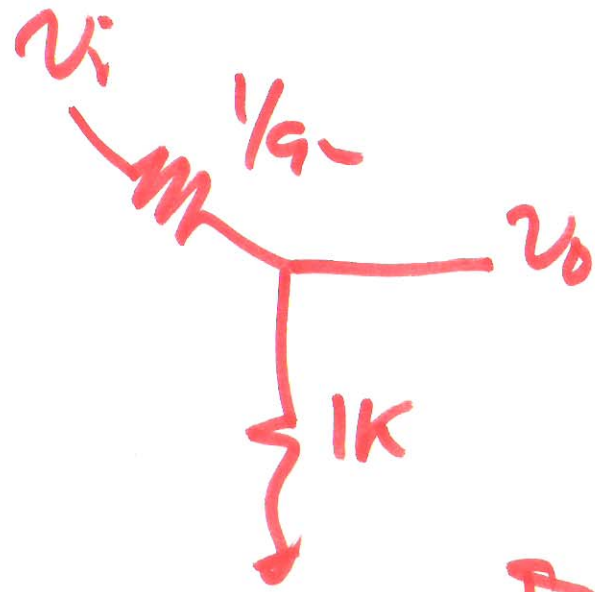
$$\frac{v_o}{v_i} = \frac{g_m \cdot 1k}{1 + g_m \cdot 1k} =$$




$$v_o = v_i \cdot \frac{1k}{1k + 1/g_m}$$


$$\frac{v_o}{v_i} \rightarrow 1$$

$$g_m \rightarrow \text{big}$$



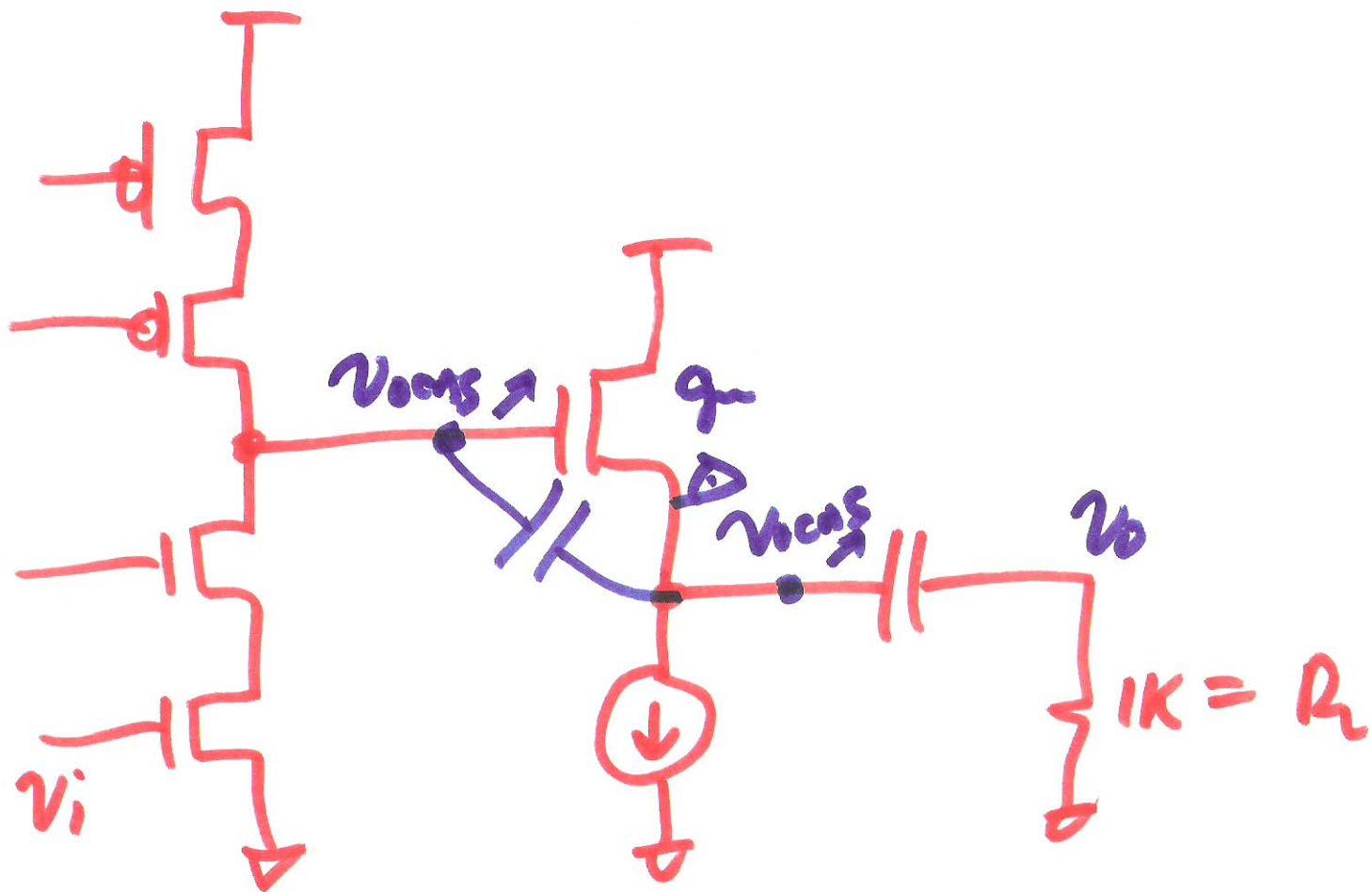

9)

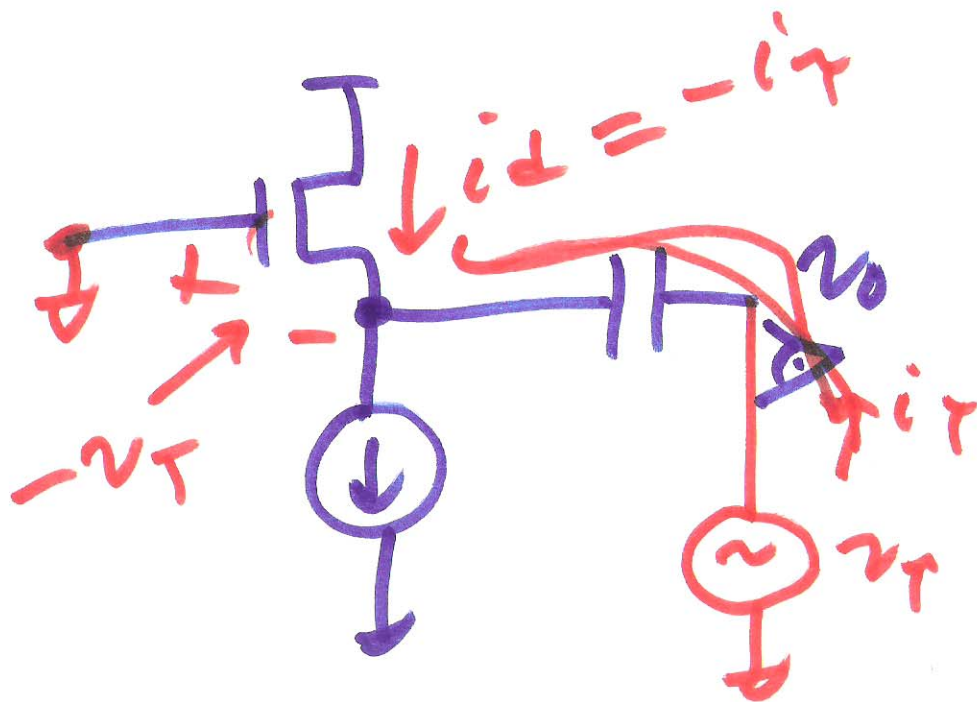


$$g_m v_{gs} = i_d$$

$$g_m (-v_T) = -i_T$$

$$\frac{v_T}{i_T} = \frac{-v_{gs}}{-i_d} = \frac{1}{g_m}$$



$$\frac{v_T}{i_T} = \frac{1}{g_m}$$

10)

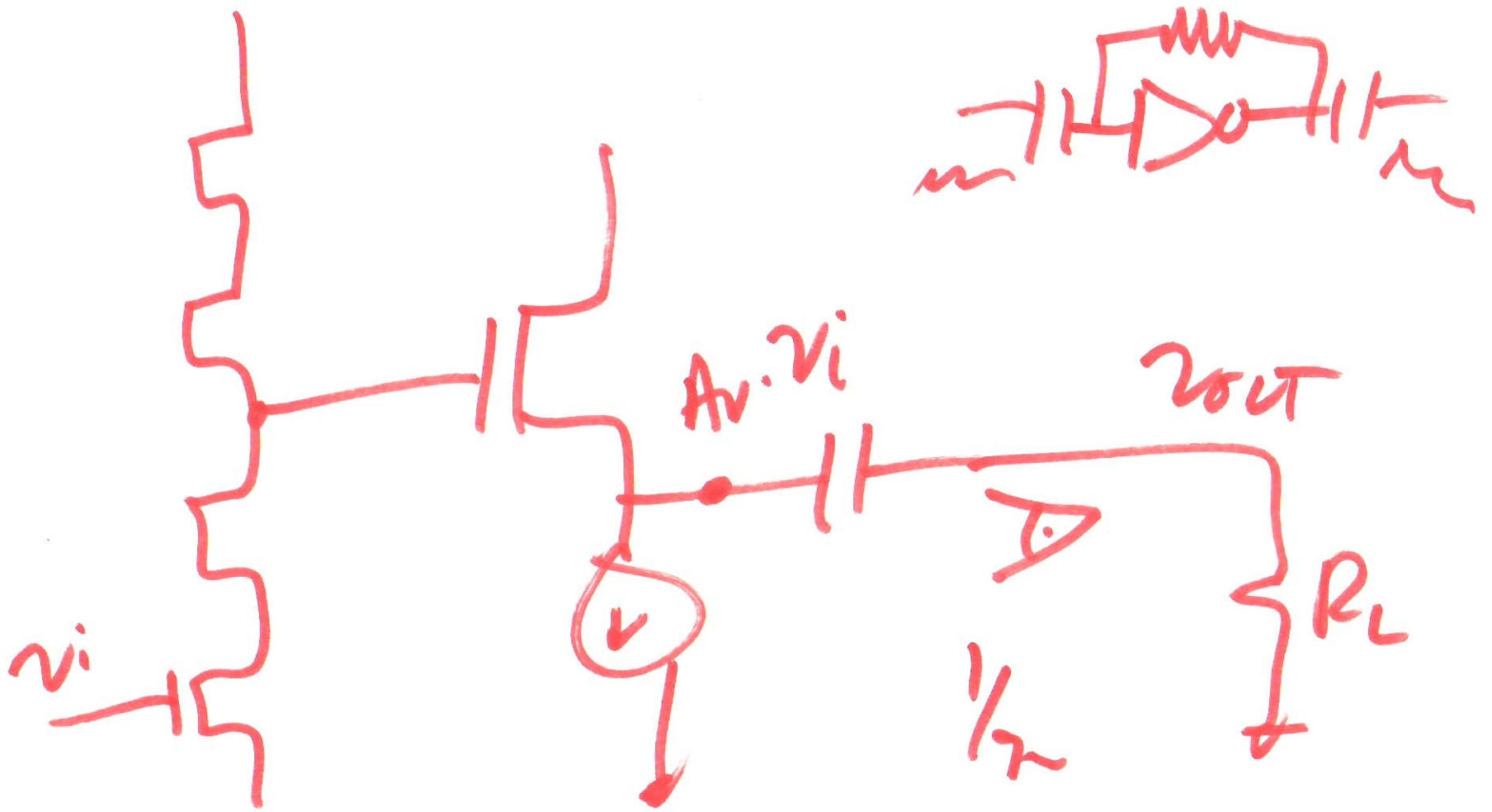

$$A_v \cdot v_i = \frac{R_L}{R_L + \frac{1}{g_m}}$$

# Class A

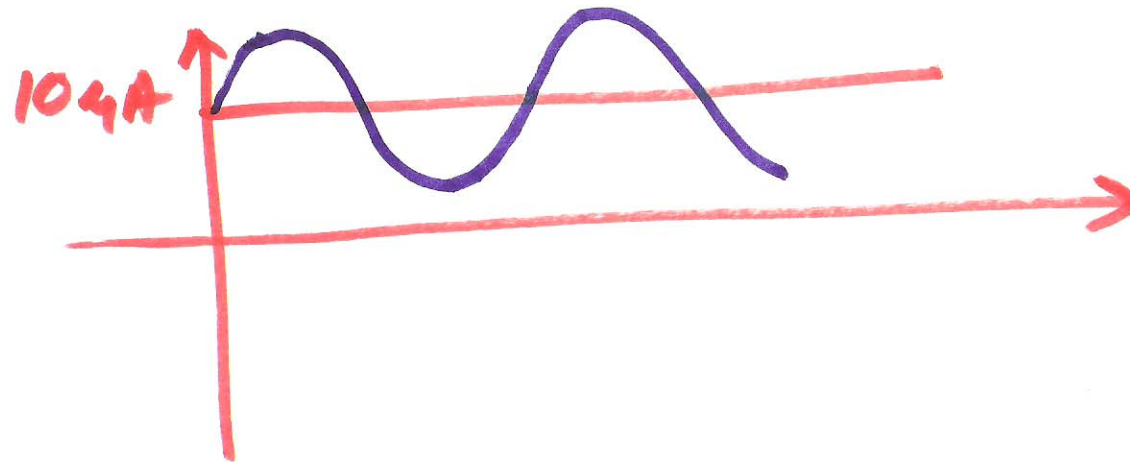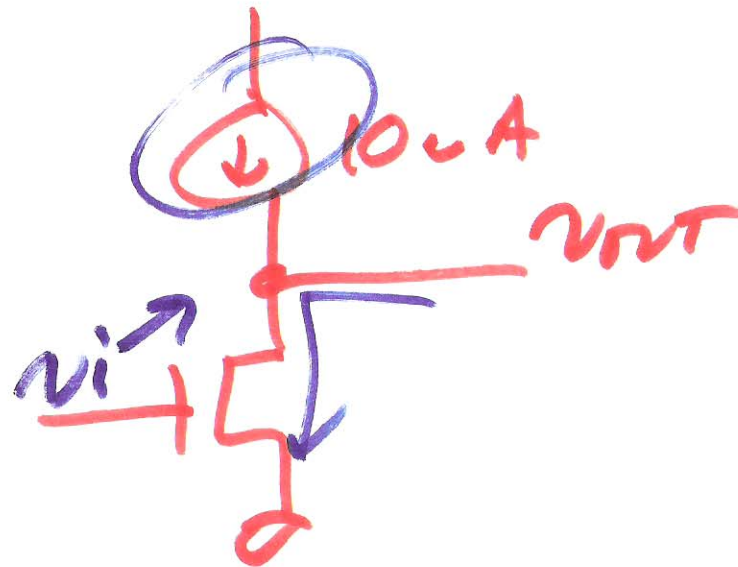

12)

# Class AB

