

EE 422 / ECU 622

Lecture 19 April 10, 2013

A21.19)

$$A_v = -g_m r_{out} || r_{op}$$

$$r_{in} = 10 \text{ M}\Omega$$

$$r_{op} = 8 \text{ M}\Omega$$

$$g_m = \sqrt{2I_D\beta} = 1504 \text{ A} \left(\frac{10}{2}, 204 \text{ A} \right)$$



$$104 \text{ A} \cdot \frac{20}{2} \rightarrow g_m = 1504 \text{ A}$$

$$A_v = -1504 \frac{\text{A}}{\text{V}} \cdot 10 \parallel 8 \text{ M}\Omega$$

$$= -150 \cdot (4.4) = -660 \frac{\text{V}}{\text{V}}$$

DC gain

CMOSedu.com

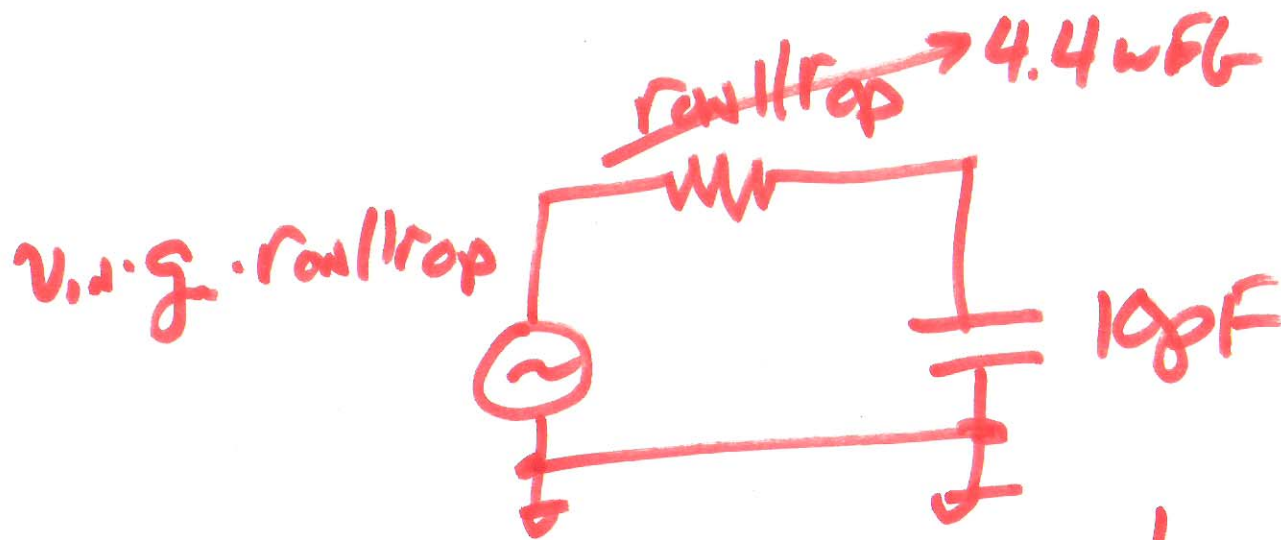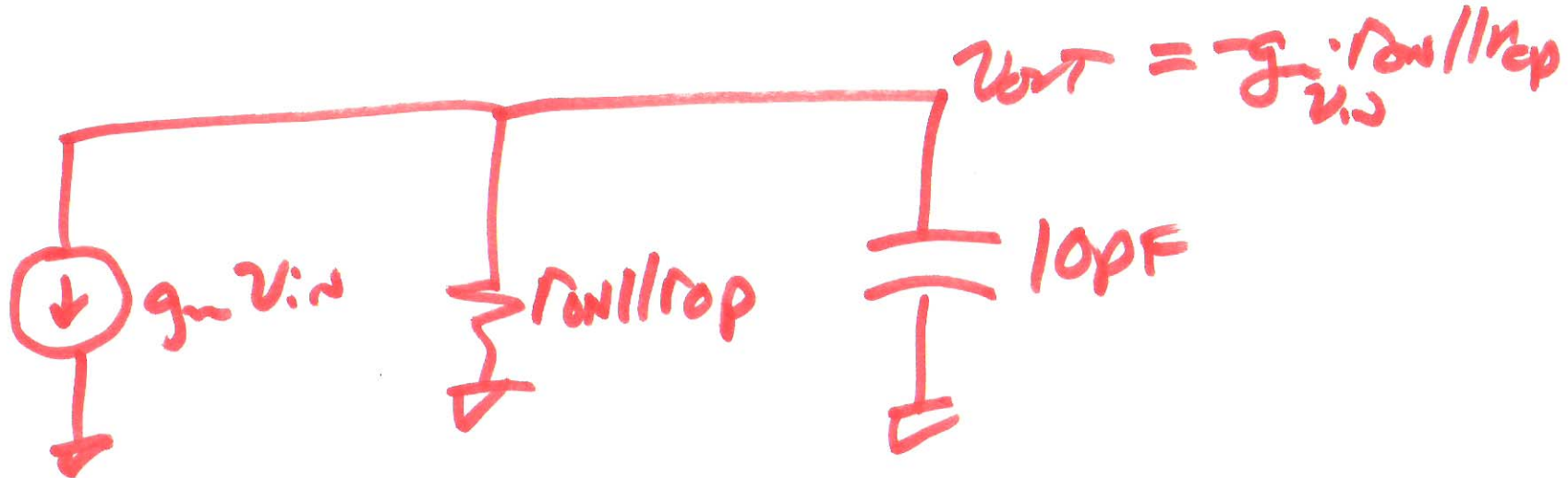


$$f_{-3dB} = \frac{1}{2\pi \cdot 4.4 \text{ M}\Omega \cdot 10 \text{ pF}}$$

$$= \frac{1}{6.28 \cdot 44 \cdot 10^{-6}}$$

CMOSedu.com


$$\approx 4 \text{ kHz} \rightarrow 3.6 \text{ kHz}$$
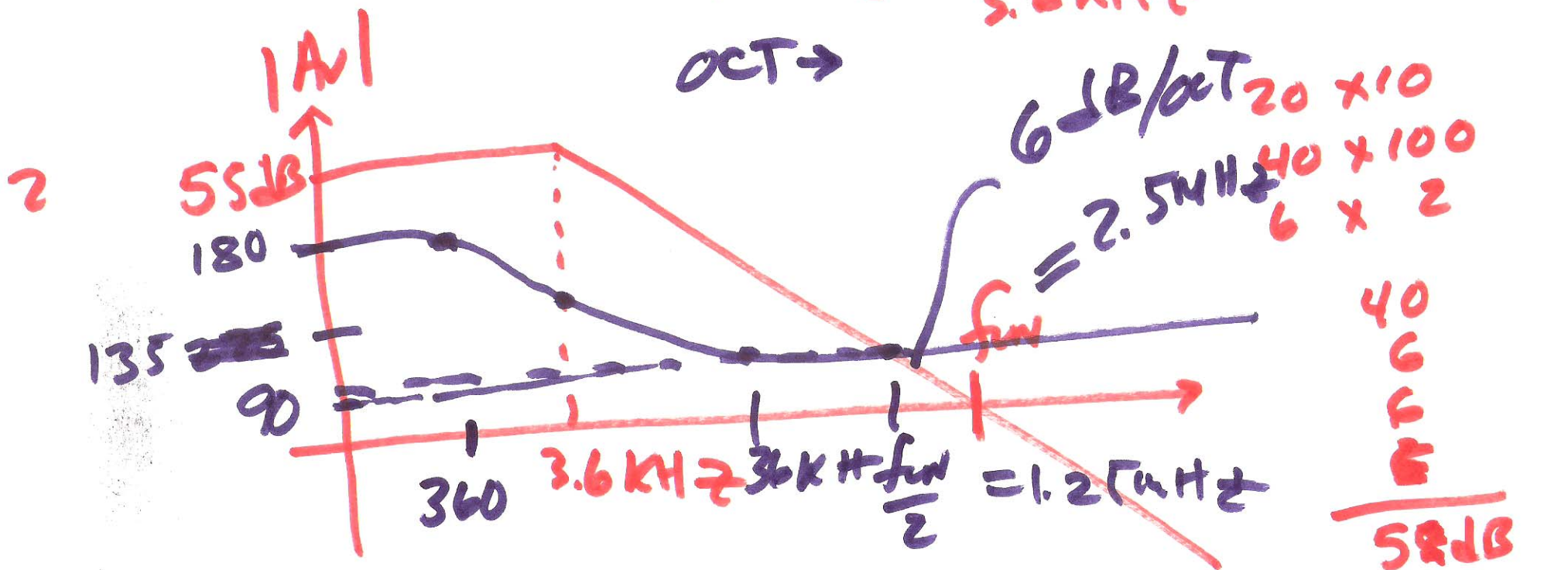
$$A_v(s) = \frac{-660 \rightarrow 180}{1 + j \frac{f}{3.6 \text{ kHz}}}$$



$$1 = \frac{660}{\sqrt{1 + \left(\frac{f_{un}}{3.6 \text{ kHz}}\right)^2}}$$

f_{un} f_{un}

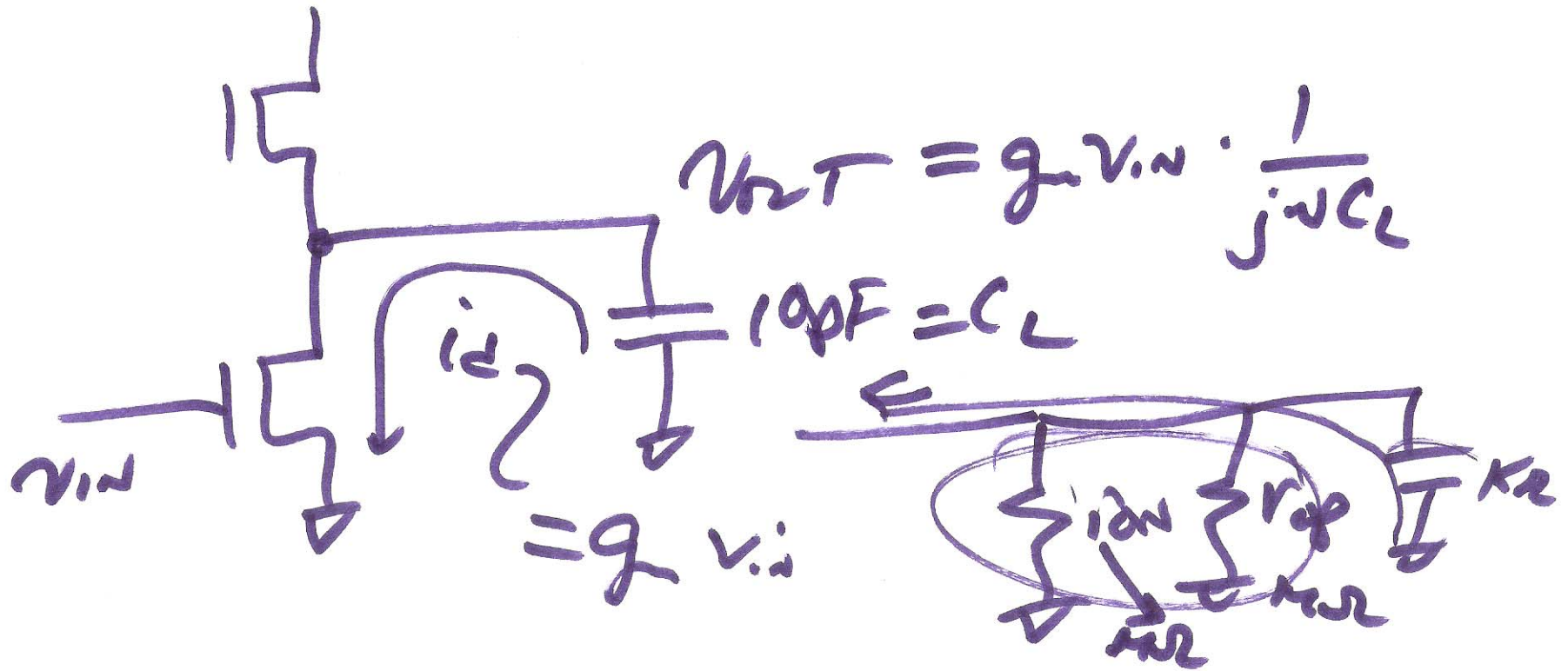

$$\left| \frac{v_{OUT}}{v_{in}} \right| = 1 = \left| \frac{g_m}{2\pi f_{in} \cdot C_L} \right|$$

$$2.5\text{MHz} = \frac{150\mu\text{A/V}}{2\pi \cdot 10\text{pF}} \leftarrow f_{in} = \frac{g_m}{2\pi C_L}$$

$$\frac{v_{out}}{v_{in}} = \frac{-g_m \cdot r_{out||r_{op}}}{1 + j \frac{f}{\frac{1}{2\pi r_{out||r_{op}} \cdot C_L}}}$$

for large f the real part is small compared to the imaginary part


$$\frac{v_{out}}{v_{in}} \approx \frac{-g_m \cdot r_{out||r_{op}}}{j \cdot 2\pi f_{out||r_{op}} \cdot C_L}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = 1 = \frac{g_m}{2\pi f_{out||r_{op}} \cdot C_L}$$


CMOSedu.com

AT ~~20~~ 1 MHz = 10⁶
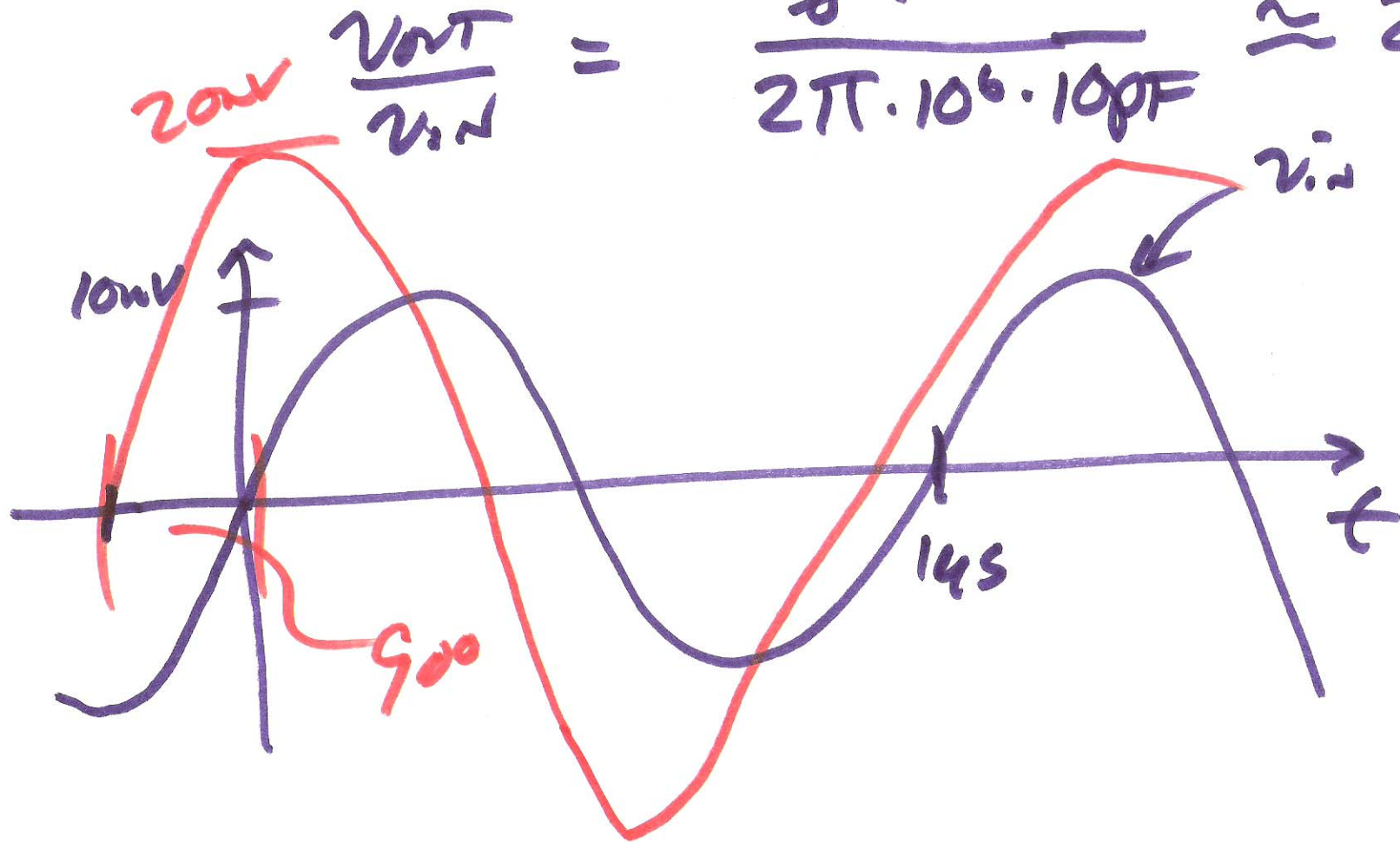
$$\frac{g_m}{2\pi \cdot 10^6 \cdot 100\text{pF}} \approx 2$$



6)

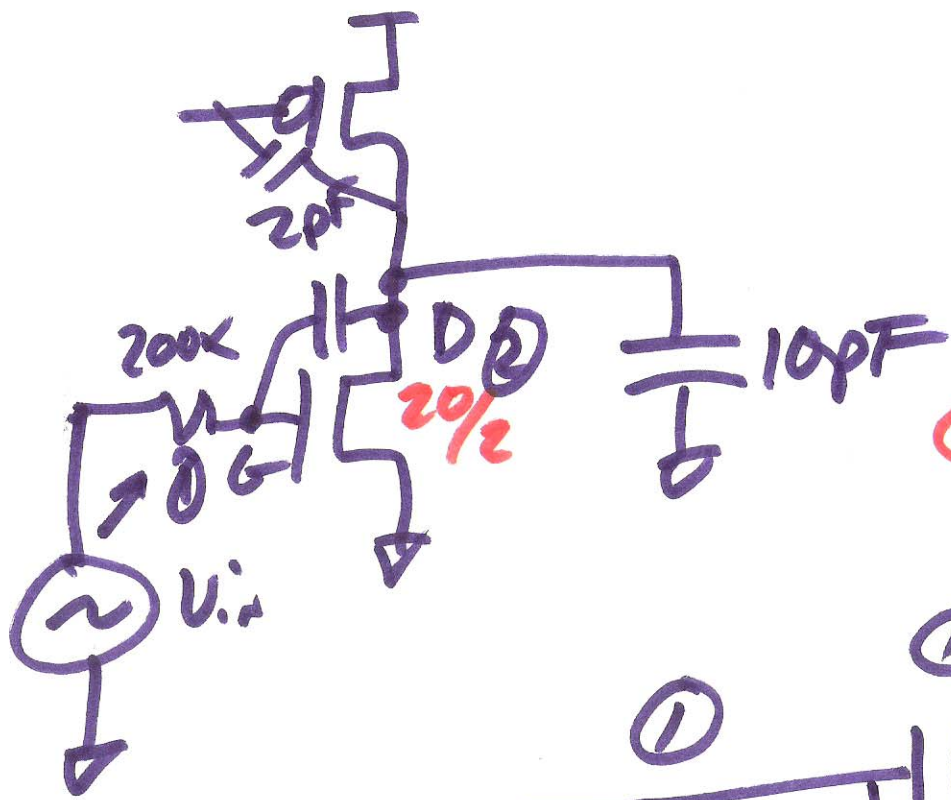


$$g_{m1} = \frac{1}{200k}$$

$$R_1 = 200k$$

$$C_1 = C_{gs} = 46.6 fF$$

$$C_2 = 10pF \approx 10pF + C_{dsp}$$


$$g_{m2} = 150 \mu/V$$

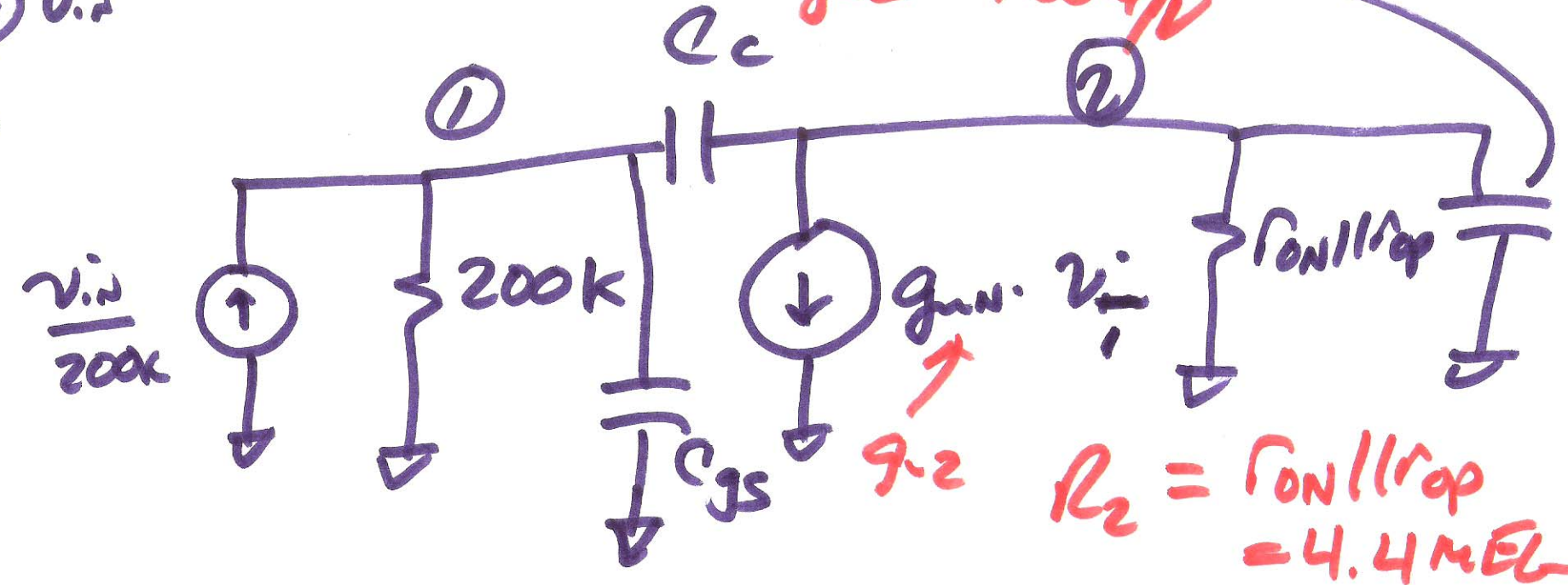

$$R_2 = r_{on} || r_{op} = 4.4 M\Omega$$

$$C_2 \approx 10pF$$

7)

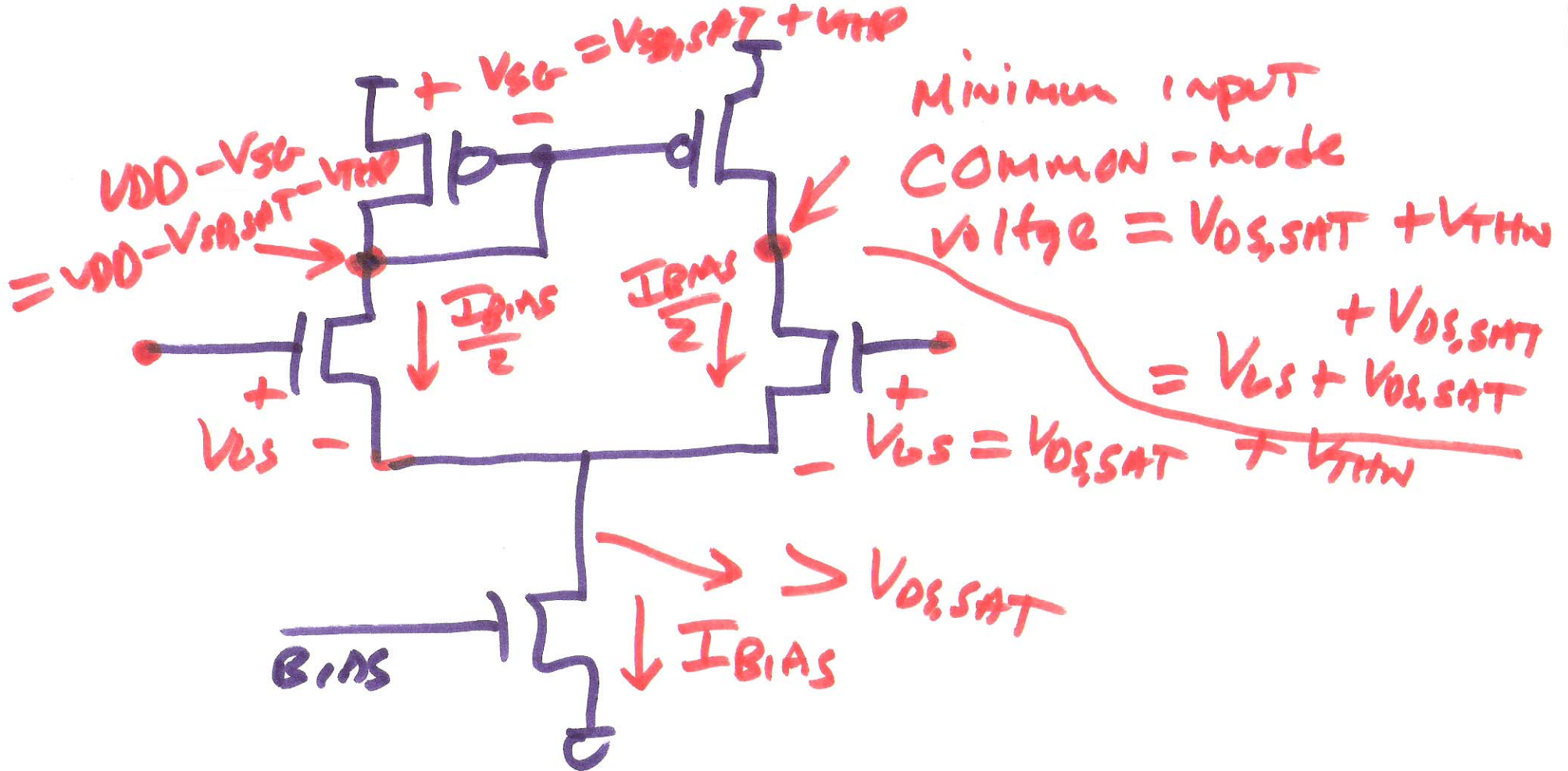

a)

