

Analog IC Design -


A21.23

$C_1 = C_{gs} + C_{gd} + C_{ds}$ 4/17/13

Lecture 27

$f_{op} = \frac{1}{204 \cdot 0.0125 \sqrt{V}} = 4 \text{ MHz}$

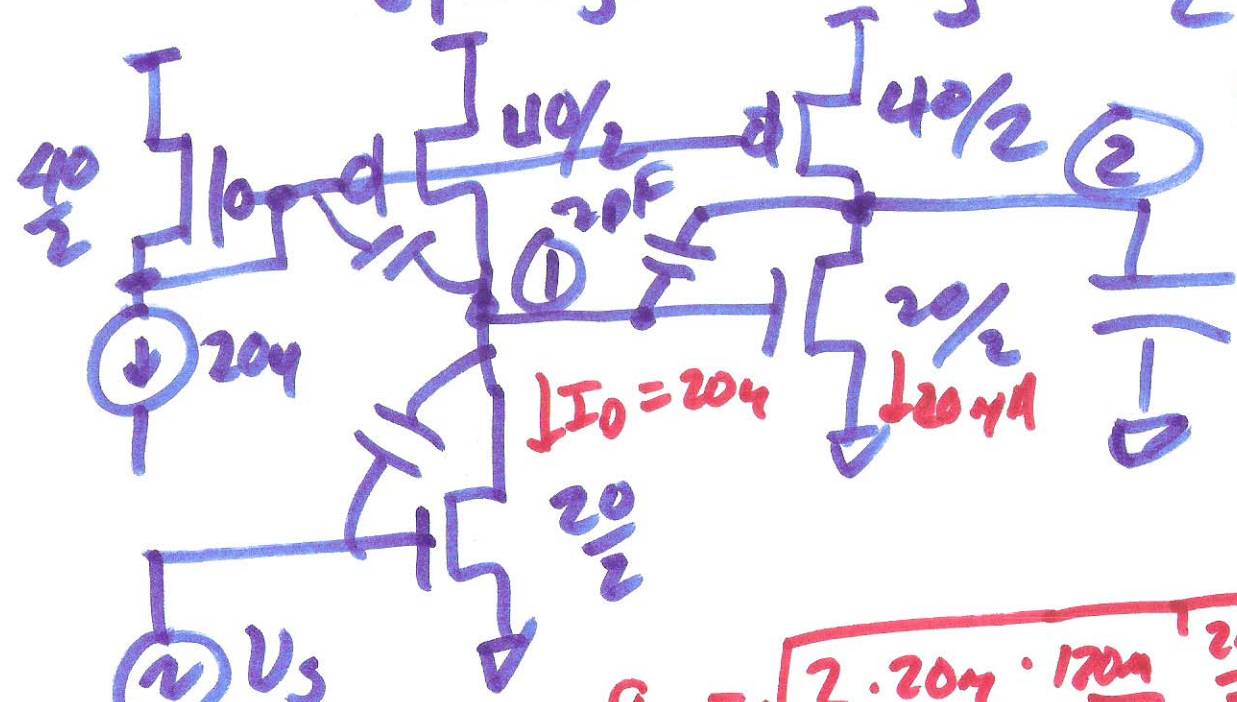$f_{on} = \frac{1}{204 \cdot 0.01} = 5 \text{ MHz}$



$g_{m1} = \sqrt{2 \cdot 204 \cdot 1200 \cdot \frac{20}{\sqrt{2}}} = \sqrt{40 \cdot 1200} \frac{\mu A}{V}$

$C_c = 2 \text{ pF}$

$R_1 = R_2 = r_{op} || r_{on} = 2.22 \text{ M}\Omega$

$g_m = 220 \frac{\mu A}{V}$

$g_{m1} = g_{m2} = g_m$

1)

$$C_1 = C_{gsN} + C_{gdN} + C_{dgP}$$

46.6

4

8

$$C_1 = 58.6 \text{ fF}$$
$$C_2 \approx 10 \text{ pF}$$

$$R_1 = R_2 = 7.2 \text{ e6}$$

$$g_{m1} = g_{m2} = 220 \mu\text{A}$$

$$g_{m1} \cdot R_1 = g_{m2} \cdot R_2 = 488 \rightarrow$$

$$g_{m1} \cdot g_{m2} \cdot R_1 \cdot R_2 = 488^2$$
$$= 240\text{k}$$

Low freq. gain \rightarrow 107dB

$$f_1 = \frac{1}{2\pi g_{m2} R_1 R_2 C_c} = \frac{1}{2\pi \cdot 488 \cdot 2.2e6 \cdot 2pF}$$

$$= \frac{1}{(2\pi)(488)(4.4e-6)}$$

$$f_1 = \frac{1}{15 \cdot 10^{-3}} = \frac{1}{.015}$$



$$f_2 = \frac{g_{m2}}{2\pi \cdot C_c} = \frac{2204}{2\pi \cdot 2PF} = \frac{2204}{2\pi \cdot 2PF} = 17.5 \text{ kHz}$$


$$f_2 = \frac{g_{m2}}{2\pi \cdot (C_1 + \frac{C_1 C_2}{2204 C_c} + C_2)} \rightarrow \frac{2204}{2\pi \cdot 10.3pF}$$

$$= \frac{2204}{2\pi (5.16f + \frac{58.6 \cdot 10pF}{2PF} + 10pF)}$$



$$f_2 = \underline{\underline{3.48 \text{ MHz}}}$$

3)

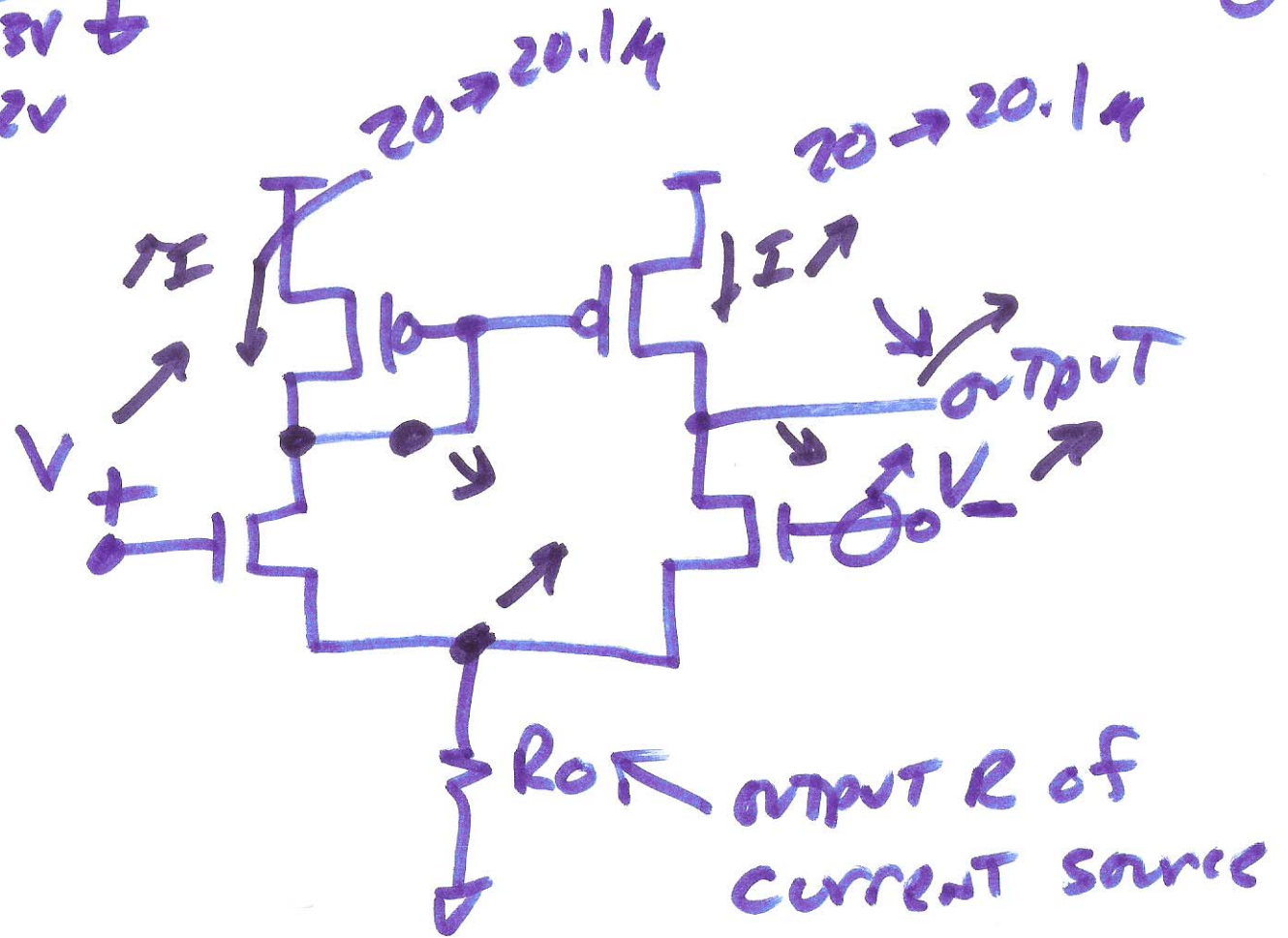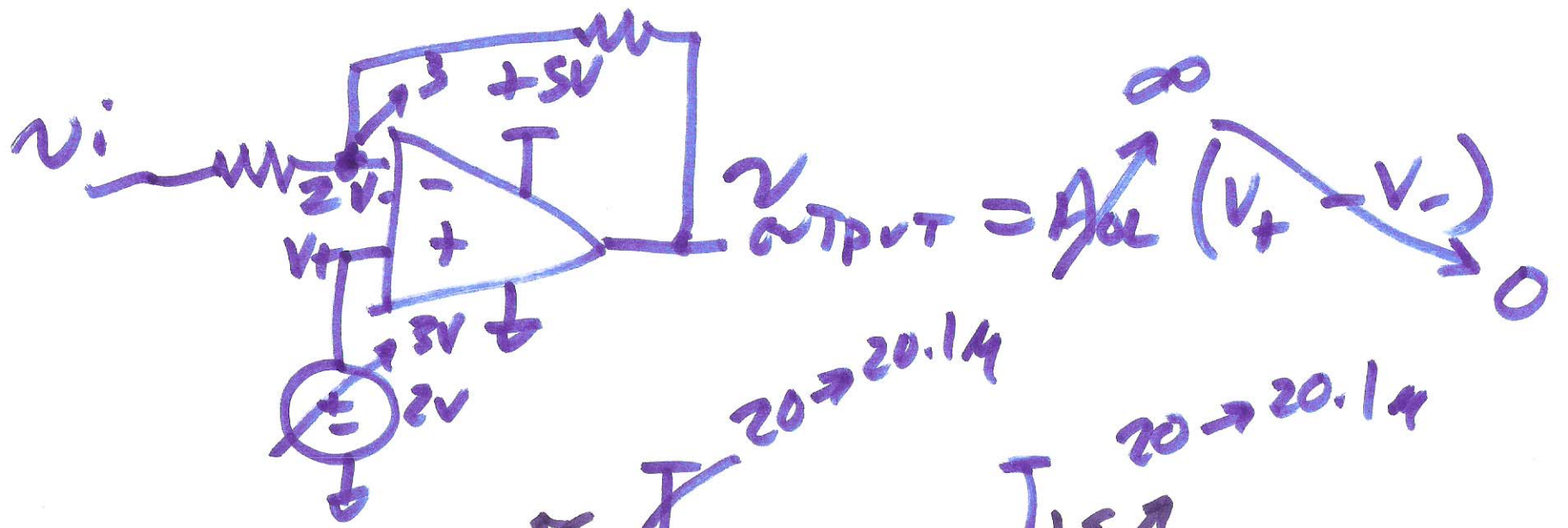




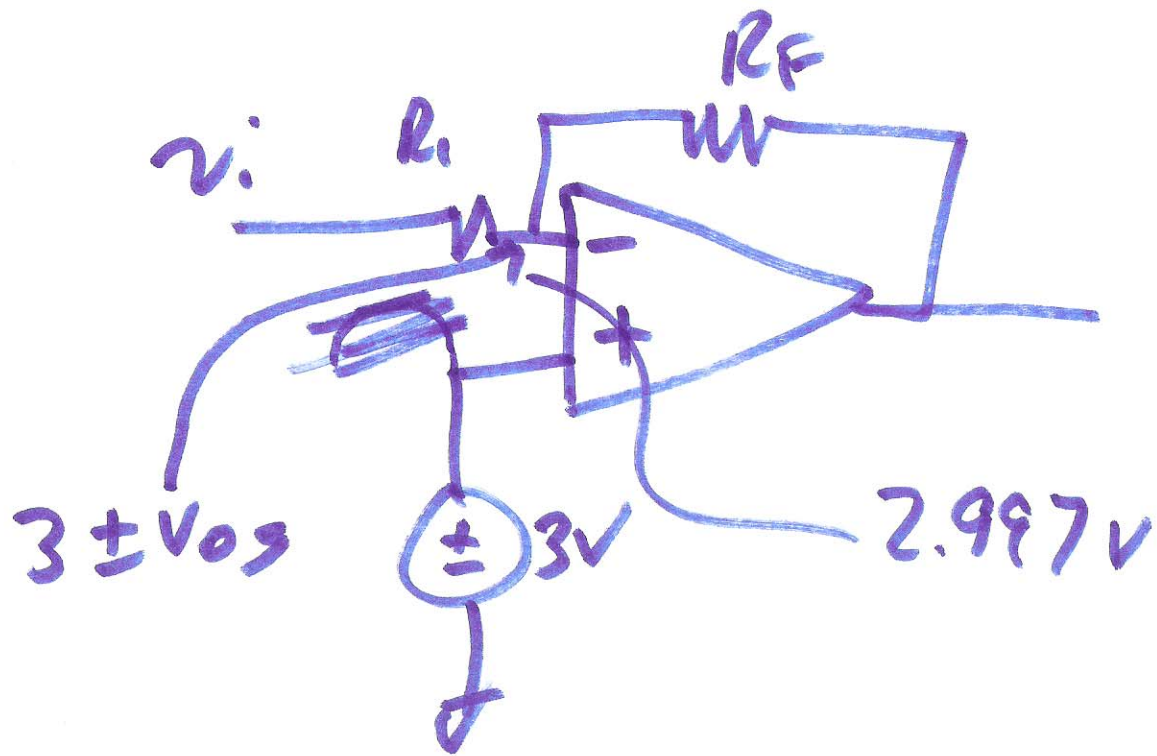


5)

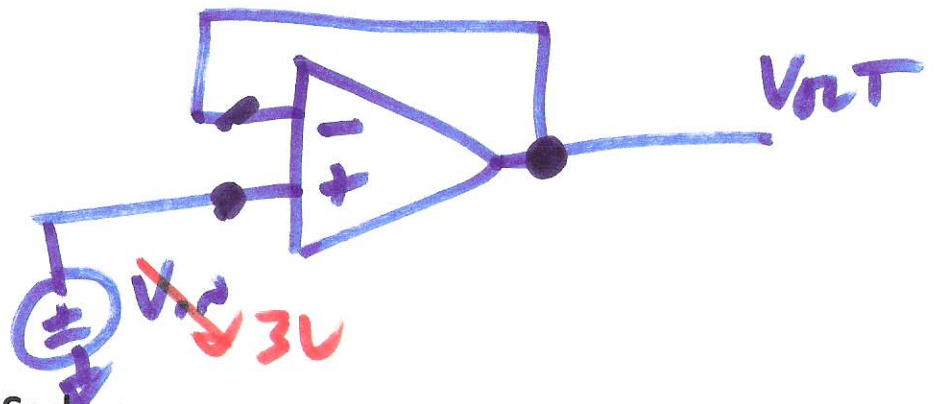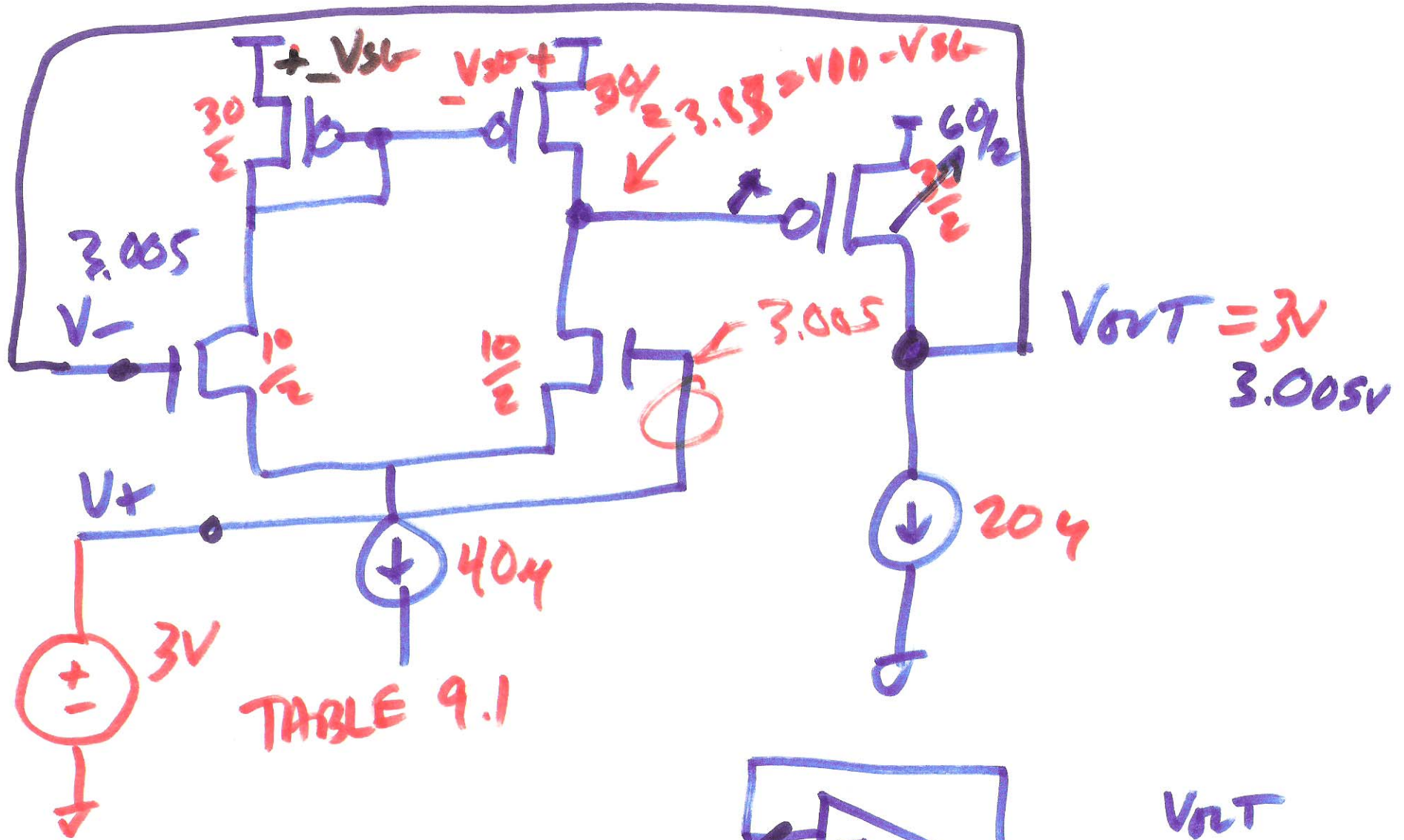


6)


$$V_{out} = A_{OL} \cdot (V_+ - V_-)$$

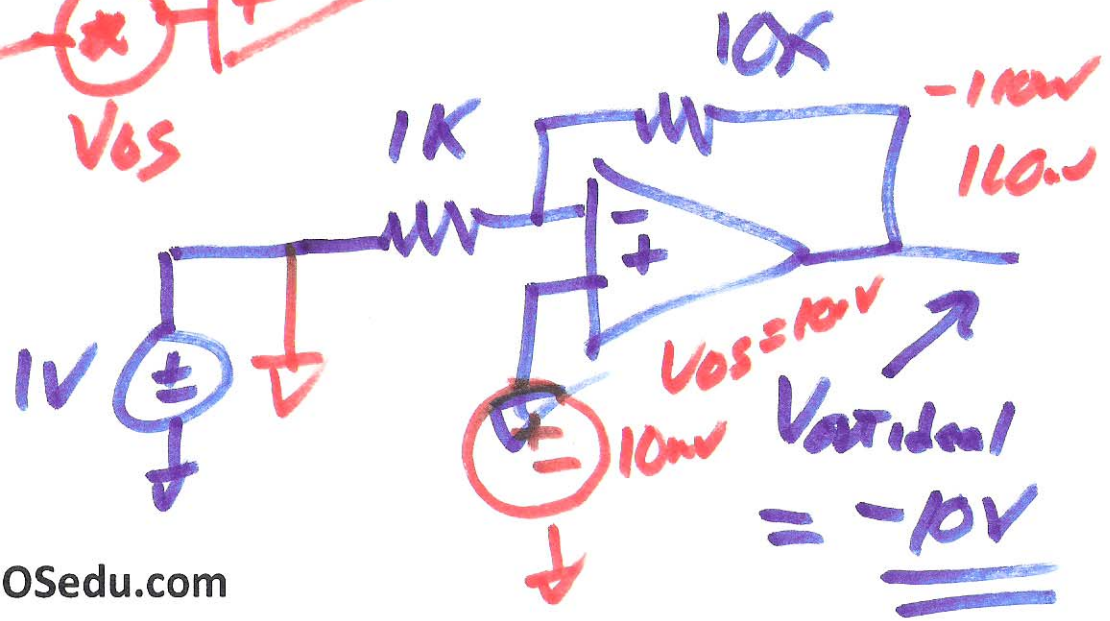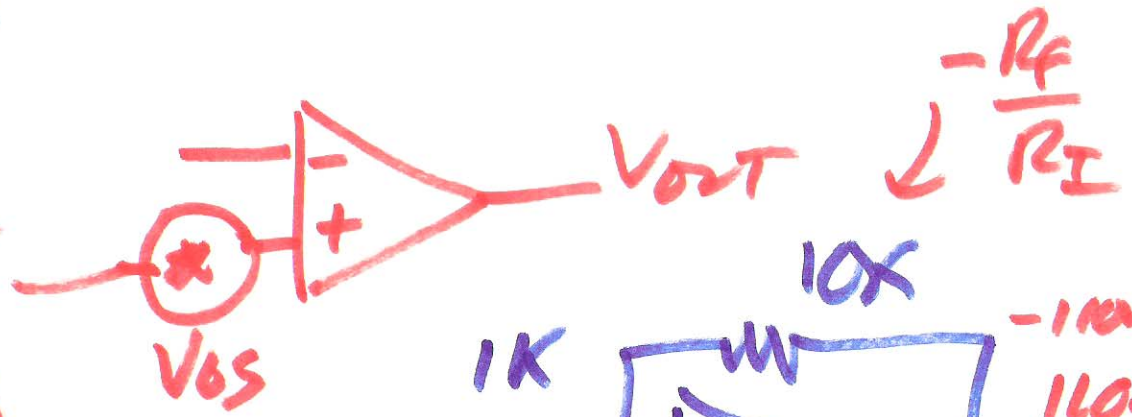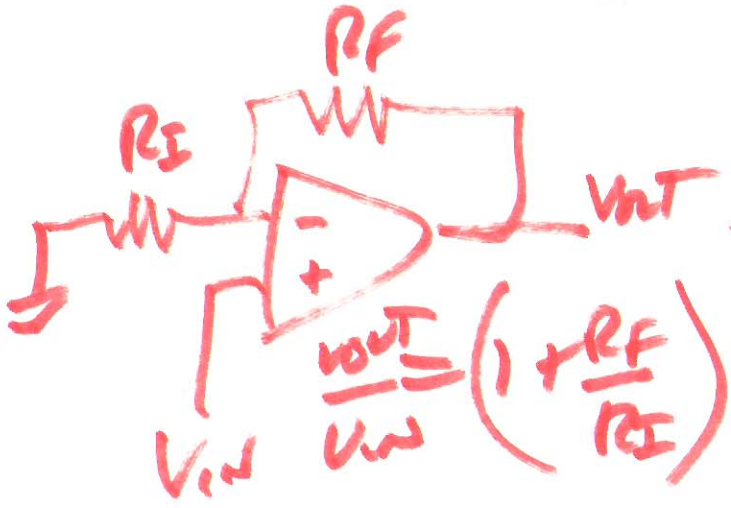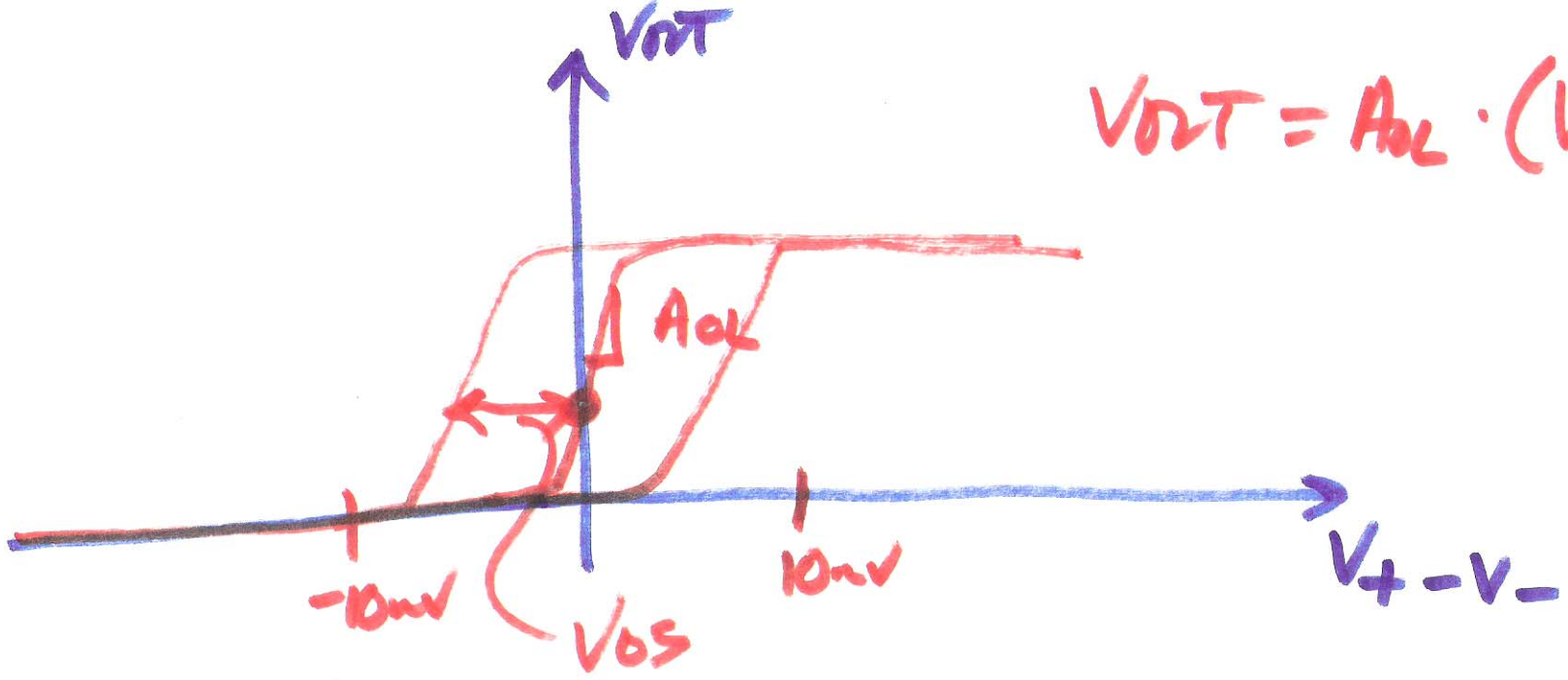

7)

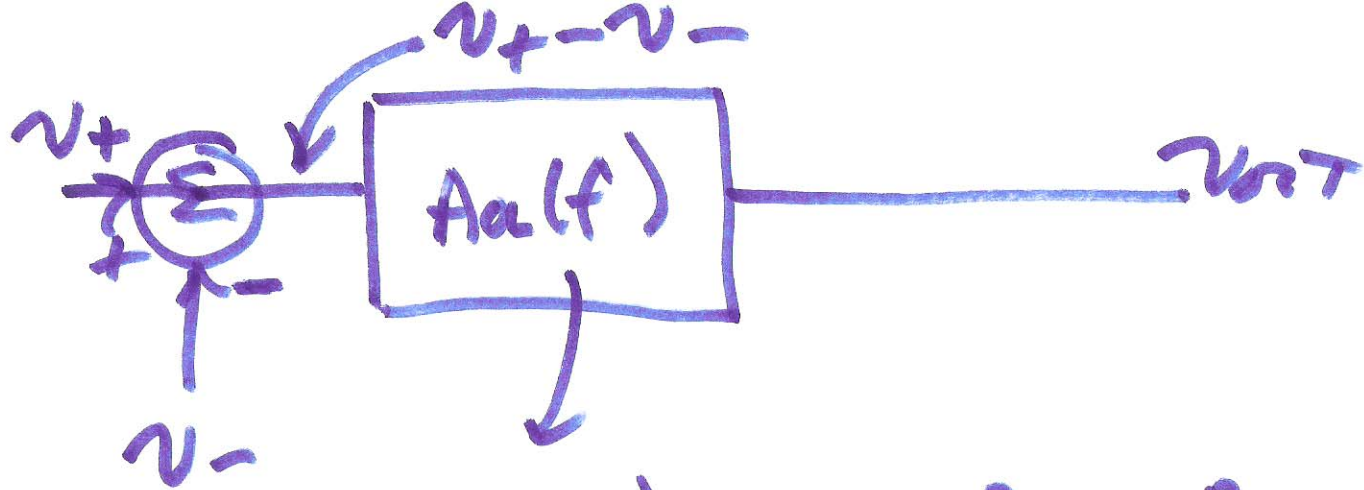
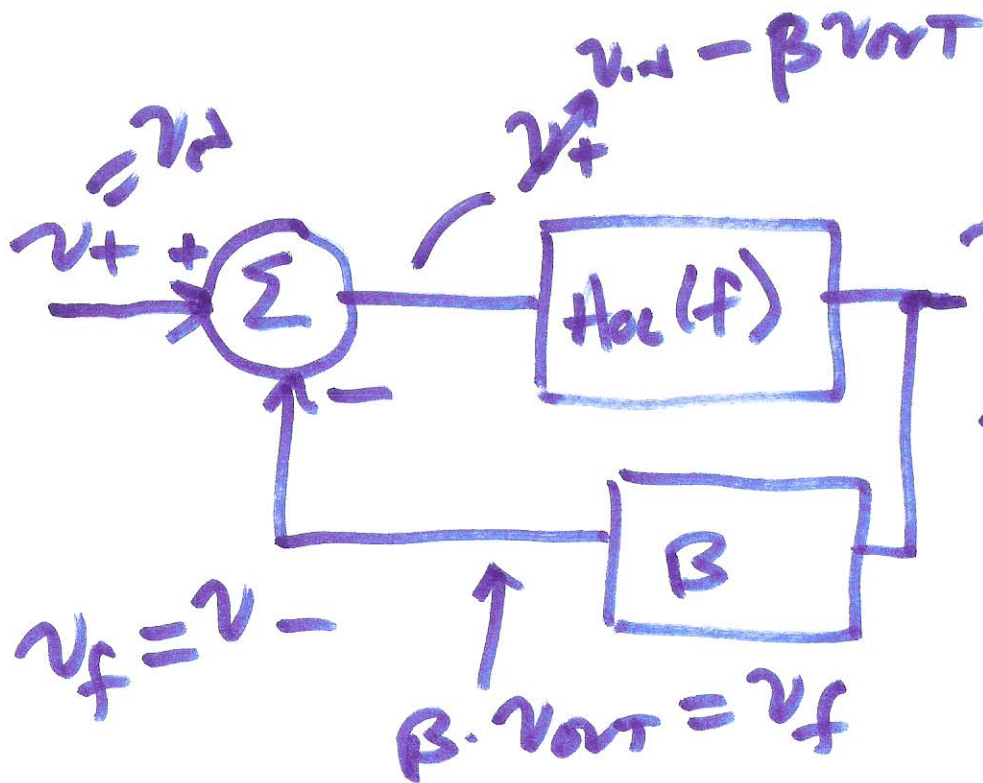
$$A_{ol}(f) = g_{m1} R_1 g_{m2} R_2 \cdot \frac{1 - j\frac{f}{f_c}}{\left(1 + j\frac{f}{f_1}\right)\left(1 + j\frac{f}{f_2}\right)}$$




$$v_{out} = A_{ol}(f)(v_+ - \beta v_{out})$$

$$\frac{v_{out}}{v_+} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

$$= \frac{1}{\frac{1}{A_{OL}} + \beta}$$

$$A_{CL} = \frac{v_{out}}{v_+} \Big|_{A_{OL} \rightarrow \infty} = \frac{1}{\beta}$$

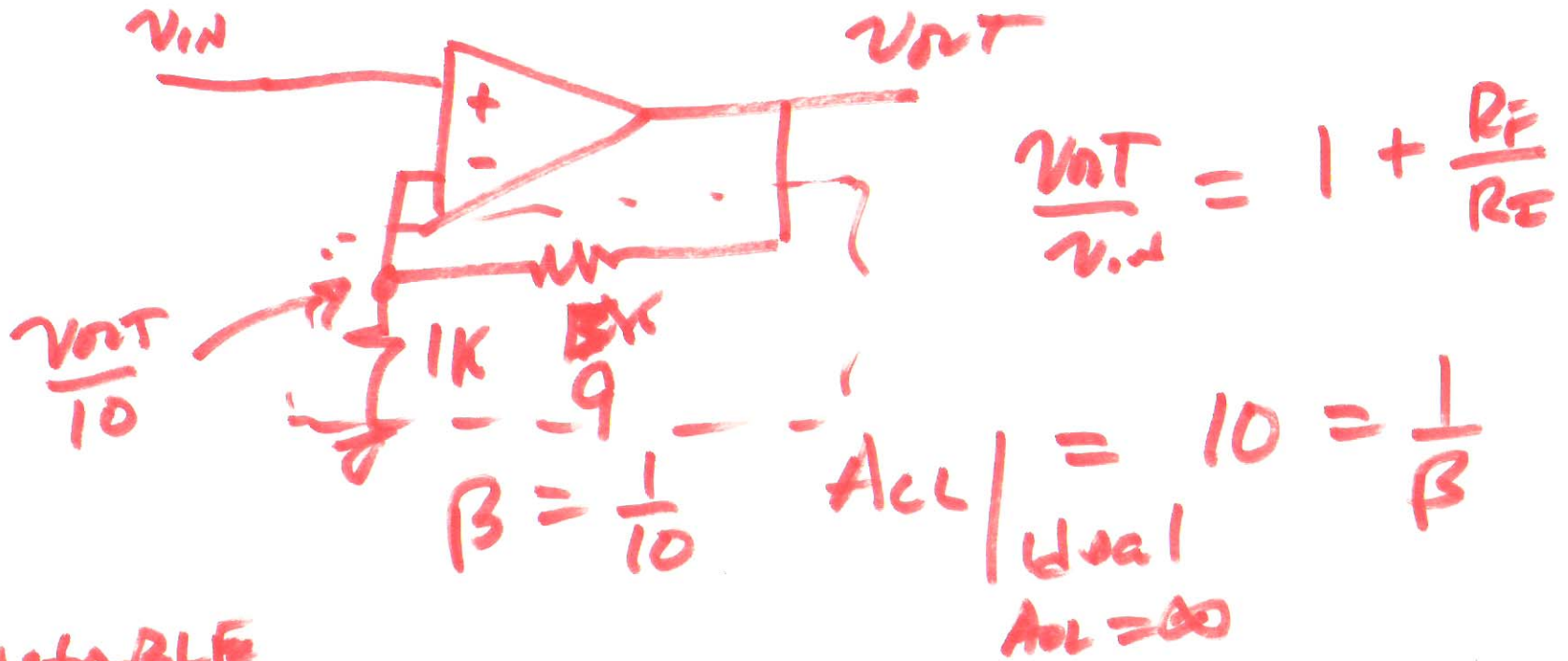

UNSTABLE

$$A_{OL}(f) \cdot \beta = -1$$

$$|A_{OL} \cdot \beta| = 1 \quad \angle A_{OL} \cdot \beta = 180^\circ$$

when all v_{OUT} feedback $\beta = 1$

$$|A_{OL}| = 1 \quad \angle A_{OL} = 180^\circ$$