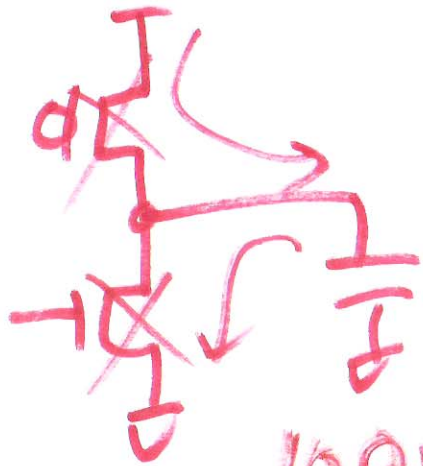


EE 422 / ECG 622

Lecture 24

4/29/13



$$I_D = \frac{k_p}{2} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$I = C \frac{dV}{dt}$$

Class AB output

$$\frac{100V}{4s} = \frac{dV}{dt} = \frac{\Delta V}{\Delta t} =$$


buffer or 100k


$$\frac{100W}{4s}$$

$$= \frac{\Delta V}{\Delta t} = \frac{I_{BIAS}}{1pF}$$

$$10^{-12} \cdot 10^2 \cdot 10^6 = I_{BIAS}$$

$$I_{BIAS} = 10^{-4} = 100\mu A$$

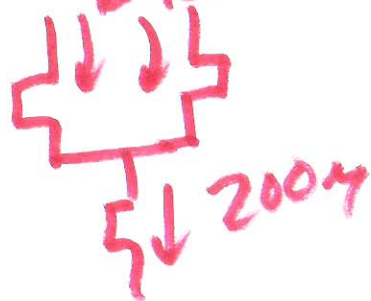

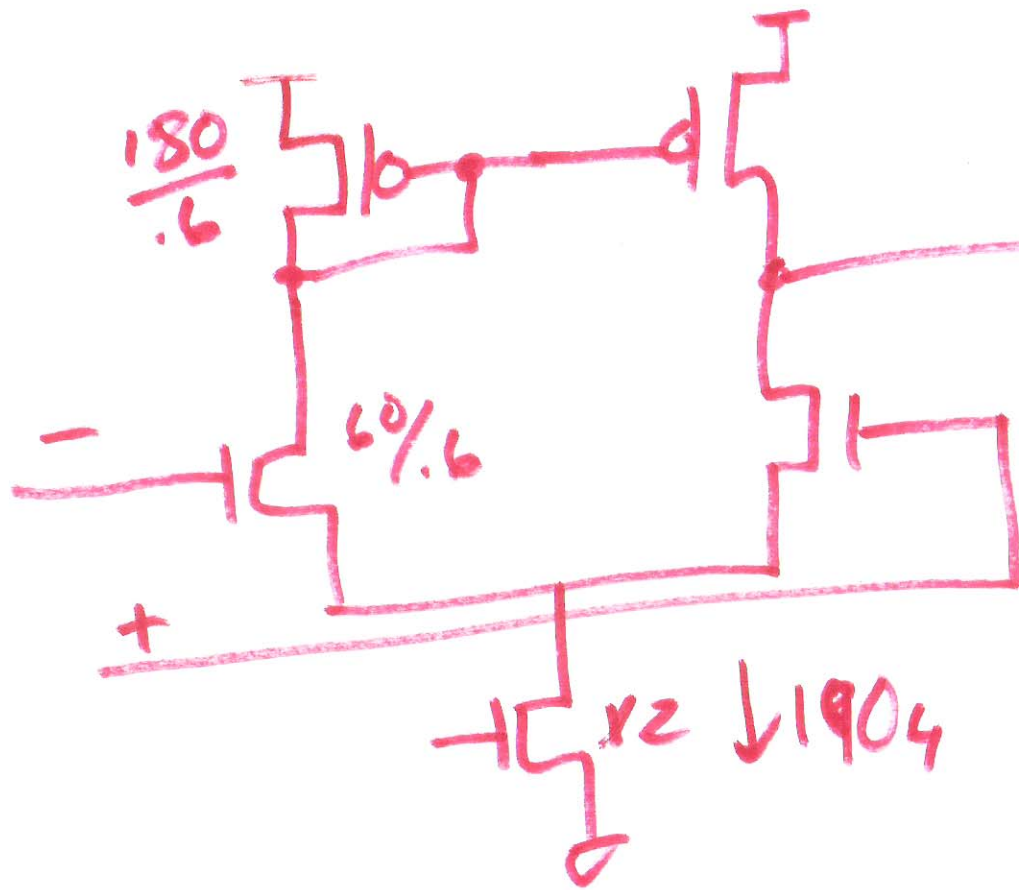

$$I_D = 904 \text{ A}$$

$$V_{ov} \approx 100 \text{ mV}$$

$$\frac{W}{L} / p = \frac{180}{.6}$$

$$\frac{W}{L} / n = \frac{60}{.6}$$

2)