
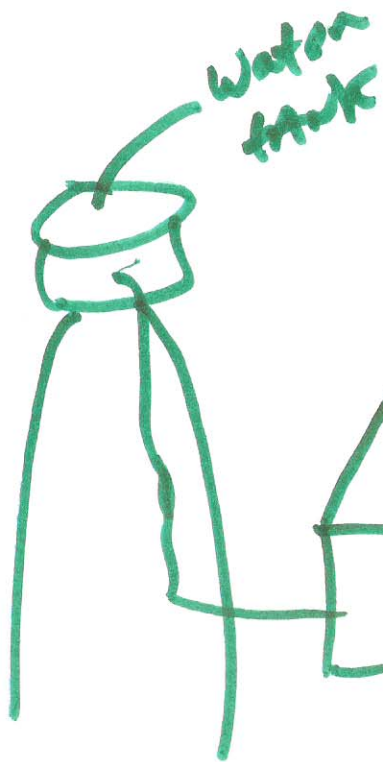


EE 422 ECG 622  
 Analog IC Design  
 Lecture 3


1/30/2013

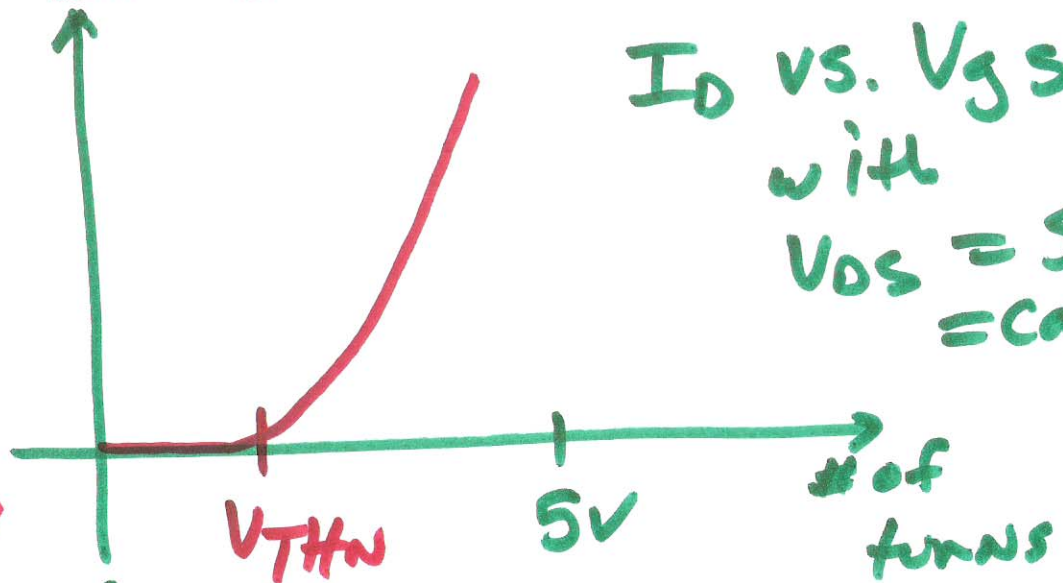

water,  $I_D$



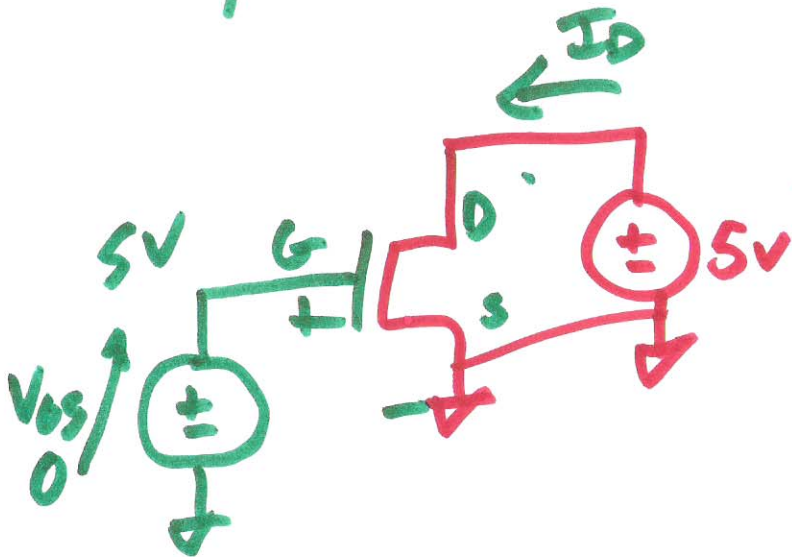$I_D$  vs.  $V_{GS}$   
 with  
 $V_{DS} = 5$   
 $= \text{const.}$



$$I_D = \frac{\beta_N}{2} (V_{GS} - V_{THN})^2$$


$$V_{DS} > V_{GS} - V_{THN}$$

$$V_{GS} > V_{THN}$$

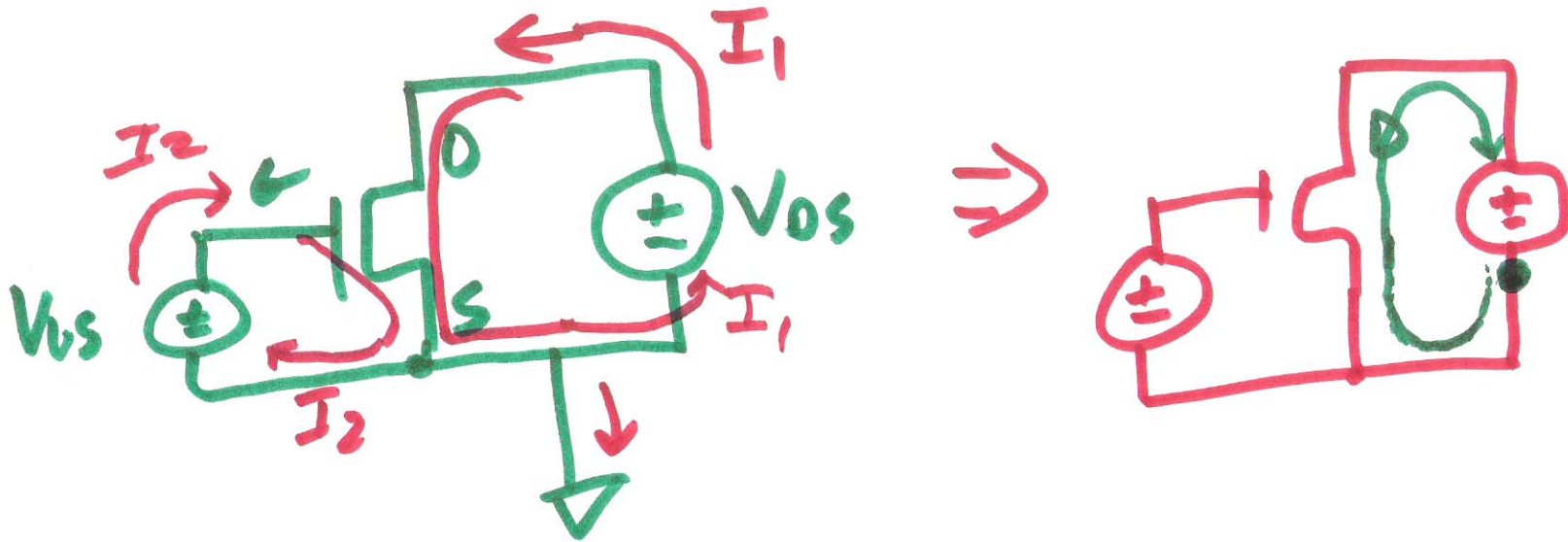
# TRANSconductance parameter


$$k_{P_N} = \mu_n \cdot C_{ox} \cdot \frac{W}{L} = 4n \cdot \frac{\epsilon_{ox}}{t_{ox}}$$

$$\beta_N = k_{P_N} \cdot \frac{W}{L} = 4n \cdot C_{ox} \cdot \frac{W}{L} = 4n \cdot \frac{\epsilon_{ox}}{t_{ox}} \cdot \frac{W}{L}$$





2)

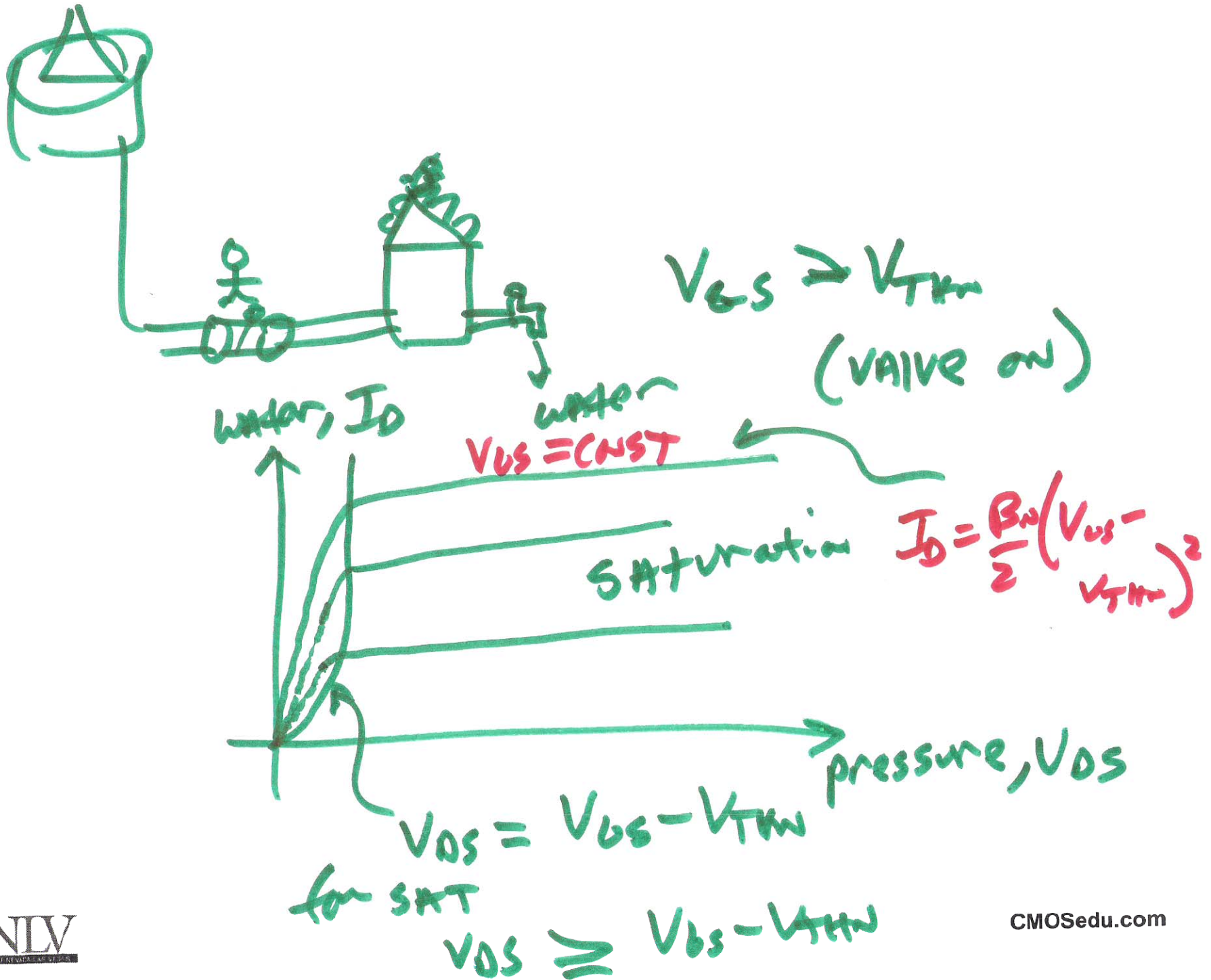

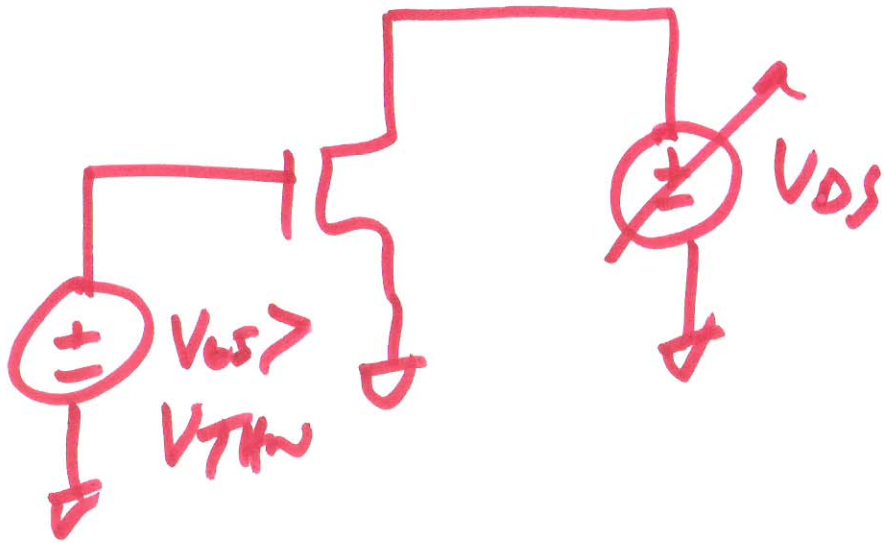

4)

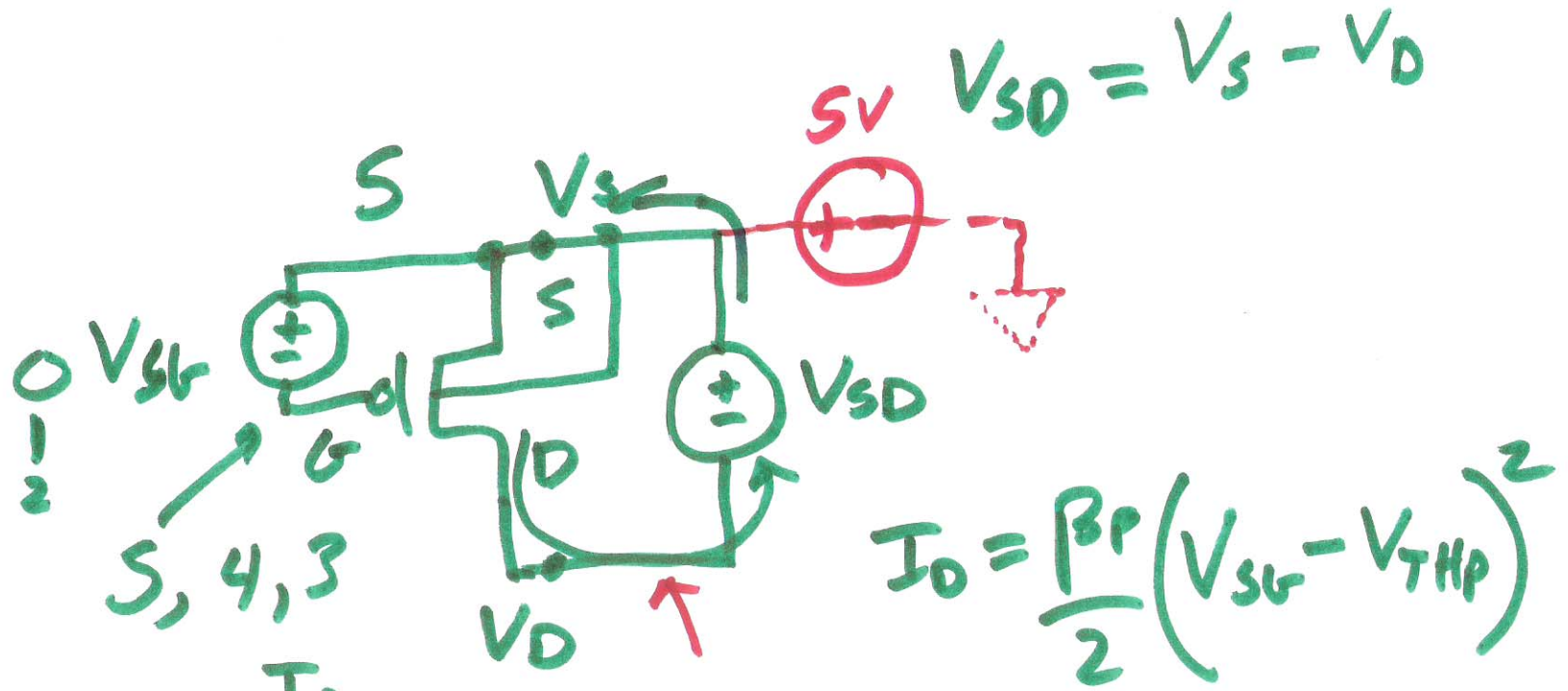

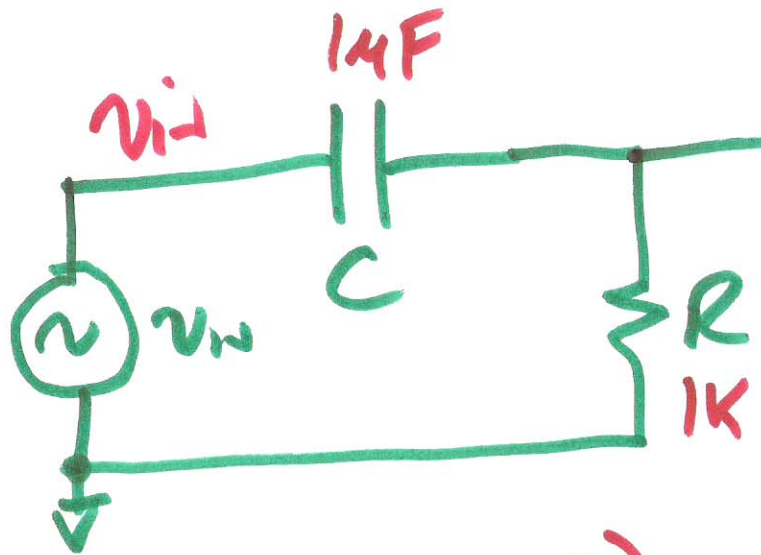

$$v_{OUT} = v_{in} \cdot \frac{R}{R + 1/sC}$$

$$\frac{v_{OUT}}{v_{in}} = \frac{0 + j\omega RC}{1 + j\omega RC}$$

$v_{in} = 1V \cdot \sin(2\pi \cdot 200 \cdot t)$   
 $v_{OUT} = ?$

mag of  $v_{in}$  of  $0 + j2\pi \cdot 200$


$$\left| \frac{v_{OUT}}{v_{in}} \right| = |v_{OUT}| = \frac{1 \cdot 10^{-3} \cdot 520}{1 + j \cdot 4\pi \cdot 10^{-3} \cdot 200}$$

$90 - \tan^{-1} \infty = 90 - 52 = 38^\circ$

$\frac{\pi}{2}$

$$|v_{OUT}| = \frac{0.52}{\sqrt{1^2 + (.4\pi)^2}}$$

6)

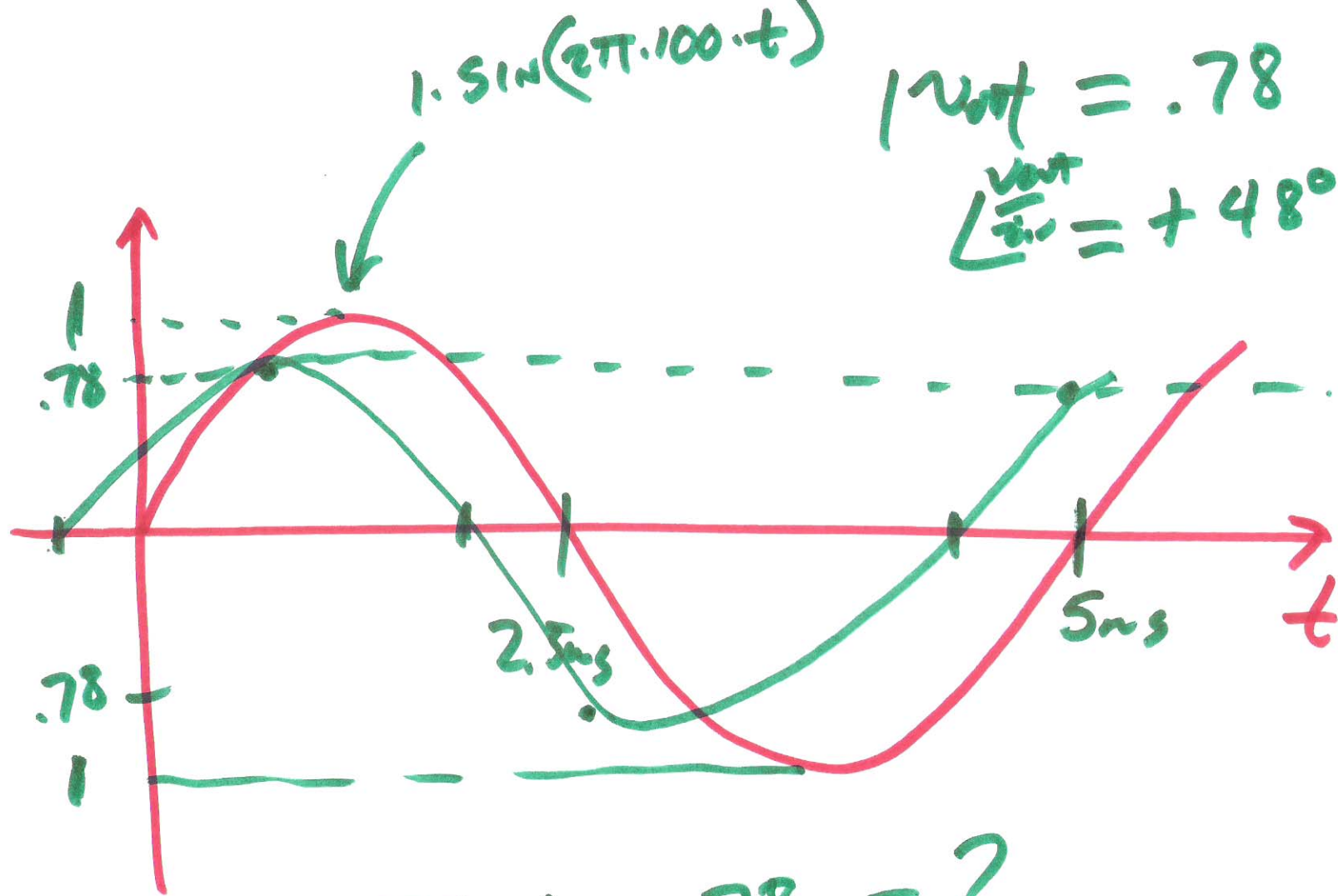

$$\begin{aligned}
 20 \log .78 &= ? \\
 &= -2.16 \text{ dB} \\
 &\text{@ } 200 \text{ Hz}
 \end{aligned}$$


$$90 \sim \tan^{-1} \frac{2\pi RC f}{1} \quad 38 = \frac{\Delta t}{5ms} \cdot 360$$

$$\Delta t = \frac{38}{360} \cdot 5ms \approx \cancel{0.5ms} = \cancel{500\mu s} \approx \underline{\underline{2\frac{1}{2}\mu s}}$$

$$\frac{0 + j2\pi RC \cdot f}{1 + j2\pi RC \cdot f}$$


$$| \cdot | = \frac{2\pi RC f}{\sqrt{1^2 + (2\pi RC f)^2}}$$

$$f = \frac{1}{2\pi RC}$$

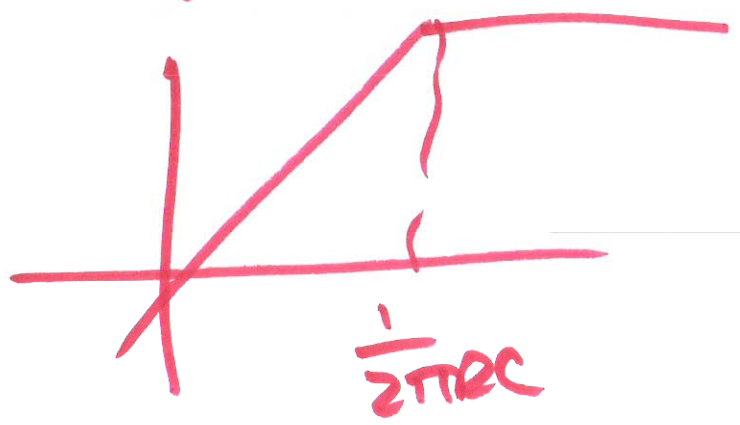



# PHASE

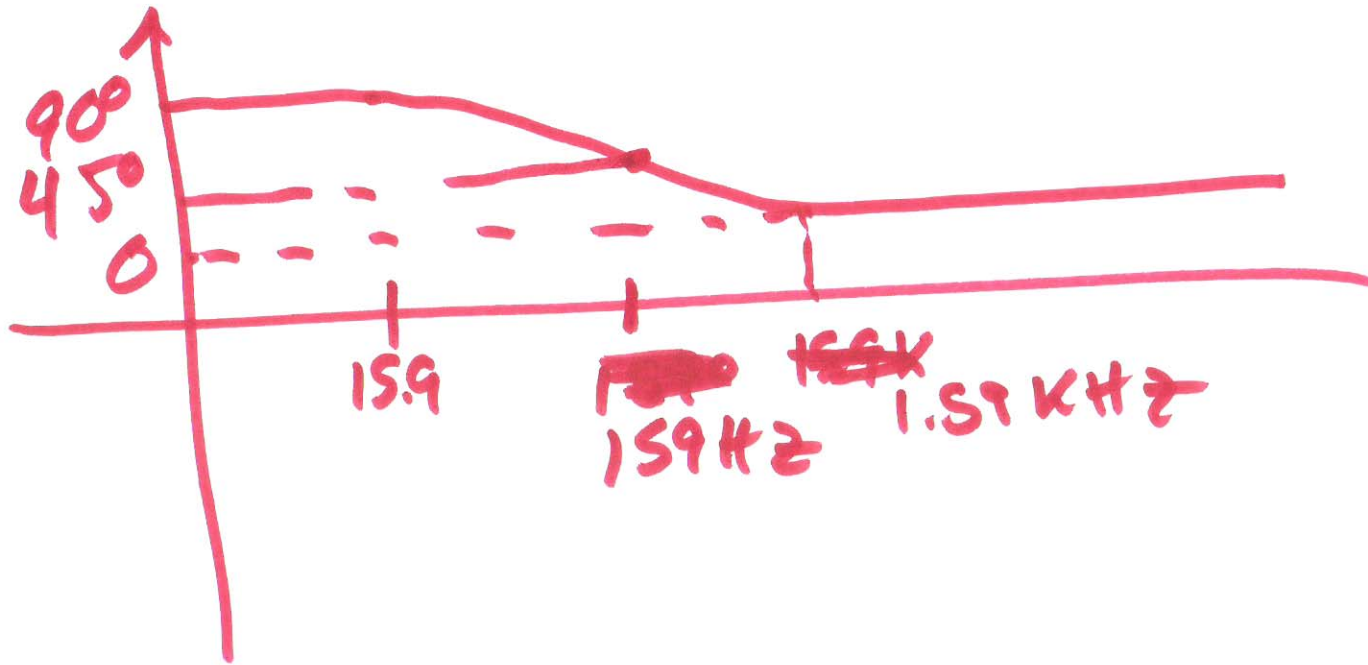

a)