

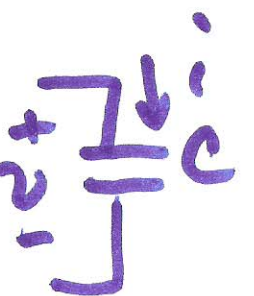


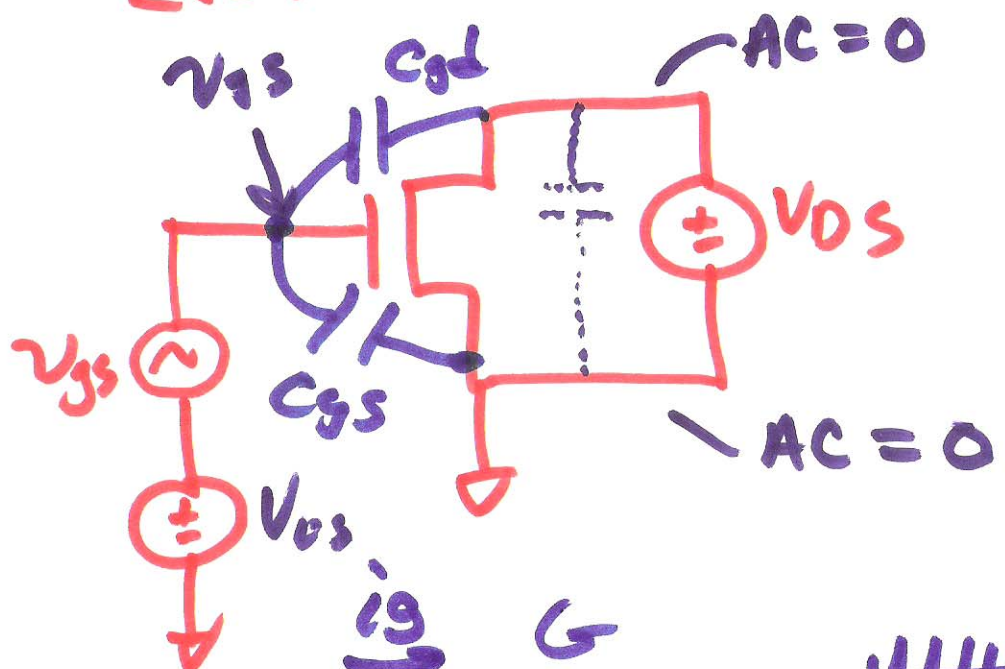EE 422 ECG 622
 Analog IC Design
 Lecture 7 2/13/13



$v = i \cdot \frac{1}{j\omega C}$

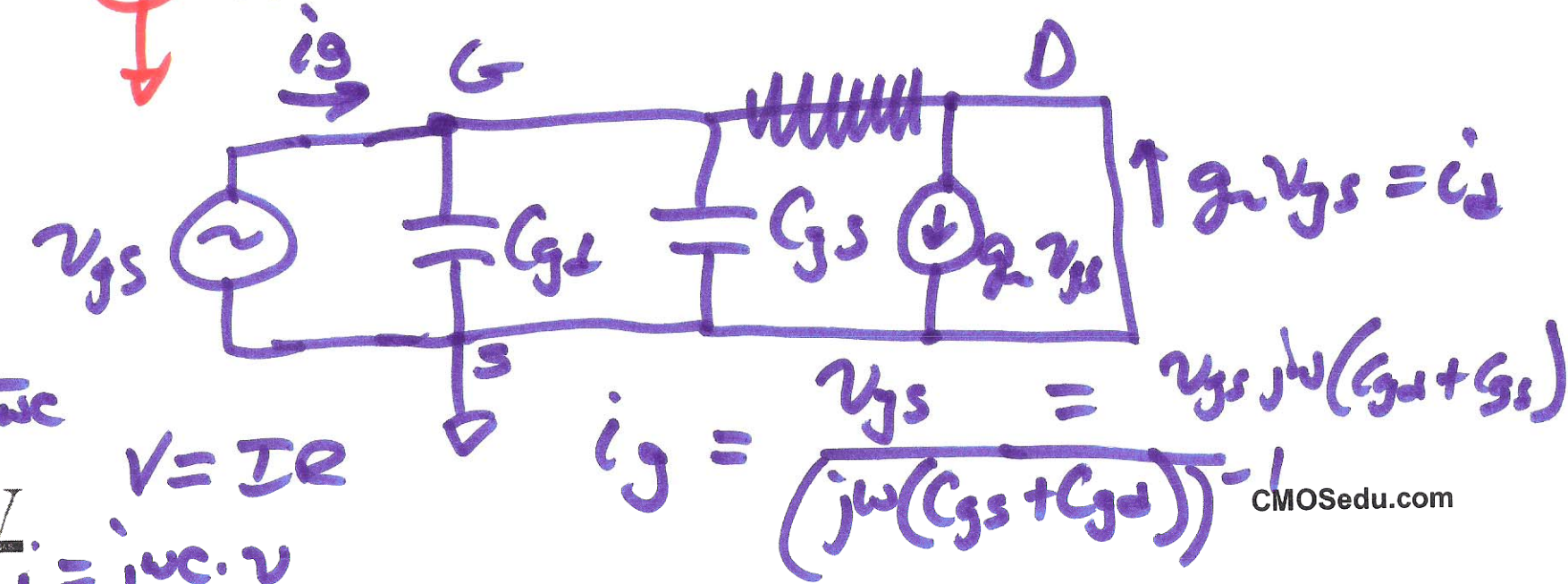

$\uparrow g_m v_{gs} = i_d$

$i_g = \frac{v_{gs}}{(j\omega(C_{gs} + C_{gd}))^{-1}}$


$V = IR$

$i = j\omega C \cdot v$

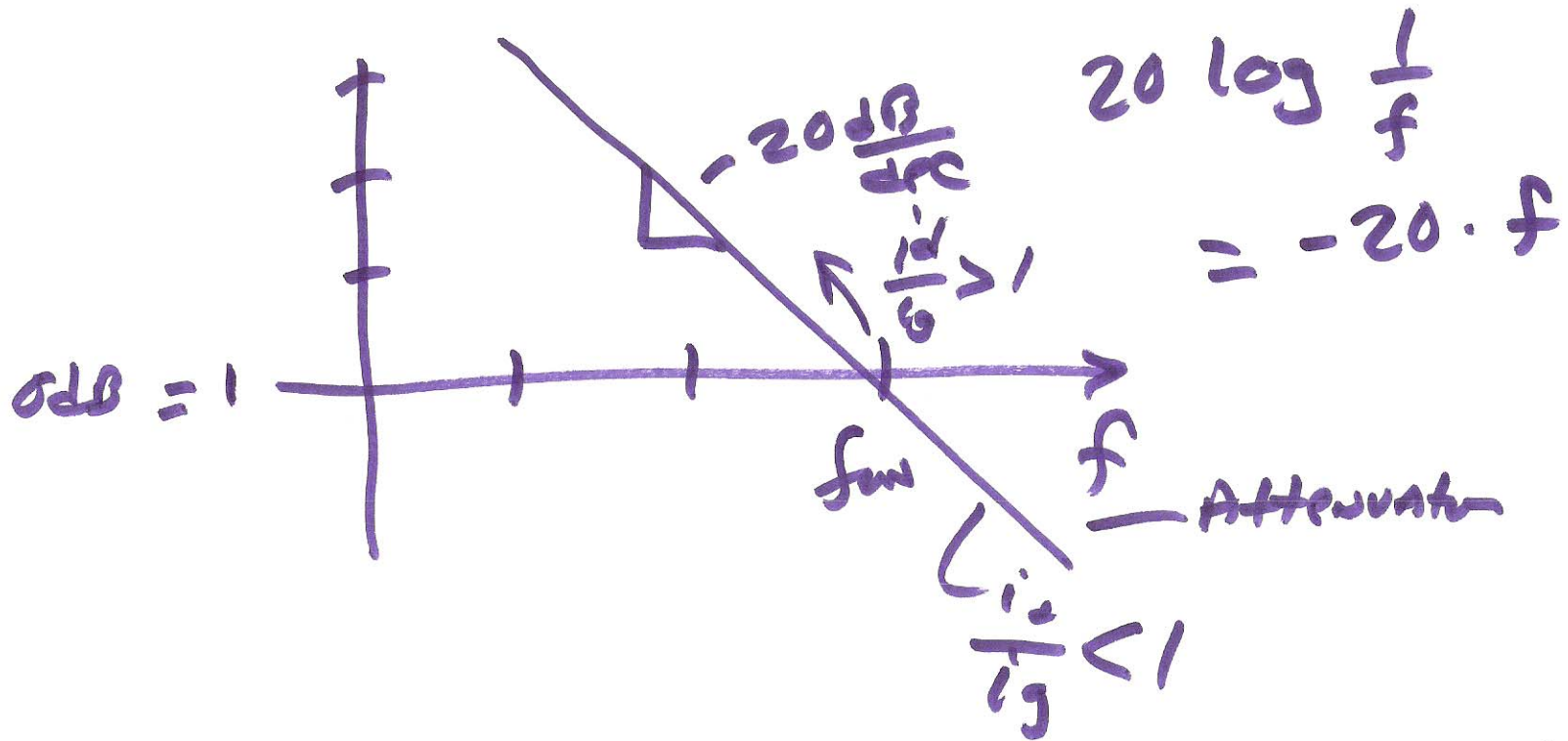1)

$$\frac{i_d}{i_g} = \frac{g_m \cdot v_{gs}}{v_{gs}(j\omega(C_{gd} + C_{gs}))}$$

$$\frac{i_d}{i_g} = \frac{g_m}{j \cdot 2\pi f (C_{gd} + C_{gs})}$$



$$\left| \frac{i_d}{v_g} \right| = \frac{k_p \cdot \frac{W}{L} \cdot (V_{GS} - V_{TH})}{2\pi \cdot f \cdot (C_{gs} + C_{gd})}$$

overdrive voltage = $V_{GS} - V_{TH} = \underbrace{V_{DS, SAT}}_{\neq 0} = V_{OV}$



excess gate voltage

$$C_{gs} = \frac{2}{3} C_{ox}' \cdot W \cdot L$$

$$C_{gd} = C_{ox}' \cdot W \cdot L_D$$

→ IN saturation.


$$C_{gs} \gg C_{gd}$$

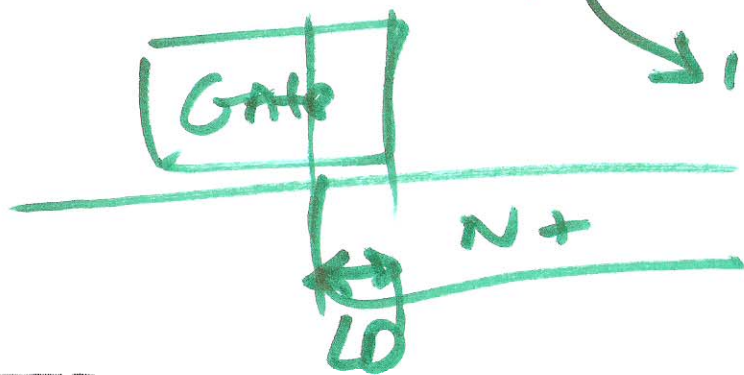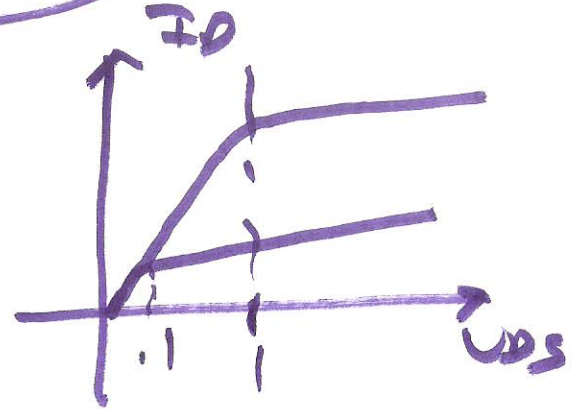

$$r_o \propto \frac{W}{L}$$

$$\left| \frac{i_d}{i_g} \right| =$$
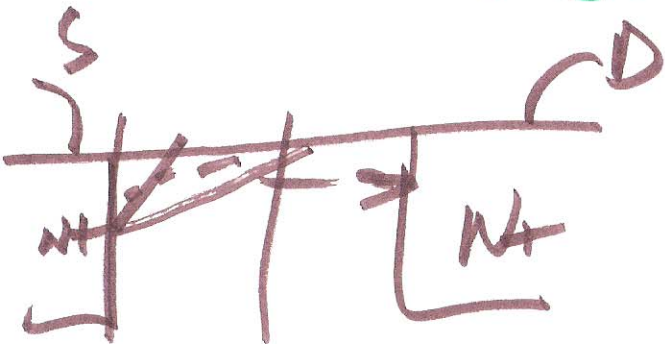
$$\frac{K_P \cdot \cancel{\frac{W}{L}} (V_{GS} - V_{THN})}{2\pi \cdot f \cdot (\frac{2}{3} C_{ox}' \cdot \cancel{W} \cdot L + C_{ox}' \cdot L \cdot \cancel{W})}$$



$$= \frac{K_P \cdot (V_{GS} - V_{THN})}{2\pi f (\frac{2}{3} C_{ox}' \cdot L^2 + L \cdot C_{ox}' \cdot L \cdot W)}$$



Left

$$\frac{W}{L_{eff}} \cdot (V_{GS} - V_{THN})^2$$


$$C_{gs} \gg C_{gd}$$

$$= \left| \frac{i_d}{i_g} \right|$$



$$\approx \left| \frac{4\mu_n \cdot \cancel{C_{ox}'} (V_{GS} - V_{THN})}{2\pi f_T \cdot \frac{2}{3} \cancel{C_{ox}'} \cdot L^2} \right|$$

Small L_g gives small gain!

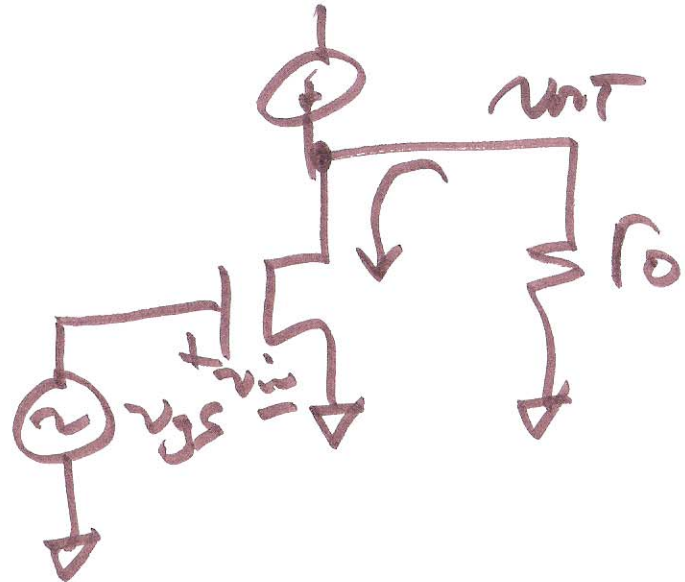

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{g_m r_o}{\cancel{g_m}}$$

$$\begin{aligned} \text{open-ckt gain} &= g r_o \\ &= \frac{\sqrt{2k_p \frac{W}{L} I_D}}{\lambda I_D} \end{aligned}$$

$$r_o = \frac{1}{\lambda I_D}$$

$$g r_o = \text{gain}$$

$$\begin{aligned} g r_o &= \frac{\sqrt{2k_p \frac{W}{L}}}{\lambda \cdot \sqrt{I_D}} \\ &= \frac{\sqrt{2k_p \frac{W}{L}}}{\lambda \cdot \sqrt{\frac{k_p \frac{W}{L}}{2} (V_{GS} - V_{TH})}} \end{aligned}$$



$$I_D = I_{D0} e^{\frac{V_{GS}}{V_T}} \text{ for subthreshold}$$

$$f_T = \frac{\mu_n \cdot (V_{GS} - V_{THN})}{2\pi \cdot \frac{2}{3} \cdot L^2}$$

$$g_m r_o = \frac{2}{\lambda \cdot (V_{GS} - V_{THN})}$$

Figure of Merit

$$G_{FT} = g_m r_o \cdot f_T = \frac{\mu_n \cdot 3 (V_{GS} - V_{THN}) \cdot 2}{4\pi \cdot L^2 \cdot (V_{GS} - V_{THN})}$$

gain \cdot f_T product = $G_{FT} \propto \frac{\mu_n}{L^2}$

General design

set $L \rightarrow$ 2 to 5 minimum

$$V_{OVN} = V_{GS} - V_{THN} = 5\% \text{ of } V_{DD}$$




$$I_D = \frac{K_P n}{2} \cdot \frac{W}{L} (V_{GS} - V_{THN})^2$$

$V_{GS} \uparrow$ $L \downarrow$

$V_{GS} = \text{constant}$

$$r_D = \frac{1}{\lambda I_D}$$

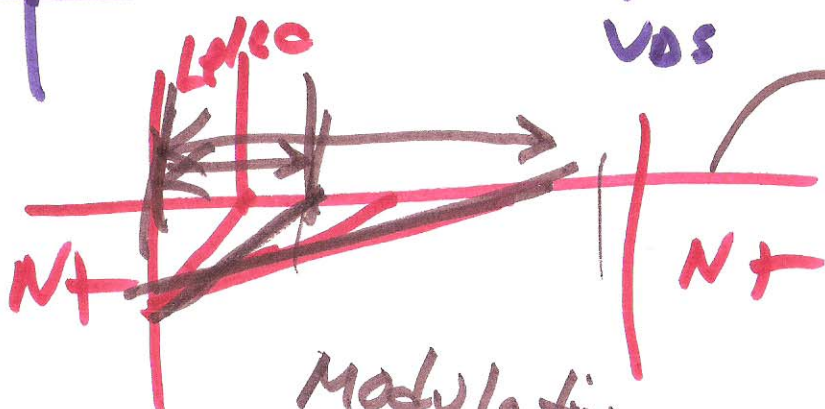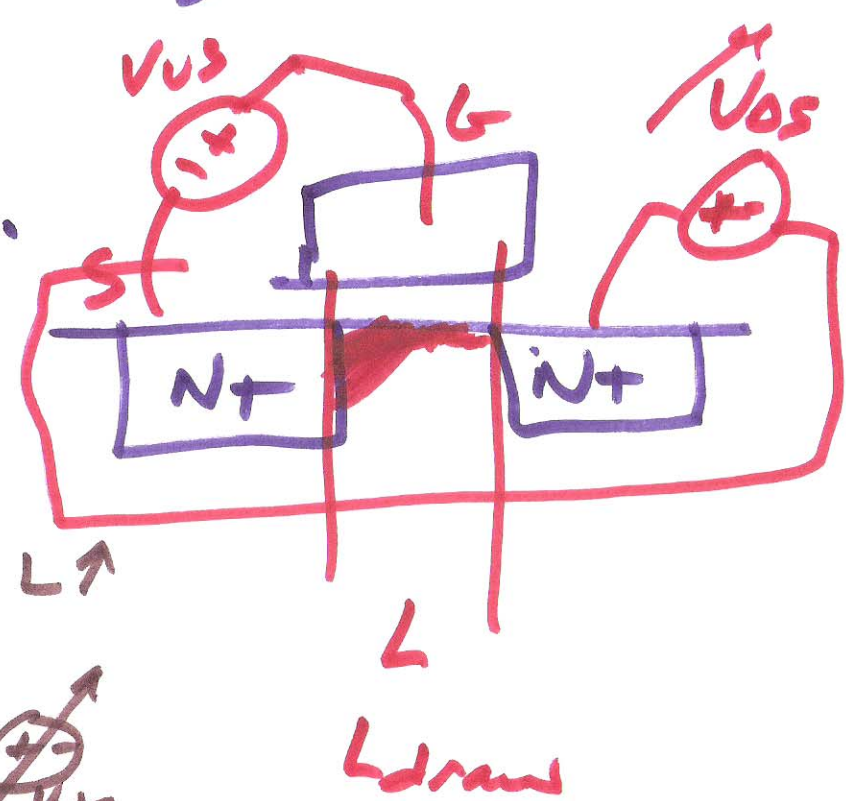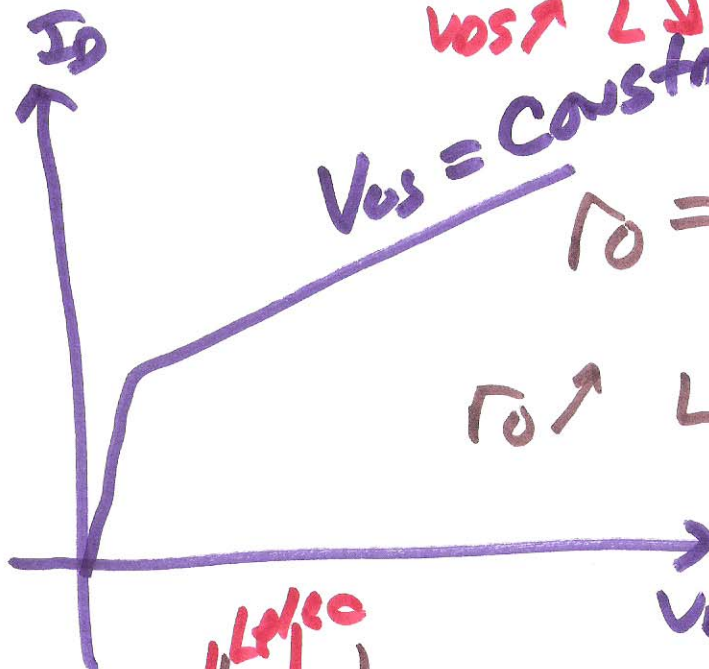$r_D \uparrow$ $L \uparrow$
 $\lambda \downarrow$ $L \uparrow$



Modulating the channel length

