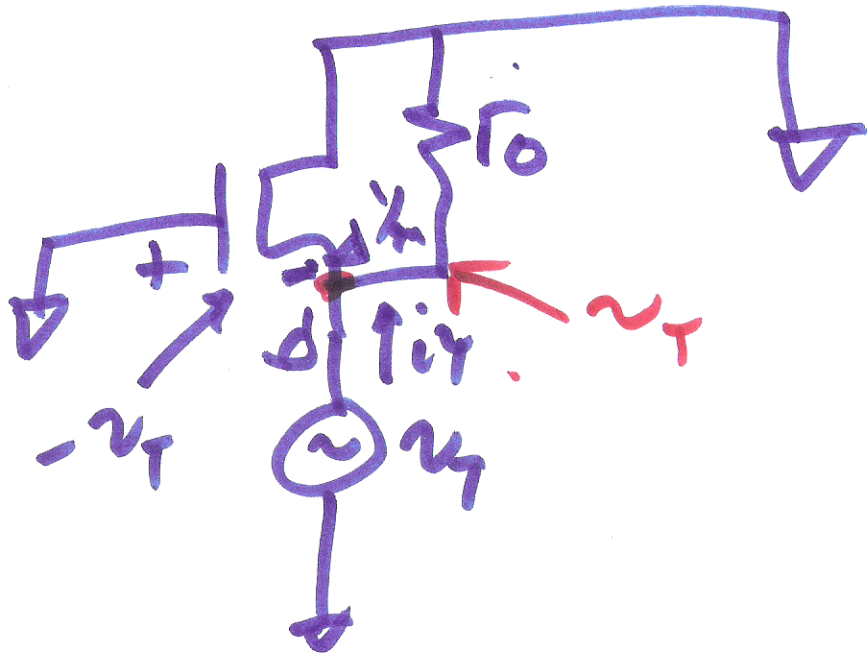




# EXACT resistance into source



$$= \frac{1}{g_m} \parallel r_o$$


$$i_T = \frac{v_T}{r_o} + (-i_s)$$

$$= \frac{v_T}{r_o} + (-g_m v_{gs})$$

$$= \frac{v_T}{r_o} + \frac{v_T}{1/g_m}$$

$$\frac{v_T}{i_T} = \left( \frac{1}{r_o} + \frac{1}{1/g_m} \right)^{-1}$$

$$= \frac{1}{g_m} \parallel r_o$$

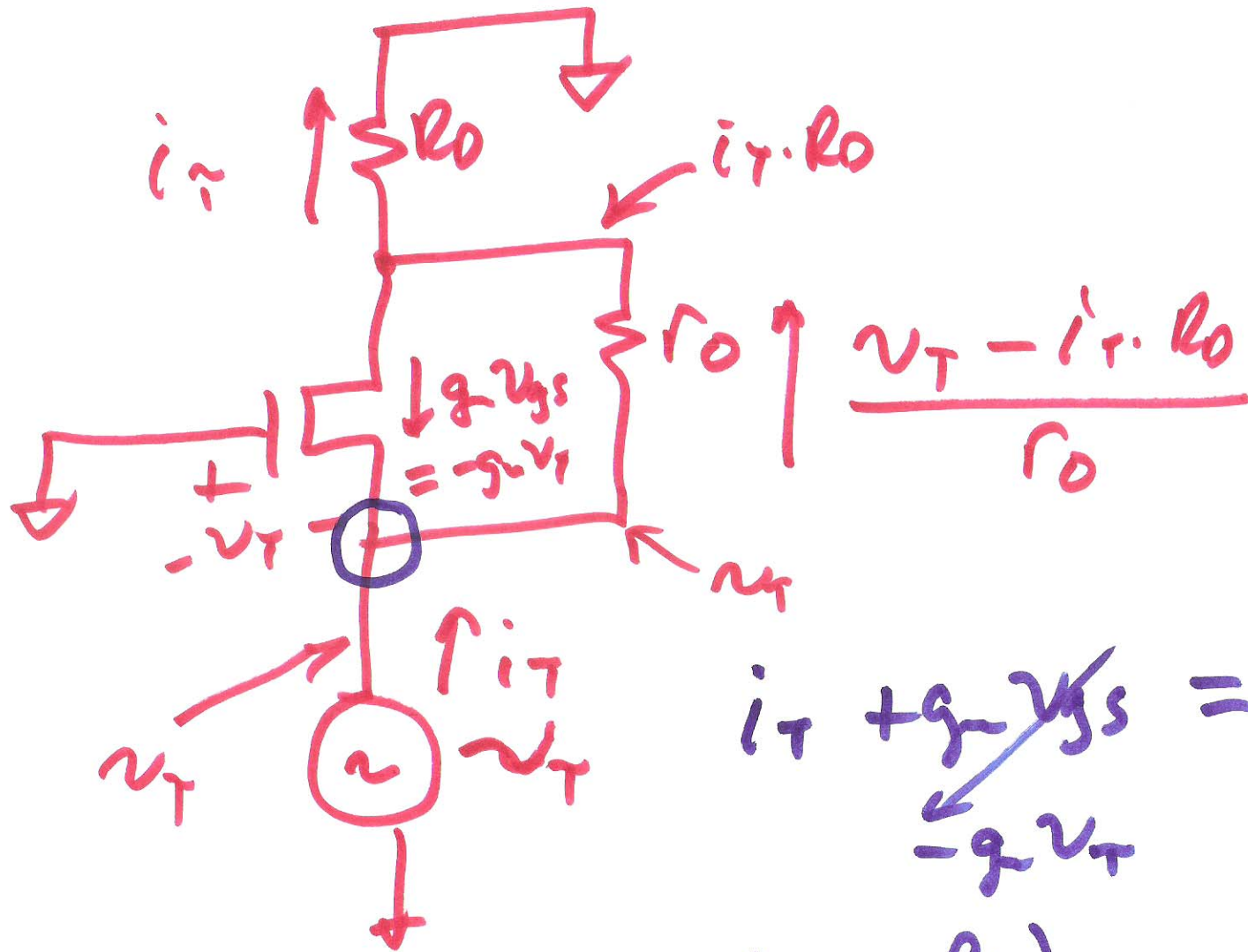


$$i_T + g_m v_{gs} = \frac{v_T - i_T R_o}{r_o}$$

$\swarrow$   
 $-g_m v_T$

$$i_T \left( 1 + \frac{R_o}{r_o} \right) = v_T \left( \frac{1}{r_o} + g_m \right)$$
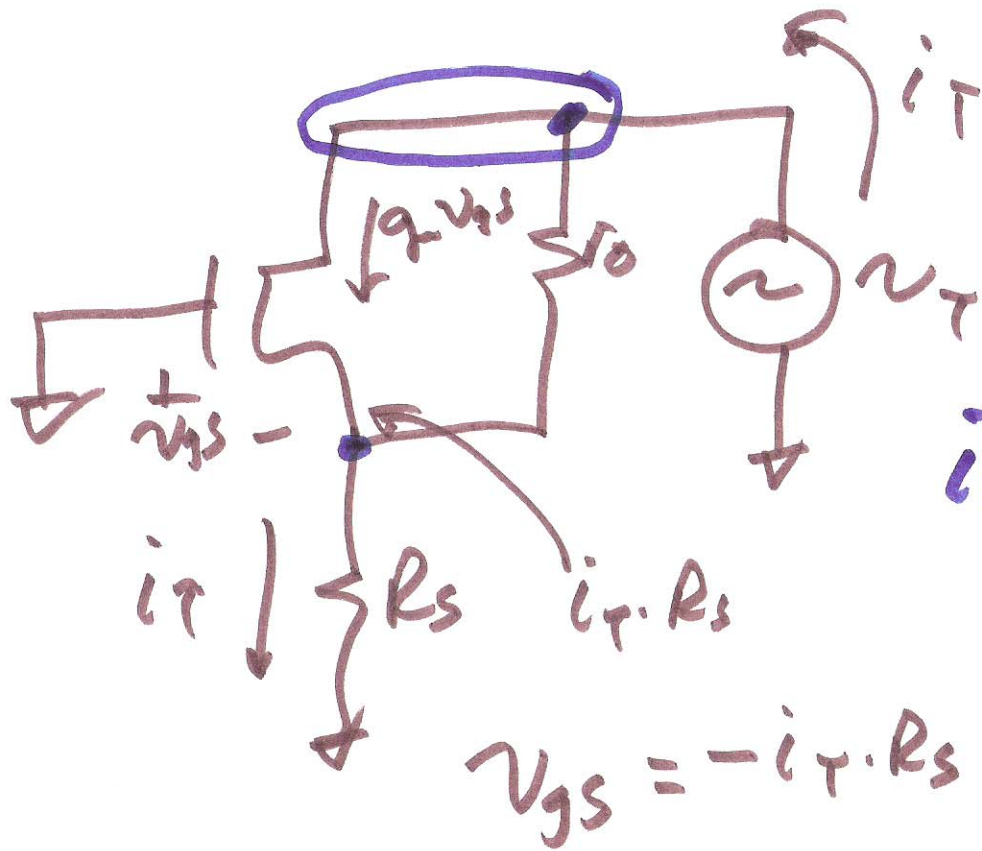
$$R_{\text{into source}} = \frac{v_T}{i_T} = \frac{1 + \frac{R_o}{r_o}}{\frac{1}{r_o} + g_m}$$





$$i_T = g_m v_{gs} + \frac{v_T - i_T R_s}{r_o}$$

$$i_T = g_m (-i_T R_s) + \frac{v_T}{r_o} - \frac{R_s}{r_o} \cdot i_T$$



$$i_T \left( 1 + g_m R_s + \frac{R_s}{r_o} \right) = \frac{v_T}{r_o}$$


$$R \text{ into drain} = \frac{v_T}{i_T} = \left( r_o + g_m R_s r_o + R_s \right)$$

5)


$$R_{\text{th train}} = r_o (1 + g_m R_s) + R_s$$

## Ch 20 current mirrors

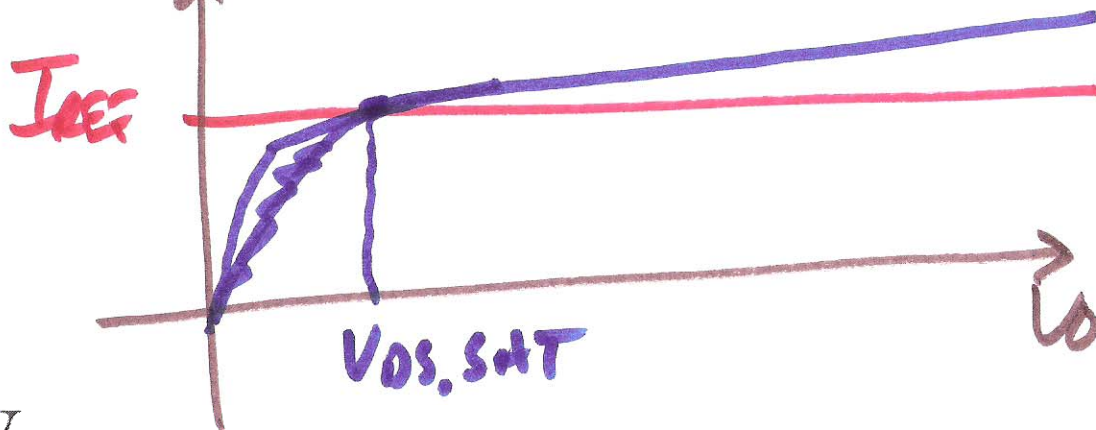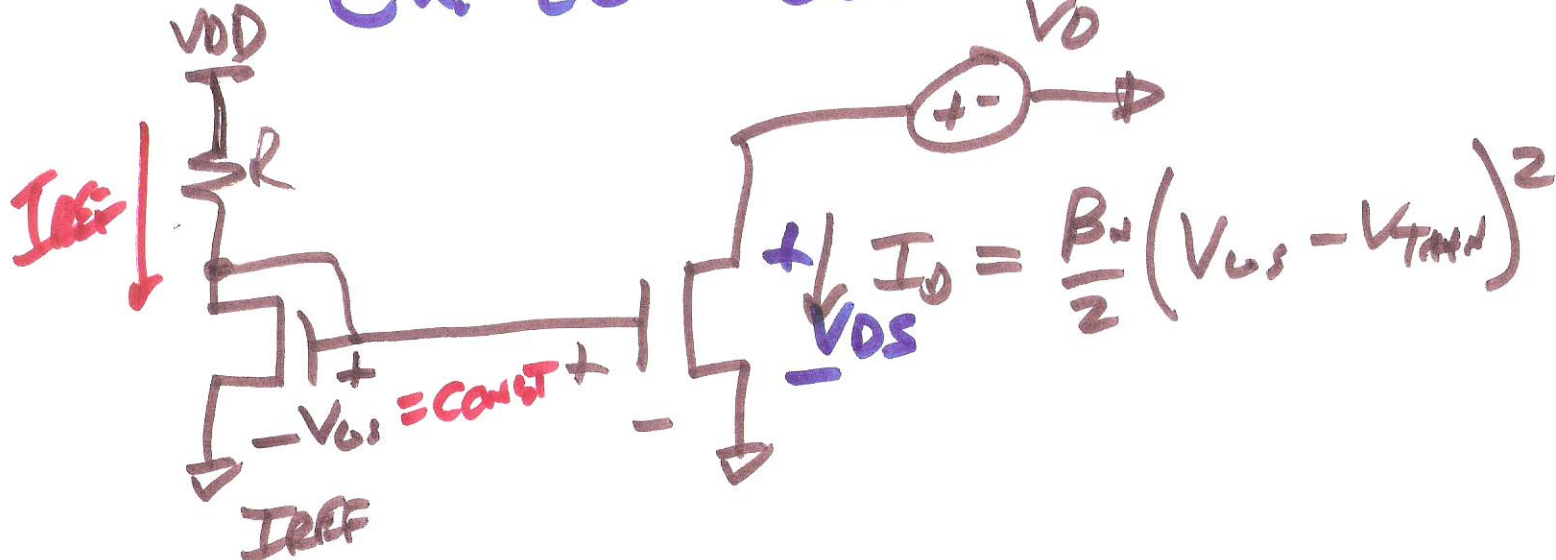


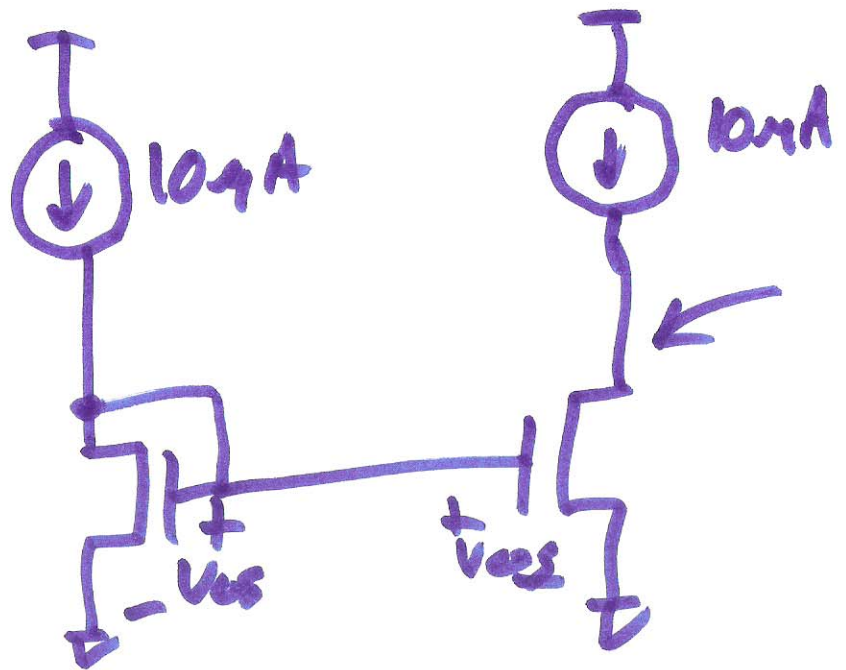


matching  $V_{DS}$  matching

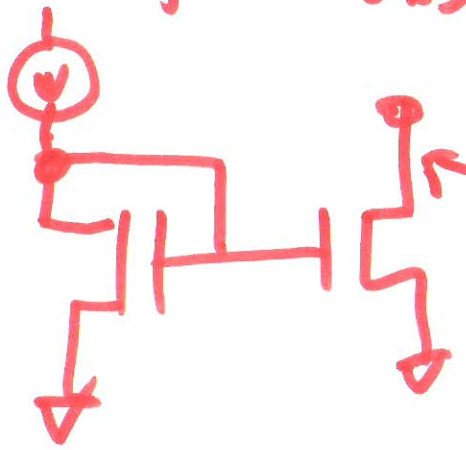

equalize the  $V_{DS}$

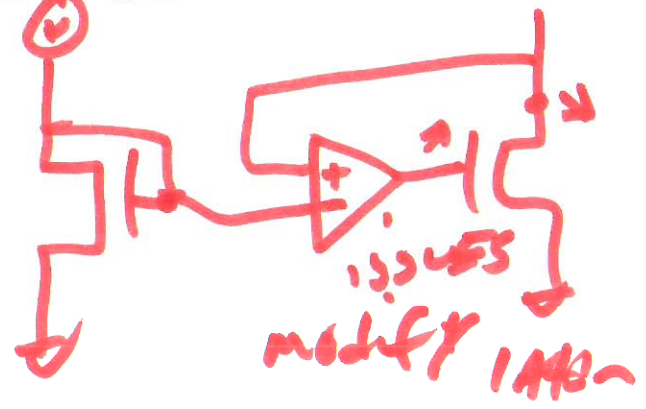

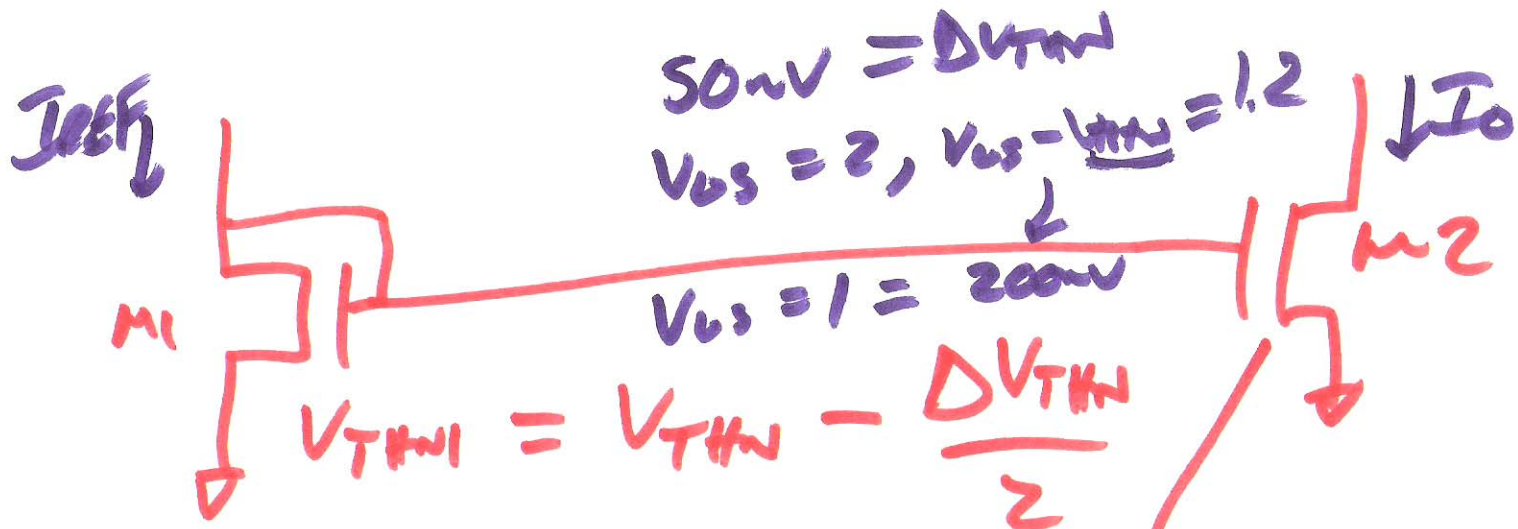

Average threshold voltage =  $V_{THN}$




$$V_{THN2} = V_{THN} + \frac{V_{THN}}{2}$$

$$\begin{aligned}
 \frac{I_{REF}^0}{I_{REF}} &= \frac{\frac{K_P W}{2L} \left( V_{GS} - \left( V_{THN} - \frac{\Delta V_{THN}}{2} \right) \right)^2}{\frac{K_P W}{2L} \left( V_{GS} - \left( V_{THN} + \frac{\Delta V_{THN}}{2} \right) \right)^2} \\
 &\approx 1 - \frac{2 \Delta V_{THN}}{V_{GS, SAT}}
 \end{aligned}$$




Matching parameter  
is  $K_P = \mu_n C_{ox}$

$$\approx 1 + \frac{\Delta K_P}{K_P}$$

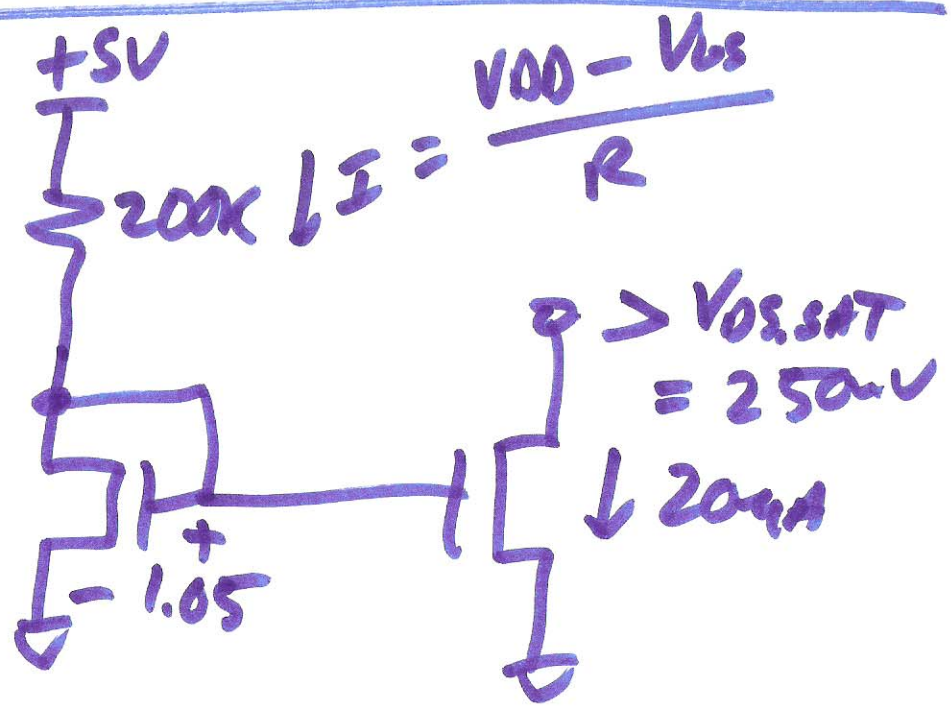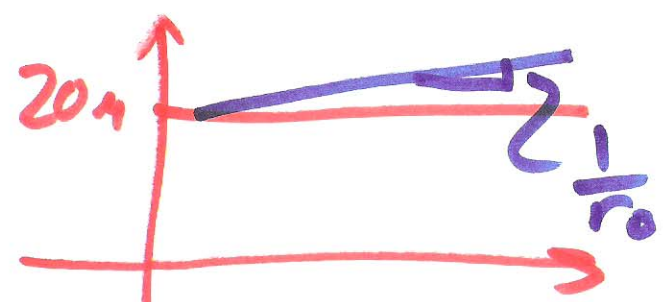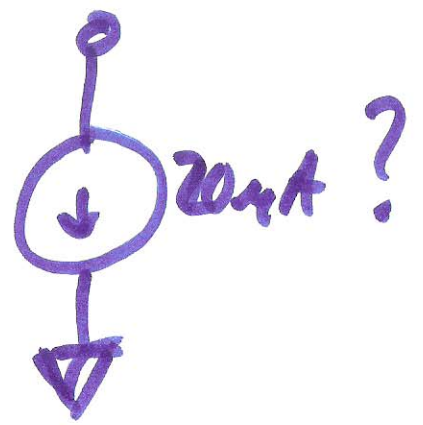

$$V_{GS} - V_{THN} = 1.05 - 0.8 = 0.25$$

Think of a resistor

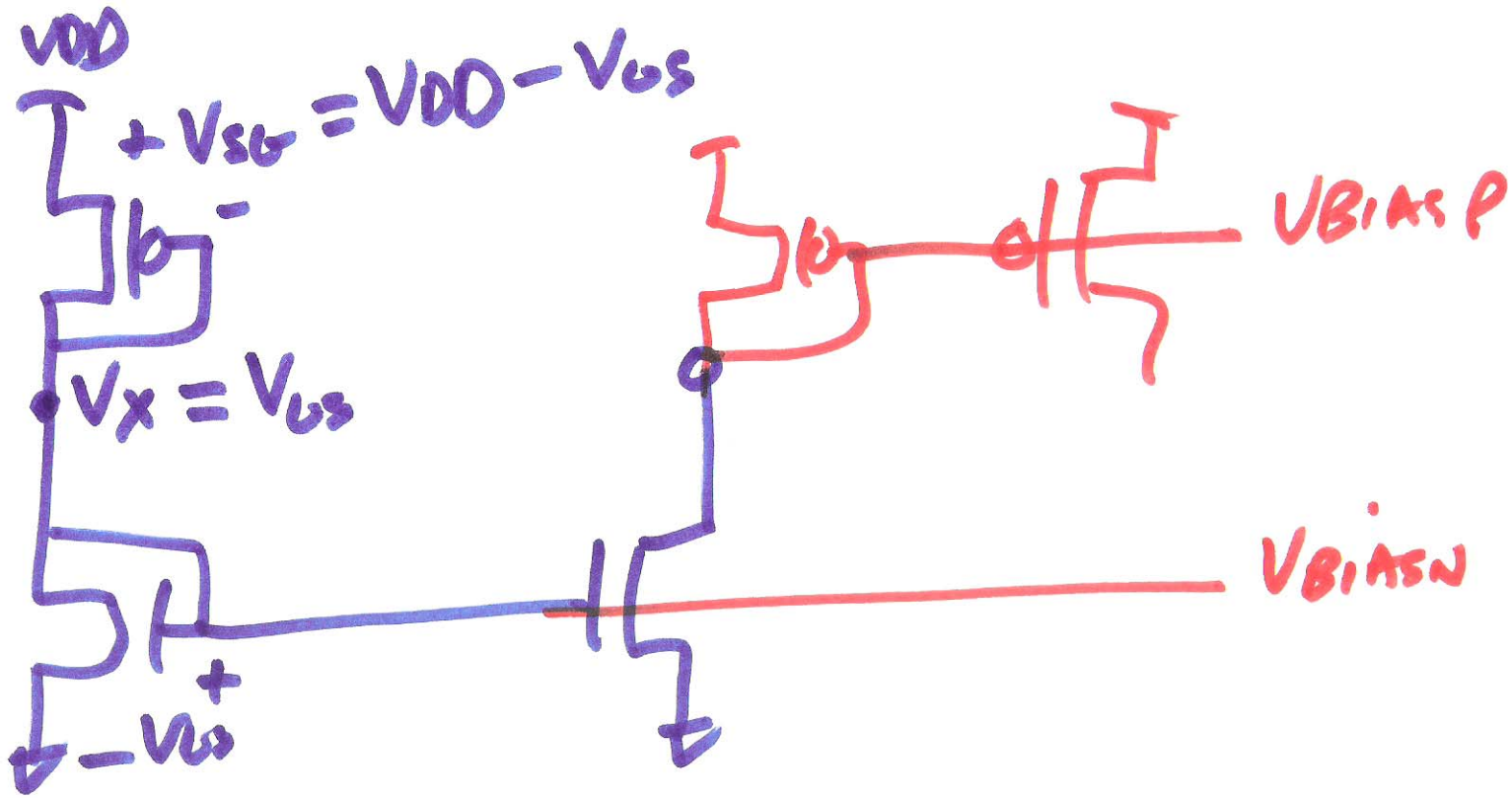

$$\frac{K_{Pp}}{2} \cdot \frac{W_p}{L_p} \left( \frac{V_{DD} - V_{cs} - V_{THp}}{V_{sg}} \right)^2 =$$

$$\frac{K_{Pn}}{2} \cdot \frac{W_n}{L_n} \left( V_{cs} - V_{THn} \right)^2$$

10)