

Study Session

3/29/13


EE 422 / ECG 622

$$f_T \propto \frac{V_{GS}}{L}$$

$$g_m r_o \propto \frac{1}{\sqrt{I_D}}$$

$$r_o \propto \frac{L}{I_D \cdot \beta}$$



$$g_m \propto \sqrt{I_D} / \sqrt{L}$$

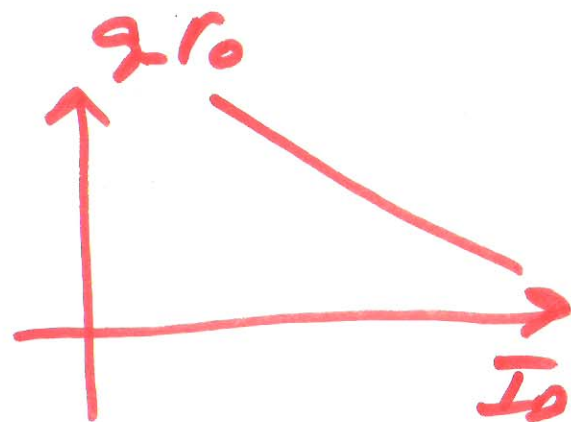

$$g_m \propto \frac{V_{GS}}{L}$$

$$g_m = \sqrt{2 \cdot K_P \cdot \frac{W}{L} \cdot I_D} = 2K_P \cdot \frac{W}{L} (V_{GS} - V_{TH})$$

AP. 11

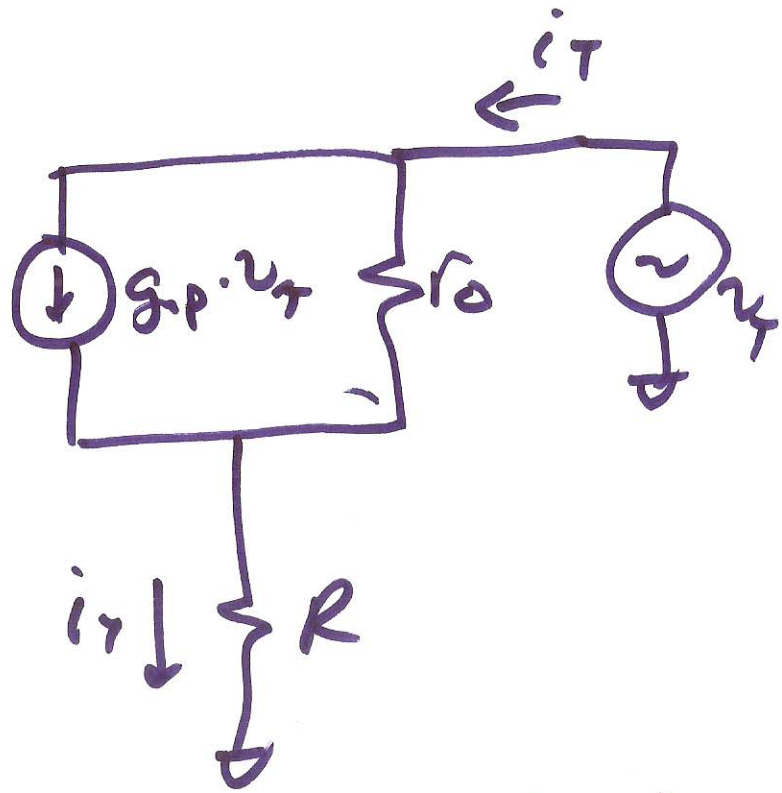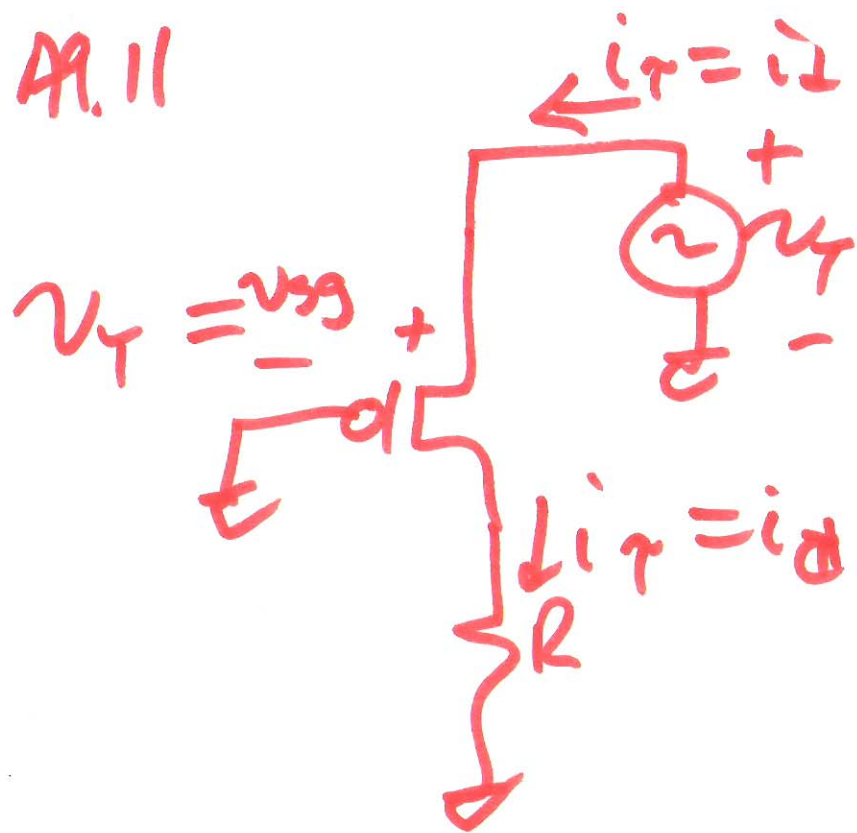

$$\frac{v_T}{i_T} = \frac{r_o + R}{1 + g_m r_o}$$

$R=0, r_o=\infty$


$$= \frac{1}{\frac{1}{r_o} + g_m} = \frac{1}{g_m}$$

$$i_T = g_m \cdot v_T + \frac{v_T - i_T \cdot R}{r_o}$$

$$i_T r_o = g_m \cdot v_T r_o + v_T - i_T \cdot R$$

$$i_T (r_o + R) = v_T (1 + g_m r_o)$$

2)

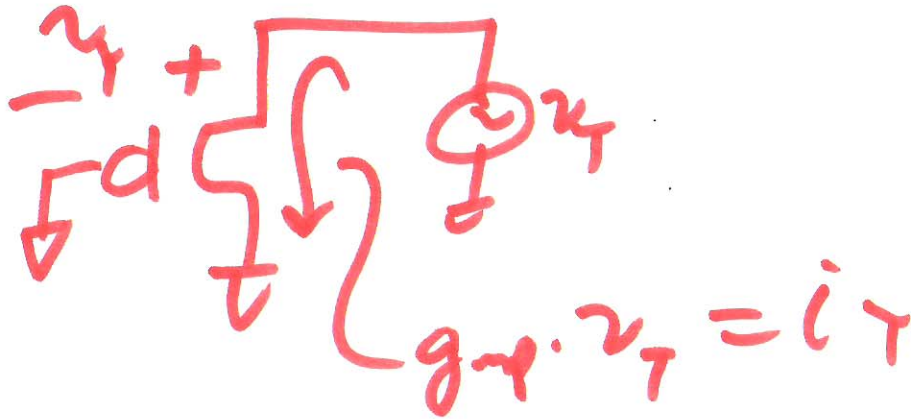

$$\frac{v_T}{i_T} = \frac{1}{g_m}$$

$$r_o = \infty$$

$$R = 0$$

3)

A20.1)

$$ax^2 + bx + c = 0$$

$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$


$$5 - \frac{750k \cdot 384\mu A}{5V}$$

$$\frac{5 - 1.2}{100k} = I_D$$

$$\frac{3.8}{100k}$$

$$\frac{3.8}{\frac{1}{10} \cdot 10^6}$$

384 μ A

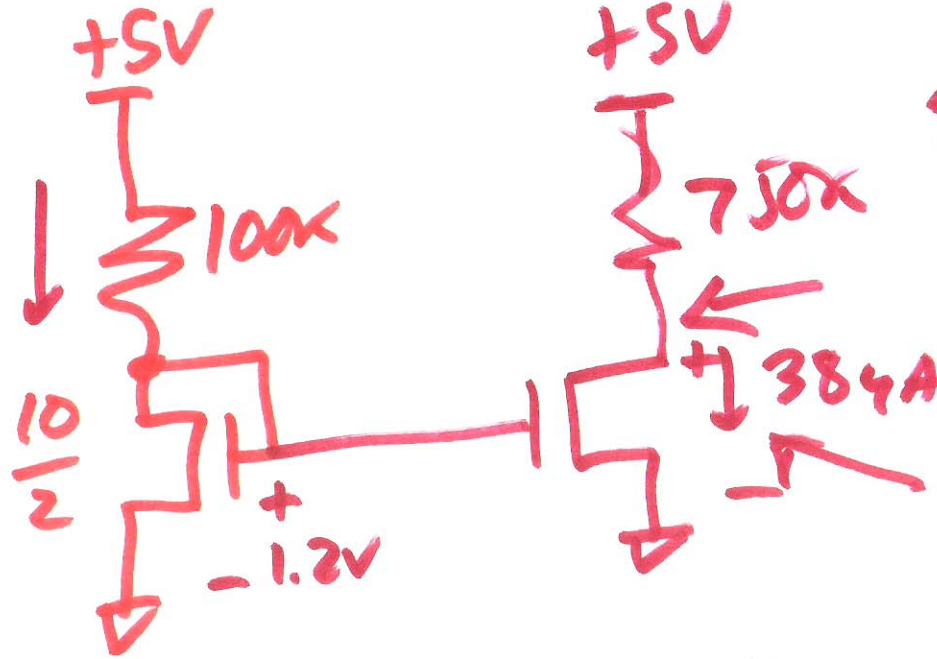

NOT in SAT!

USE triode Eq!


$$V_{GS} = 1.2V$$

$$5 - I_D \cdot 100k - V_{GS} = 0$$

$$5 - \frac{KP}{2} \cdot \frac{10}{2} \cdot \frac{10}{2} (V_{GS} - V_{THN})^2 - V_{GS} = 0$$

$$V_{GS} = 1.2V \text{ (for example)}$$

4)

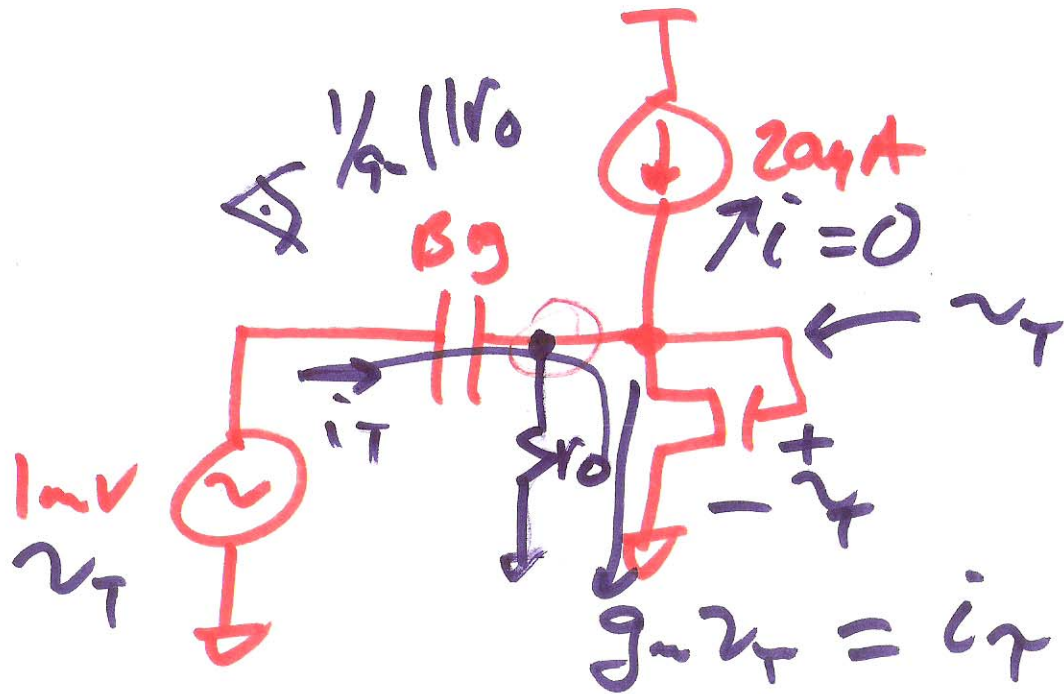

$$i_T = \frac{v_T}{r_o} + g_m v_T$$


$$\frac{v_T}{i_T} = \frac{1}{\frac{1}{r_o} + g_m}$$

$$g_m v_T = i_T = i_d \quad (r_o = \infty)$$


$$\frac{v_T}{i_T} = \frac{1}{g_m} \quad (r_o \neq \infty)$$

$$\frac{v_T}{i_T} = \frac{1}{g_m} \parallel r_o$$

5)

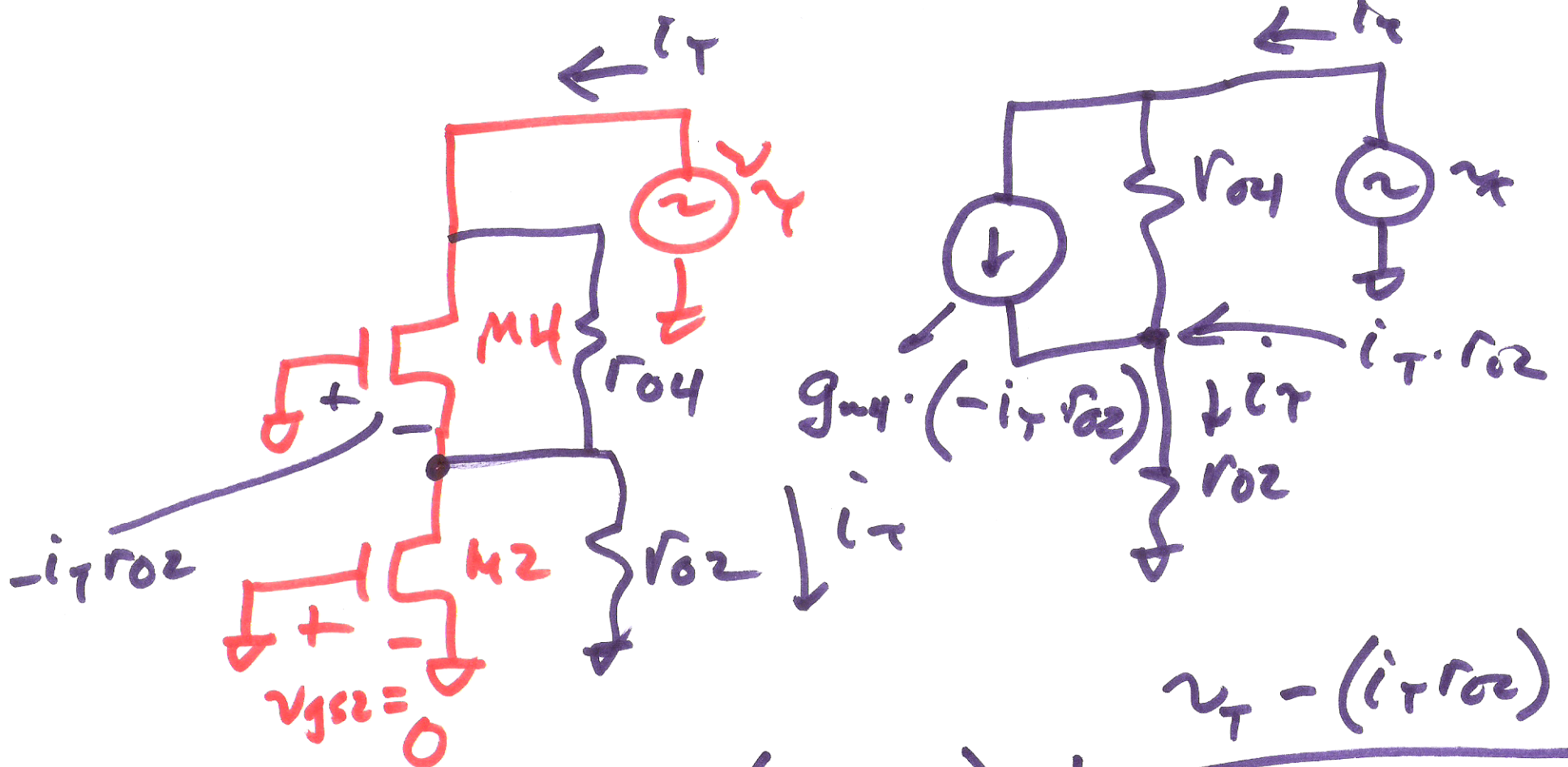

$$-i_T r_{o2}$$

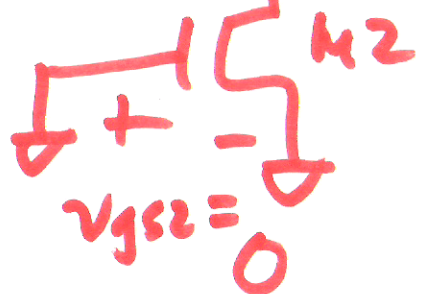


$$i_T = g_{m4}(-i_T \cdot r_{o2}) + \frac{v_T - (i_T r_{o2})}{r_{o4}}$$

$$i_T (r_{o4} + g_{m4} r_{o2} \cdot r_{o4} + r_{o2}) = v_T$$

$$R_{ocms} = \frac{v_T}{i_T} = r_{o4} (1 + g_{m4} r_{o2}) + r_{o2} \approx g_{m4} r_{o2} r_{o4}$$


6)

Regulated drain

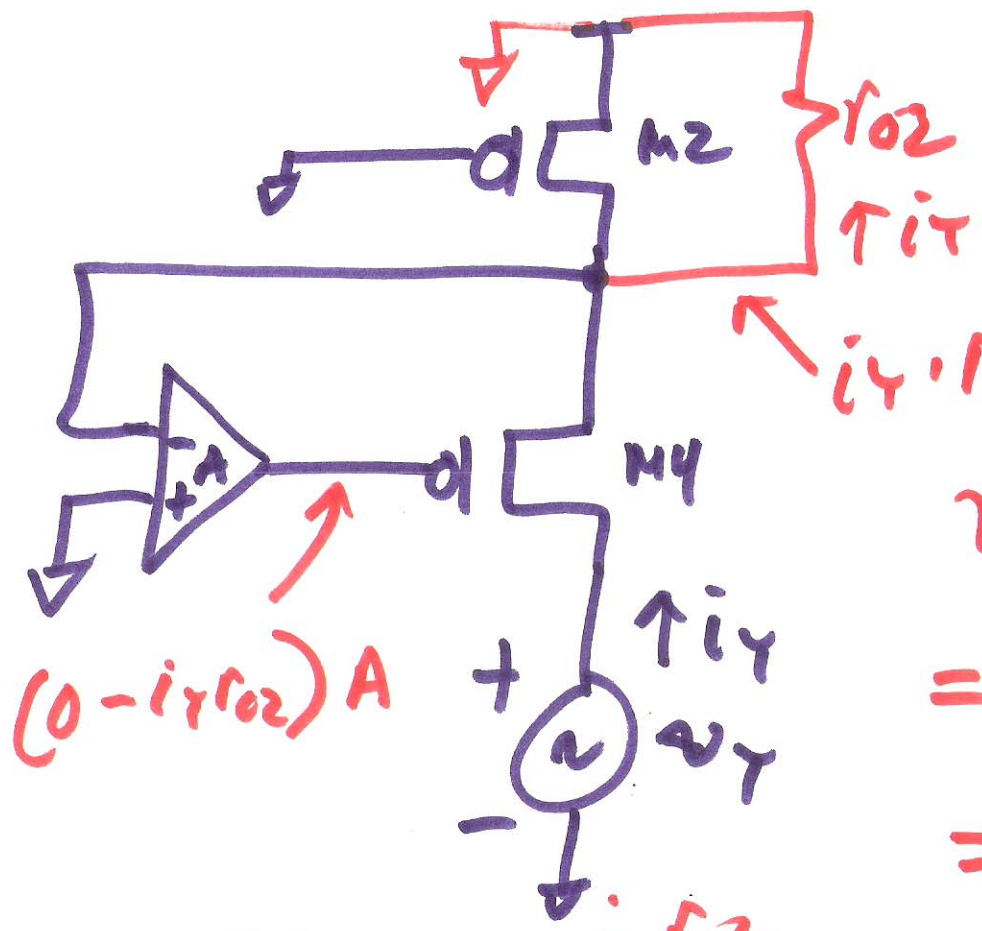

$$\begin{aligned}
 v_{sg4} &= v_{s4} - v_{g4} \\
 &= i_Y \cdot r_{O2} - (-i_T r_{O2} A) \\
 &= i_T r_{O2} (1 + A)
 \end{aligned}$$
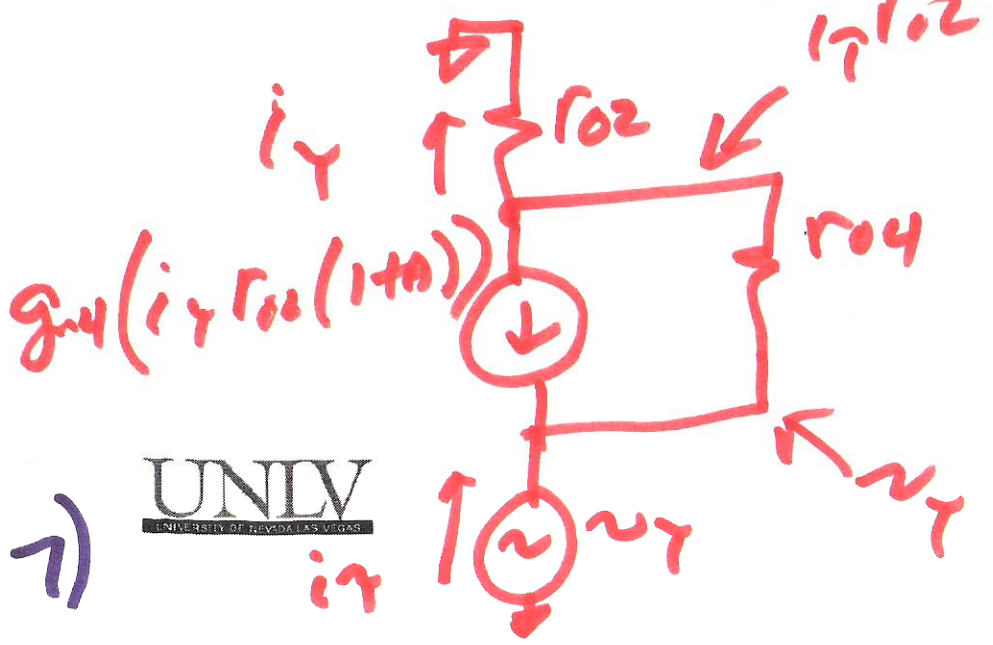
$$\begin{aligned}
 & i_T + g_{m4} (i_T r_{O2} (1 + A)) \\
 & + \frac{i_T \cdot r_{O2} - v_T}{r_{O4}}
 \end{aligned}$$



$$i_Y (r_{O4} + g_{m4} r_{O2} (1+A) + r_{O2}) = v_T$$

$$\frac{v_T}{i_Y} = r_{O4} + r_{O2} + g_{m4} r_{O2} (1+A) r_{O4}$$