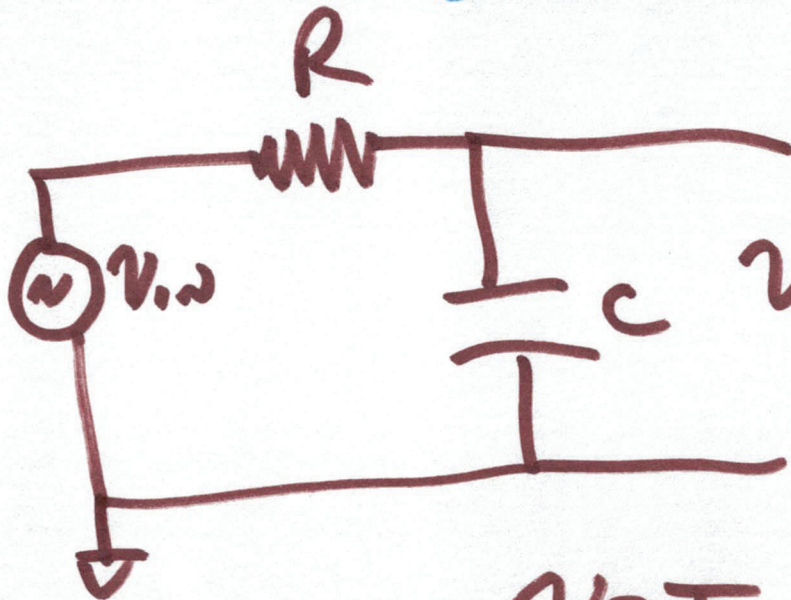


EE 442 / EEL 642

Power Electronics

Lecture 121

October 10, 2022




$$v_{out} = v_{in} \cdot \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R}$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + sRC}$$

$$s = j\omega$$

$$\left| \frac{v_{nT}}{v_{i2}} \right| = \frac{1 + j\omega 0}{1 + j\omega RC} = \frac{\sqrt{1^2 + 0^2}}{\sqrt{1^2 + (2\pi f \cdot RC)^2}}$$

$$\left| \frac{v_{nT}}{v_{i2}} \right| = \frac{1}{\sqrt{1 + (2\pi f RC)^2}} = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{cH}}\right)^2}}$$

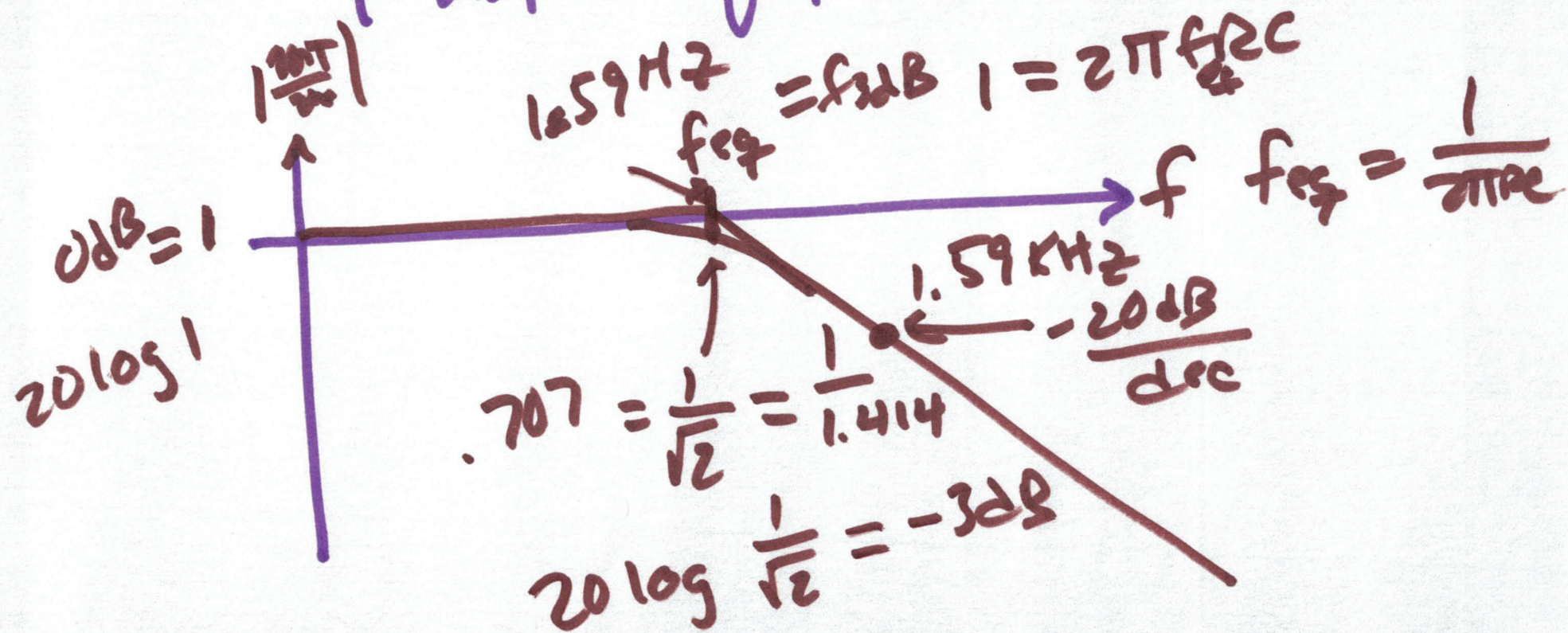

2)

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{\sqrt{1 + \left( \frac{f}{f_{3dB}} \right)^2}} \approx \frac{f_{3dB}}{f}$$

$f \gg f_{3dB}$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{159 \text{ Hz}}{f} = \frac{159}{1590} = \frac{1}{10}$$


1 decade

$\times 10$

1.59 kHz

$$20 \log \frac{1}{10} = -20 \text{ dB}$$

$$20 \log 10^{-1} = -20 \log 10$$

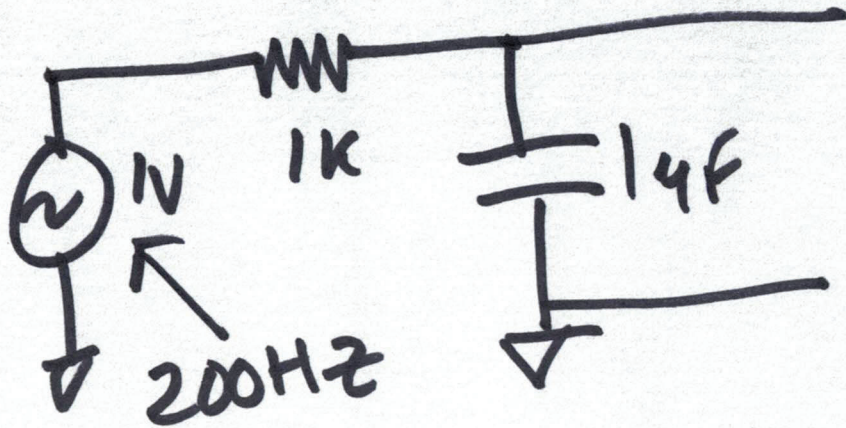

$$f_{3dB} = \frac{1}{2\pi \cdot 10^3 \cdot 10^{-6}}$$

$$= 159.15 \text{ Hz}$$


$$V_{out} = 1 \cdot \frac{1}{\sqrt{1 + \left(\frac{200}{159}\right)^2}} = 0.622 \text{ V} = V_{out}$$

4)

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j \frac{f}{f_{3dB}}} = \frac{1 + j0}{1 + j2\pi fRC}$$

$$\angle \frac{V_{out}}{V_{in}} = \tan^{-1} \frac{0}{1} \Rightarrow -\tan^{-1} \frac{2\pi fRC}{1}$$
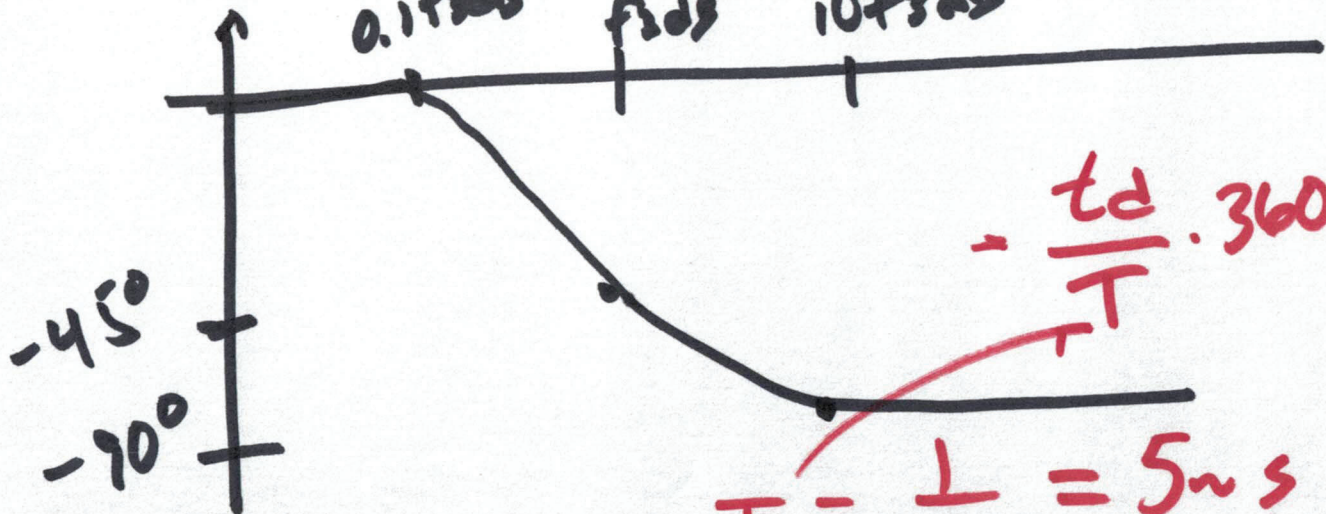
$$\frac{f_{3dB}}{10} = 0.1 f_{3dB} \quad \Rightarrow \quad -\tan^{-1} \frac{f}{f_{3dB}} = -\tan^{-1} \frac{200}{159} = -51.5^\circ$$




$$-\frac{td}{T} \cdot 360 = -51.5^\circ$$


leggi

$$T = \frac{1}{200} = 5 \text{ ns} \quad \boxed{t_d = .72 \text{ ns}}$$

5)

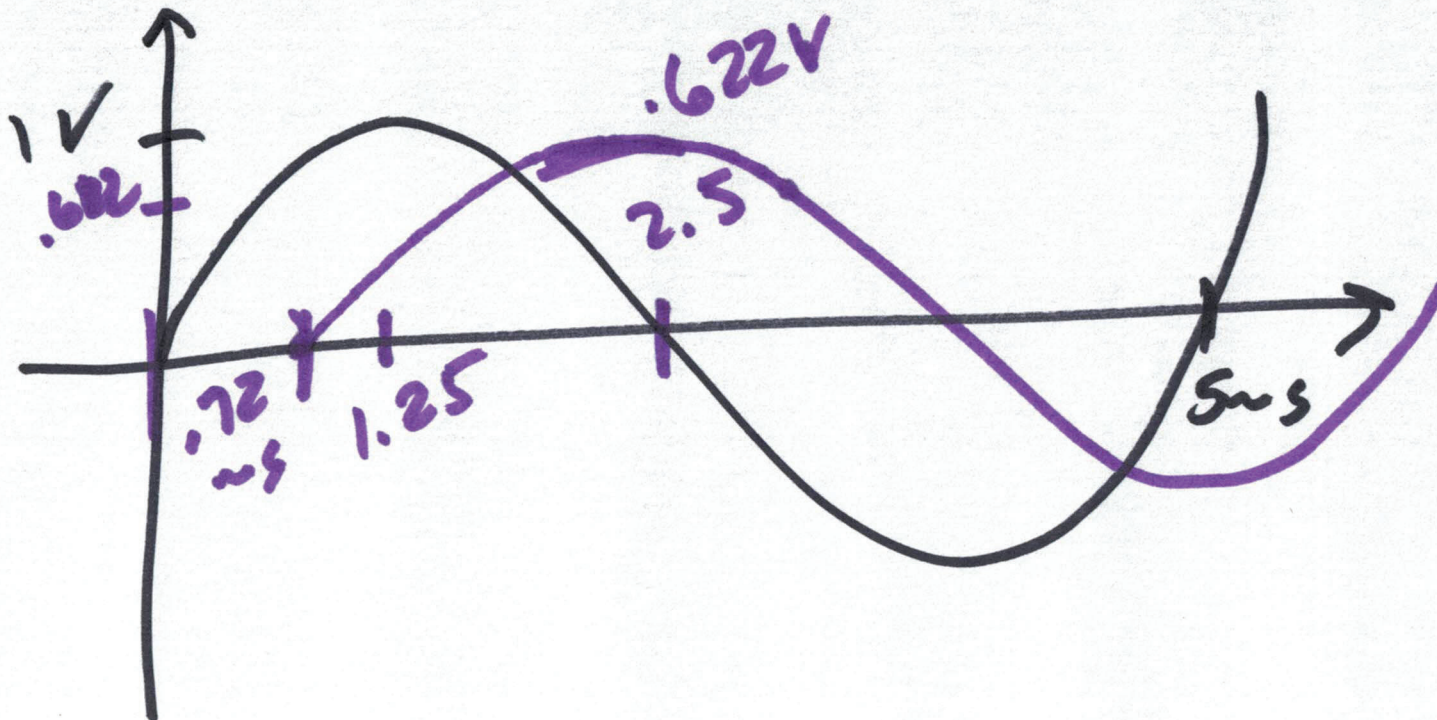

6)

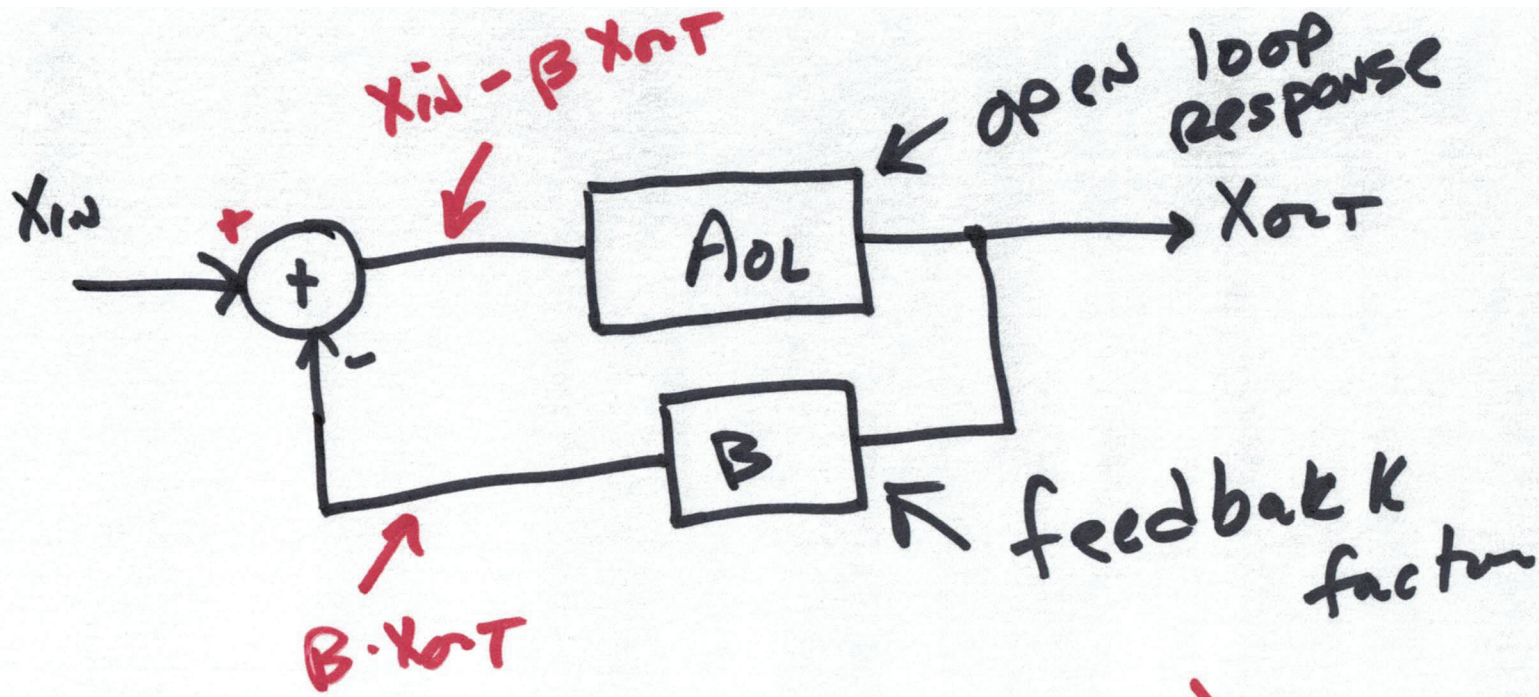


$$X_{out} = A_{OL} (X_{in} - \beta X_{out})$$

$$X_{out} (1 + \beta A_{OL}) = A_{OL} \cdot X_{in}$$



$$\frac{X_{out}}{X_{in}} = \frac{A_{OL}}{1 + \beta A_{OL}}$$

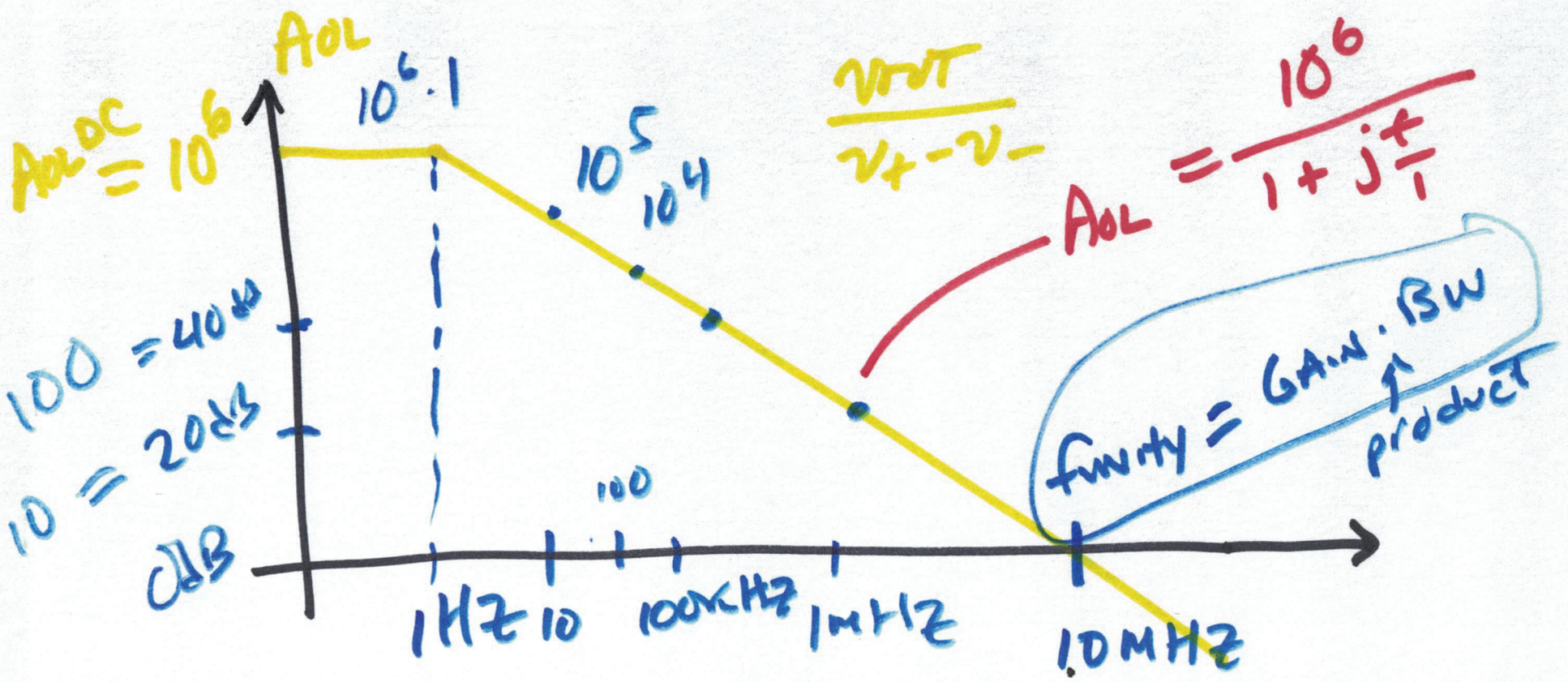loop gain  $\rightarrow$   
 $-1$  unstable





# Voltage follower

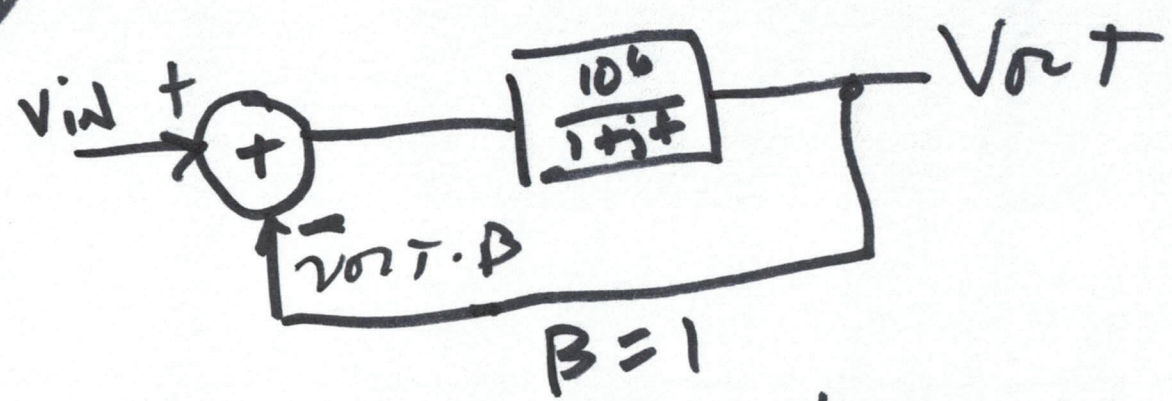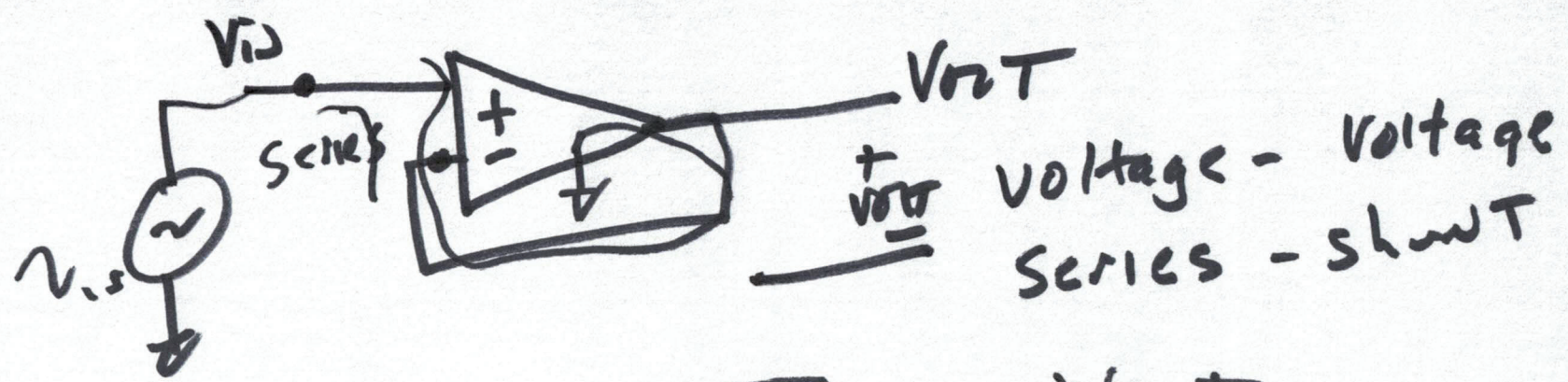


$$\frac{v_{out}}{v_{in}} = \frac{\frac{10^6}{1+jf}}{1 + \frac{10^6}{1+jf}} = \frac{10^6}{1+jf+10^6}$$



a)

$$\frac{V_{out}}{V_{in}} \approx \frac{1}{1 + j \frac{f}{10^6.1}}$$

Gain.BW = 10

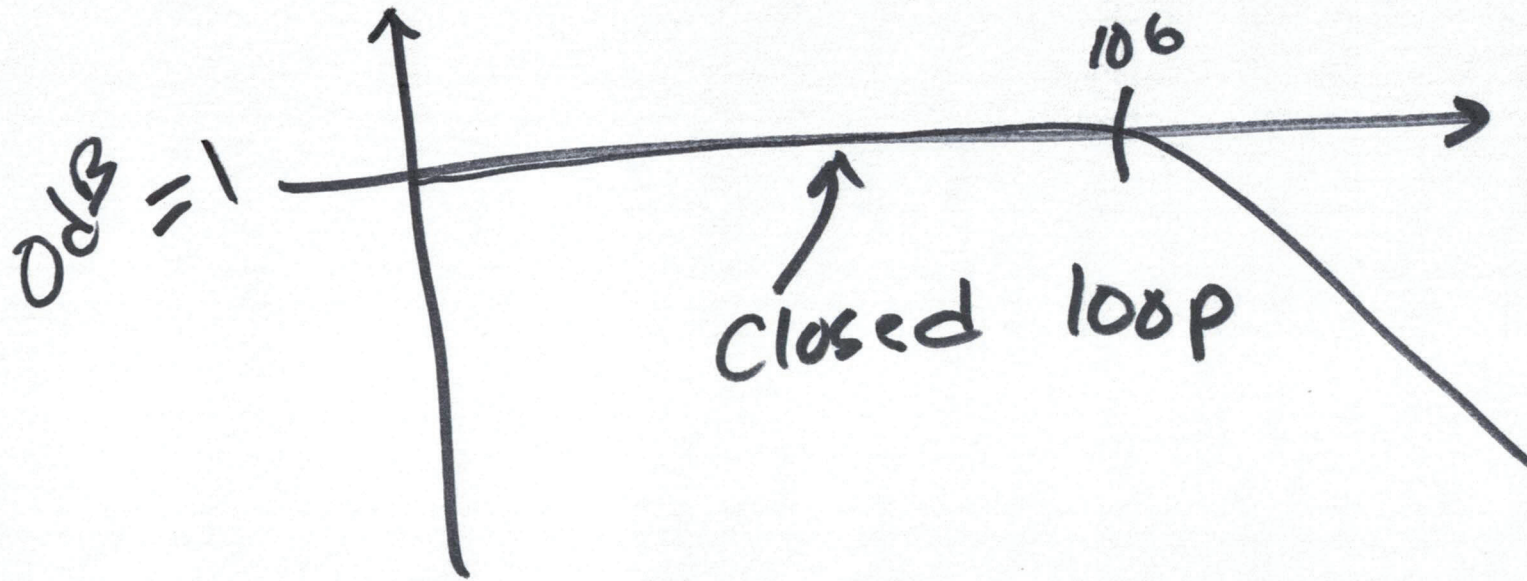

107

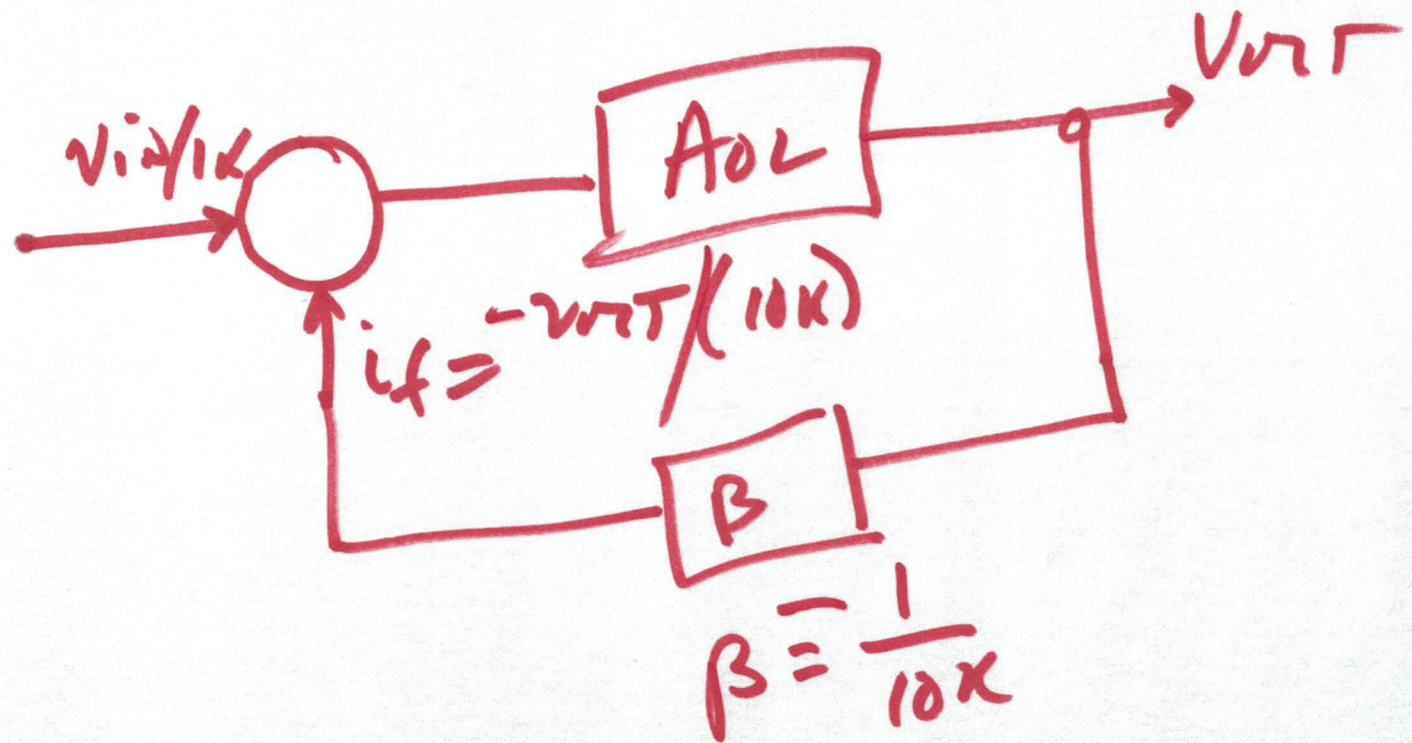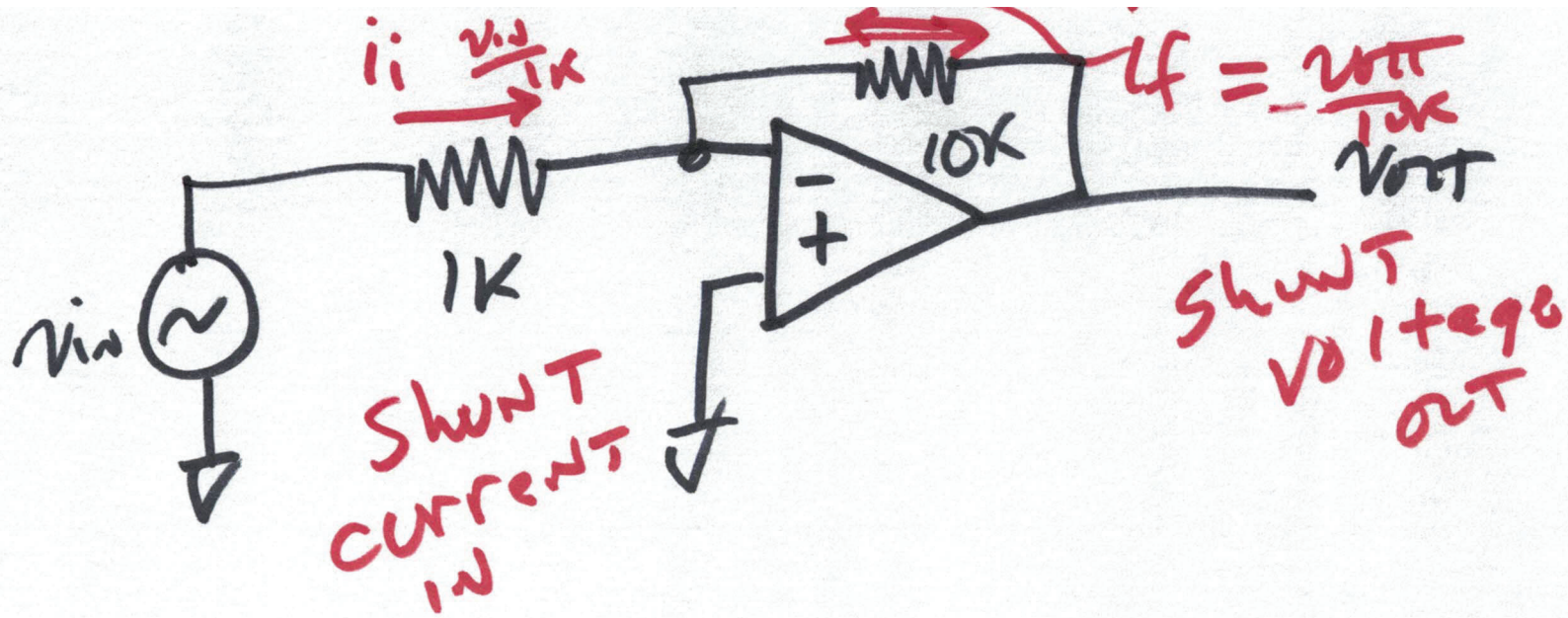

$$\frac{V_{out}}{i_i} = \frac{A_{OL}}{1 + A_{OL} \cdot \beta} = \frac{1}{\frac{1}{A_{OL}} + \beta}$$

$$v_i = i_i \cdot 1K$$

$$i_i = \frac{v_i}{1K}$$

$$= \frac{1}{1 + j \frac{f}{10^6}} \cdot \frac{1}{10^4}$$

$$\frac{V_{out}}{i_i} = \frac{1}{\frac{1}{10^6} + j \frac{f}{10^6 \cdot 1}} \rightarrow \frac{1}{10^4}$$

$\frac{v_i}{1K}$

Gain · BW product

12)

$$\frac{v_{out}}{v_i} = \frac{\approx \frac{1}{1K}}{\frac{1}{10^6} + j \frac{f}{10^6 \cdot 1} \approx \frac{1}{10K}}$$

$$= - \frac{10K}{1K}$$

$$= \frac{\frac{1}{10^3} + j \frac{f \cdot 10^3}{10^5 \cdot 1} + \frac{10^3 \cdot 10^3}{10^6}}{\frac{1}{10^3} + j \frac{f \cdot 10^3}{10^5 \cdot 1} + \frac{10^3 \cdot 10^3}{10^6}}$$


$$\approx - \frac{10K}{1K}$$

$$1 + j \frac{f}{10^5}$$

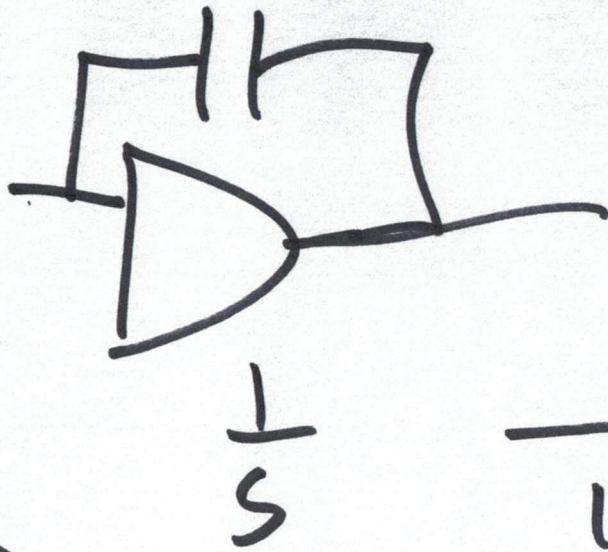(3)

$$\frac{\frac{1}{1K}}{\frac{1}{10^6} + j \frac{f}{10^6 \cdot 1} + \frac{1}{10K}}$$

$$\frac{\frac{10^6}{10K}}{1 + j \frac{f}{1} + 10^2} = \frac{\frac{10^4}{1K}}{1 + j \frac{f}{10^2} + \frac{1}{10^2}}$$



$$\frac{A_{OL}}{1 + \beta A_{OL}}$$

$$|\beta A_{OL}| = 1$$
$$\angle \beta A_{OL} = 180$$
$$\beta A_{OL} = -1$$