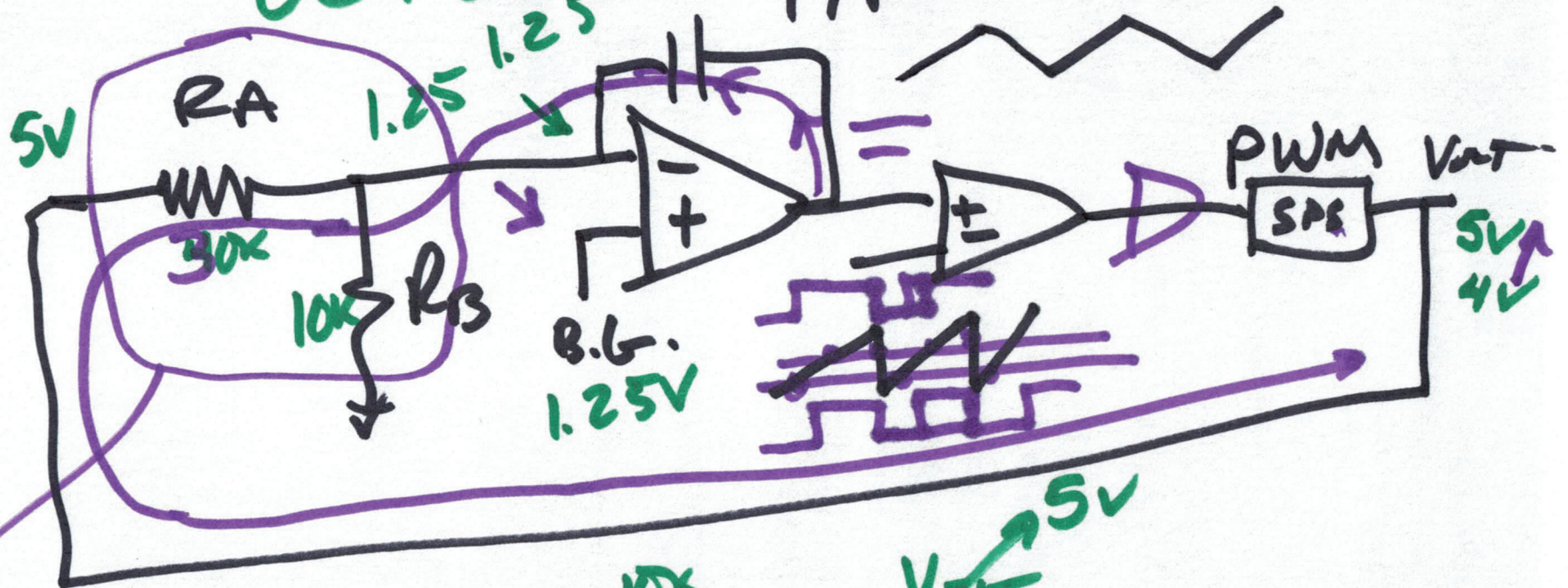


EE 442 Power Elec.

Lecture 12

October 12, 2022

TYPE-I



$$\beta = \frac{R_B}{R_A + R_B} \cdot 1.25 = \frac{10k}{10k + 30k} \cdot V_{out} \rightarrow 5V$$

$$A_{cl} = \frac{A_{ol}}{1 + \beta A_{ol}} = \frac{V_{out}}{V_{in}} = \frac{1}{\frac{1}{A_{ol}} + \beta}$$

$A_{ol} \rightarrow \infty$

$$A_{cl} = \frac{V_{out}}{V_{in}} = \frac{1}{\beta}$$

$$= \frac{R_A + R_B}{R_B} = \frac{390k + 10k}{10k}$$




$$A_{cl} = 4$$

$$V_{out} = V_{in} \cdot A_{cl}$$


$$= 1.25V \cdot 4 = 5V$$

2)

AOL

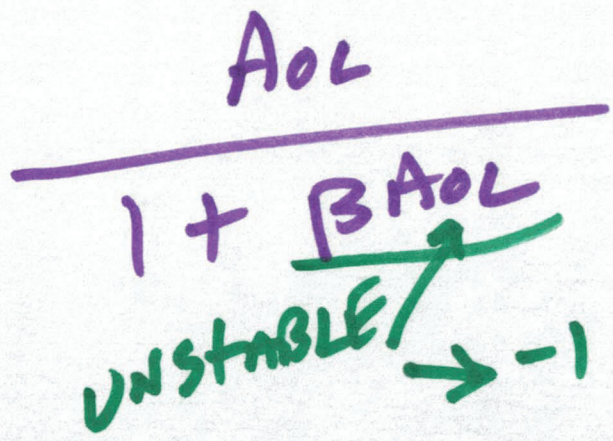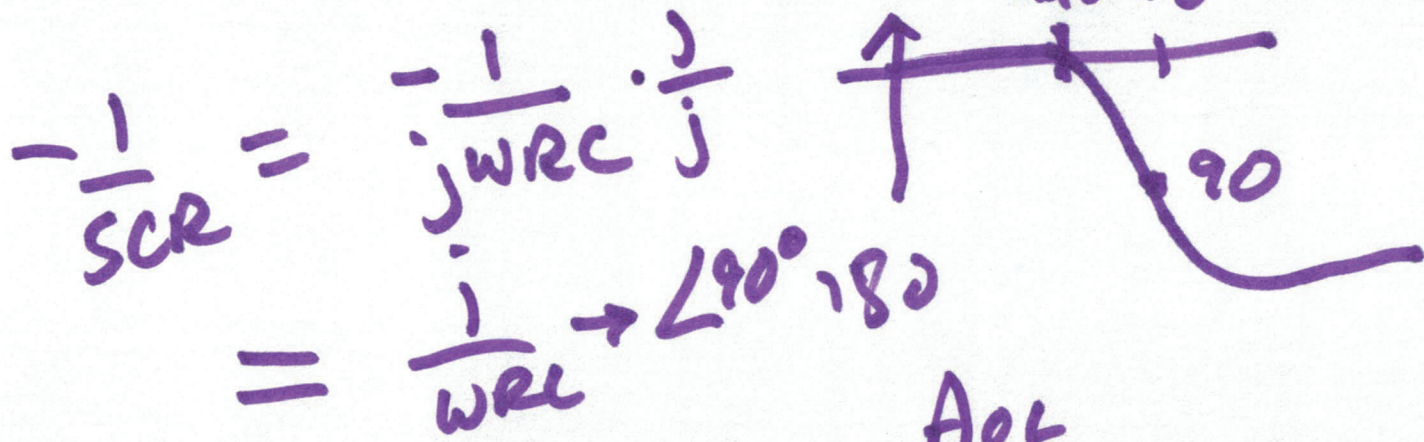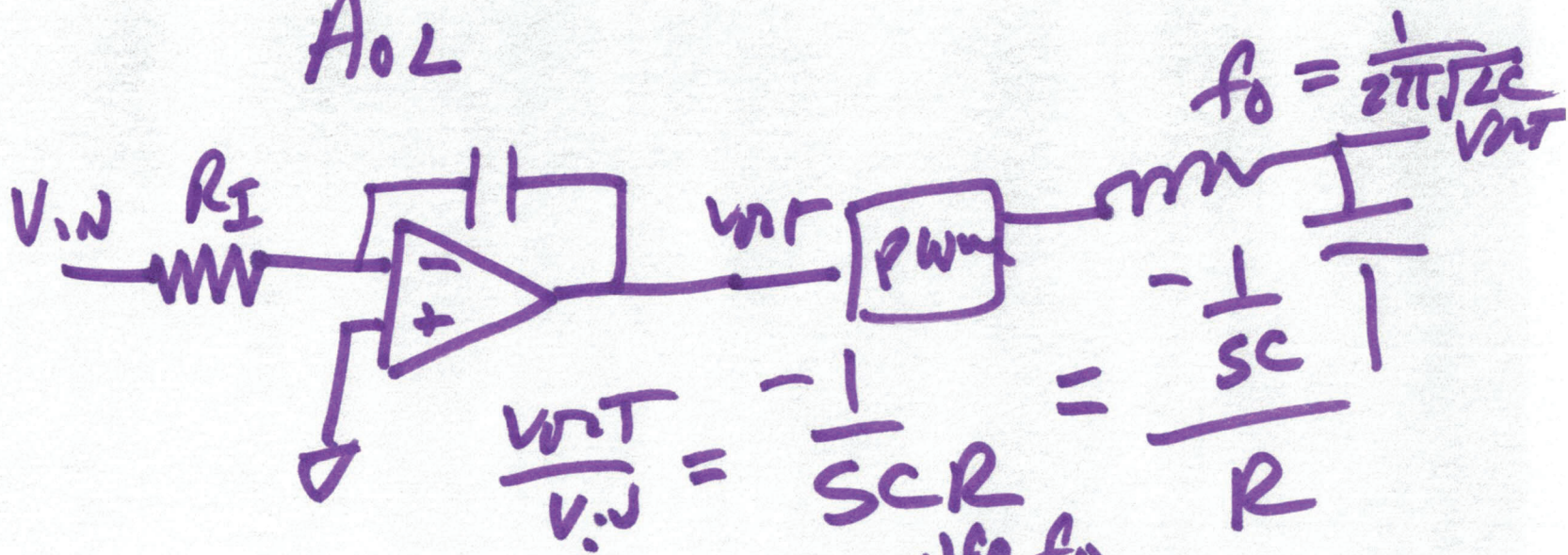
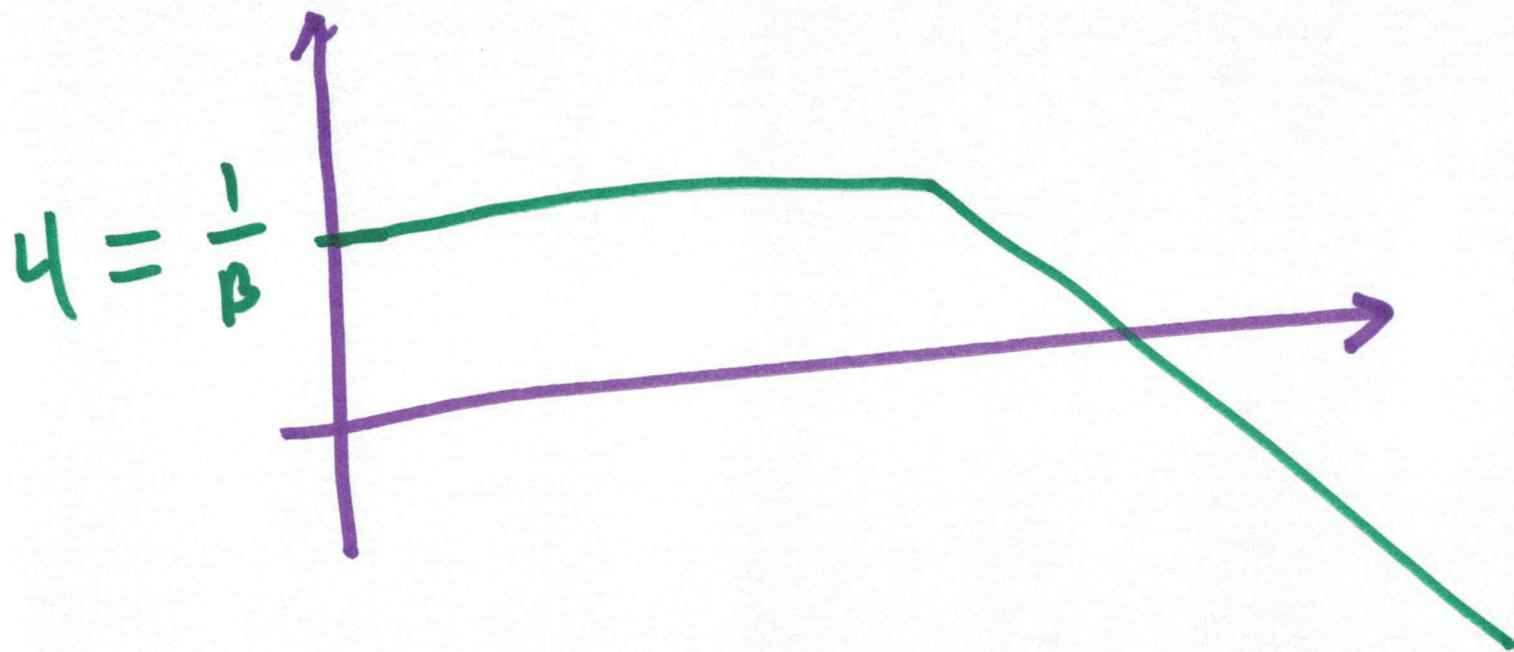
$$A_{CL} = \frac{\frac{1}{sCR}}{1 + \beta \cdot \frac{1}{sCR}} = \frac{1}{\beta} \cdot \frac{1}{\frac{sCR}{\beta} + 1}$$




Loop Gain = βA_{OL}

$\beta A_{OL} = -1$

$|\beta A_{OL}| = 1$
 $\angle \beta A_{OL} = \pm 180$

WORST CASE
 $\beta = 1$


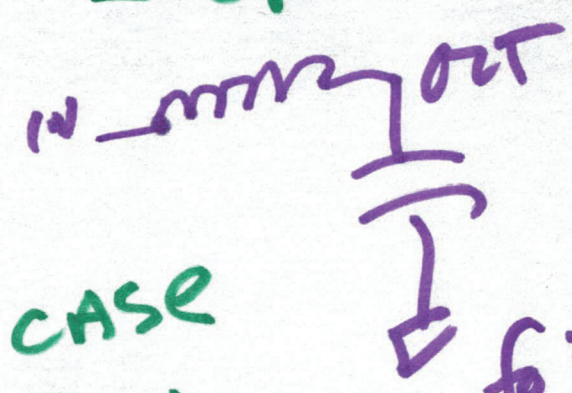


$f_0 = \frac{1}{2\pi RC}$


$|A_{OL}| = \left| \frac{1}{sRC} \right|$

$1 = \left| \frac{1}{sRC} \right|$

$1 = \left| \frac{1}{j\omega RC} \right|$

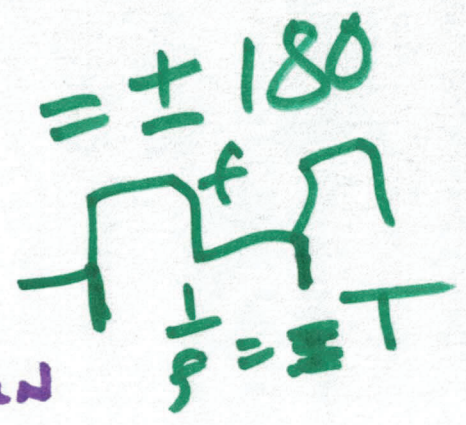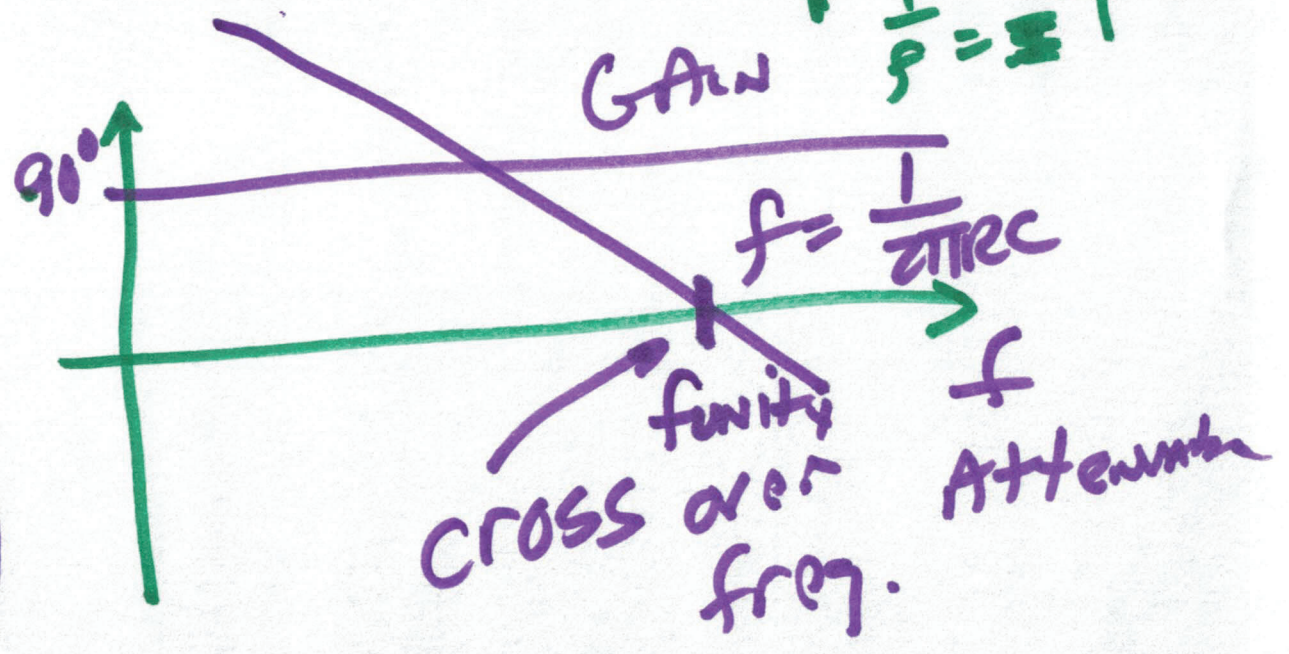

5)

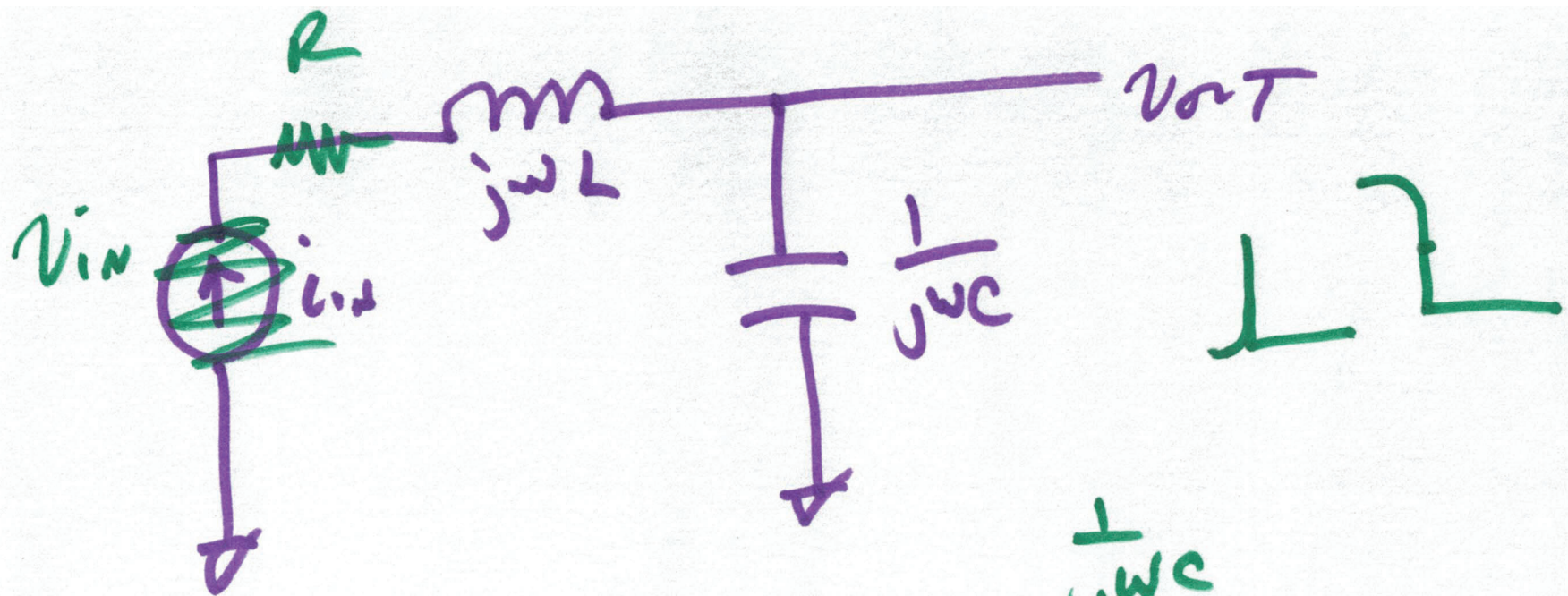

$$v_{out} = v_{id}$$

$$\frac{1}{j\omega C} + R + j\omega L$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{1 + j\omega RC + s^2 LC}$$

6)

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

$$s = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4 \cdot \frac{1}{LC}}}{2}$$

$$R \rightarrow 0$$

$$s = \frac{1}{\sqrt{LC}} \cdot \pm j$$

$$j\omega = \frac{1}{\sqrt{LC}} \pm j$$

$$f_0 = \pm \frac{1}{2\pi\sqrt{LC}}$$