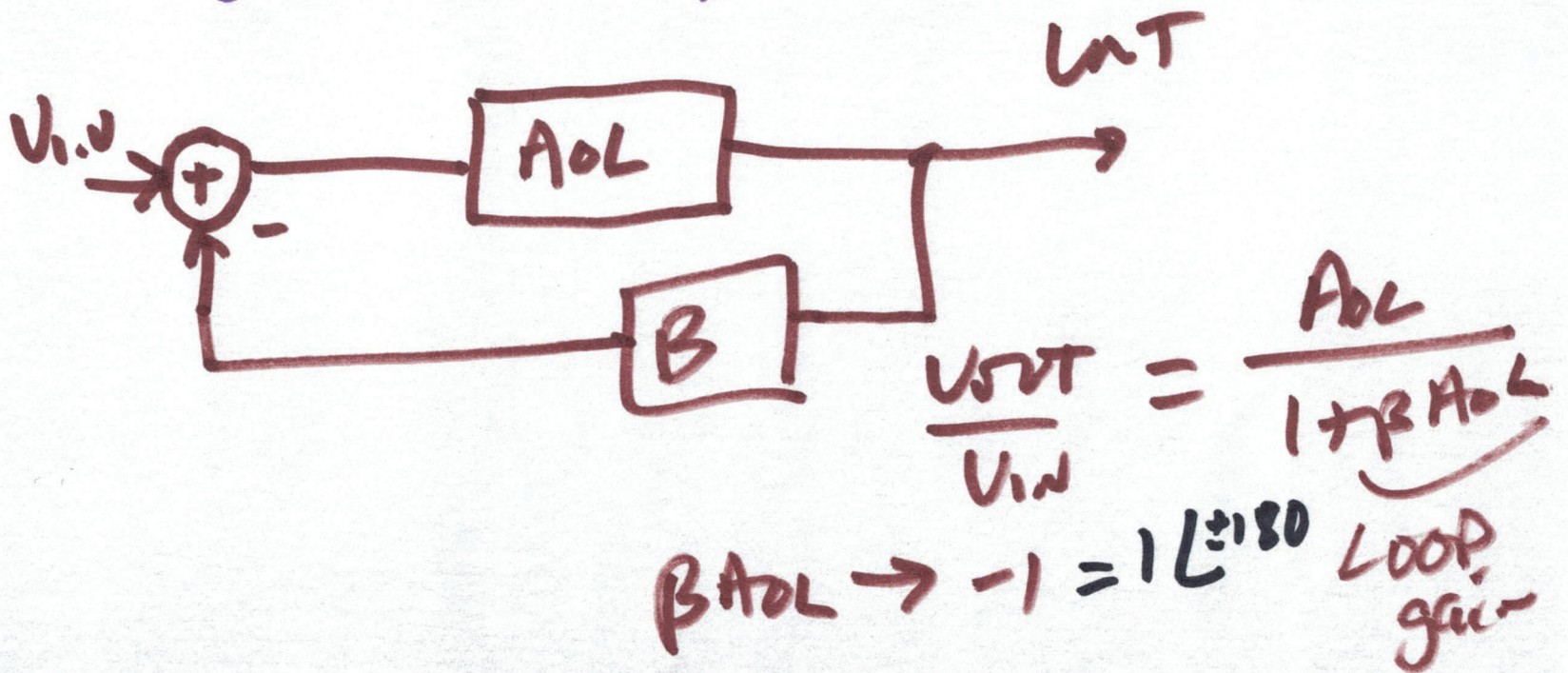




# EE 442 / ECE 642

## Power Electronics

Lecture 13


OCT. 17, 2022



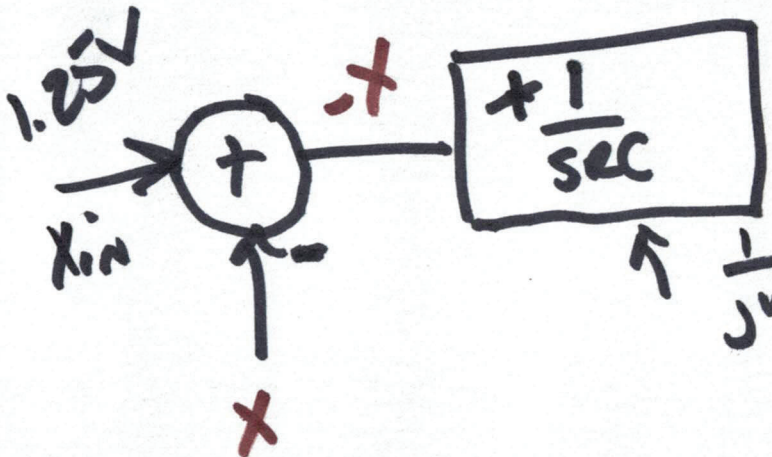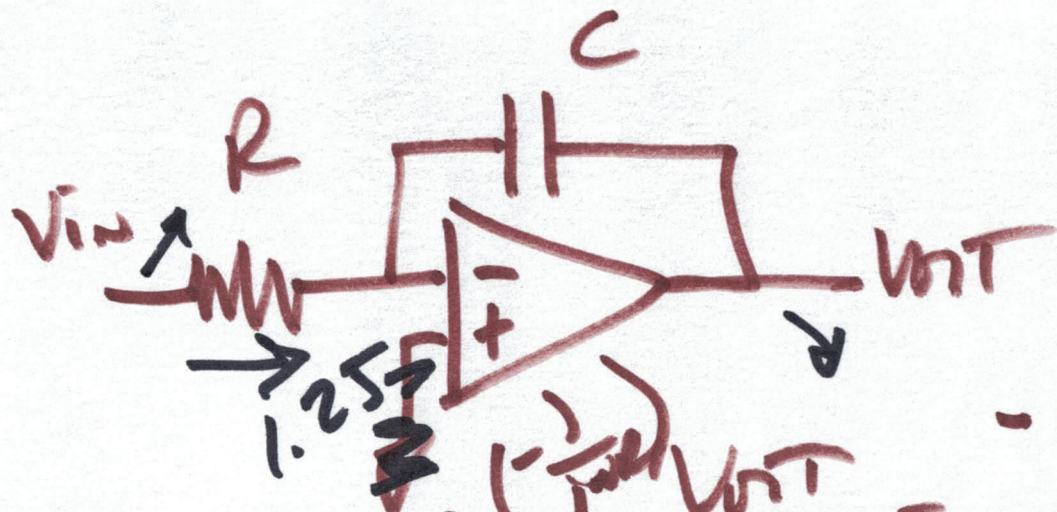


$$\begin{aligned}
 \frac{V_{out}}{V_{in}} &= \frac{-\frac{1}{sC}}{R} \\
 &= -\frac{1}{sRC} \\
 &= \frac{j}{\omega RC} = \frac{j}{\omega RC} \angle 90^\circ \\
 &\Rightarrow \frac{1}{\omega RC} \angle 90^\circ
 \end{aligned}$$
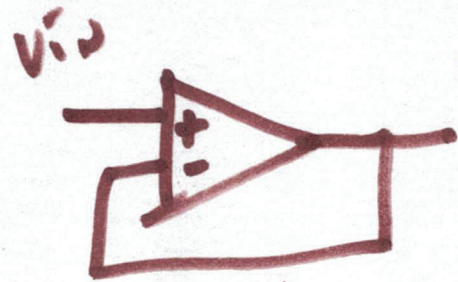
$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}} \rightarrow \frac{1}{\frac{1}{A_{OL}} + \beta} = \frac{1}{\beta}$$



$$\beta = 1$$

$$A_{CL} = \frac{1}{\beta} = 1$$

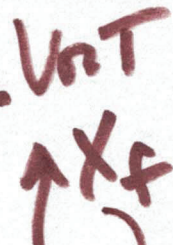

$$X_f = \beta \cdot v_o$$



$$v_o \cdot \frac{R_B}{R_B + R_A}$$

$$1.25 \times 1.6$$


$\beta$

$$A_{CL} = \frac{1}{\beta} = 1 + \frac{R_A}{R_B}$$

$$1 + \frac{6}{10} = 1.6$$

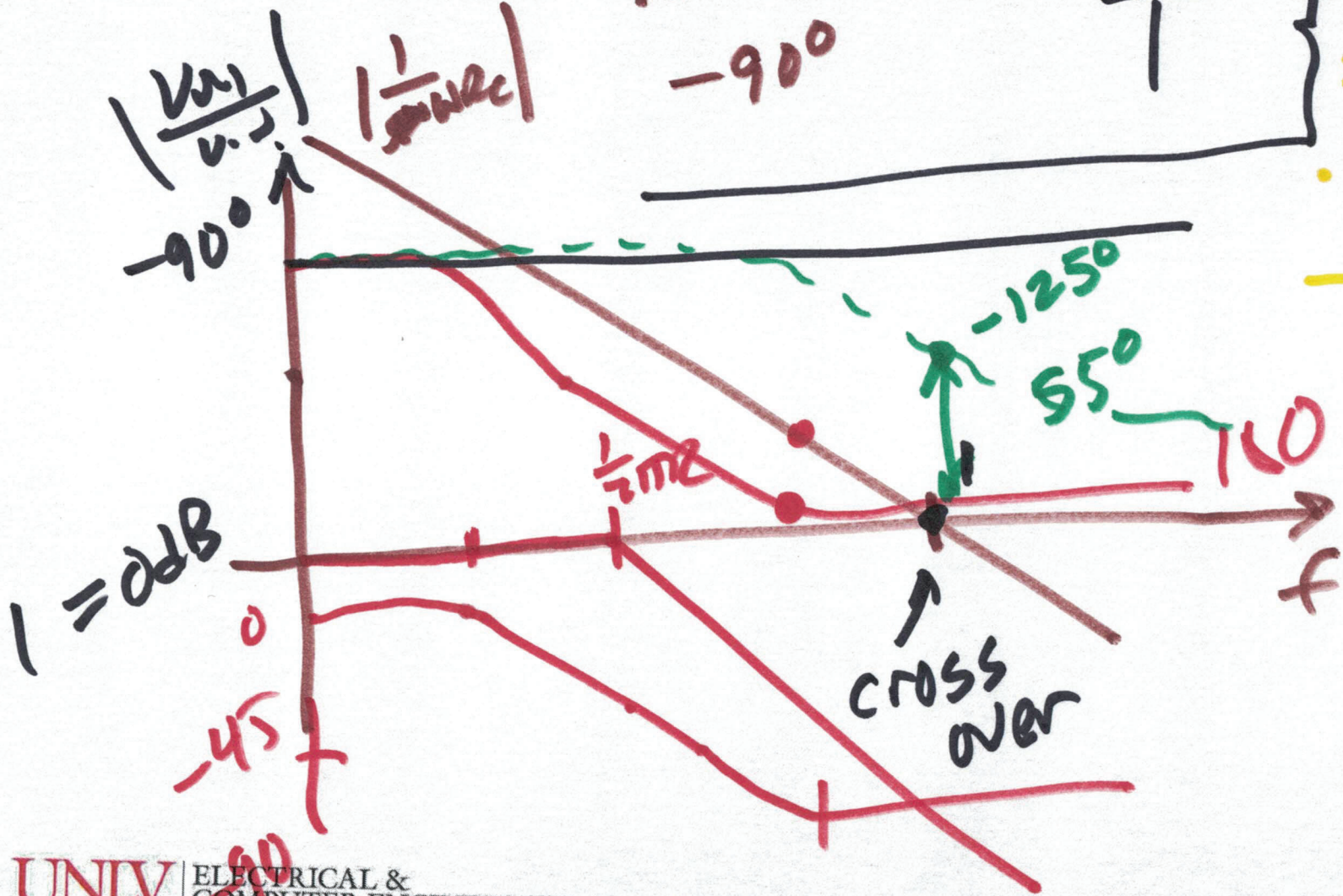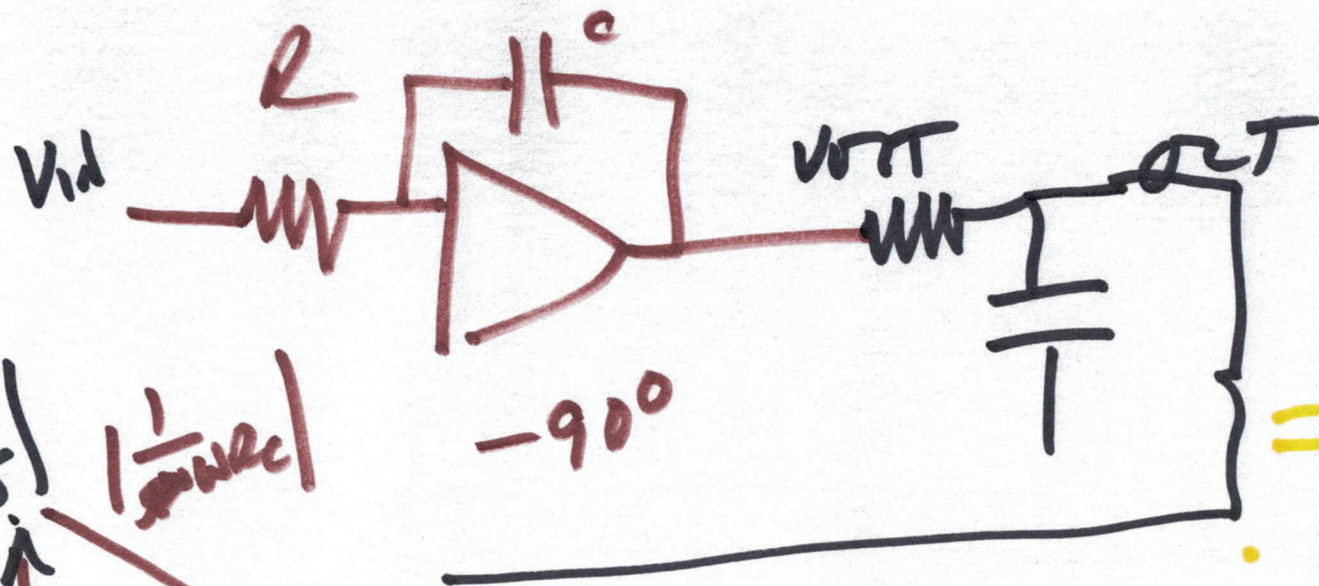

41

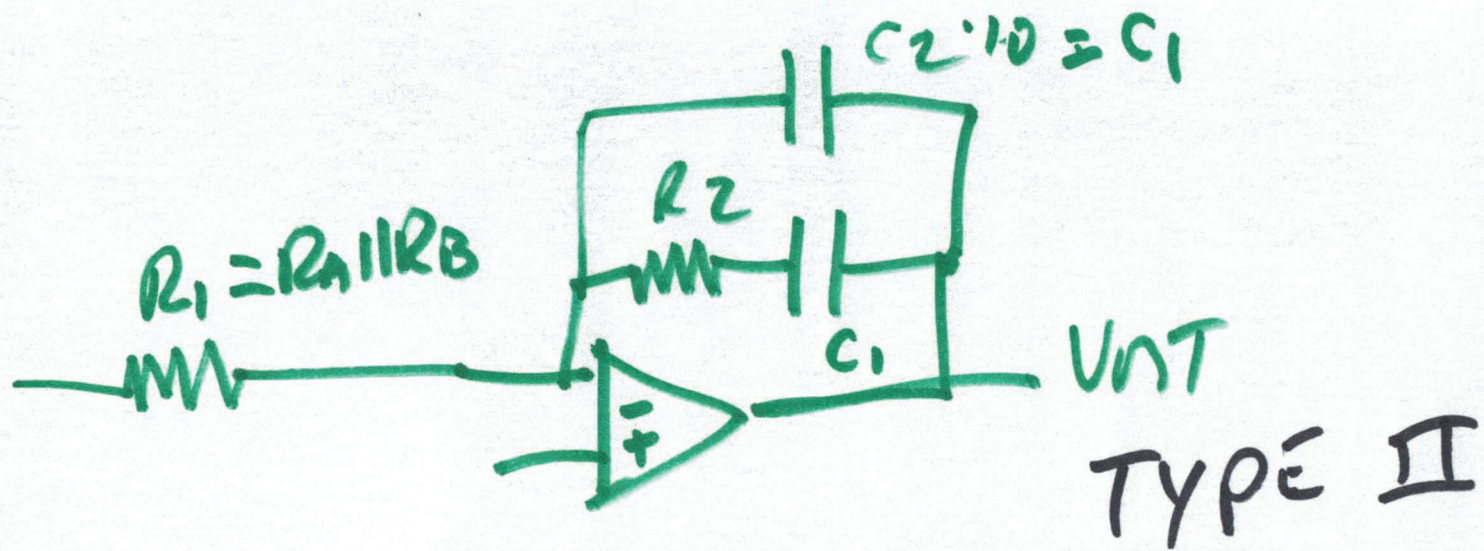

$$\frac{V_{out}}{V_{in}} = - \frac{R_2 + \frac{1}{j\omega C_1}}{R_1}$$

ACTIVE PI

$$= \underbrace{-\frac{R_2}{R_1}}_{\text{proportional}} + \underbrace{-\frac{1}{j\omega R_1 C_1}}_{\text{integral}}$$

$$\frac{V_{out}}{V_{in}} = - \frac{1 + j\omega C_1 R_2}{j\omega R_1 C_1} = - \frac{(1 + j \frac{f}{f_z})}{j \frac{f}{f_{un}}}$$

$$f_z = \frac{1}{2\pi C_1 R_2}, \quad f_{un} = \frac{1}{2\pi R_1 C_1}$$

$$\theta = \frac{t_d}{T} \cdot 360$$

$$= t_d \cdot f \cdot 360$$

