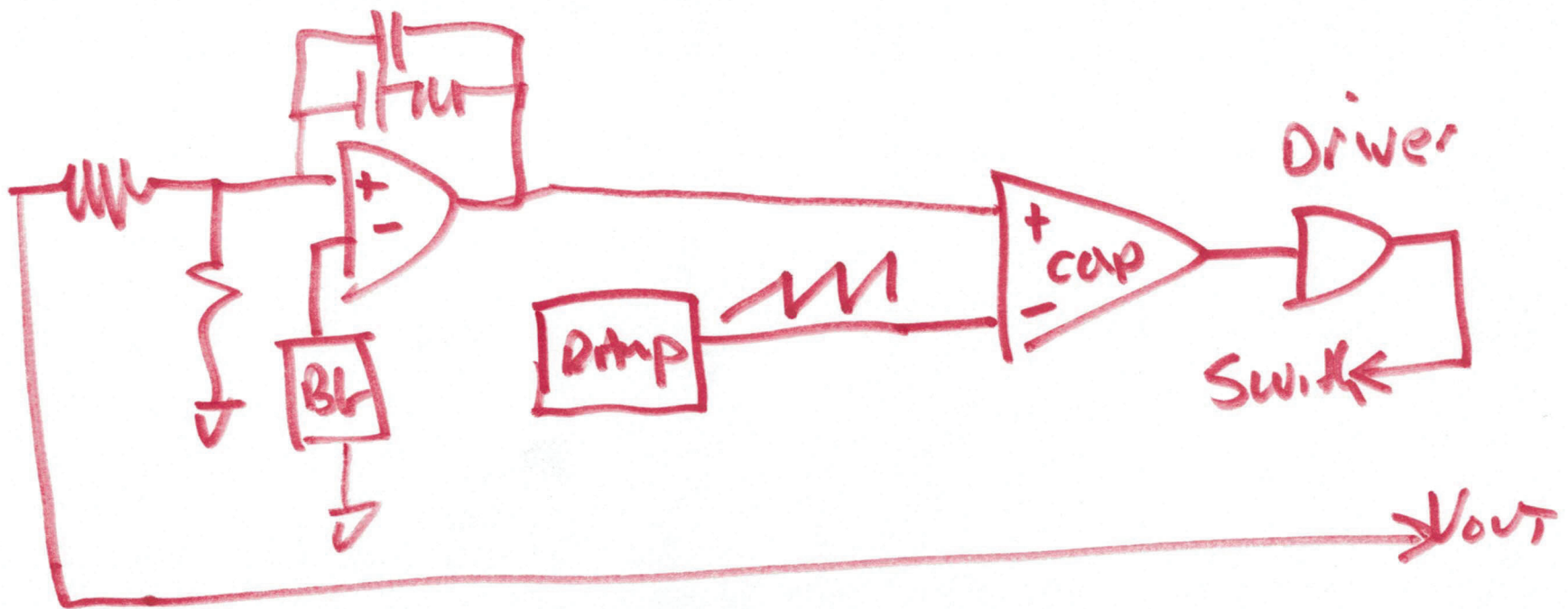




EE 442 / ECG 642

power Electronics


Lecture 18

NOVEMBER 2, 2022




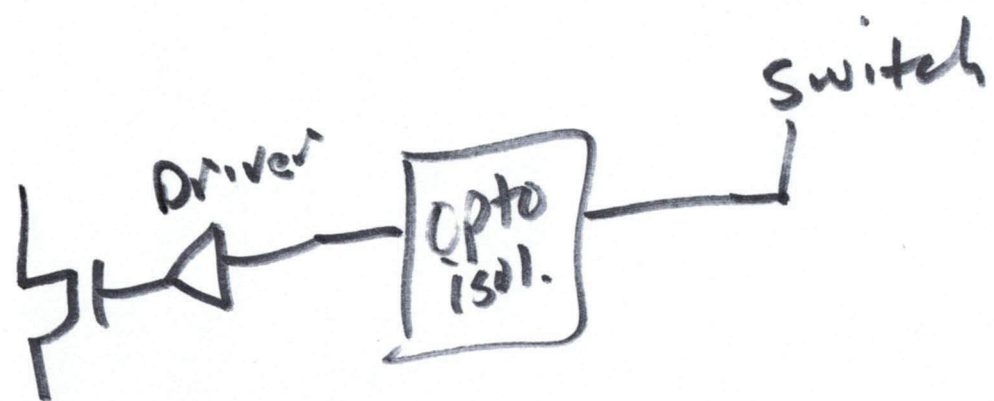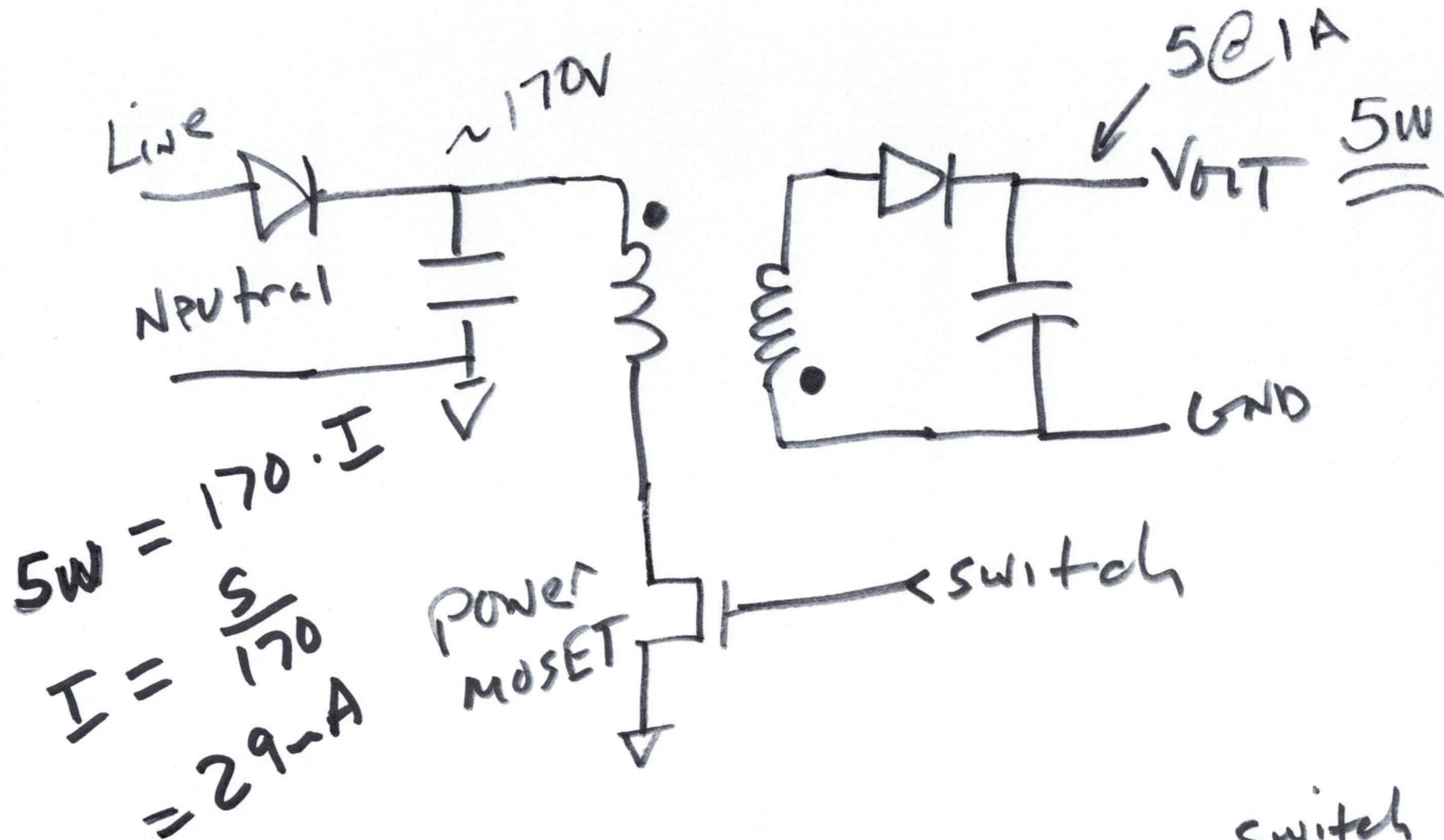


2)

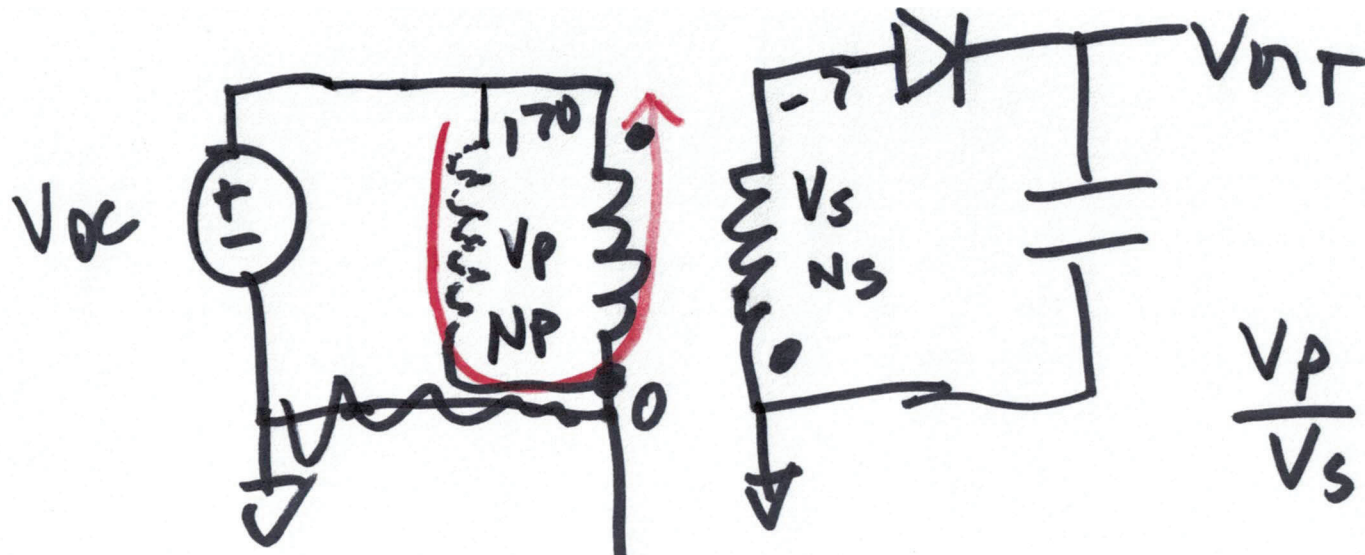

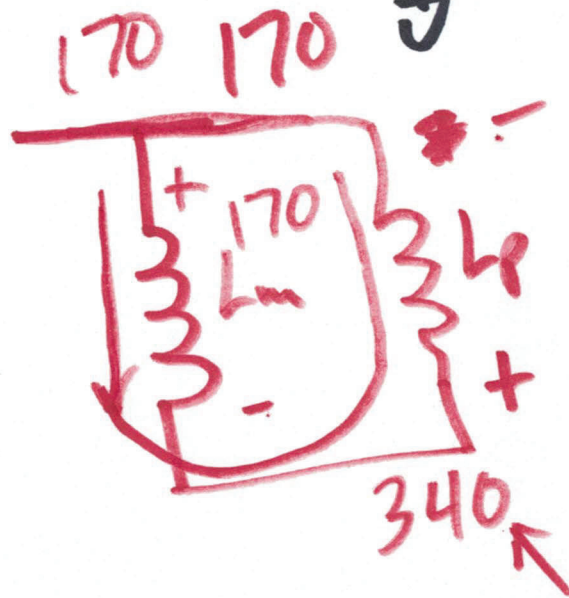
$$\frac{V_p}{V_s} = \frac{N_p}{N_s} = \sqrt{\frac{L_p}{L_s}}$$



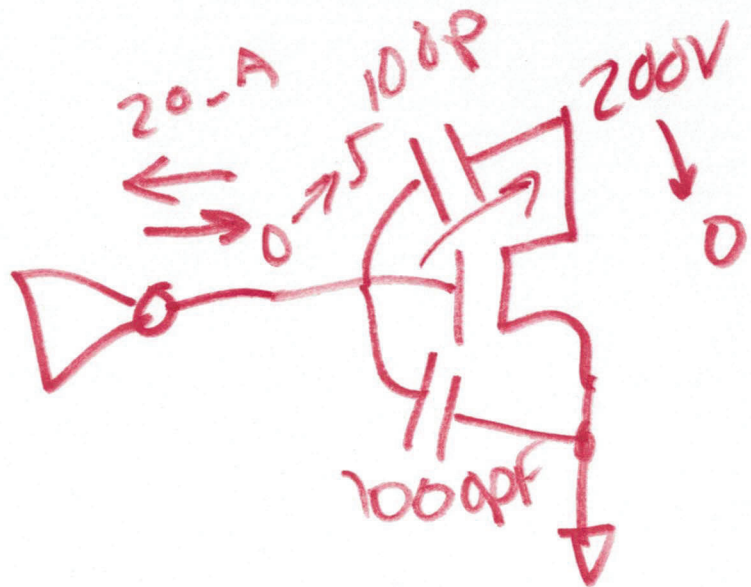

$$205V \cdot 100pF$$

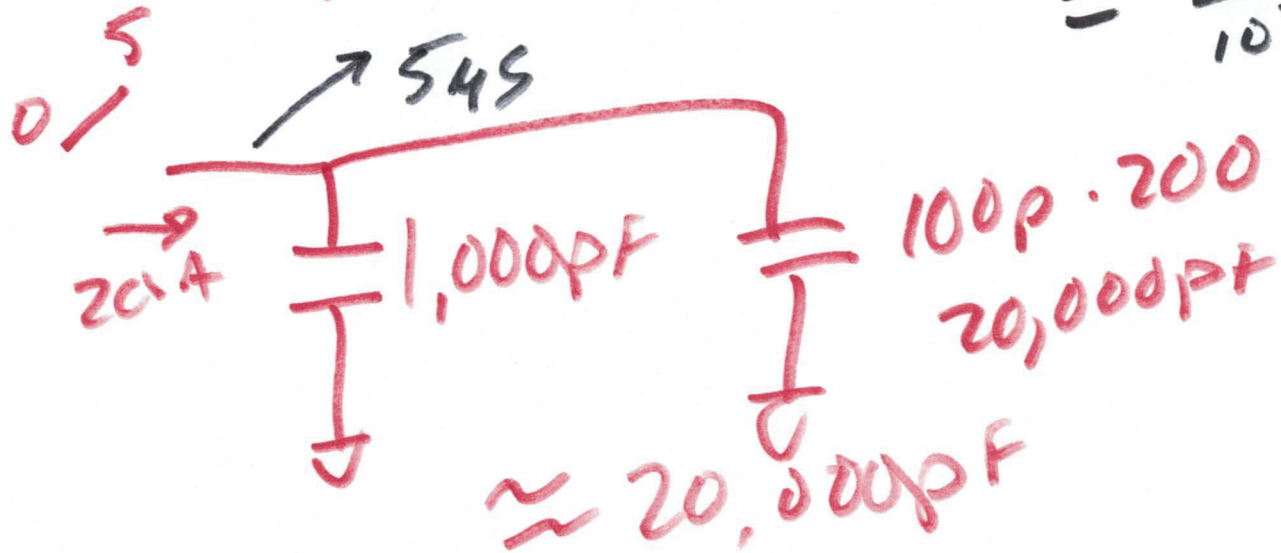
$$\frac{I}{C} = \frac{dV}{dt} = \frac{20nA}{20nF} = \frac{10}{10^{-9}} = \frac{1V}{4S}$$



$$\approx 20,000pF$$

4)

push-pull converter

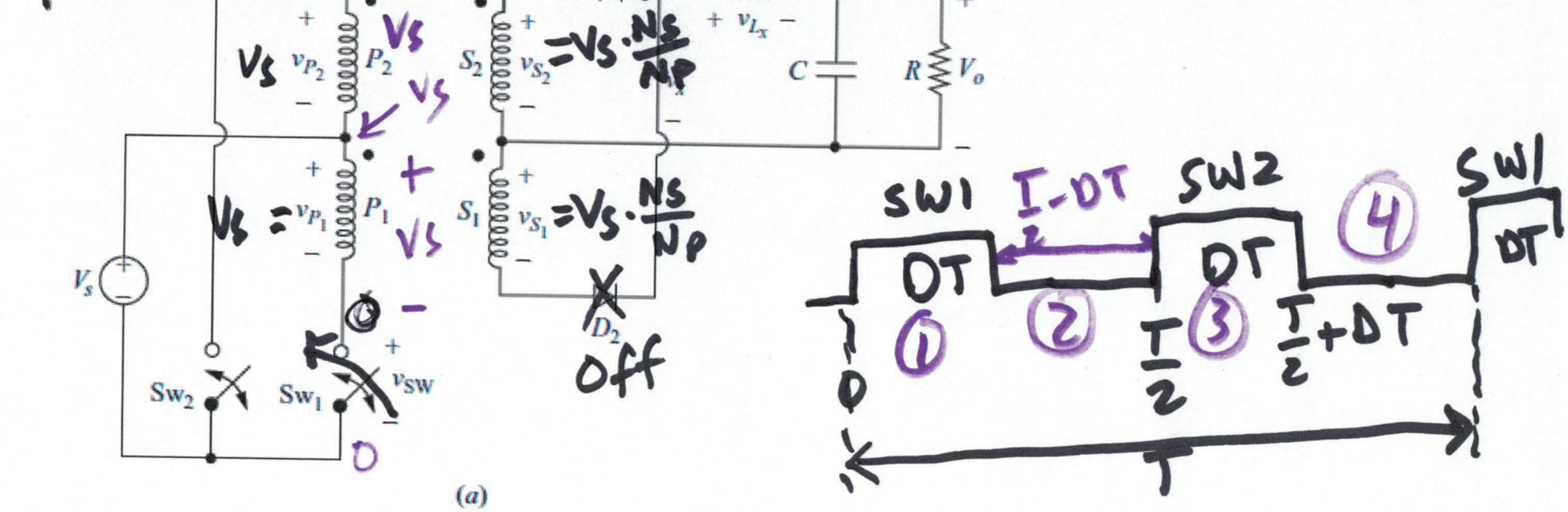


Sw1 closed

$$V_{Lx} = V_s \cdot \frac{N_s}{N_p} - V_o$$

$$\frac{V_s \frac{N_s}{N_p} - V_o}{L_x} = \frac{D i_{Lx}}{DT}$$
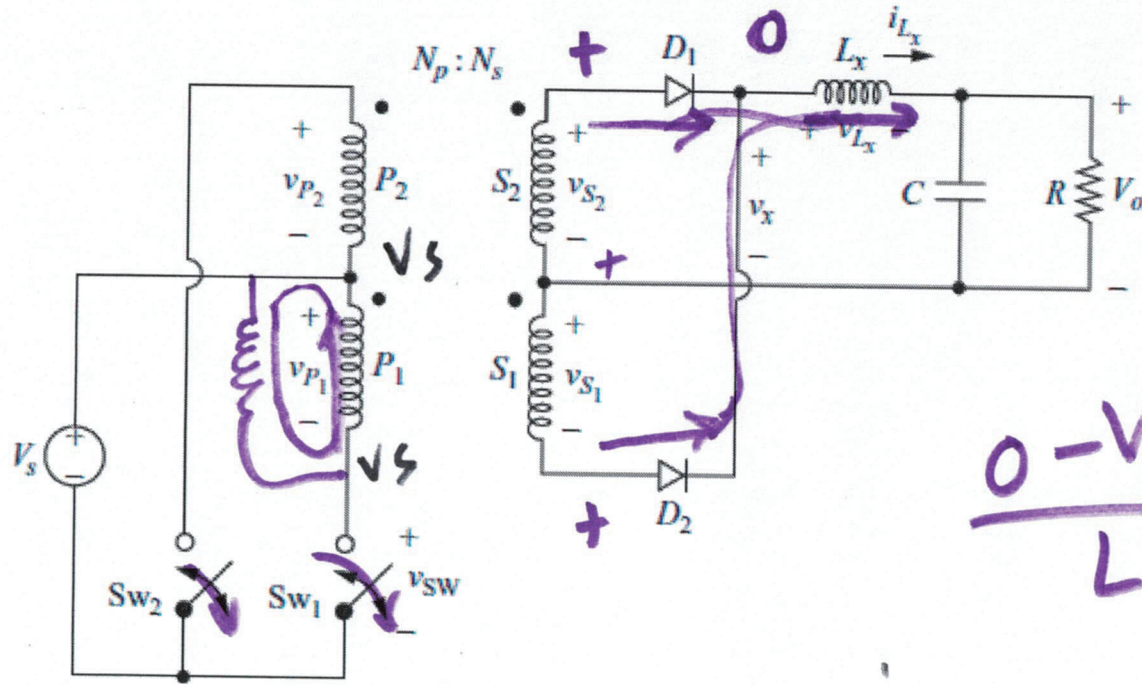
$$D i_{Lx} = DT \left(\frac{V_s \frac{N_s}{N_p} - V_o}{L_x} \right)$$



(a)

$$\frac{0 - V_o}{L} = \frac{\Delta i_{Lx} \text{ slope}}{\frac{T}{2} - DT}$$

$$\Delta i_{Lx} \text{ peak} = \frac{-V_o}{L \cdot T \left(\frac{1}{2} - D\right)} = -\frac{V_o}{L} \left(\frac{1}{2} - D\right) T$$


$$-\frac{V_0}{L_x} \left(\frac{1}{2} - 0 \right) T = DT \left(\frac{V_s \frac{N_s}{N_p} - V_0}{L_x} \right)$$

$$+\frac{V_0}{2} \cancel{DT} = DV_s \left(\frac{N_s}{N_p} \right) - DV_0$$



$$\left(-D + \frac{1}{2} + D \right) \frac{V_0}{2} = DV_s \left(\frac{N_s}{N_p} \right)$$

$$\frac{V_0}{2} = DV_s \left(\frac{N_s}{N_p} \right)$$
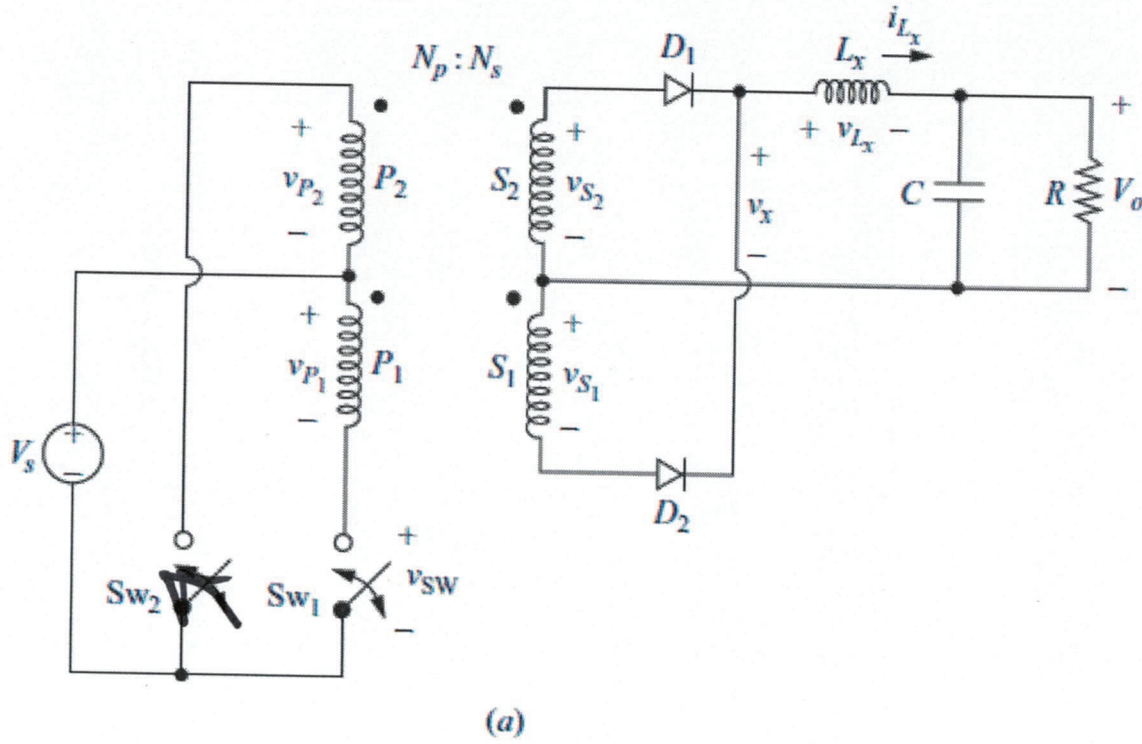
$$V_0 = 2V_s \left(\frac{N_s}{N_p} \right) D$$



full bridge

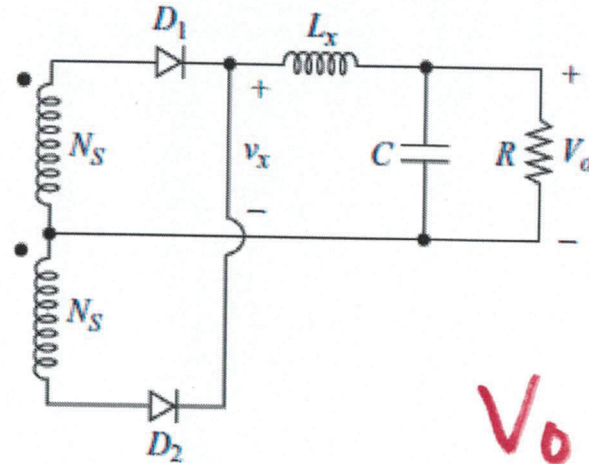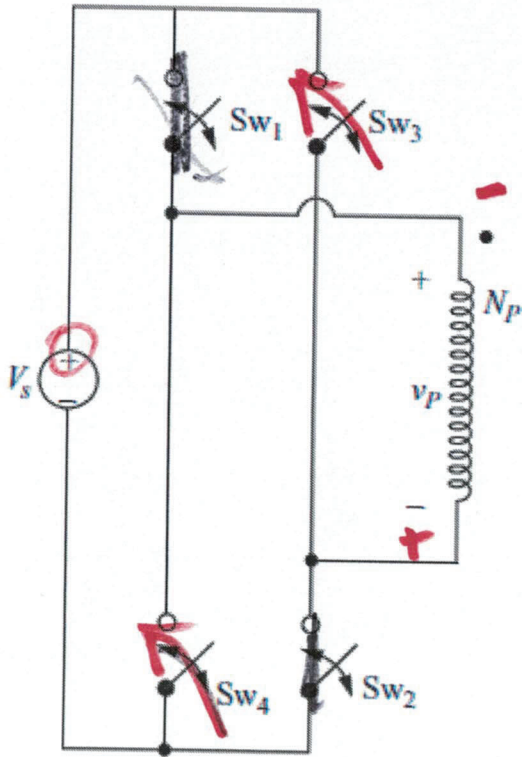

$$V_o = 2V_s \frac{N_s}{N_p} \cdot D$$

