

EE 442 / ECG 642 Power Electronics

Dec. 7, 2022



Lecture 24

$$v = L \frac{di}{dt}$$

$$5 - 3 = 5 \cdot \frac{\Delta i}{t}$$

$$\frac{2}{5} \cdot t = \Delta i$$


$$0 - 3 = \frac{\Delta i}{t}$$

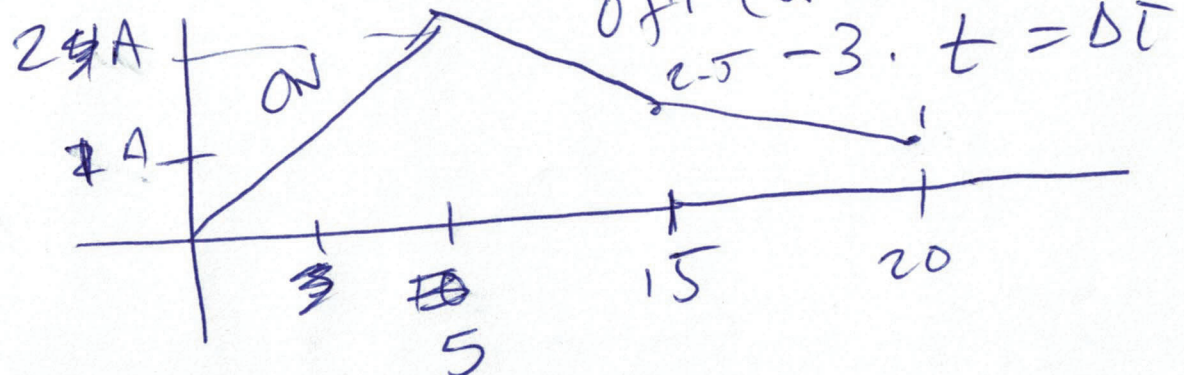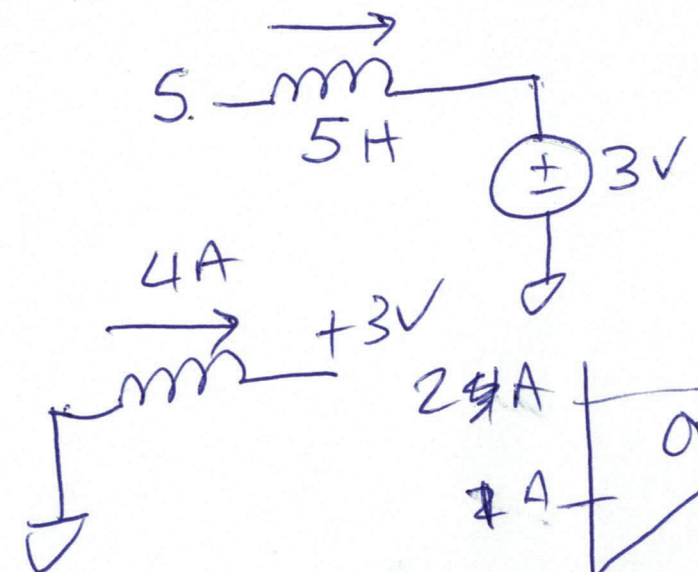

$$1.25 = V_{out} \cdot \frac{100k}{100k + 6k}$$

$$V_{out} = 1.25 \cdot \frac{16}{10} = 1.25 \cdot \frac{8}{5} = 2V$$

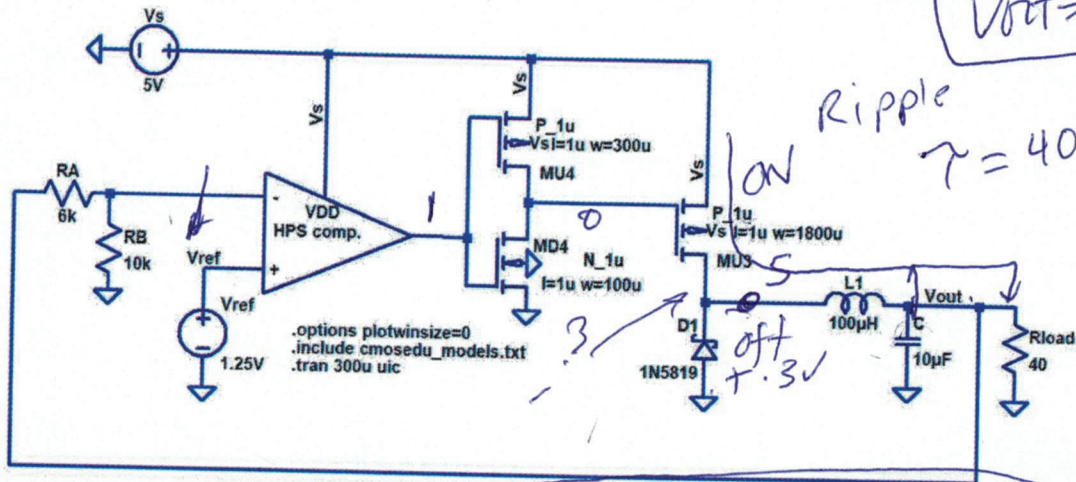9. For the following circuit, determine the current in the inductor, the average output voltage, and the ripple in the output voltage. As always, show your hand calculations for credit. Assume steady-state operation. (25 points)



T_{ON} = Time comp output is high

$$I_{AVG} = \frac{2}{40} = 50mA$$

T_{OFF} = Time comp out is low

$$V = L \frac{di}{dt}$$

$$5 - 2 = 100 \mu H \cdot \frac{\Delta I}{T_{ON}}$$

$$T_{ON} \cdot \frac{3}{100 \mu} = \frac{2.3}{100 \mu} \cdot T_{OFF}$$

$$\Delta I = T_{ON} \cdot \frac{3}{100 \mu}$$

$$\frac{T_{ON}}{T_{OFF}} = \frac{2.3}{3}$$

$$-0.3 - 2 = 100 \mu \cdot \frac{\Delta I}{T_{OFF}}$$

$$I = C \frac{dV}{dt} \Rightarrow 50mA = 10 \mu \cdot \frac{\Delta V}{T_{OFF}}$$


$$\Delta I = T_{OFF} \cdot \frac{3}{100 \mu}$$

$$\Delta V_{ripple} = \frac{50mA \cdot T_{OFF}}{10 \mu F}$$

21


$$V = L \frac{dI}{dt}$$

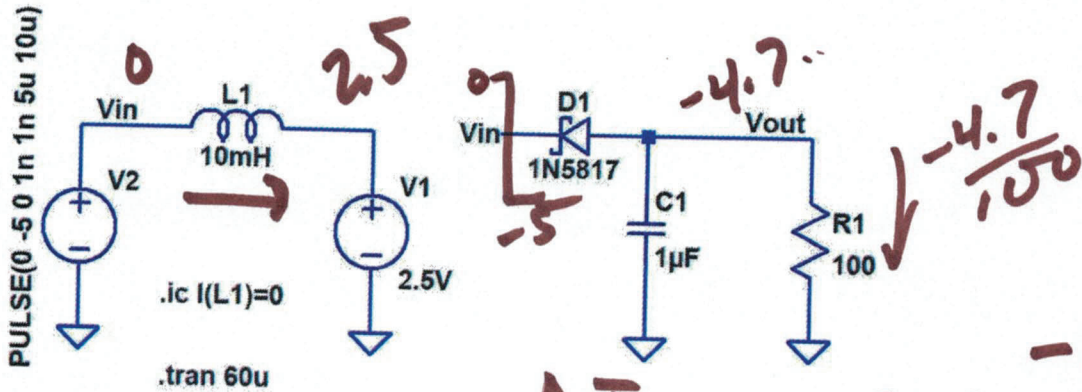8. Determine the currents flowing in L1 and R1 in the following circuits. (10 points)



$$0 - 2.5 = 10\text{m} \cdot \frac{\Delta I}{5\mu} \rightarrow \Delta I = \frac{-12.5\mu}{10\text{m}} = -1.25\text{mA}$$

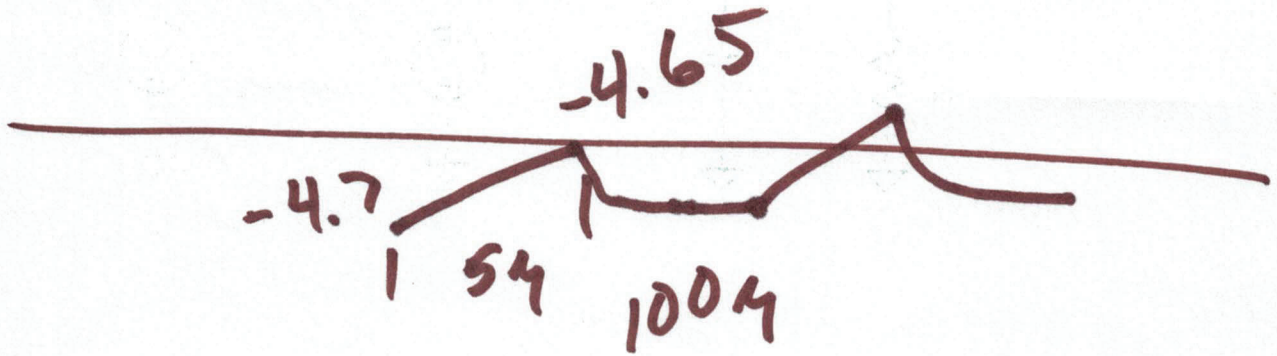
$$-5 - 2.5 = 10\text{m} \cdot \frac{\Delta I}{5\mu} \rightarrow \Delta I = \frac{-37.5\mu}{10\text{m}} = -3.75\text{mA}$$



3)

$$\frac{I_s}{I_p} = \frac{V_p}{V_s} = \frac{N_1}{N_2} = \sqrt{\frac{L_p}{L_s}}$$

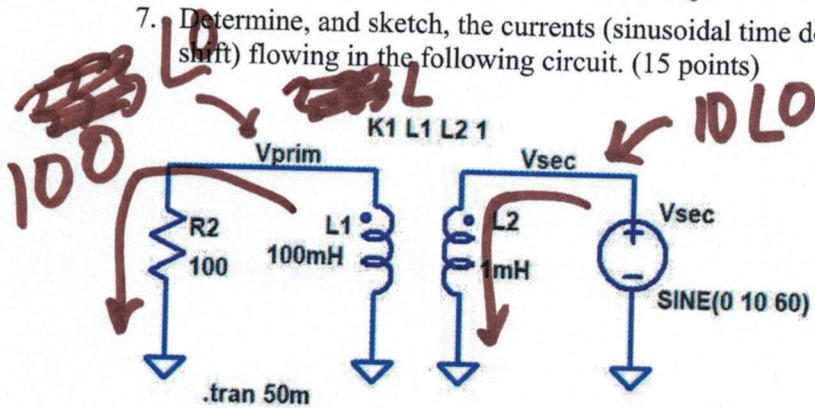7. Determine, and sketch, the currents (sinusoidal time domain equations that show phase shift) flowing in the following circuit. (15 points)



$$\sqrt{\frac{100}{1}} = 10 = \frac{V_p}{V_s}$$


$$V_{sec} = 10 L_0$$

$$V_{pri} = 100 L_0$$

$$I_{pri} = \frac{100 L_0}{100} = 1 L_0$$

$$I_{pri} = 10 L_0$$

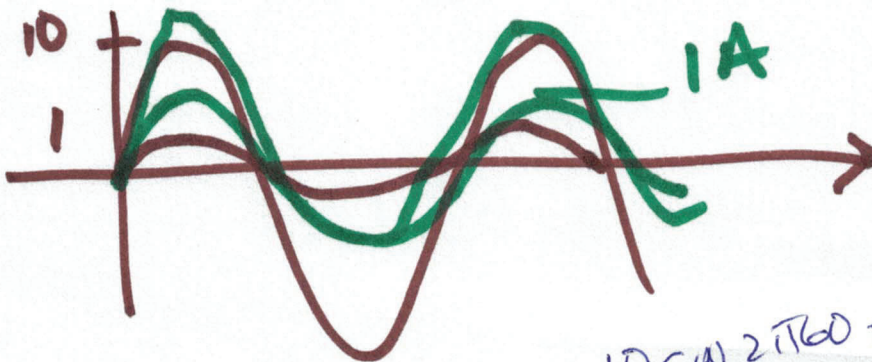
$$I_{mag} = \frac{10 L_0}{j \cdot 2\pi \cdot 60 \cdot 10^{-3}} = 2.65 L_0 - 90^\circ$$



$$I_{sec} = 10 \sin(2\pi 60 t) + 2.65 \sin(2\pi 60 t - 90^\circ)$$

1)

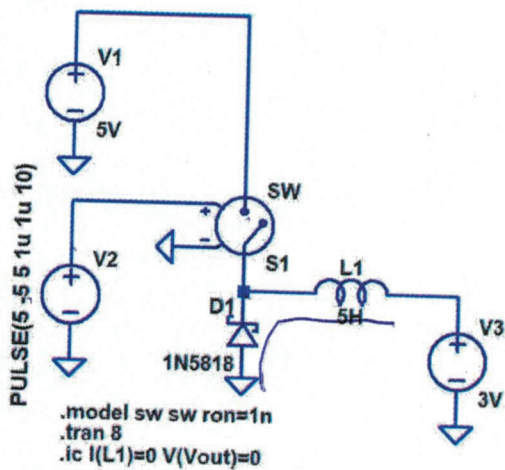6. Estimate, and sketch, the current flowing in the inductor in the following circuit. (15 points)



~~$I_{out} = 5$~~
 ~~$T_{off} = 10$~~


$T_{off} = 5$

$T_{on} = 10$

$$V = L \cdot \frac{di}{dt}$$


$$5 - 3 = 5 \cdot \frac{\Delta I}{t \cdot 10^{-6}}$$

$$\Delta I = \frac{2}{5} \cdot t$$

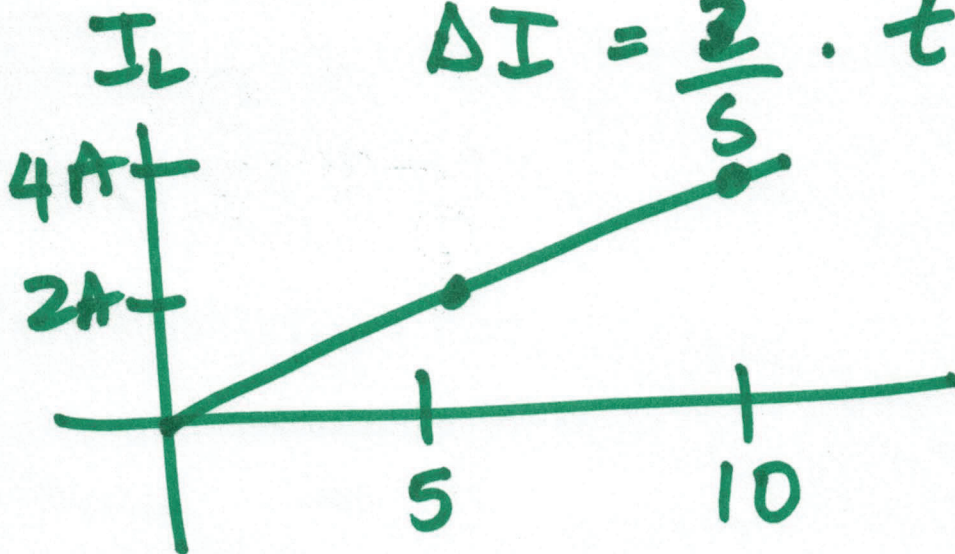

5)

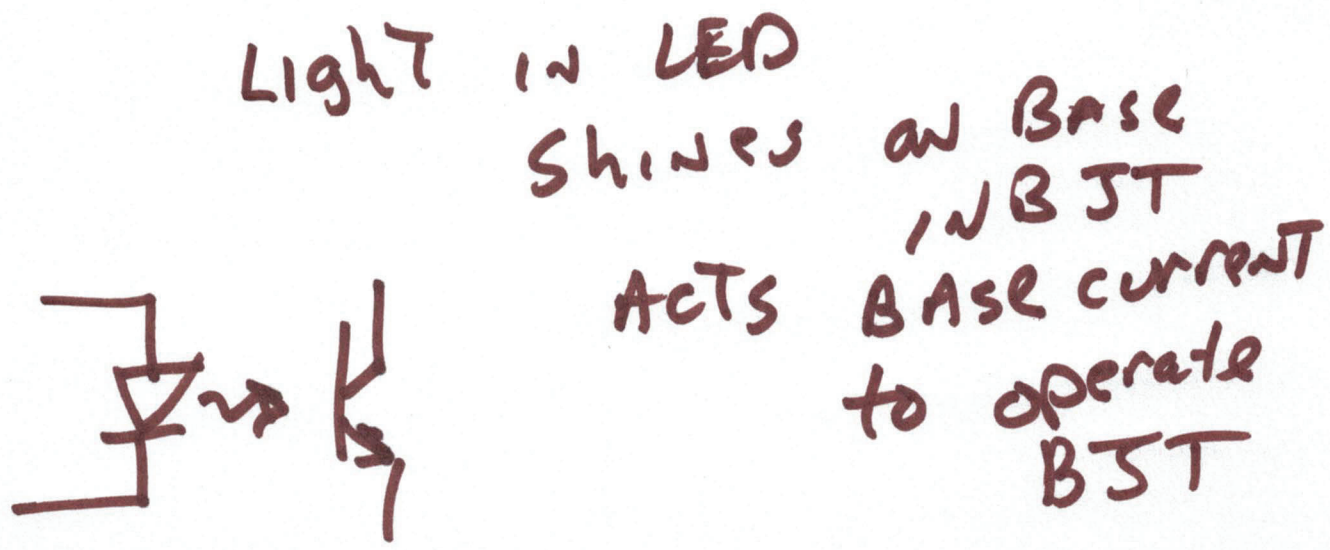4. Explain how an opto-isolator works? (5 points)



5. What is the average power used to charge/discharge a 1uF capacitor between 5V and ground at 100MHz? What is using, and what is storing, the energy in this situation? (5 points)

10uF using energy

10ns storing energy

5V

10uF

10ns

$$CV = Q = 10\mu F \cdot 5 = 50\mu C$$
$$I_{AVG} = \frac{50\mu C}{10ns} = 5000 A!$$
$$P_{AVG} = 5 \cdot 5000 = 7.5 kW!$$


↑ POWER SUPPLY

6)

$$S = S \cdot \frac{dI}{dt} \quad V = L \frac{di}{dt} = L \cdot \frac{SA}{t}$$

$\Delta I = 1$

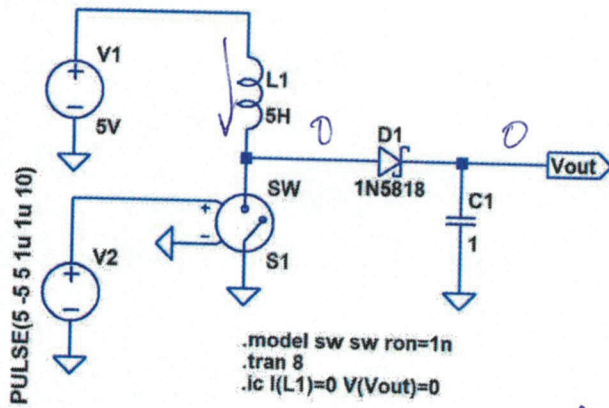
3. Estimate, and plot, the output voltage in the following circuit. (15 points)



$$S = S \cdot \frac{\Delta I}{5}$$

$$\Delta I = SA$$

inductor current

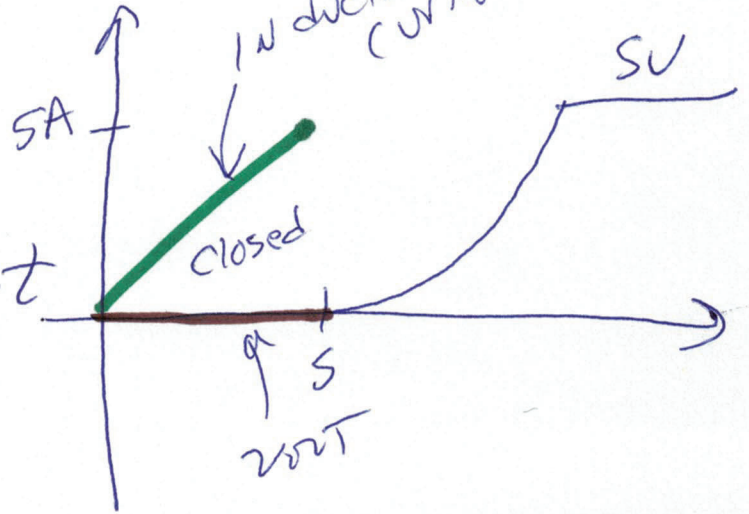

$$I = C \frac{dV}{dt}$$

$$I_L = 1 \cdot \frac{\Delta V_{nt}}{t} = 1A \cdot t$$

$$\Delta V_{nt} = 1t^2$$


7)

NAME: _____


Closed book and notes.

Show your work for credit and put a box around your answers.

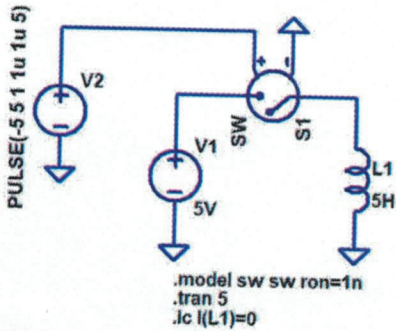- Determine, and sketch, the current flowing in the inductor in the following circuit. (5 points)


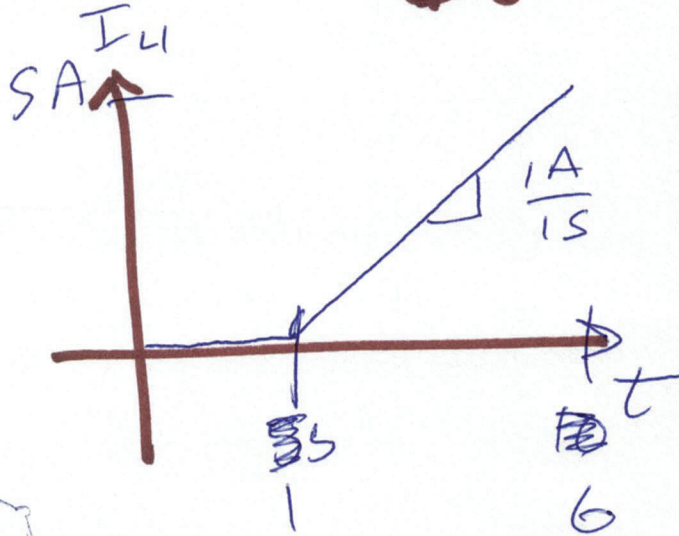
$$5 = 5 \cdot \frac{\Delta i}{\Delta t}$$



- Explain, in your own words, what the difference between reverse recovery time and storage time is in a diode. (5 points)

storage time → time to remove stored charge
 reverse recovery time = storage time plus time to charge diode's depletion CAP

2)