

EE 442 / ECE 642

Power Electronics

Sept. 12, 2022

Lecture 4


$$V_m = 200V, R = 1K, C = 1\mu F$$

$$\omega = 377$$

$$RC = 1S$$

$$T = \frac{1}{60} = 16.67ms$$

$$RC \gg \frac{1}{\omega} T$$

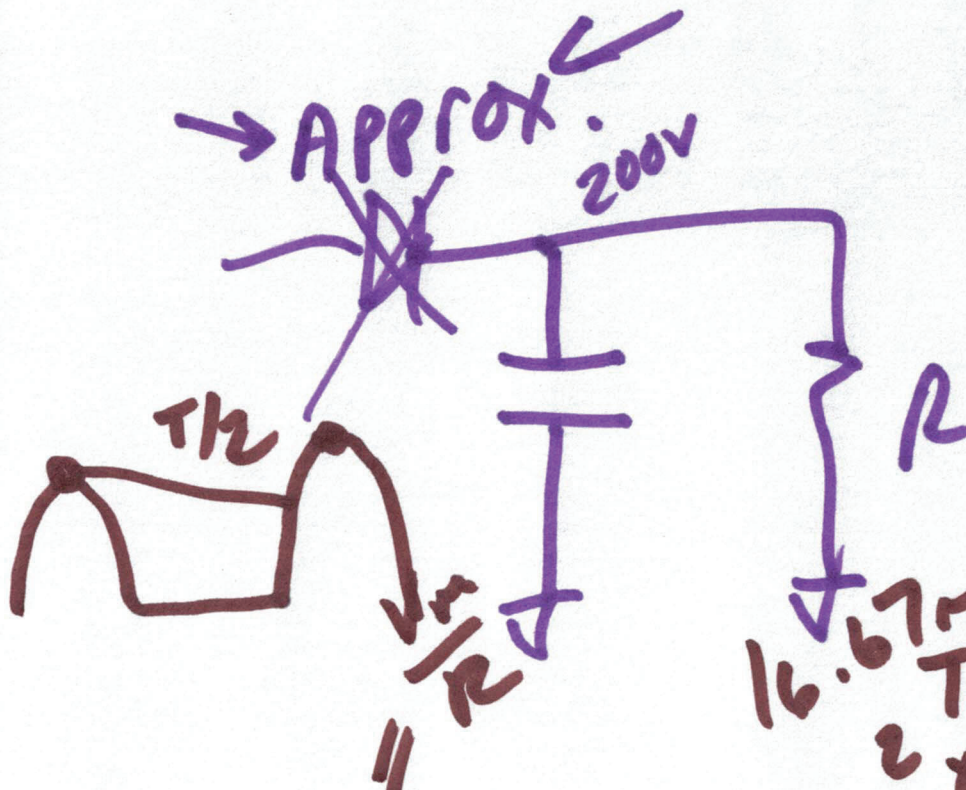

$$I = C \frac{dV}{dt}$$

$$I = C \frac{\Delta V}{\Delta t}$$

$\Delta V = \text{ripple}$

$$T = \Delta t = \frac{T}{2} \approx 8.3 \text{ms}$$

$$\Delta V = \frac{I \cdot \Delta t}{C} = \frac{0.2 \cdot 8.3 \text{ms}}{1 \mu\text{F}} \quad I = \frac{200}{1\text{k}} = 200 \mu\text{A}$$


$$\Delta V = 1.66 \text{V} \times 2$$

3.2V

$$\Delta V = \frac{V_{in}}{fRC} = \frac{I}{f \cdot C} = \frac{I}{C}$$

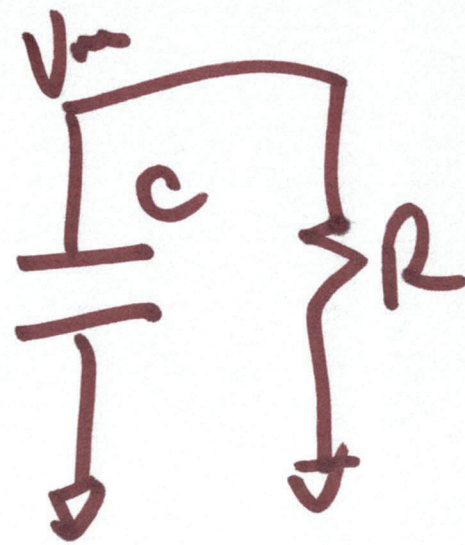2)

$$V_m \cdot e^{-t/RC} = \Delta V = 200 e^{-\frac{16.6 \mu s}{15}}$$



$$\Delta V = 196.7$$


$$\Delta V = 200 - 196.7 = 3.3 \text{ V}$$

3)

INSTANTANEOUS power

$$p(t) = i(t) \cdot v(t)$$
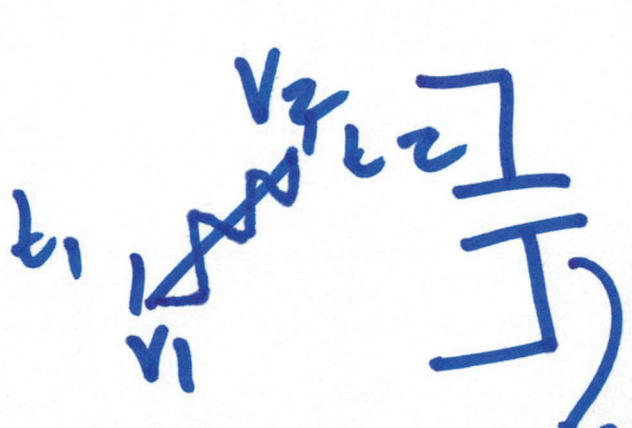
$$\text{Energy} = \int_{t_1}^{t_2} p(t) \cdot dt$$




$$\mathcal{E} = \int_{t_1}^{t_2} \frac{Q}{t_2 - t_1} \cdot (v_2 - v_1) \cdot dt$$

$$Cv = Q$$

$$C(v_2 - v_1) = Q$$

$$\mathcal{E} = \int_{t_1}^{t_2} \frac{C(v_2 - v_1)^2}{t_2 - t_1} dt$$

4)

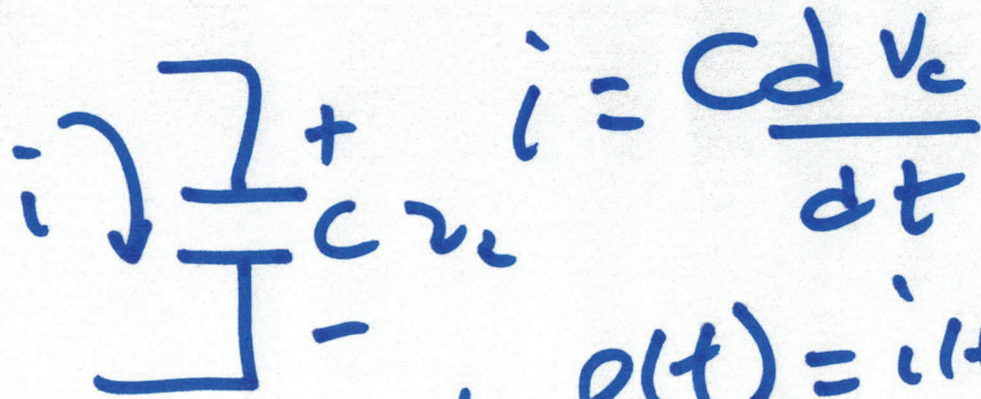

$$i = C \frac{dv_c}{dt}$$

$$P(t) = i(t) \cdot v_c(t)$$

$$\int_{v_1}^{v_2} P(t) dv = C v_c(t) \cdot \frac{dv_c(t)}{dt}$$

$$= C \int_{v_1}^{v_2} v \cdot dt$$

$$\Sigma = \frac{1}{2} C v^2$$

$$\Sigma = \frac{1}{2} C v^2$$

5)

$$\Sigma_f = \int_0^{V_f} \frac{dQ}{C} \cdot dV = \int_0^{V_f} C \cdot V \cdot dV$$

$$\Sigma_f = \frac{1}{2} C V_f^2$$

$$\Sigma_L = \frac{1}{2} L I^2$$

$$i \cdot v = L \frac{di}{dt} \cdot i = \frac{d\Sigma}{dt} = p(t)$$


power from a DC source

$$P_{DC} = \frac{1}{T} \int_{t_0}^{t_0+T} v(t) \cdot i(t) \cdot dt$$

v_{DC}


$$P = \frac{V^2}{R} = I^2 R = VI = \frac{1V^2}{10} = \frac{1}{10}$$

100mW

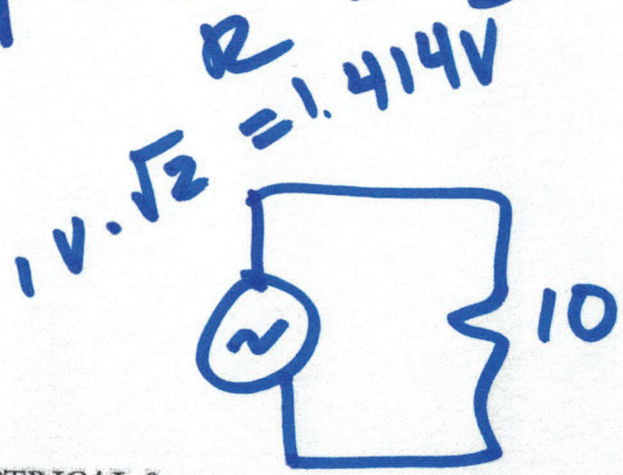

TRUE (Real) Power

$$P = \frac{V^2}{R}$$

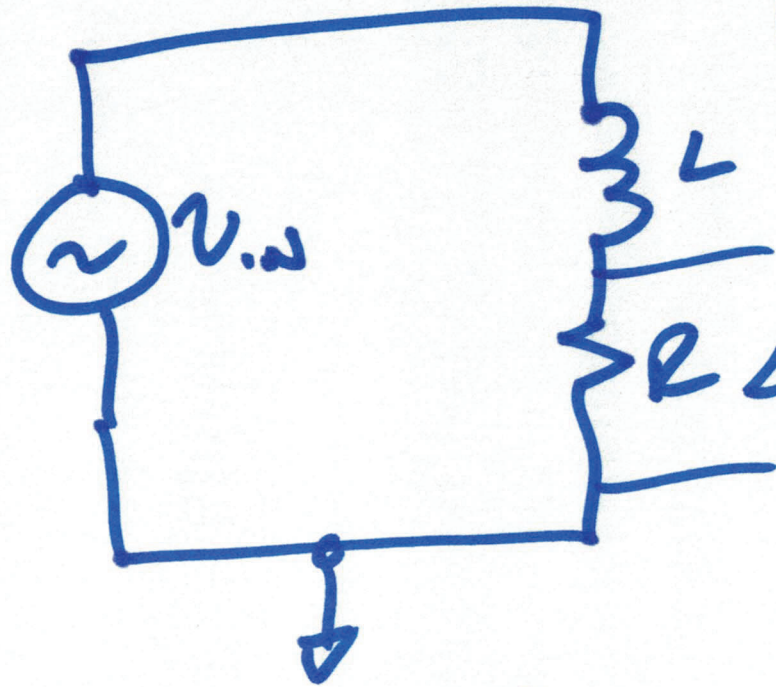


$$P = \frac{v_{i,rms} \cdot R}{R + j\omega L} \cdot \frac{v_{i,rms} \cdot R}{R + j\omega L} \cdot \frac{1}{R}$$

WATTS

$\frac{V^2}{R}$

Reactive Power Q

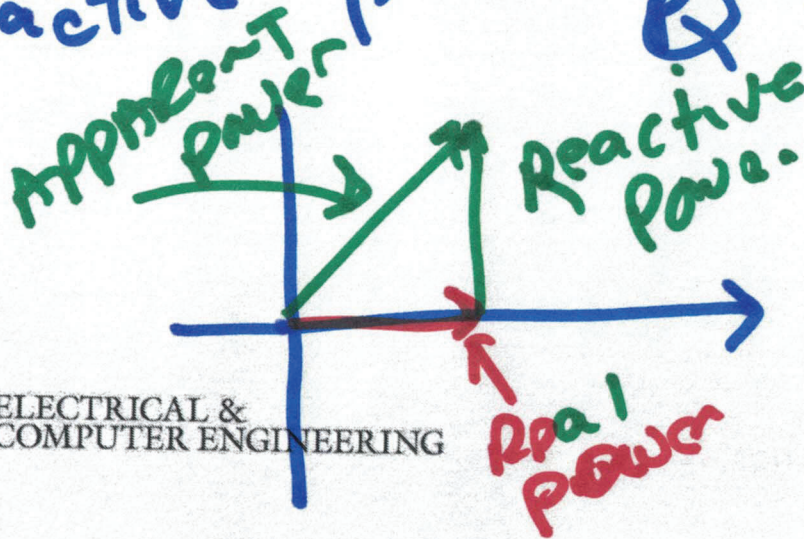

$$Q = \frac{v_{i,rms} \cdot j\omega L}{R + j\omega L} \cdot \frac{v_{i,rms} \cdot j\omega L}{R + j\omega L} \cdot \frac{1}{j\omega L}$$

$\frac{V^2}{X} \leftarrow \text{Reactance}$

VAR

CMOSedu.com

8)

APPARENT POWER

$$S = \frac{v_{in}^2}{j\omega L + R} = P + Q_{VAR}$$


WATTS

$$= \frac{v_{in}^2 R + j\omega L \cdot v_{in}^2}{(j\omega L + R)^2} = P + Q$$


$$= \frac{v_{in}^2 \cdot (j\omega L + R)}{(j\omega L + R)^2}$$

$$(j\omega L + R)^2$$

VA

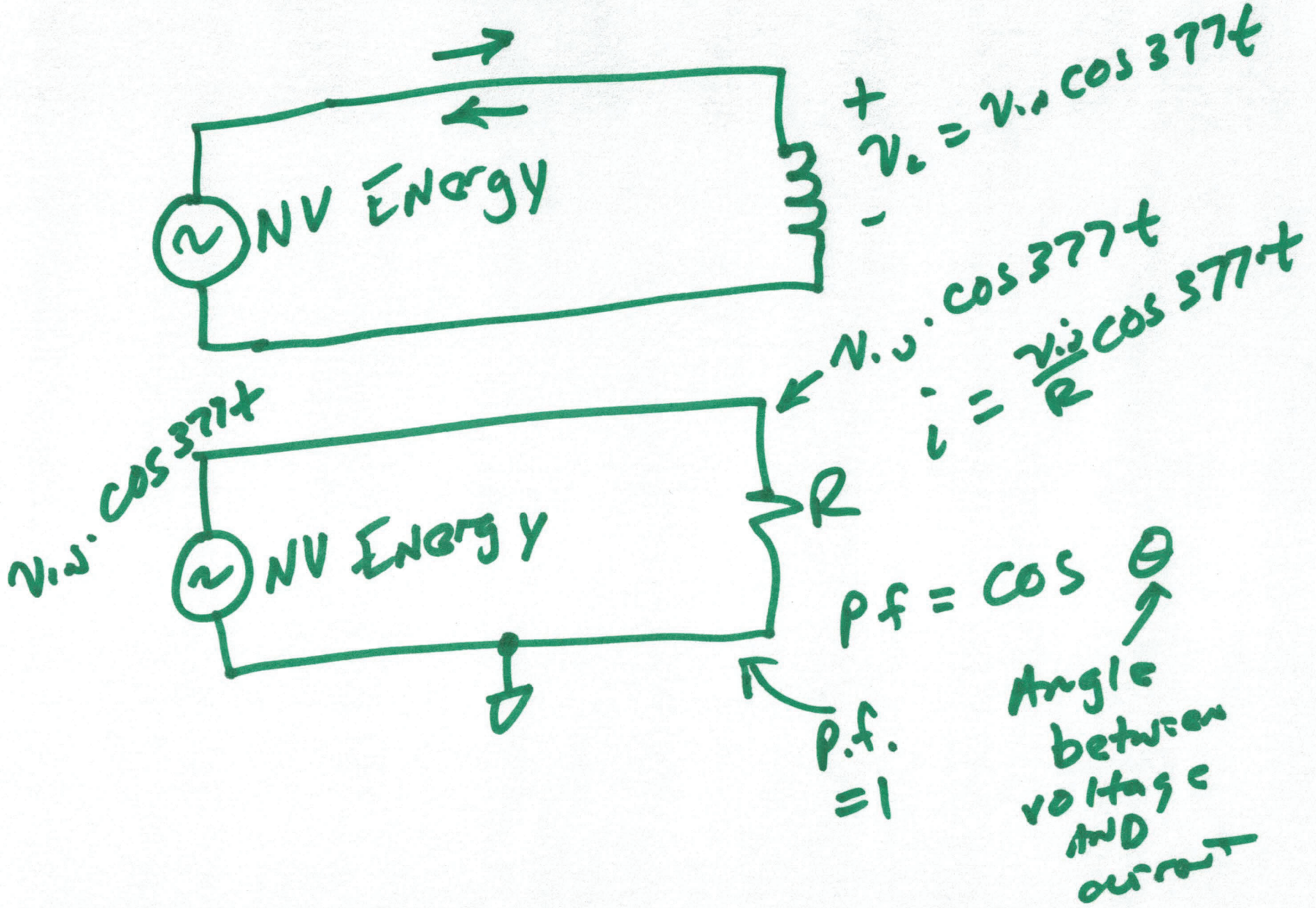

10)

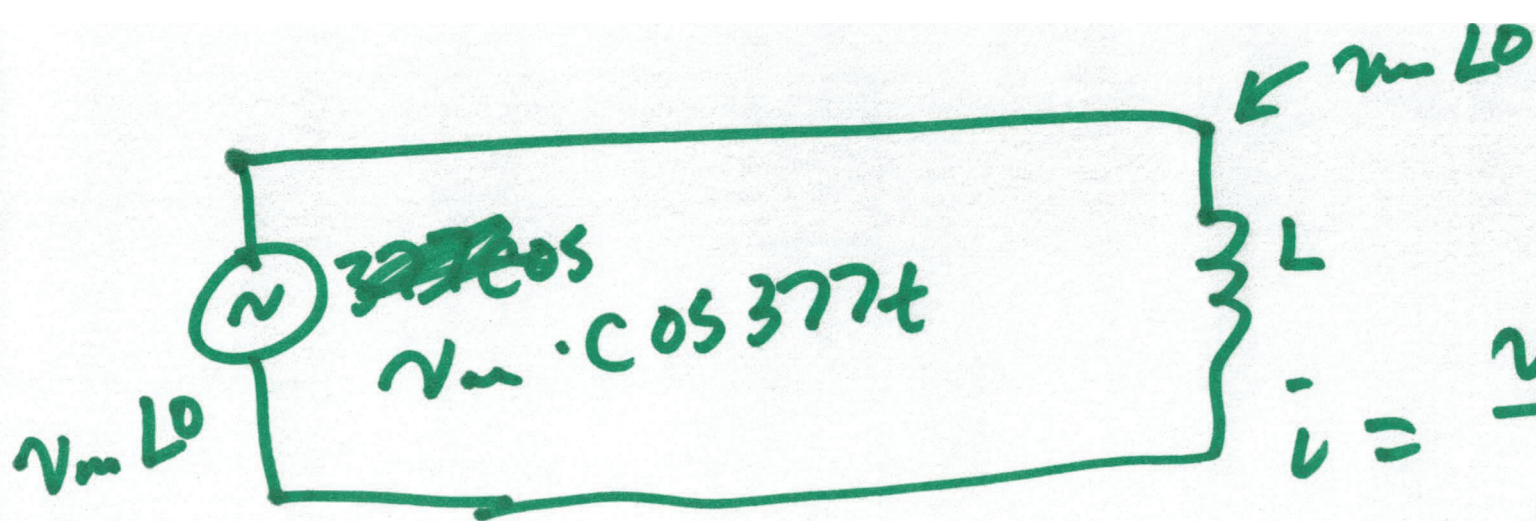

$$i = \frac{v_m L_0}{j\omega L}$$

$$= \frac{v_m L_0}{2\pi f \cdot L \angle 90}$$

$$= \frac{v_m}{2\pi f \cdot L} \angle -90$$

$$\omega = \frac{1}{2\pi \sqrt{L \cdot C}}$$

$$i(t) = \frac{v_m}{2\pi f \cdot L} \cos(377t - 90)$$

$$\text{p.f.} = \cos(\pm 90)$$

$$= 0$$

bad

11)