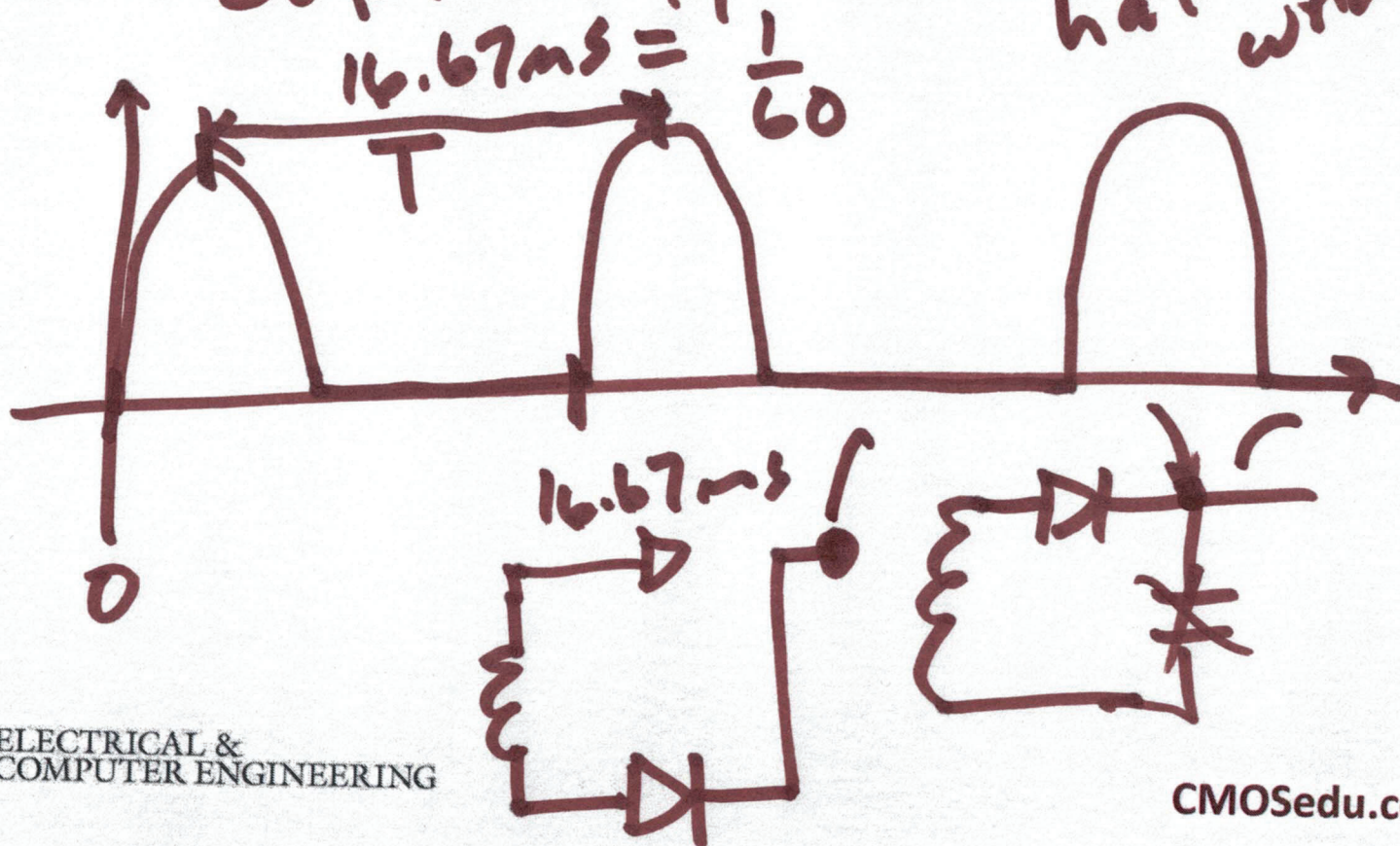


EE 442 / ECG 642



Power Electronics

Lecture 5


Sept 14, 2022
half wave



Full wave

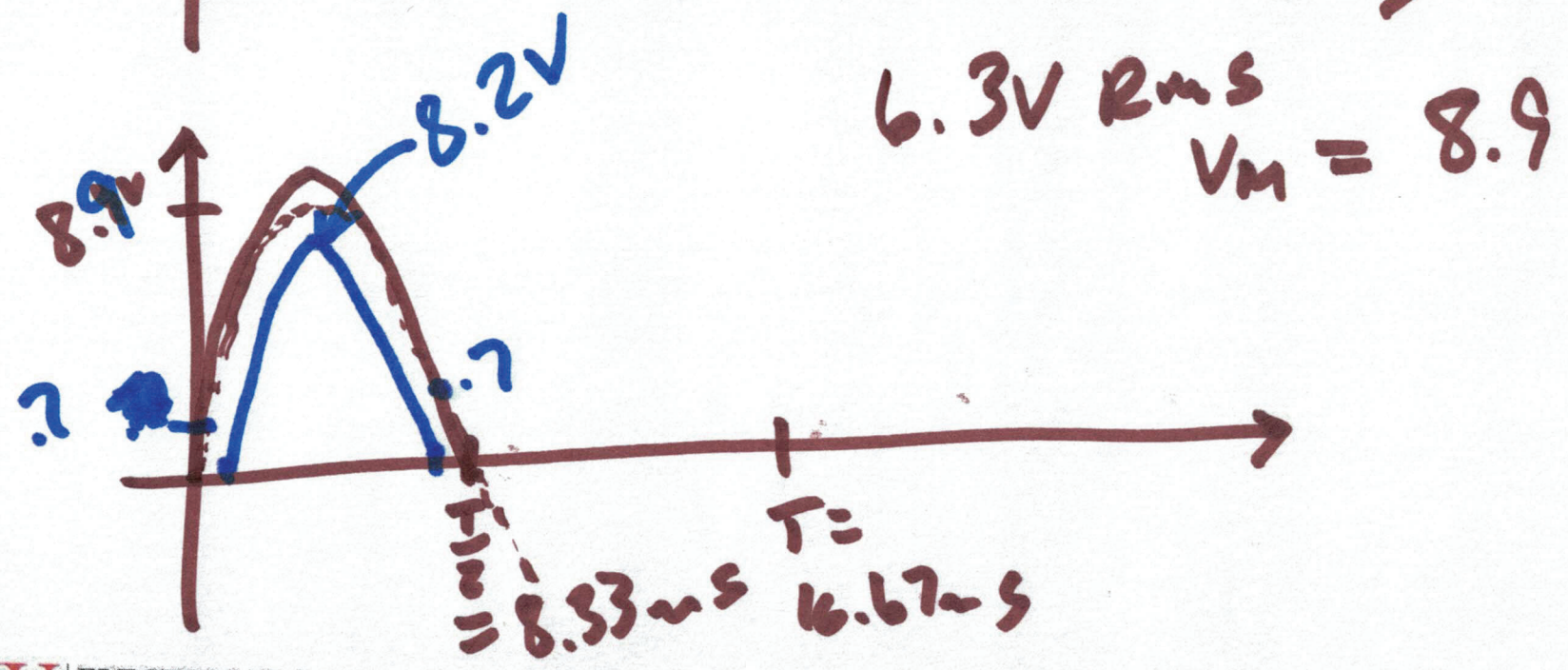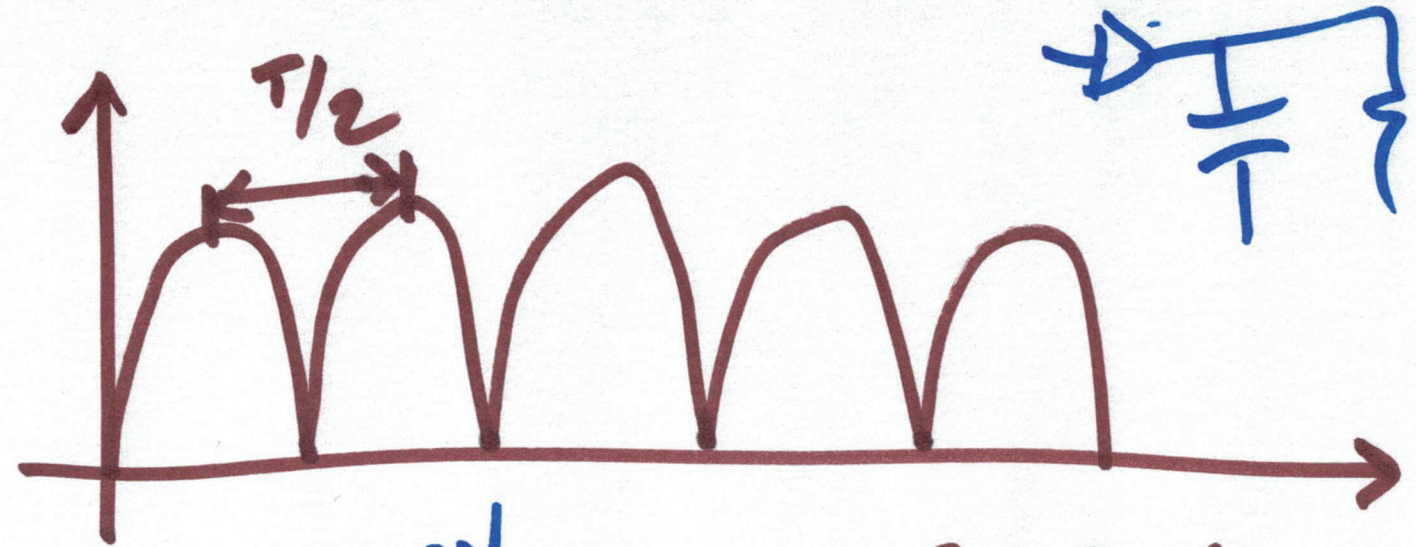

2)


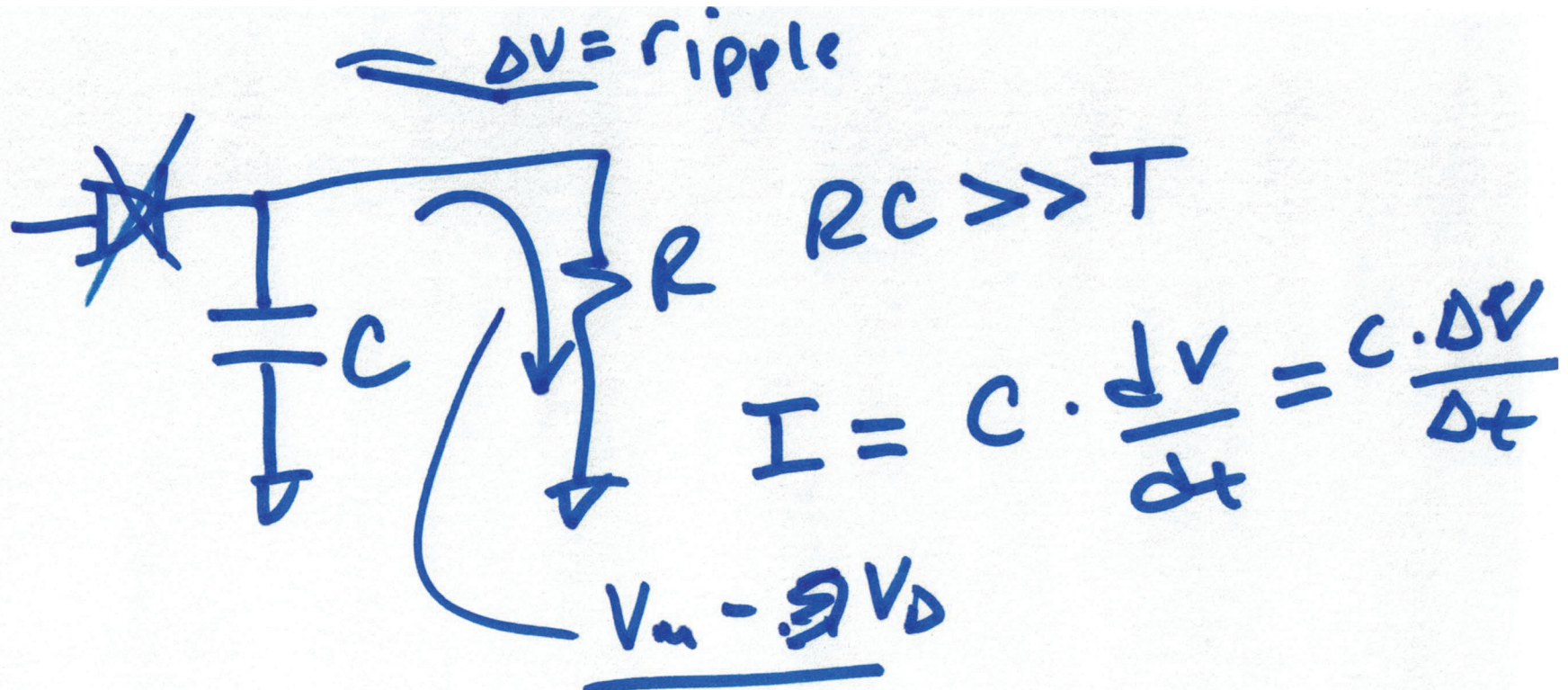


$$\frac{V_m - V_o}{R} = C \cdot \frac{\Delta V_{\text{ripple}}}{T}$$

APPROX

$$\Delta V_{\text{ripple}} = \frac{(V_m - V_o) T}{RC} = \frac{1}{f} \cdot \frac{(V_m - V_o)}{RC}$$


half-wave

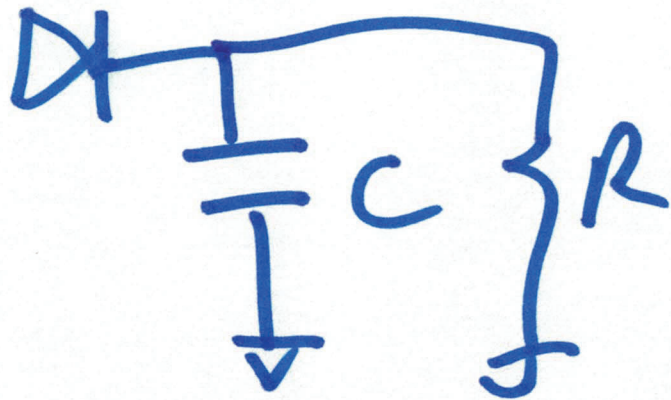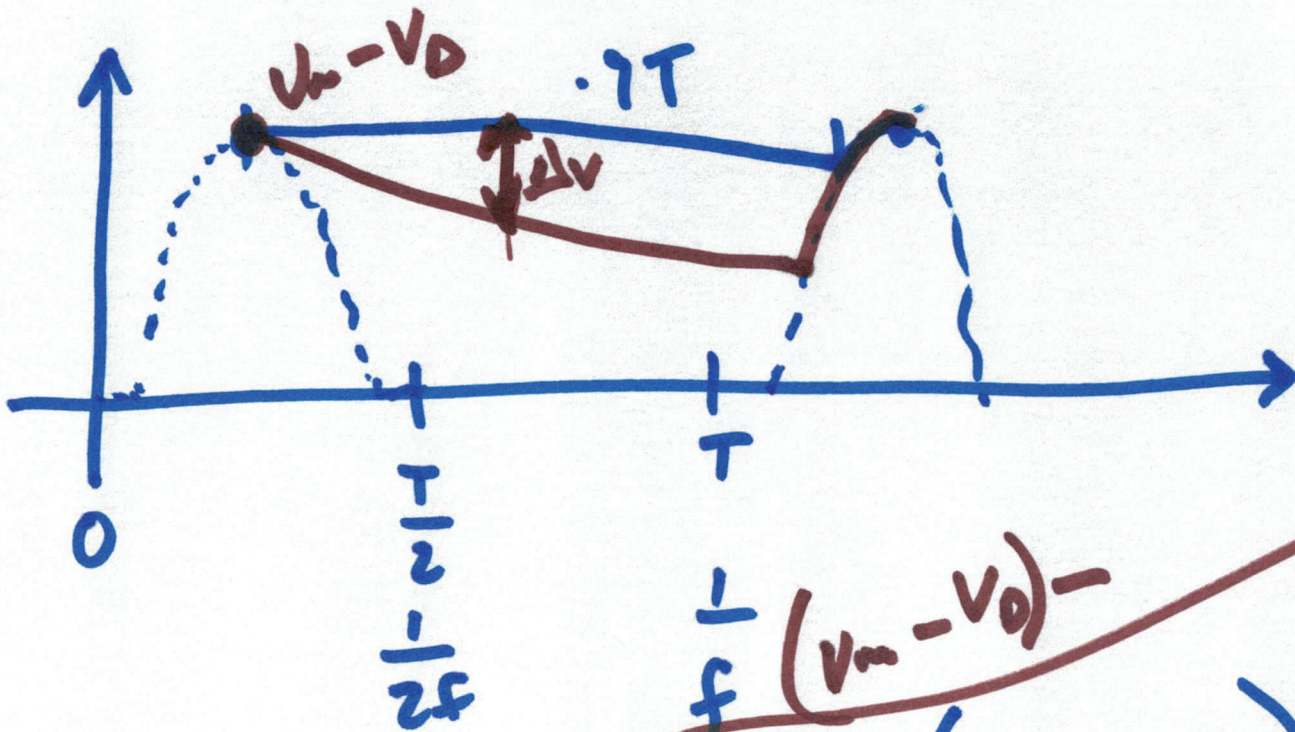


$$V_{OUT} \Delta V = (V_m - V_0) e^{-\frac{0.7T}{RC}}$$


$V_m - V_{OUT}$
 $8 \rightarrow 7.8$
 $8 \rightarrow 7.8$

Switching Power Supply

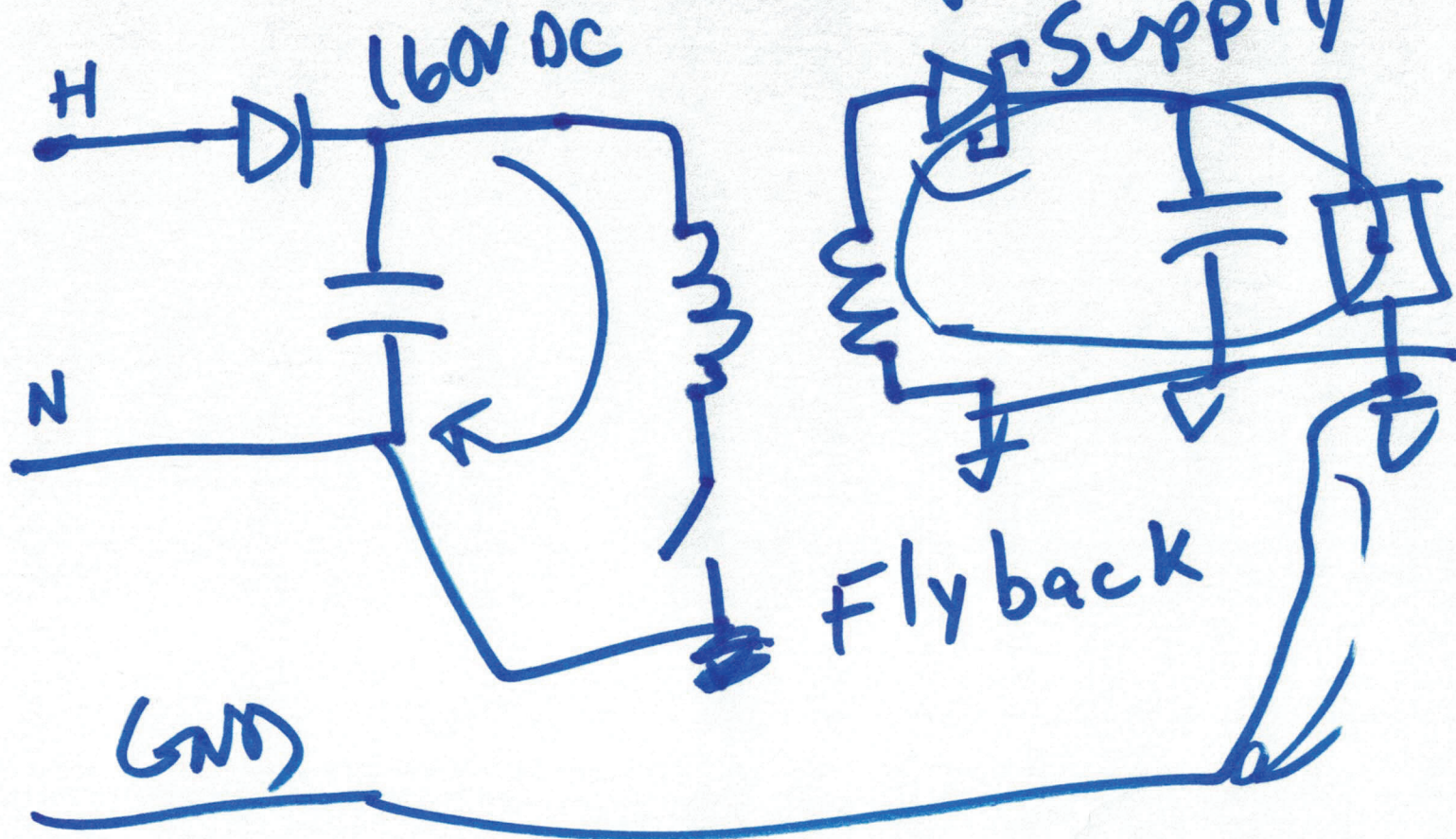

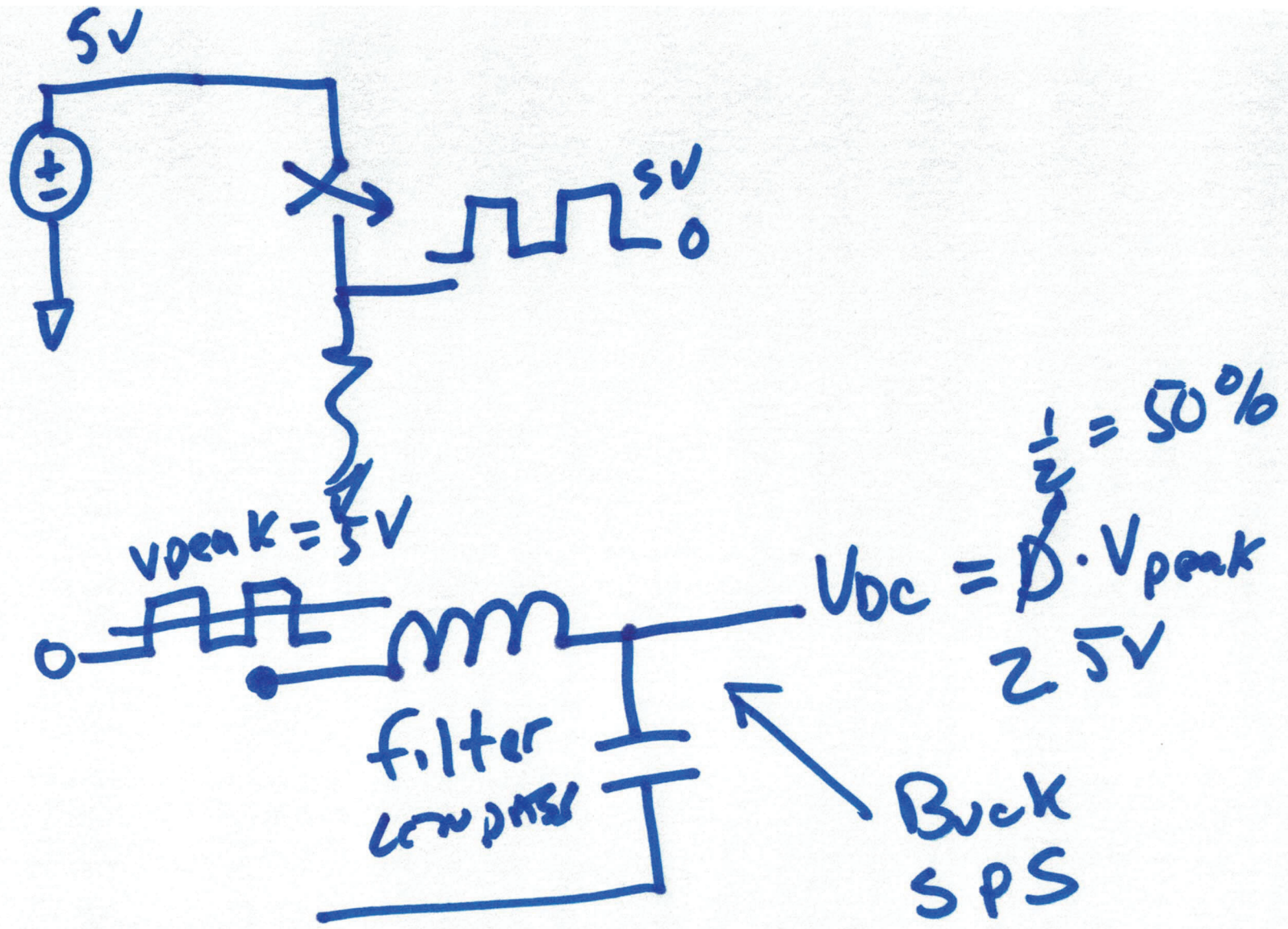

6)

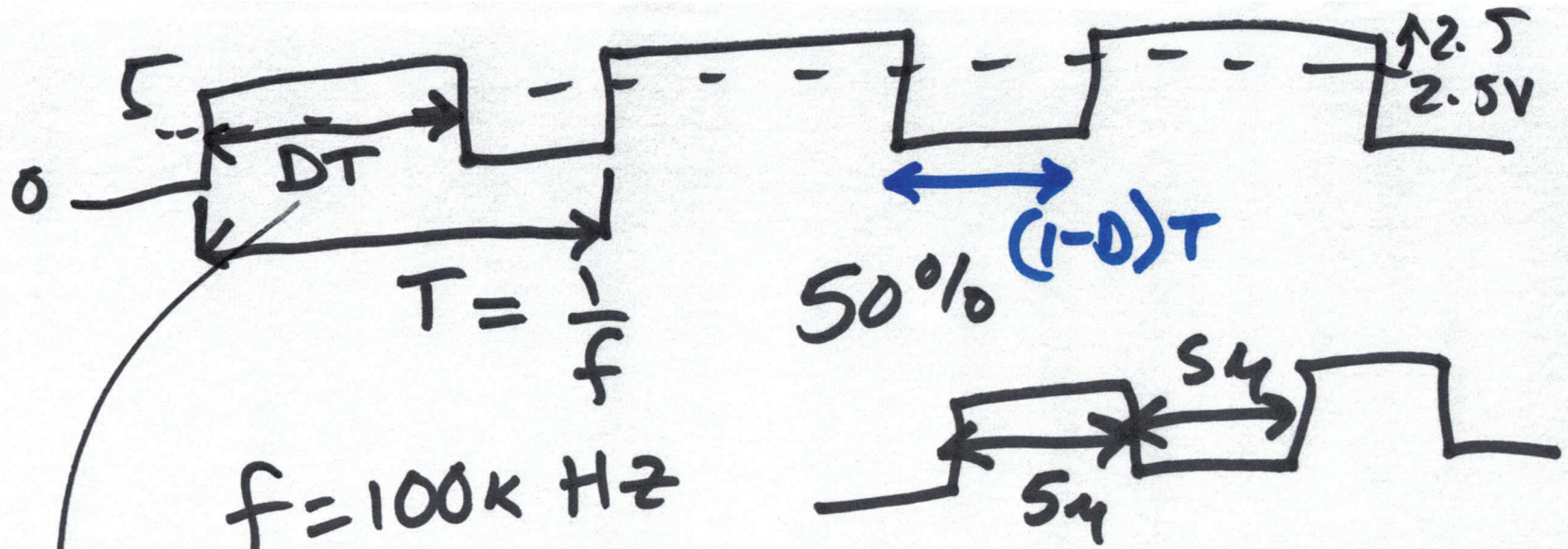



$$f = 100 \text{ kHz}$$

$$T = 10 \mu\text{s}$$

duty cycle

$$V_{\text{peak}} = 5 \text{ V}$$


$$V_{\text{offset}} = 2.5 \text{ V}$$

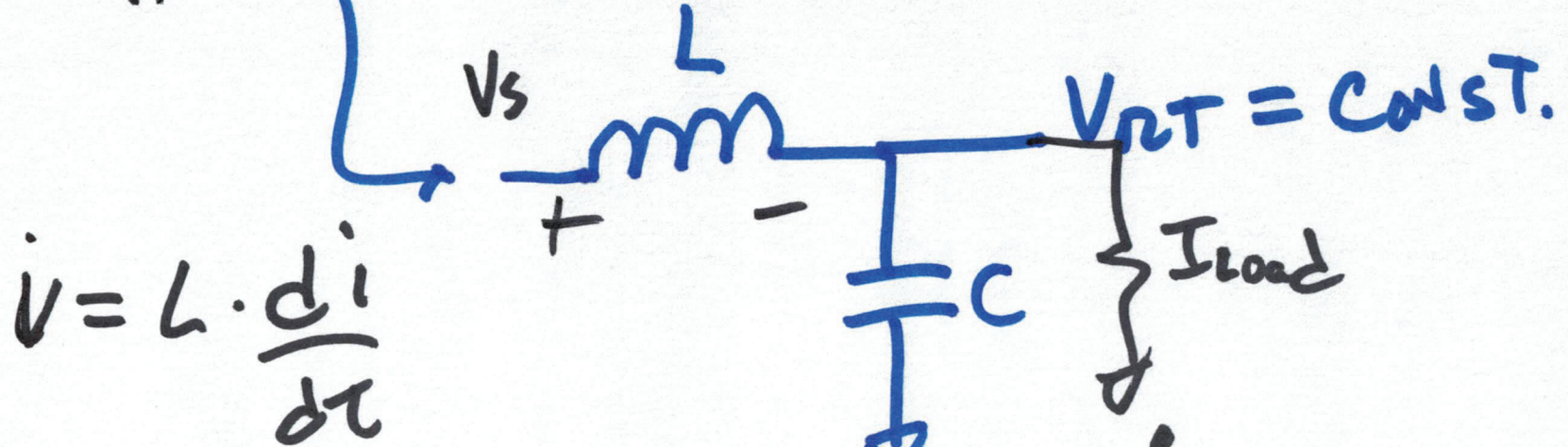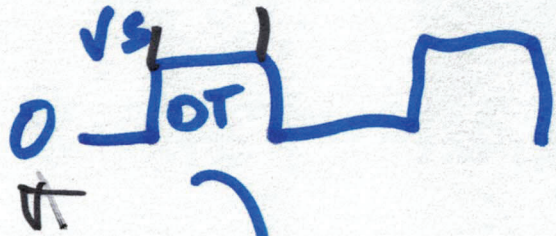

$$v = L \cdot \frac{di}{dt}$$

$$V_s - V_{OUT} = L \cdot \frac{di}{dt} = L \cdot \frac{\Delta i_L}{D \cdot T}$$
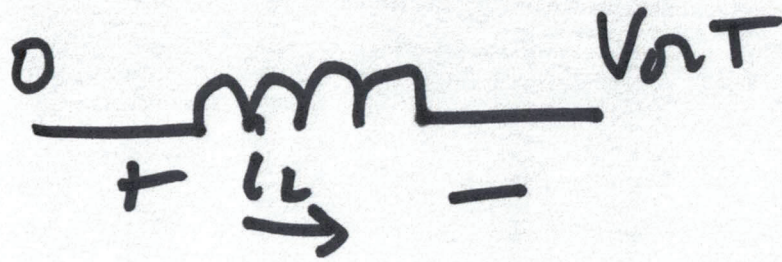
$$\Delta i_{L,up} = \frac{(V_s - V_{OUT}) \cdot D \cdot T}{L}$$



$$L \cdot \frac{\Delta i_{L,down}}{(1-D)T} = 0 - V_{out}$$

$$\frac{(V_s - V_{out})DT}{\downarrow} = |\Delta i_{L,down}| = \left| \frac{(-V_{out})(1-D)T}{\downarrow} \right|$$

$$= \Delta i_{L,up}$$

$$V_{out} = DV_s$$

$$(V_s - V_{out})DT - V_{out}(1-D)T = 0$$

$$V_s \cdot DT - V_{out} = 0$$