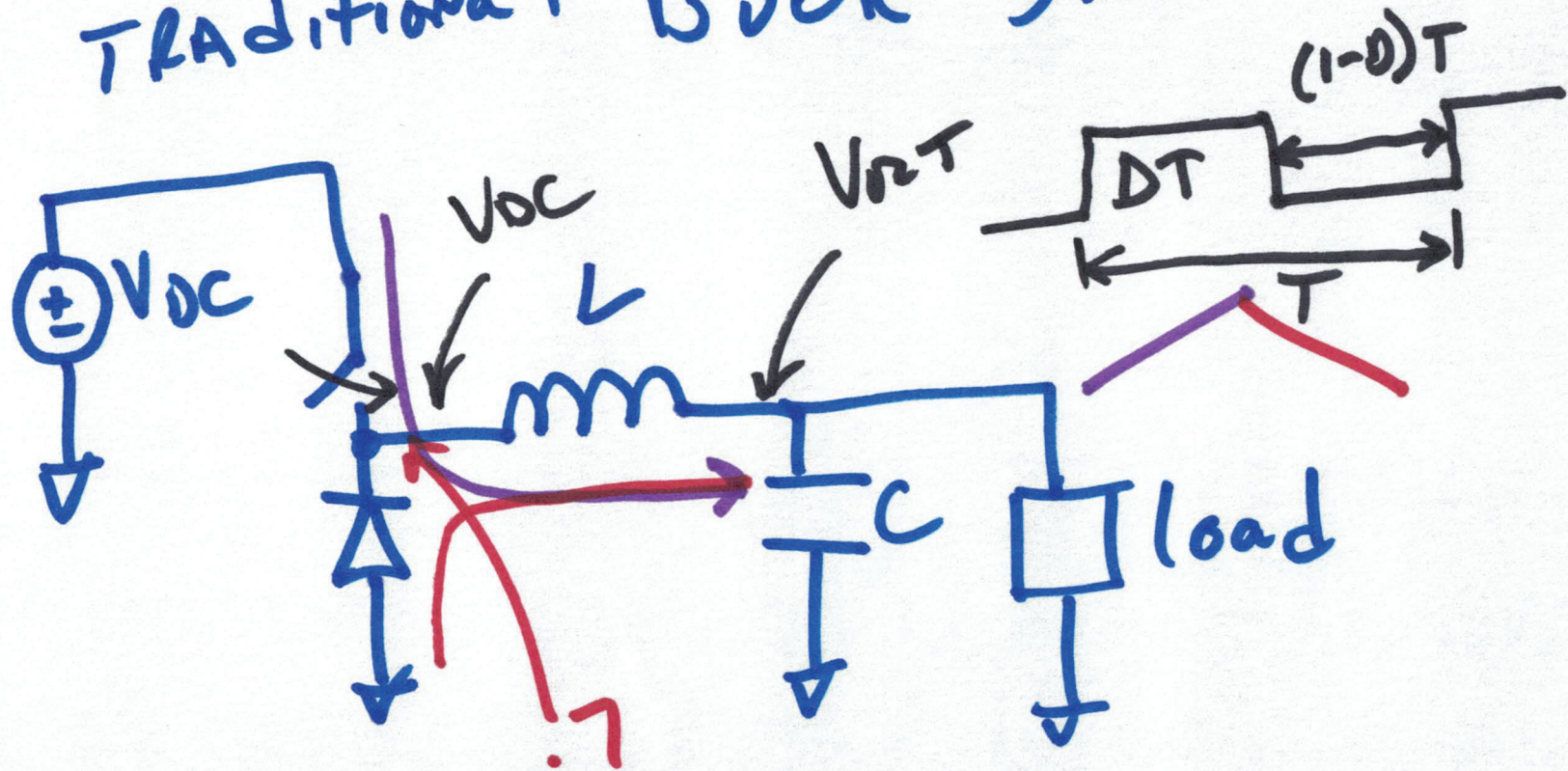



EE 442 / ECE 642 Power Electronics

Sept. 19, 2022

Lecture 6

Traditional Buck SPS




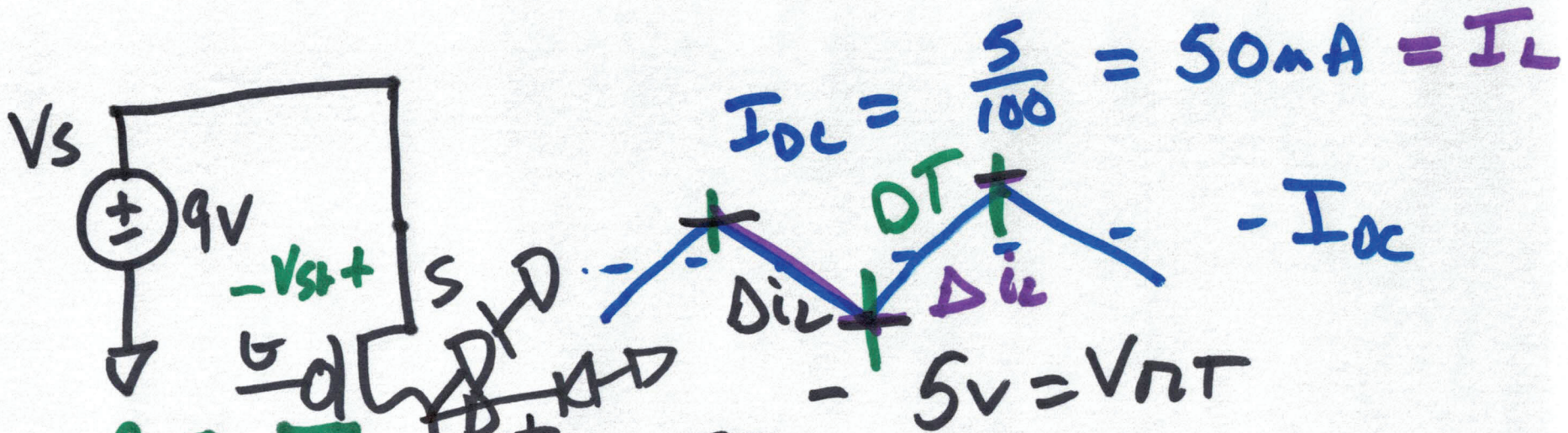

$$V = L \cdot \frac{di}{dt}$$

$$V_s - V_{nT} = L \cdot \frac{\Delta i_L}{D \cdot T}$$
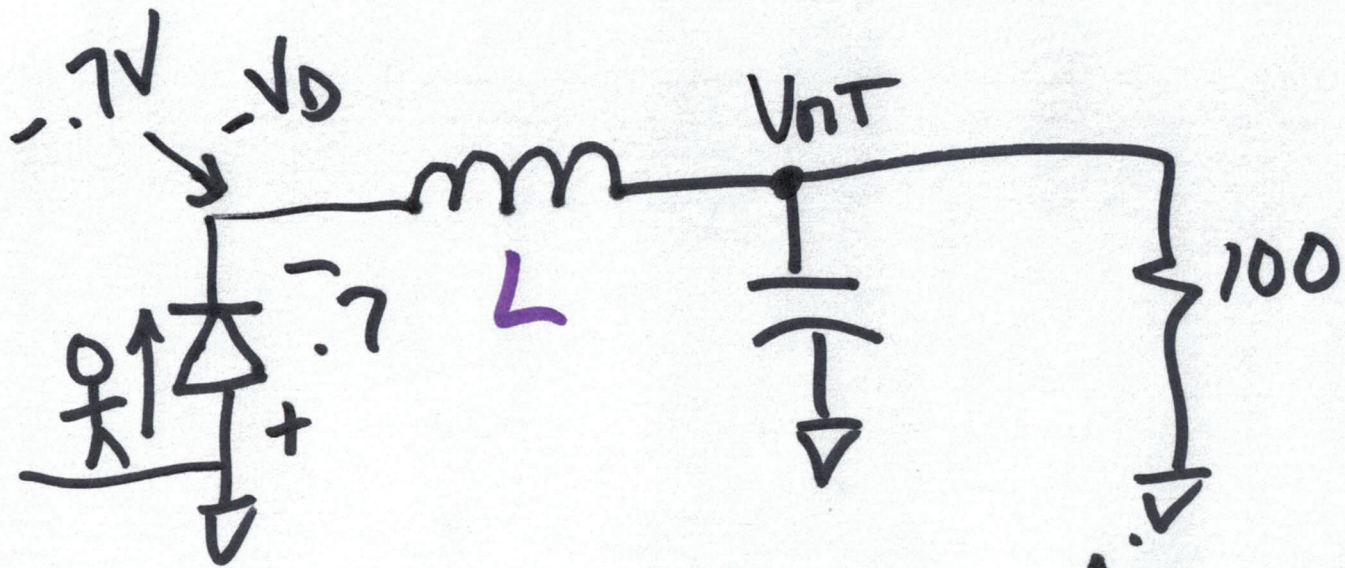
$$\Delta i_L = \frac{D \cdot T}{L} (V_s - V_{nT})$$



$$-V_D - V_{OT} = L \cdot \frac{\Delta i_L}{(1-D)T}$$

$$\Delta i_L = \frac{(-V_D - V_{OT})(1-D)T}{L}$$

3)

$$\frac{D \cdot T}{K} (V_s - V_{NT}) = \left| \frac{(-V_D - V_{NT}) (1-D)T}{K} \right|$$

$$DV_s - \cancel{DV_{NT}} = +V_D + V_{NT} - DV_D - \cancel{DV_{NT}}$$

if $V_D = 0$

$V_{NT} = DV_s$

$$V_{NT} = DV_s - V_D + DV_D$$

$$V_{NT} = DV_s - (1-D)V_D$$

~~$$5 = 0.9 - 0.3 \cdot 6$$~~

$D = 0.58$

$$5 + 0.18 = \frac{5.18}{0.9}$$

4)

$$5 = D \cdot 9 - (1 - D) \cdot 7$$

$$5 = 9D - .7 + .7D$$

$$5.7 = 9.7D$$

$$D = .59$$

$$D_i = 5 \mu A$$

$$5 \mu A = \frac{.59 \cdot 10 \mu (9 - 5)}{L}$$

$$I_{AVG} = 50 \mu A = \frac{5}{100}$$

$$L = 4.72 \mu H$$


$$\Delta V = 25 \text{ mV}$$

$$I = 50 \text{ nA}$$



$$I = C \frac{dV}{dt}$$

$$50 \text{ nA} = C \cdot \frac{\Delta V}{\Delta t}$$
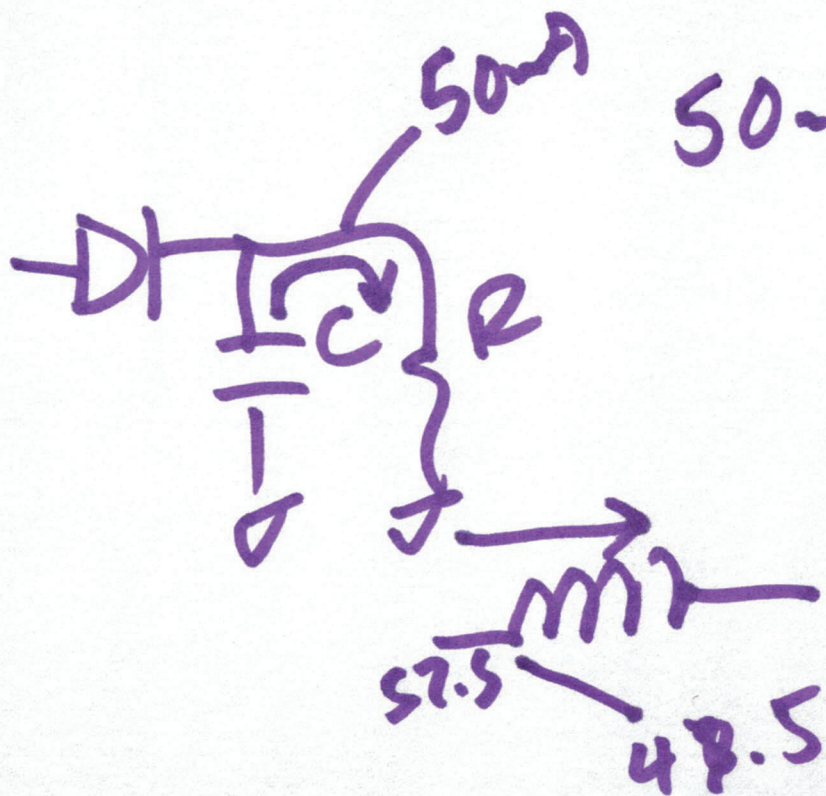
$$C = \frac{50 \text{ nA} \cdot 10 \text{ ns}}{25 \text{ mV}}$$
$$= 20 \text{ fF}$$



V_s SYNCHRONOUS Buck

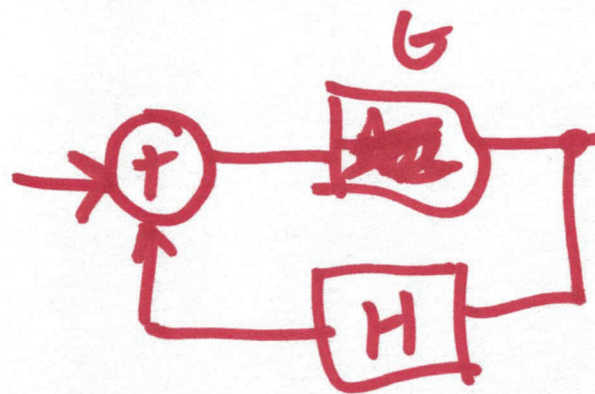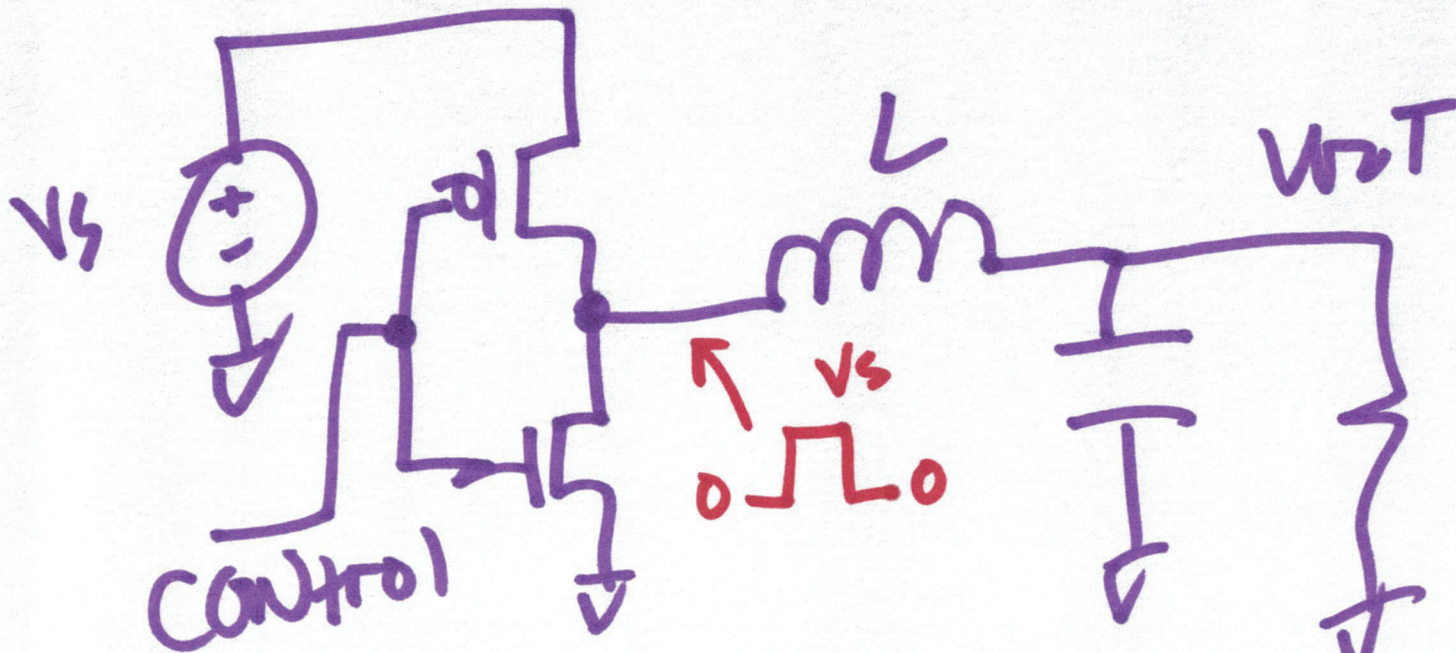


$$D \cdot V_s = V_{OUT}$$

$$D \cdot 9 = 5$$

$$\frac{OUT}{IN} = \frac{G}{1+GH} D = \frac{5}{9} = .56$$
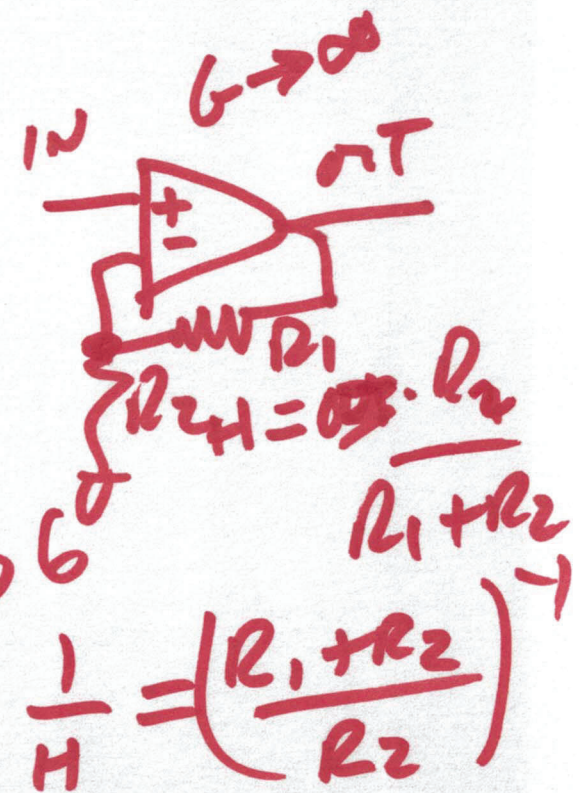
$$= \frac{1}{\frac{1}{G} + H} = \frac{1}{H} \quad (G \rightarrow \infty)$$



$$\frac{1}{H} = \left(\frac{R_1 + R_2}{R_2} \right)^{-1}$$