

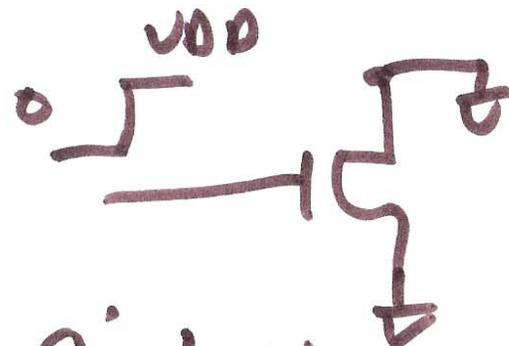


Lecture 20 April 15, 2011

CURRENT Starved oscillator

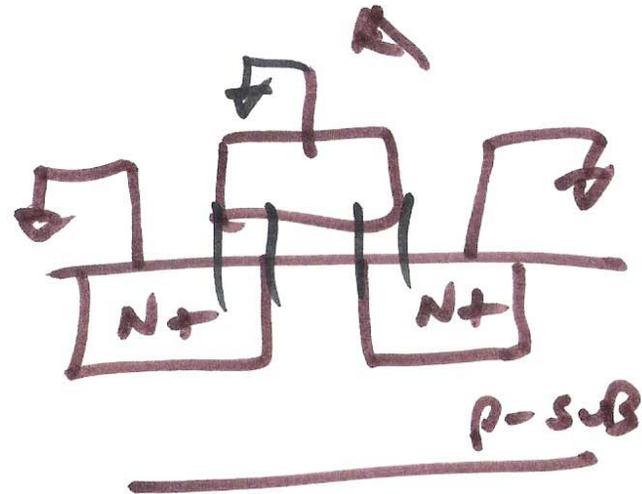

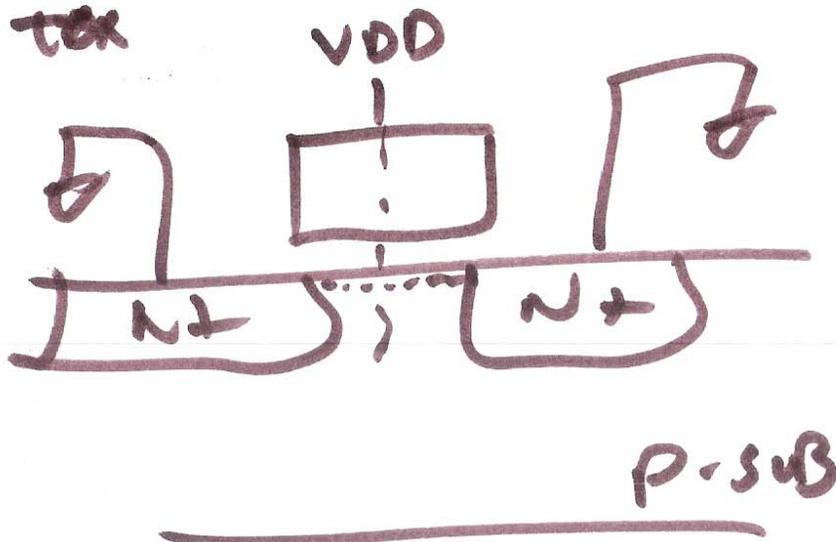
$$\frac{t_{ol}}{T} \cdot L \cdot W = C_{ox} \cdot L \cdot W$$




$$C_{in} = C_{GDO} \cdot W + C_{GSO} \cdot W$$

$$C_{in} = \frac{1}{2} C_{ox}' \cdot L \cdot W + \frac{1}{2} C_{ox}' \cdot L \cdot W$$

$$= C_{ox}' \cdot L \cdot W = C_{ox}$$

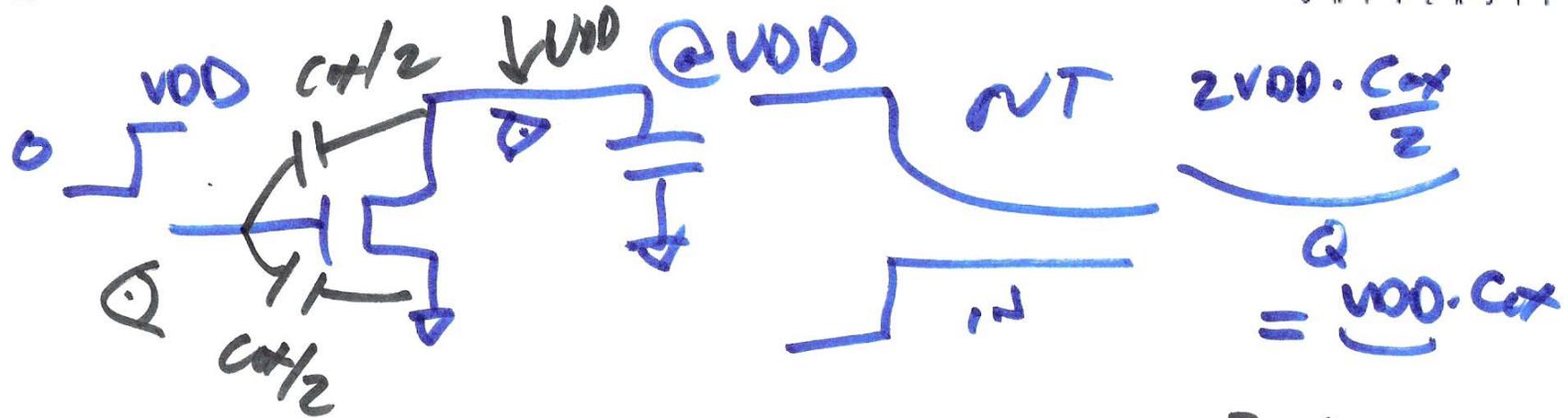

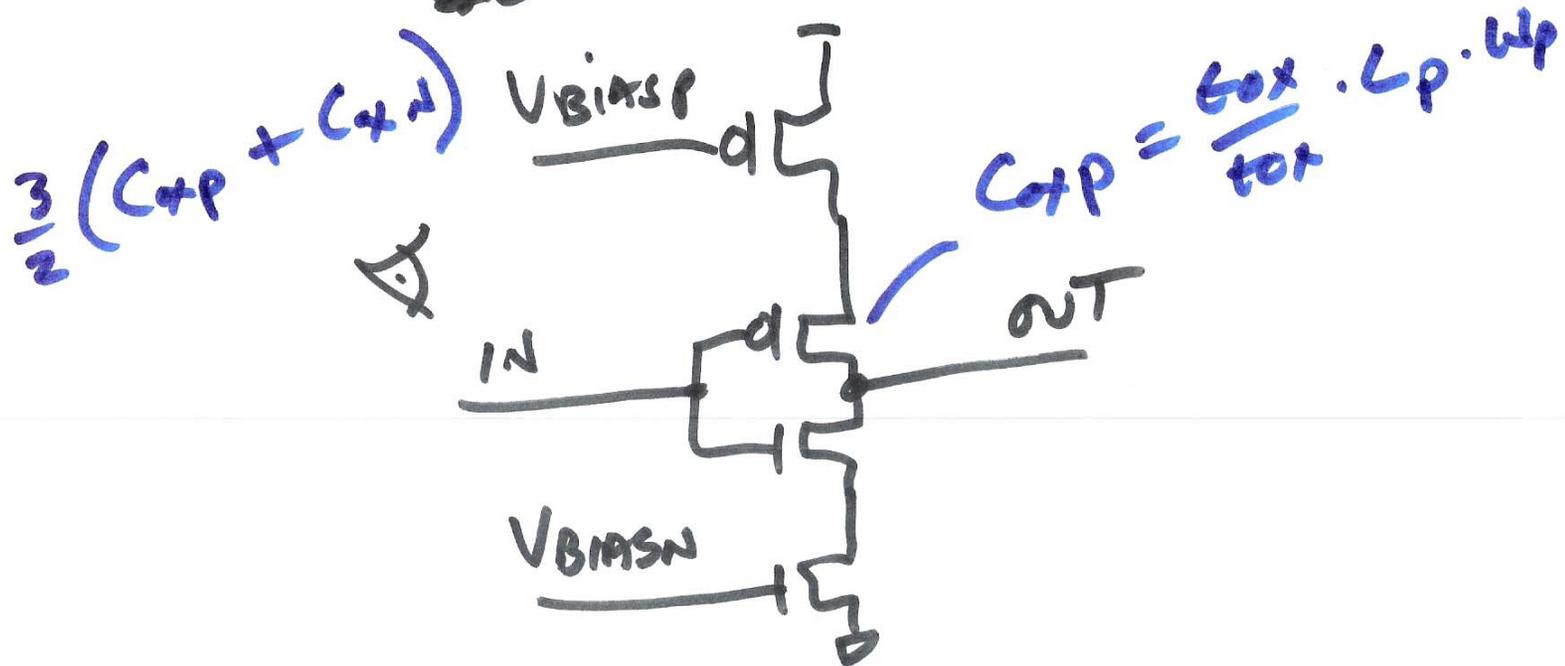
$$\frac{3}{2} C_{ox} = \frac{3}{2} C_{ox}' \cdot L \cdot W = \frac{3}{2} \frac{\epsilon_{ox}}{t_{ox}} \cdot L \cdot W$$



$$C_{oxP} = \frac{\epsilon_{ox}}{t_{ox}} \cdot L_p \cdot W_p$$

Handwritten notes on the right margin: IN , $+ \frac{3}{2}$, and $+ C$.

2)

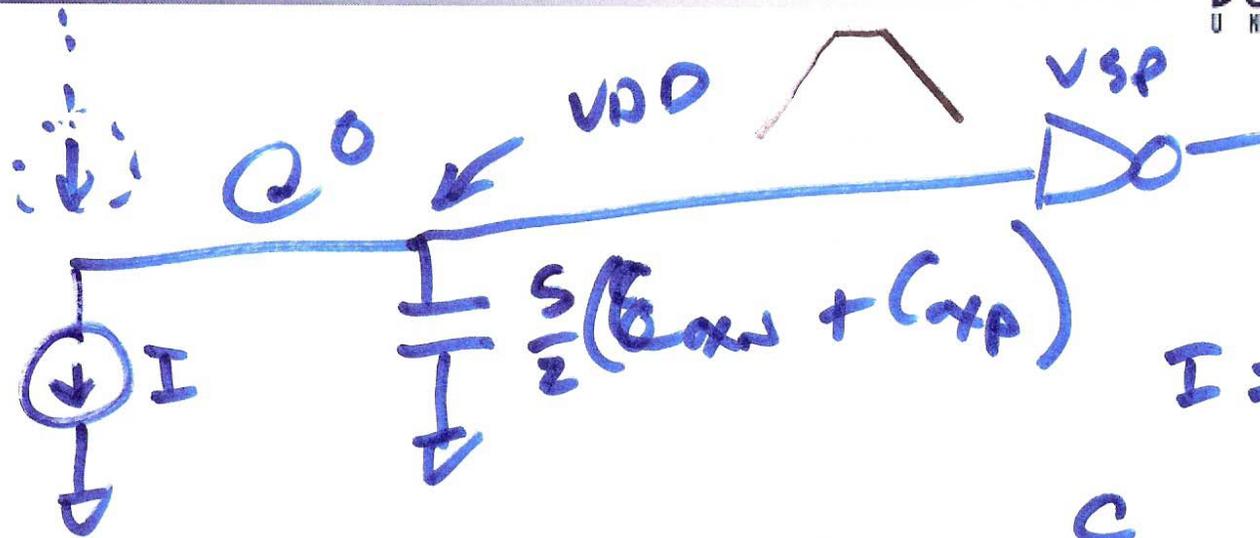

$$I = C \frac{dv}{dt}$$

$$t_{dis} = \frac{C}{I} \cdot (VDD - VSP)$$

$$t_{charge} = \frac{C}{I} \cdot VSP$$

$$f_{osc} = \frac{1}{N(t_{charge} + t_{discharge})}$$

$$= \frac{1}{11 \cdot \left(\frac{4.6f}{254} \cdot \frac{14}{2} \right)}$$

$$= 16 \text{ kHz}$$

$$\text{delay of a stage} = \frac{C}{I} \cdot VDD$$


$$2.5 \cdot (1.85 \text{ ns}) = 4.6 \text{ ns}$$

4)

$$C_{TOT} = 1.85 \text{ fF} \cdot 2.5 = 4.6 \text{ fF}$$


$$f_{osc} = \frac{5 \mu}{11 \cdot 4.6 \text{ fF} \cdot 1 \text{ V}} = 97.75 \text{ MHz}$$
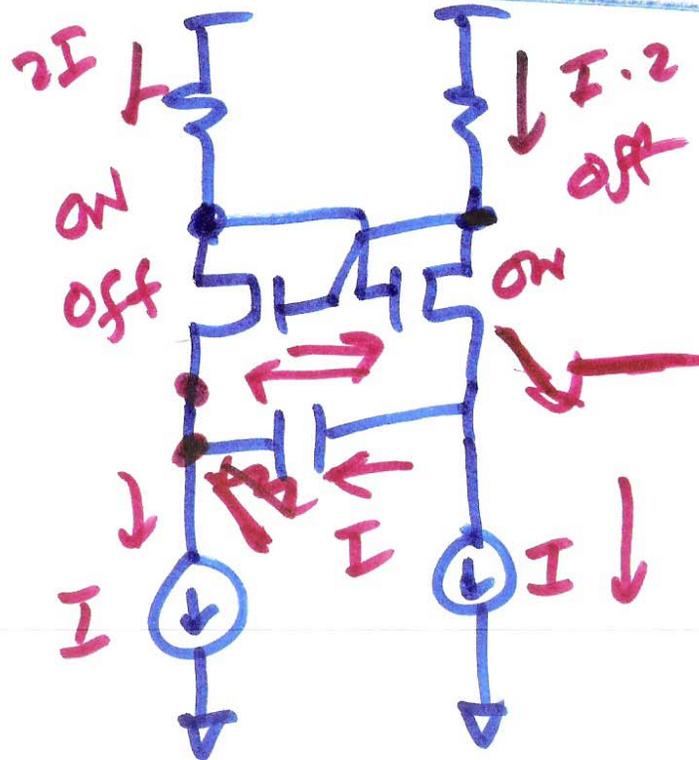
$$\underline{\underline{10.23 \text{ ns}}}$$




5)


XOR PD Loop Filter

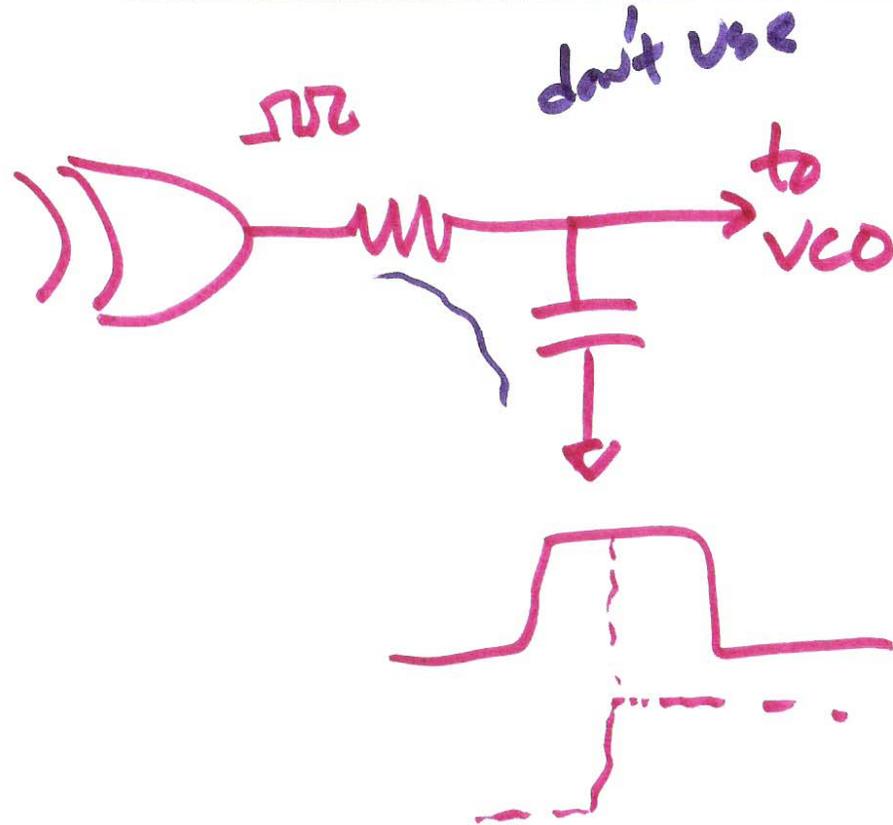


569

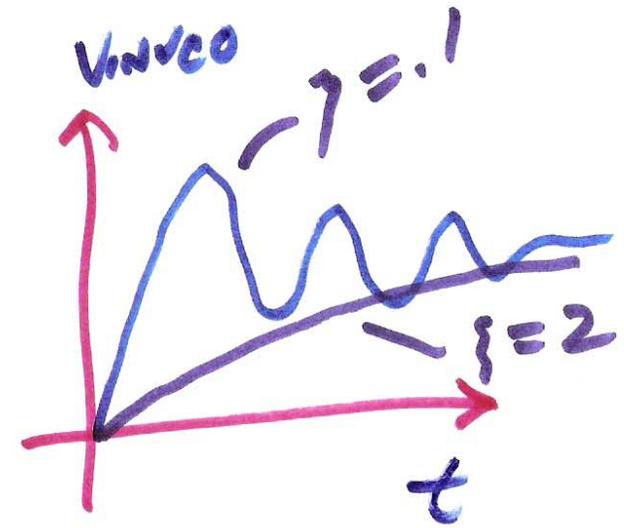
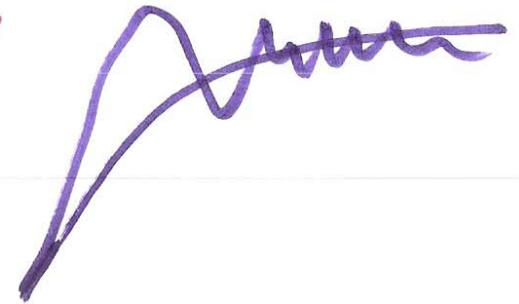
$$\rho = \frac{1}{2} \sqrt{\frac{N}{K_{PD} \cdot K_{VCO} \cdot RC}}$$



6)

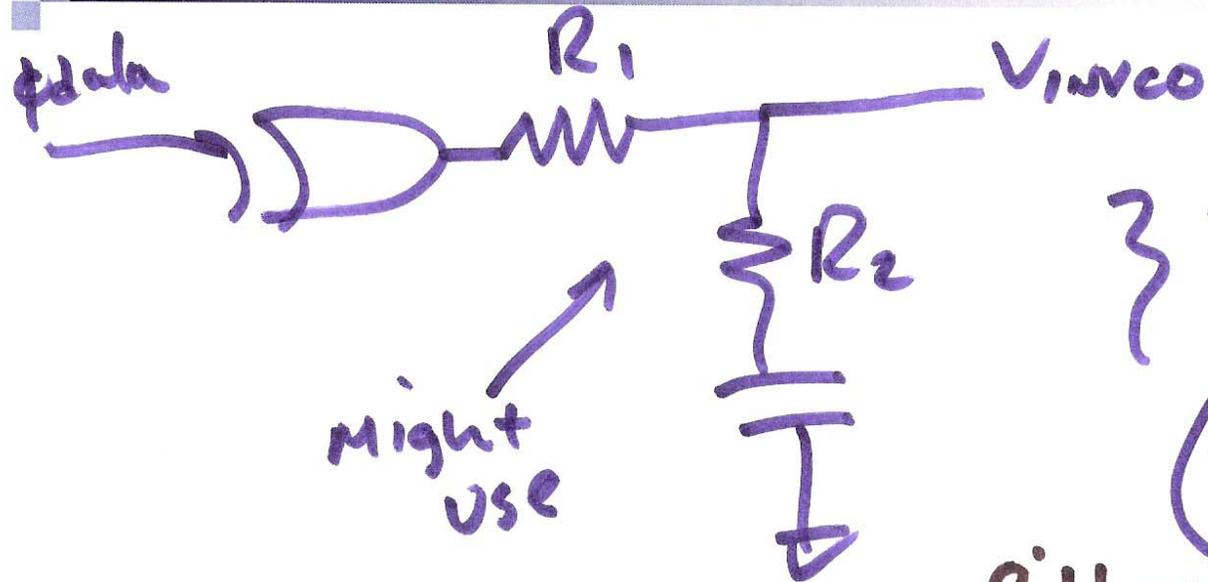


$$\omega_n = \frac{1}{2} \sqrt{\frac{K_p K_{vco}}{N(R_1 + R_2)C}}$$

Active PI loop filter

$$K_F = \frac{R_2 + \frac{1}{sC}}{R_1}$$

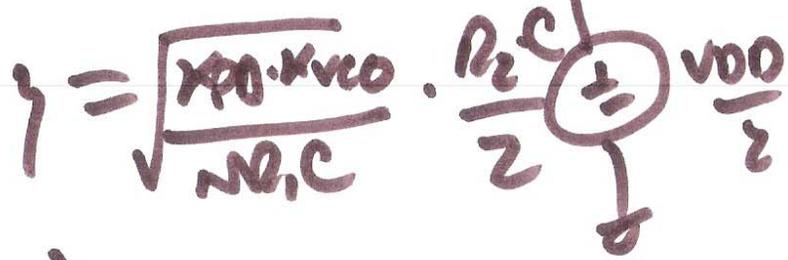
$$\omega_n = \sqrt{\frac{K_p K_{vco}}{N R_1 C}}$$



$\frac{R_2}{R_1} + \frac{1}{sRC}$
 proportional integral


→

tri-state

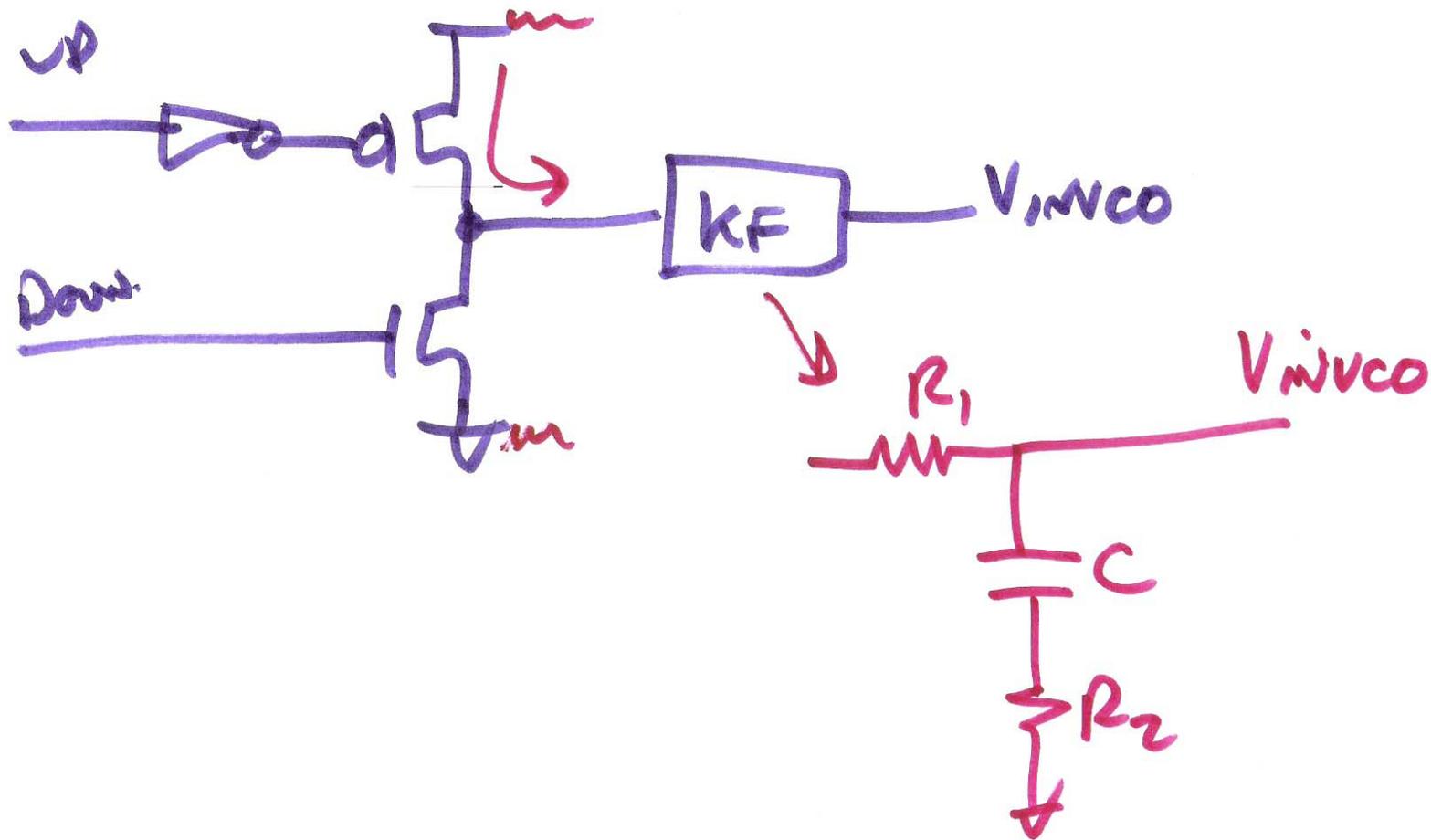

8)

Charge pump

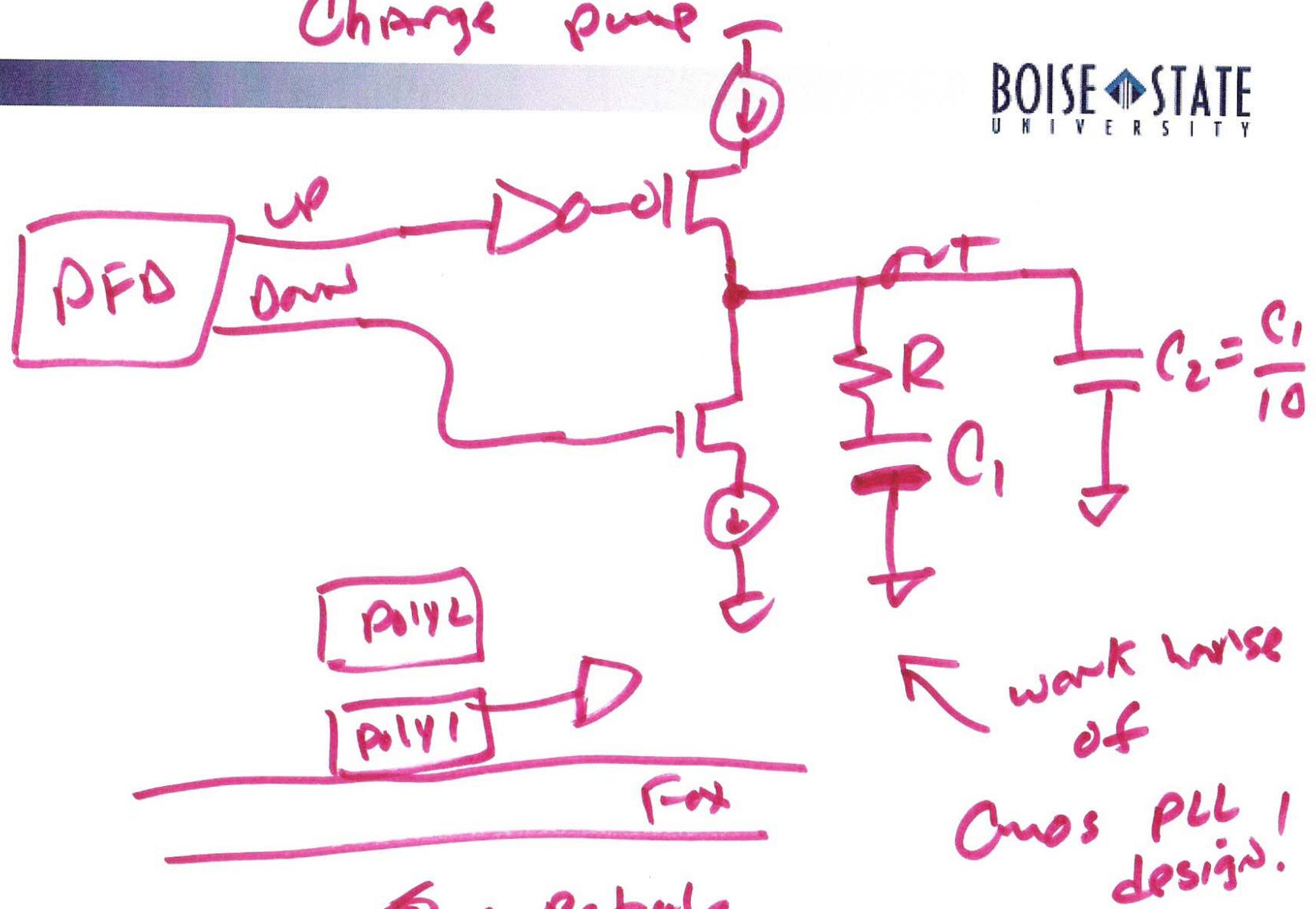

↳ Substrate

$$\omega_{LN} = \sqrt{\frac{K_{PDI} \cdot K_{VCO}}{N C_1}}$$

$$\} = \frac{\omega_{LN}}{2} \cdot RC_1$$

9)