 


2)



2Gb: x4, x8, x16 DDR2 SDRAM
Functional Block Diagrams

Figure 4: Functional Block Diagram – 256 Meg x 8



1. How many bits does this DRAM store?

2Gb

2. How many address pins are needed for the row address?

$32K = 2^{15}$

15 pins

3. If this is a x8 part how many bits come out of the part with the rising edge of DQS? the falling edge of DQS?

8 bits in either case


4. If there are 8k column lines what is the page size (how many 8-bit words can be addressed with column addresses for a single row address)?

page size = 1K

5. If the array size is 512 rows by 512 columns how many arrays are "opened" (a row line goes high) when a row address is applied to the part?

512 bits


16 ARRAYS

 


- Good sense - Amp
- 1) Kickback noise is small
 - 2) MEMORY all nodes actively driven
 - 3) Don't WANT current flow from VDD → gnd. reduce current!

3)

Making a better sense Amp

 

4)

 

5)

