


Lecture 10

Sept. 17,


$$V_{\text{off}} = 0. \text{VDD}$$

3

= 6.5 2010

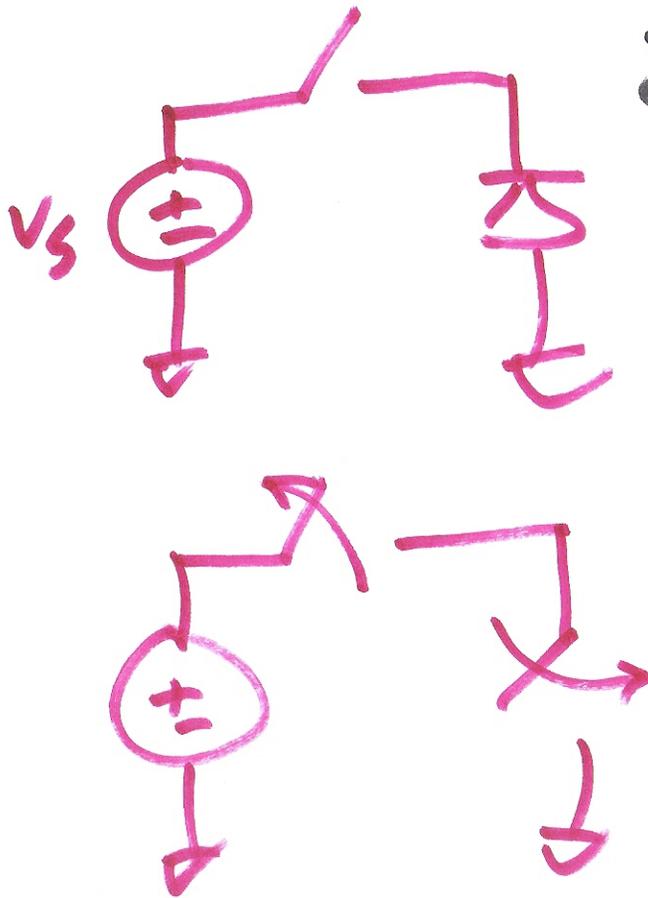

VDD



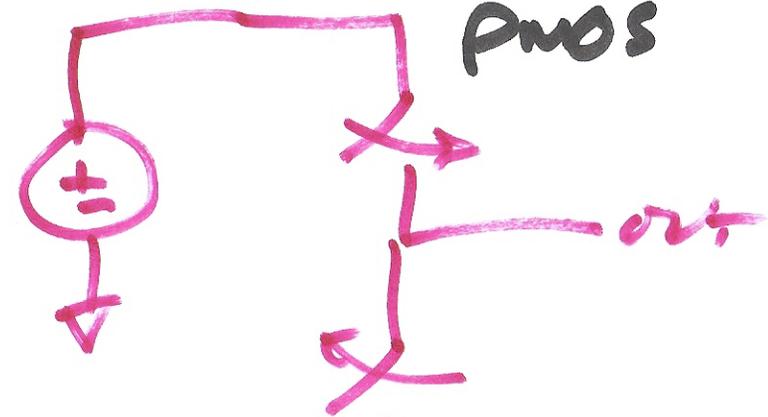


3V @ 1mA

f = 10 MHz

11


100W

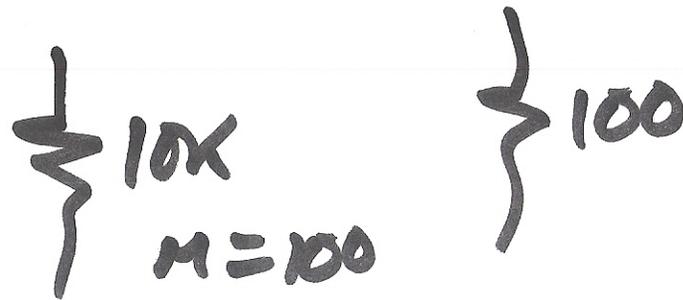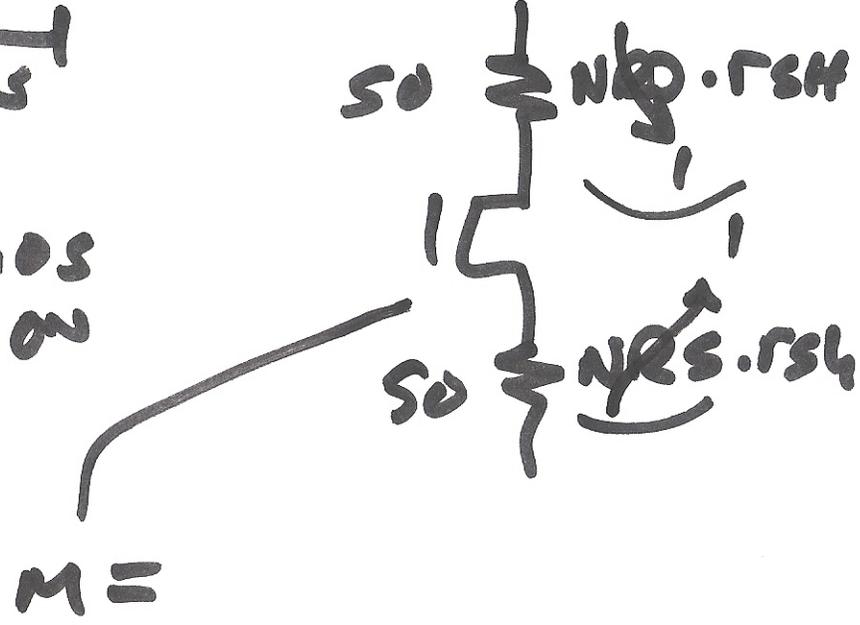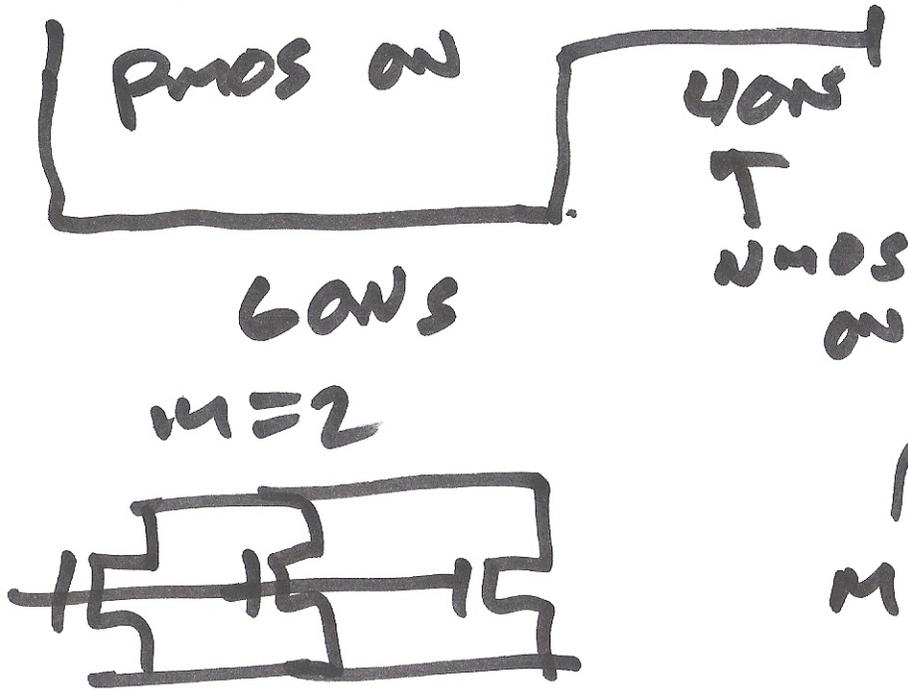

2)

$$Cv = Q$$

$$\Delta V = 10\text{mV}$$

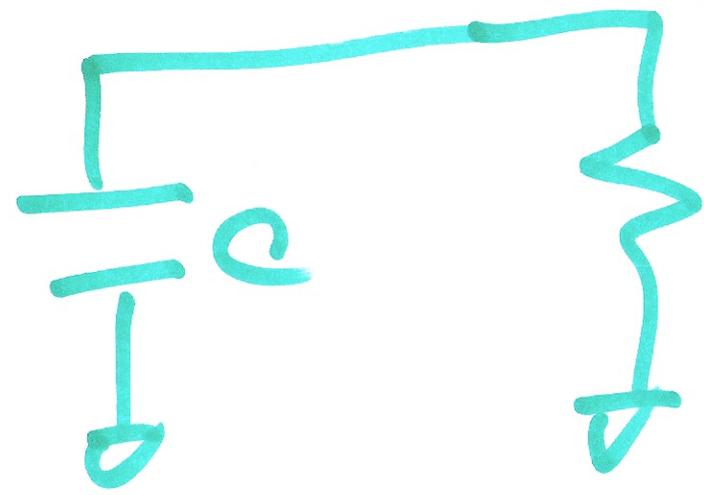

$$\Delta I = \frac{10\text{mV}}{R}$$

$$= \frac{10\text{mV}}{3\text{K}}$$

$$= 3.33\mu\text{A}$$



$$\Delta V \cdot C = \Delta Q$$

$$5\text{mV} \cdot C = \Delta Q$$

$$5\text{mV} \cdot C = 3.33\mu\text{A} \cdot 40\text{ns}$$

$$\frac{135 \times 10^{-26}}{5} \approx \underline{\underline{2.7\text{pF}}}$$

$$C = \frac{3.33\mu\text{A} \cdot 40\text{ns}}{5\text{mV}}$$

4)