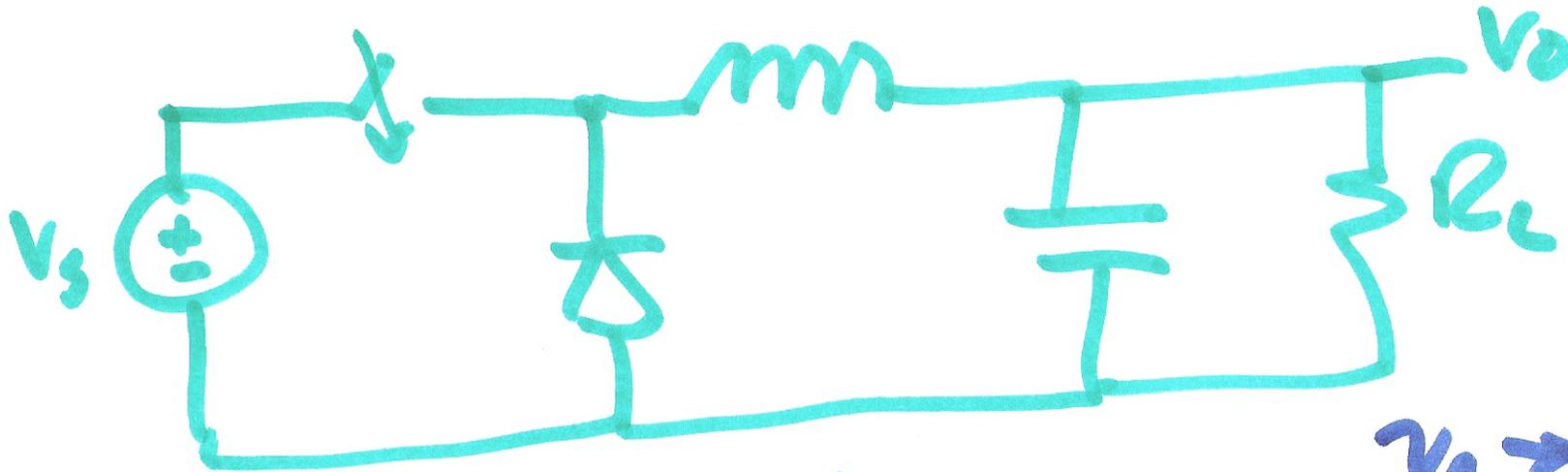


ECE 5472 Power Electronics



Lecture 20

OCT. 11, 2010






$$V_o = V_s \cdot D$$

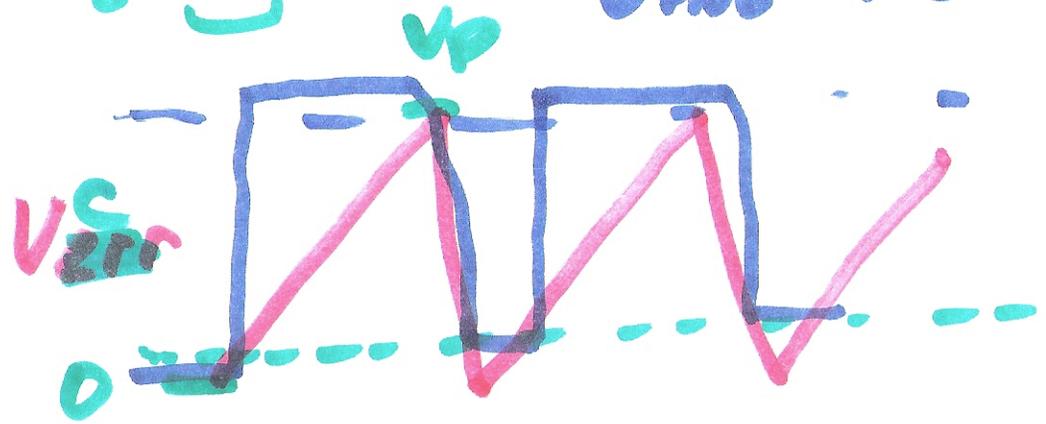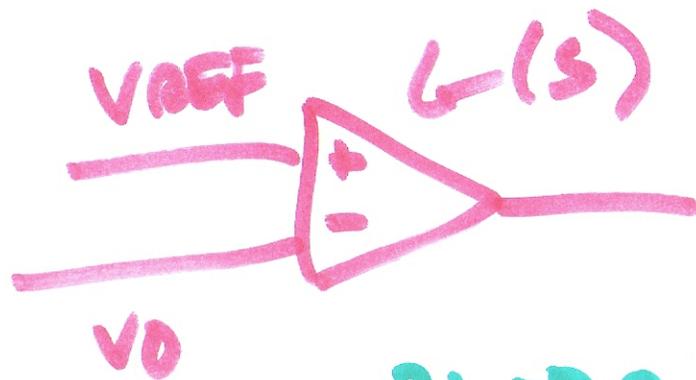$V_c \rightarrow V_p$
 $V_{avg} \rightarrow 0$




1)

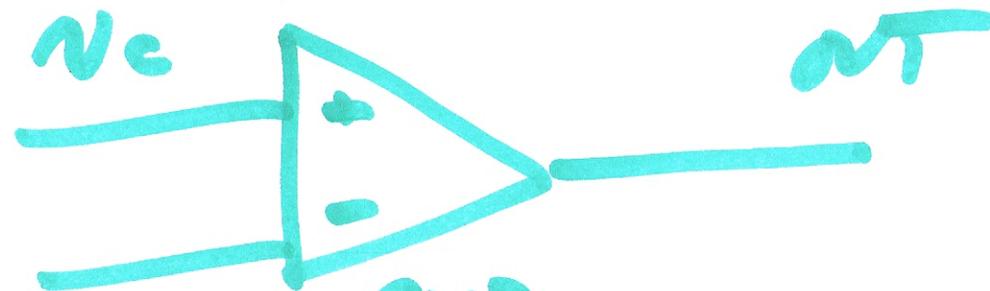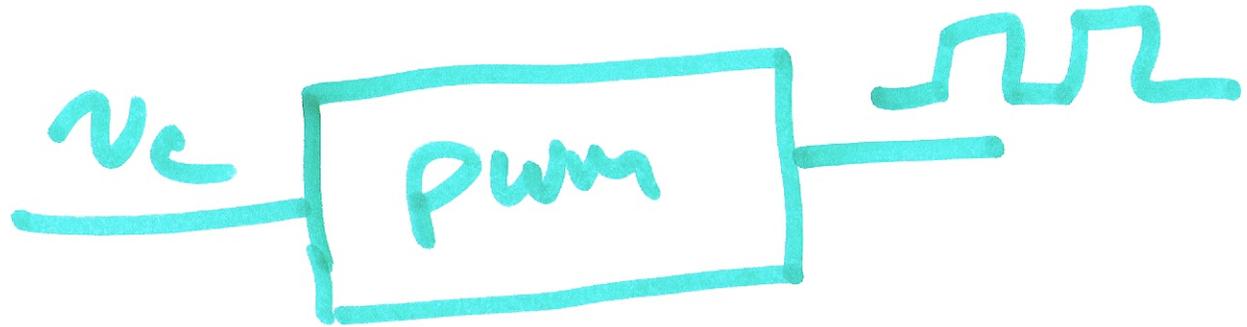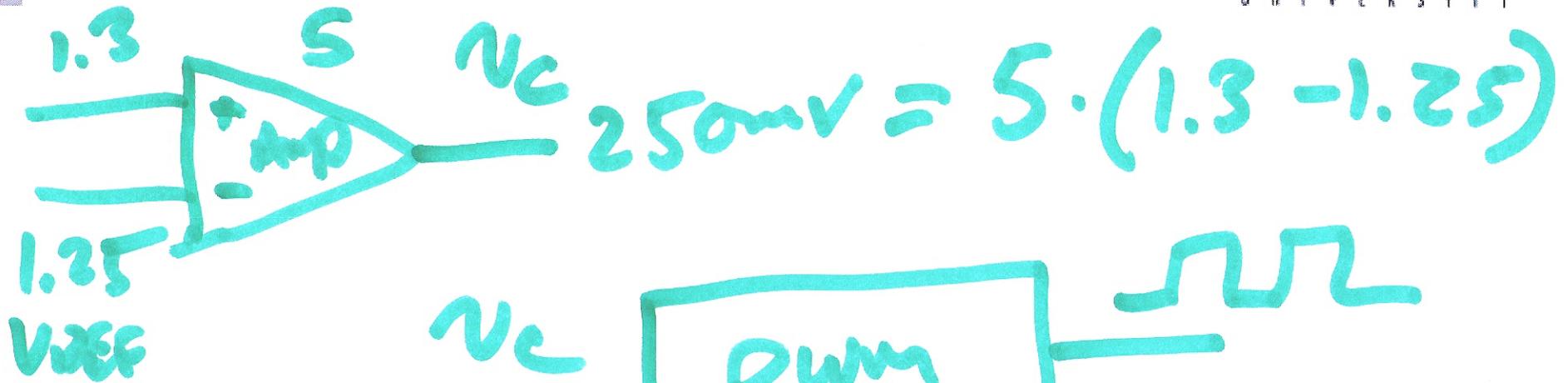


2)

$$K_{pwm} = \frac{1}{V_p} d$$

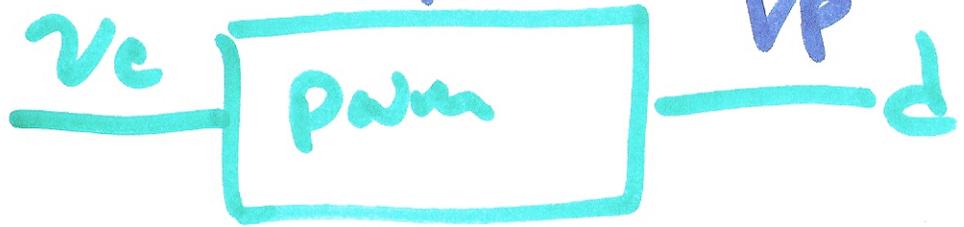

$$V_c = V_p (1-d) \text{ inv.}$$

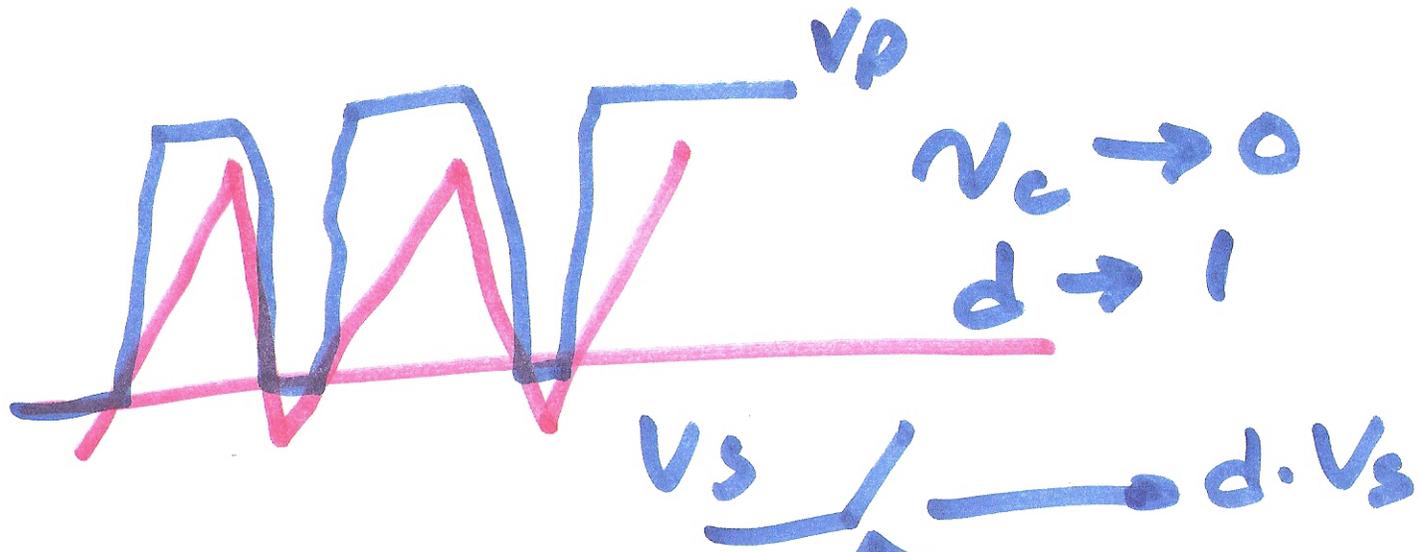


$$V_s \rightarrow d \cdot V_s$$

from

book

$$V_c = V_p \cdot d$$

3)

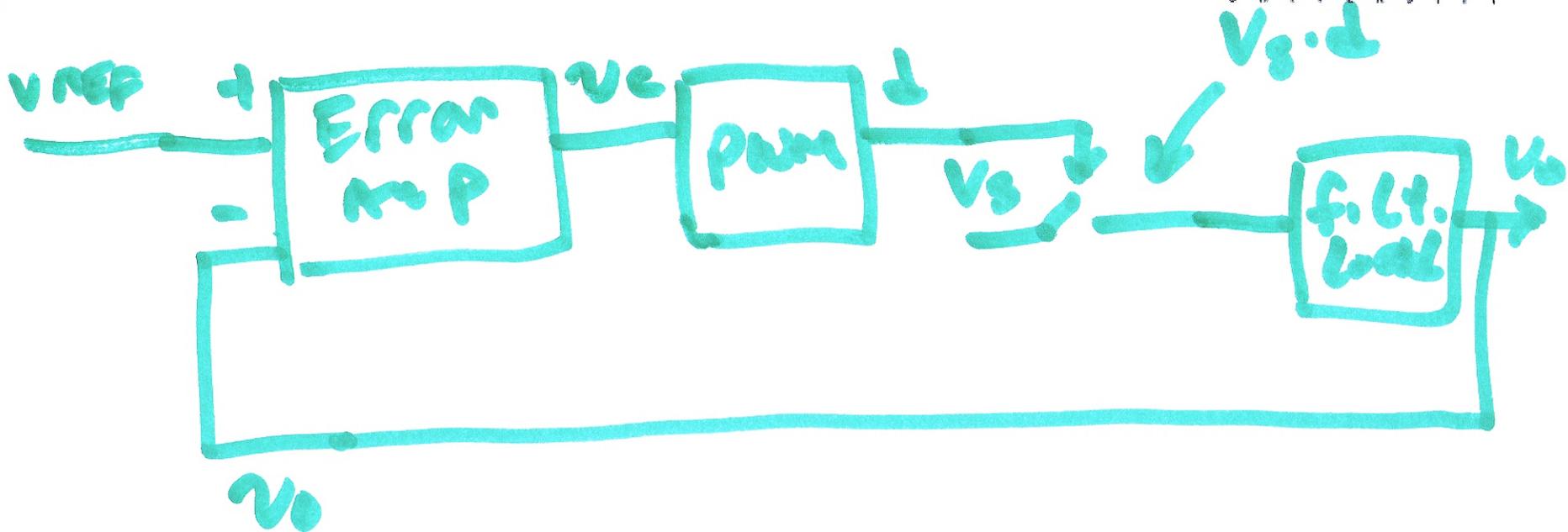

4)