

Lecture 37

NOV. 29, 2010



2V @ 100mA $R_L = 20$

$$L_{min} = \frac{(1-D)R_L}{2f}, \quad f \approx 1 \text{ MHz}$$

$5 \rightarrow 3, V_o = 0. V_s$

$$\frac{R_L}{4.5} \cdot 4 \leftarrow D \rightarrow 0.6$$
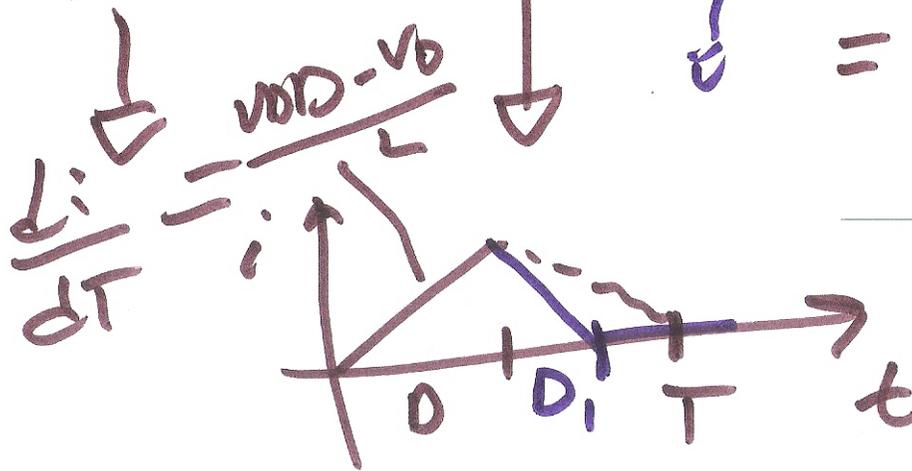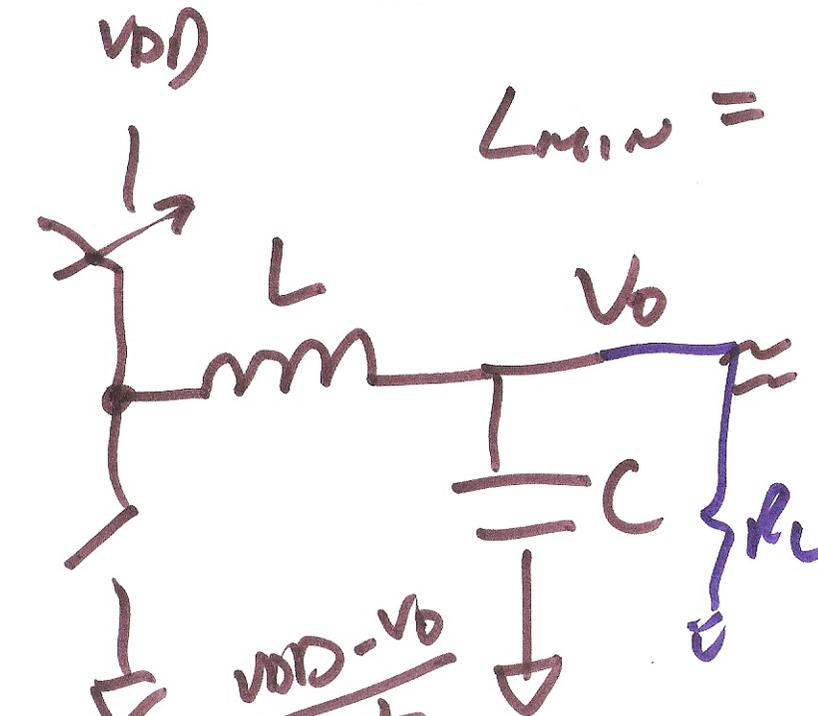
$$= \frac{20}{4 \text{ MHz}} = \boxed{5 \mu\text{H}}$$



$V_o = D \cdot V_s$ Cont. modes

$V_o = V_s \cdot \frac{D}{D - D_1}$ discont.


1)

Eq. 6-20

$$C = \frac{1-D}{8L \left(\frac{\Delta v}{v_0}\right) f^2}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

1 MHz

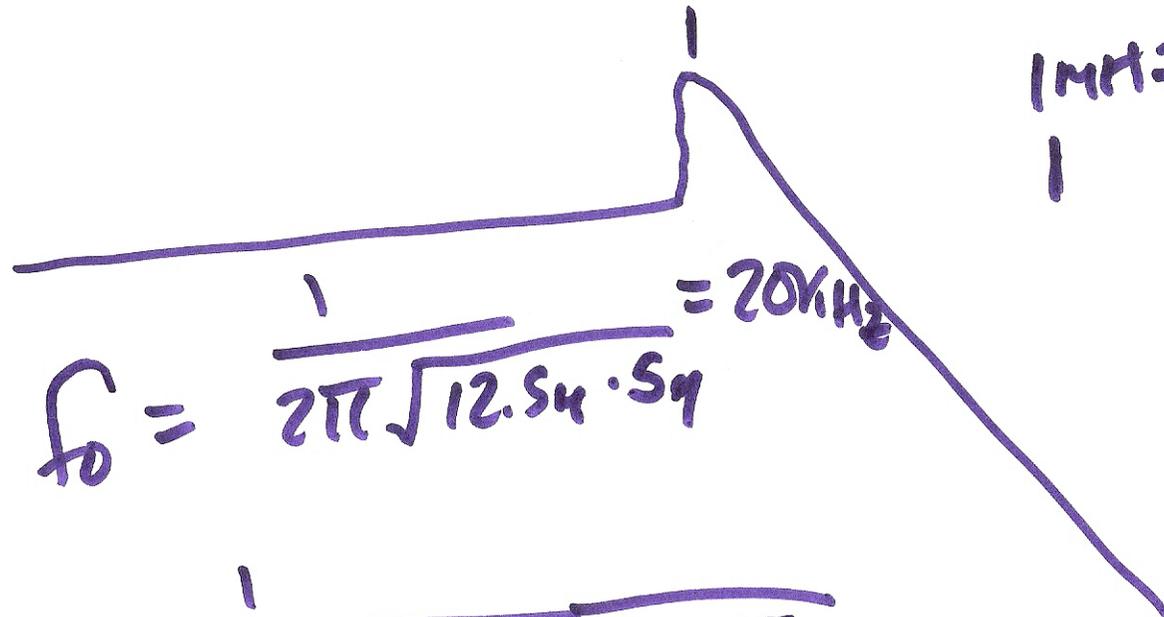



$$f_0 = \frac{1}{2\pi\sqrt{12.54 \cdot 59}} = 20 \text{ kHz}$$

$$C = \frac{1}{16.5 \mu \cdot .001 \cdot 10^{12} \cdot 6}$$

$$= \frac{1}{.08} \mu\text{F} = 12.54 \text{ F}$$

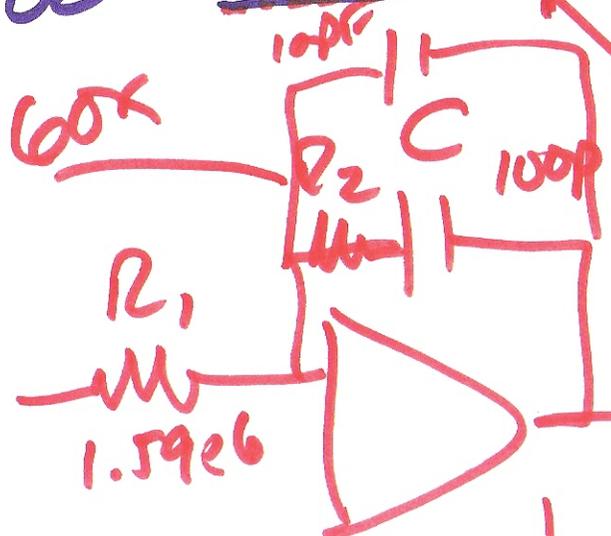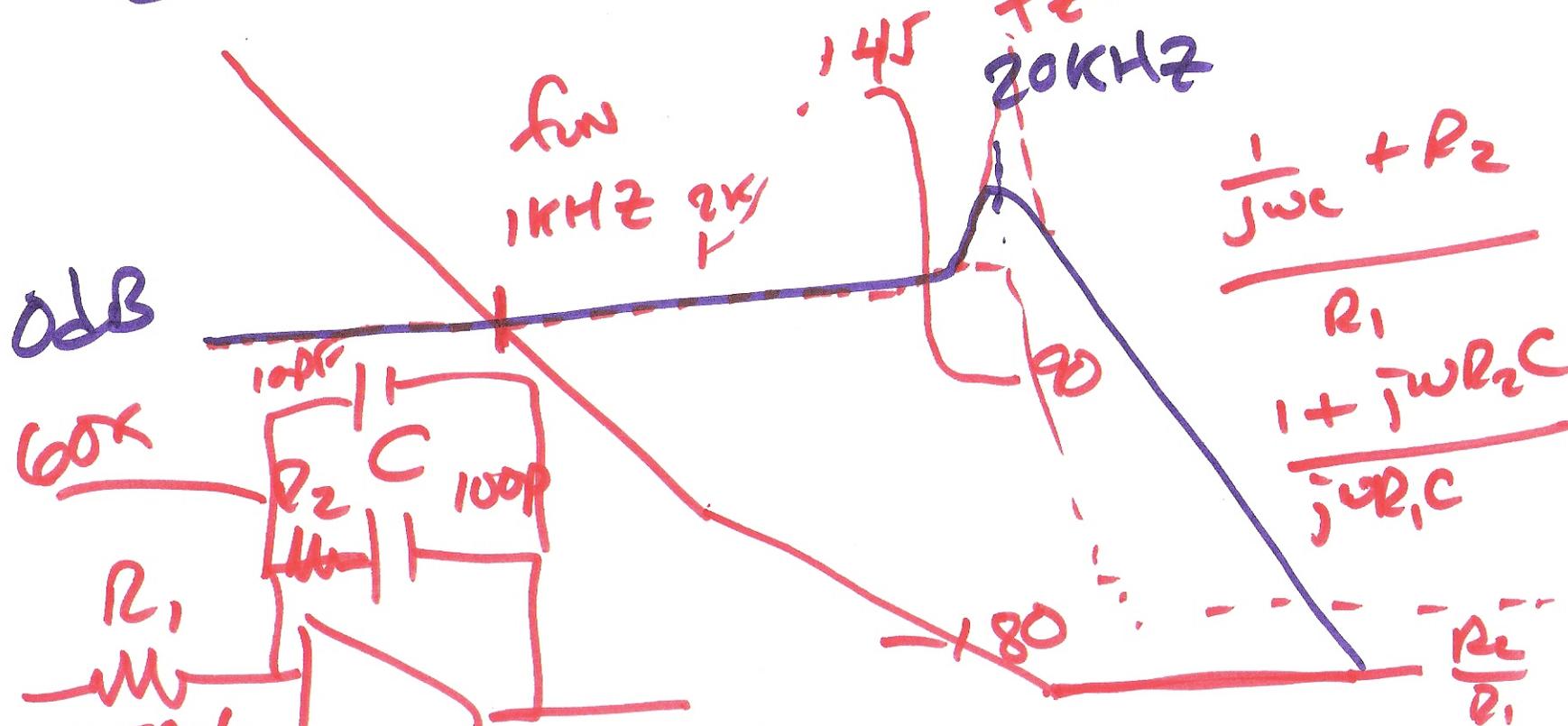2)

$f_0 = 20 \text{ kHz}$
 $L = 5 \mu\text{H}, C = 12.5 \mu\text{F}$
 $f = \frac{1}{2\pi R_2 C}$



$$\frac{\frac{1}{j\omega C} + R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C}$$

$$\left| \frac{1}{f \cdot 2\pi R_2 C} \right| = 1 \quad R = \frac{1}{2\pi \cdot 10^3 \cdot 100 \text{ pF} \cdot \frac{1}{2\pi} \cdot 10^7} \cdot 10^{-10}$$

3)