

Lecture 38 Dec. 3,



2010

$$\frac{198.6 \text{ mW}}{219 \text{ mW}} =$$

Talk about discontinuous current.



LTSPICE!

$$i_L \frac{V_s - V_o}{L}$$

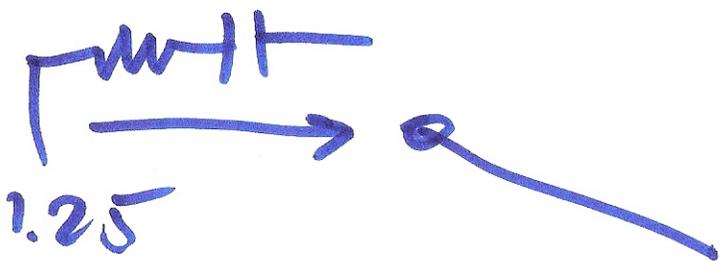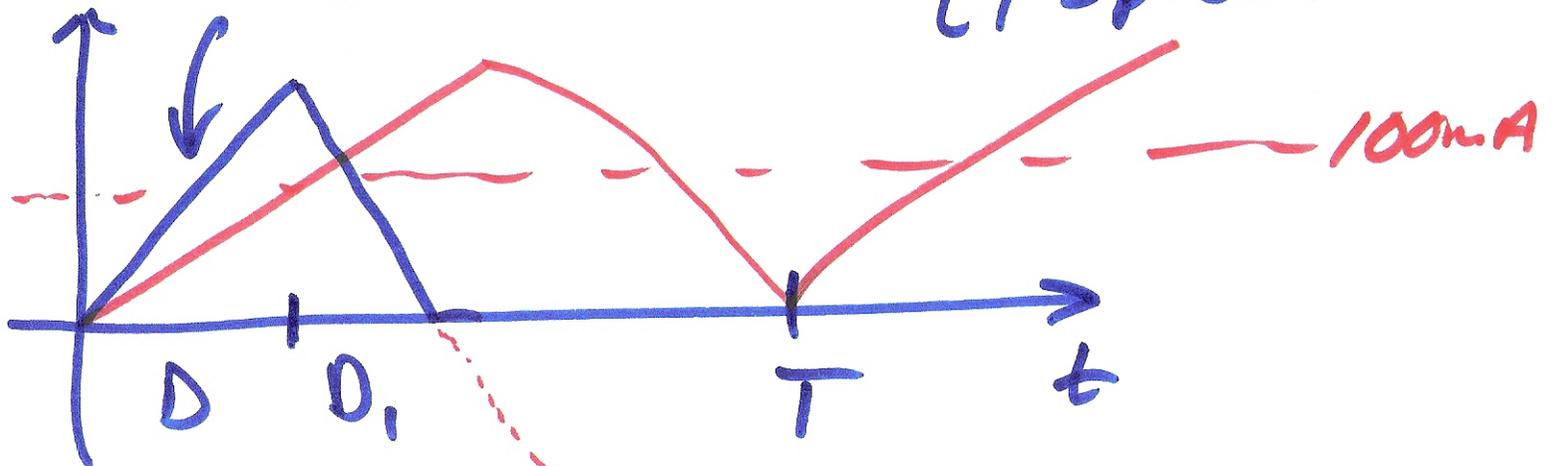


1)

# Ch. 8 inverters

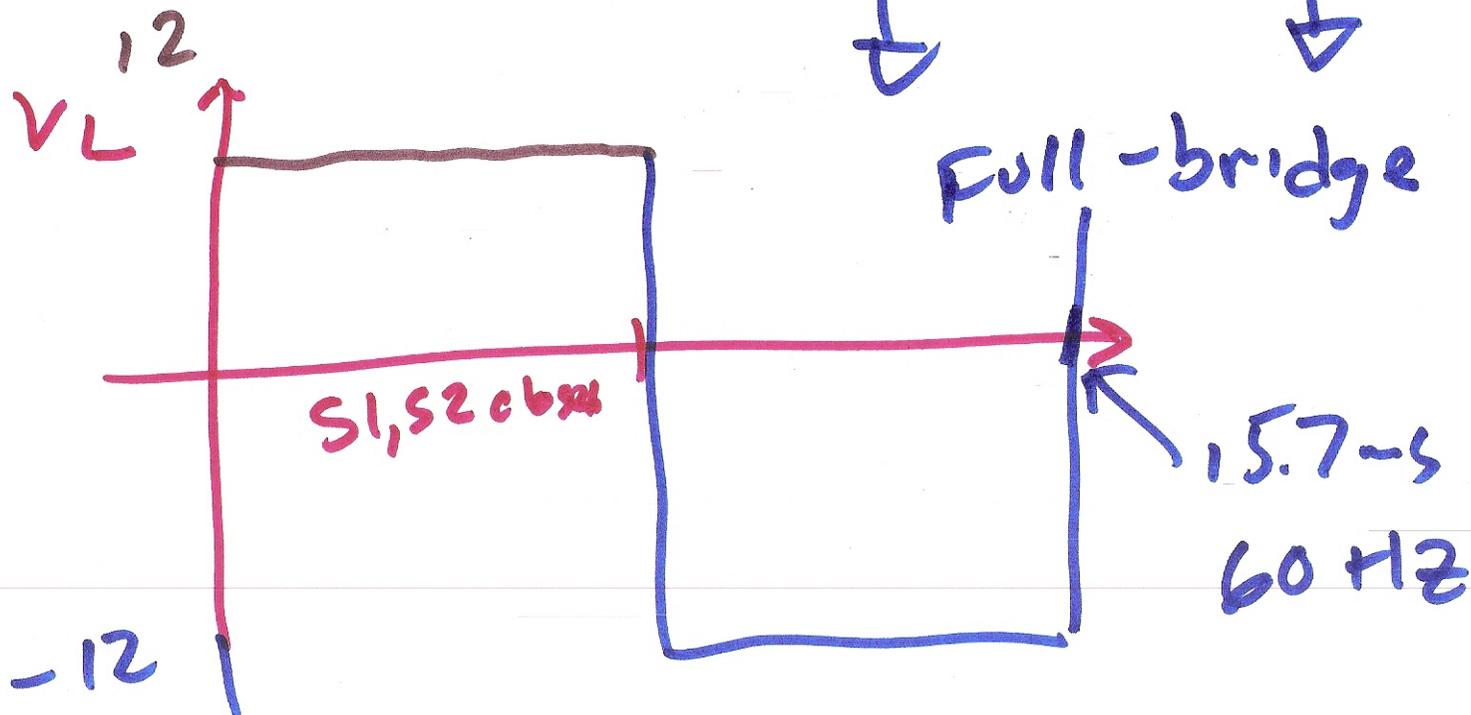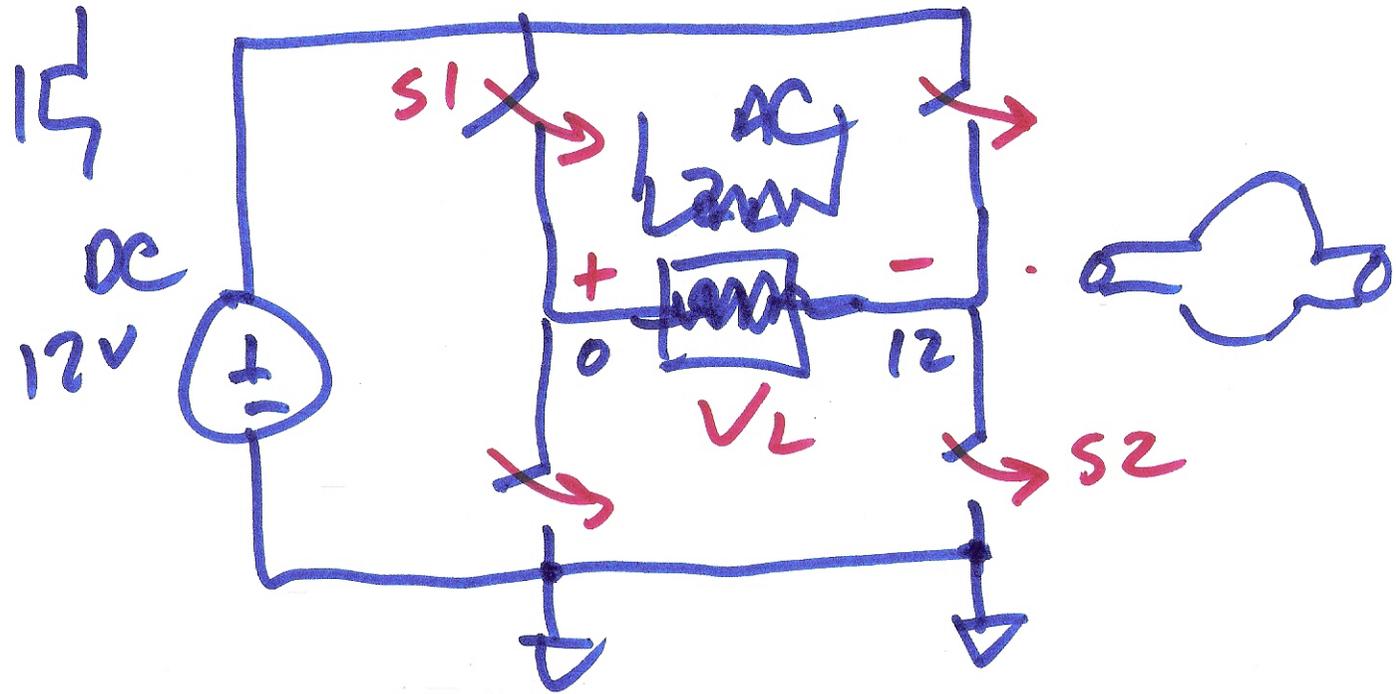

2)

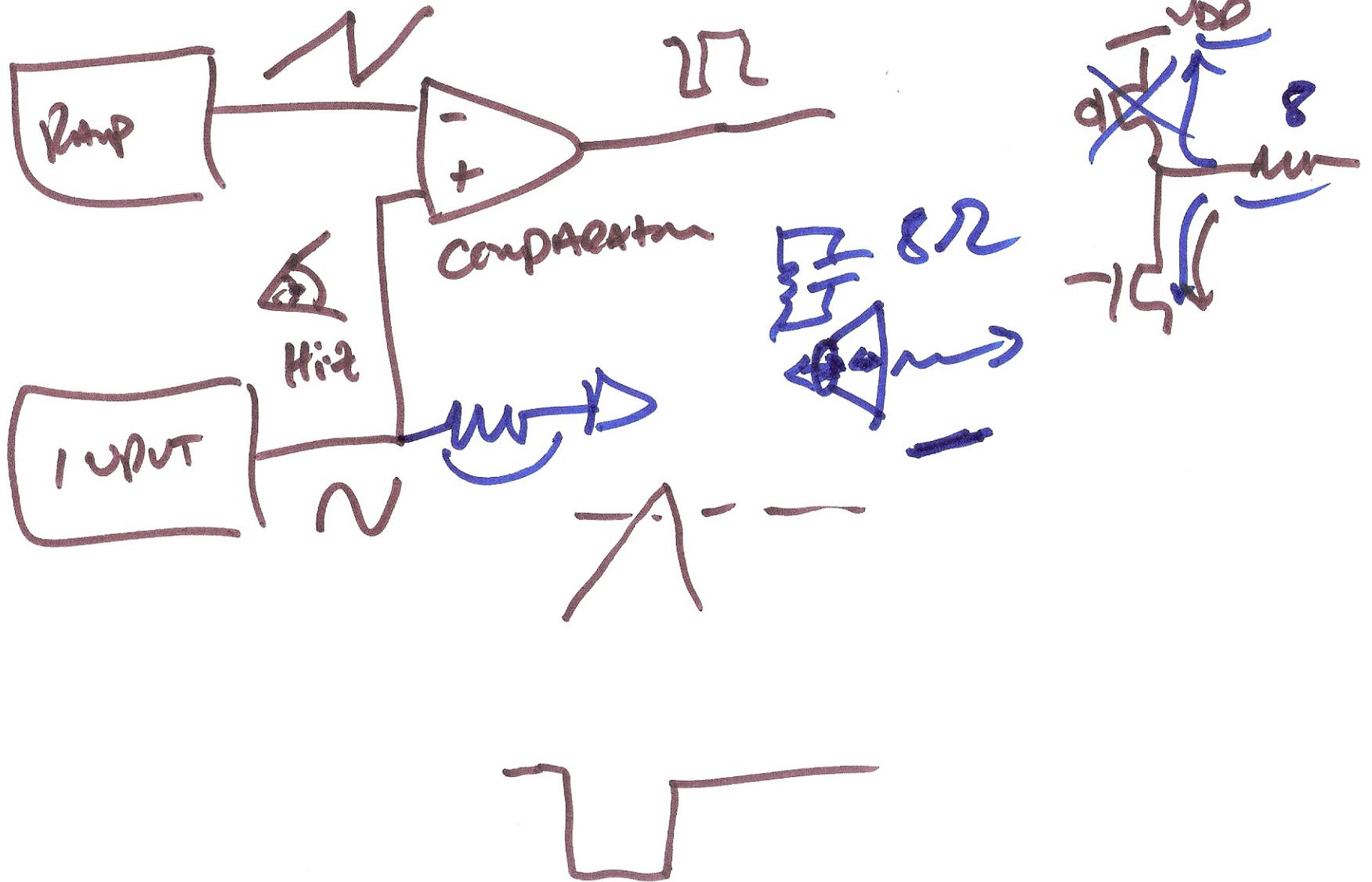

3)