
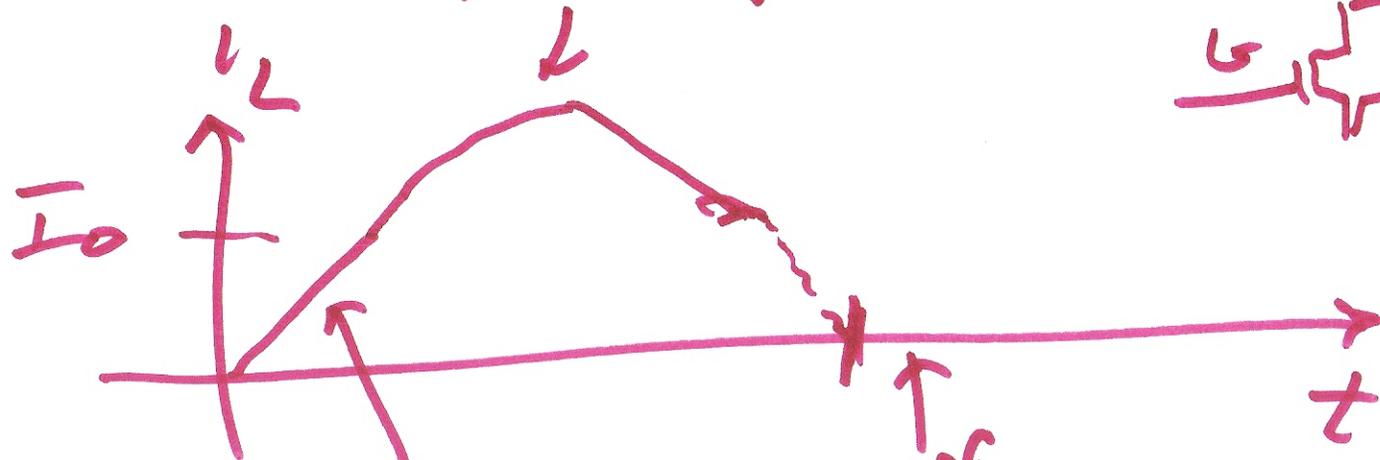


Lecture 40

12/8/2010

RESONANT

ZCS


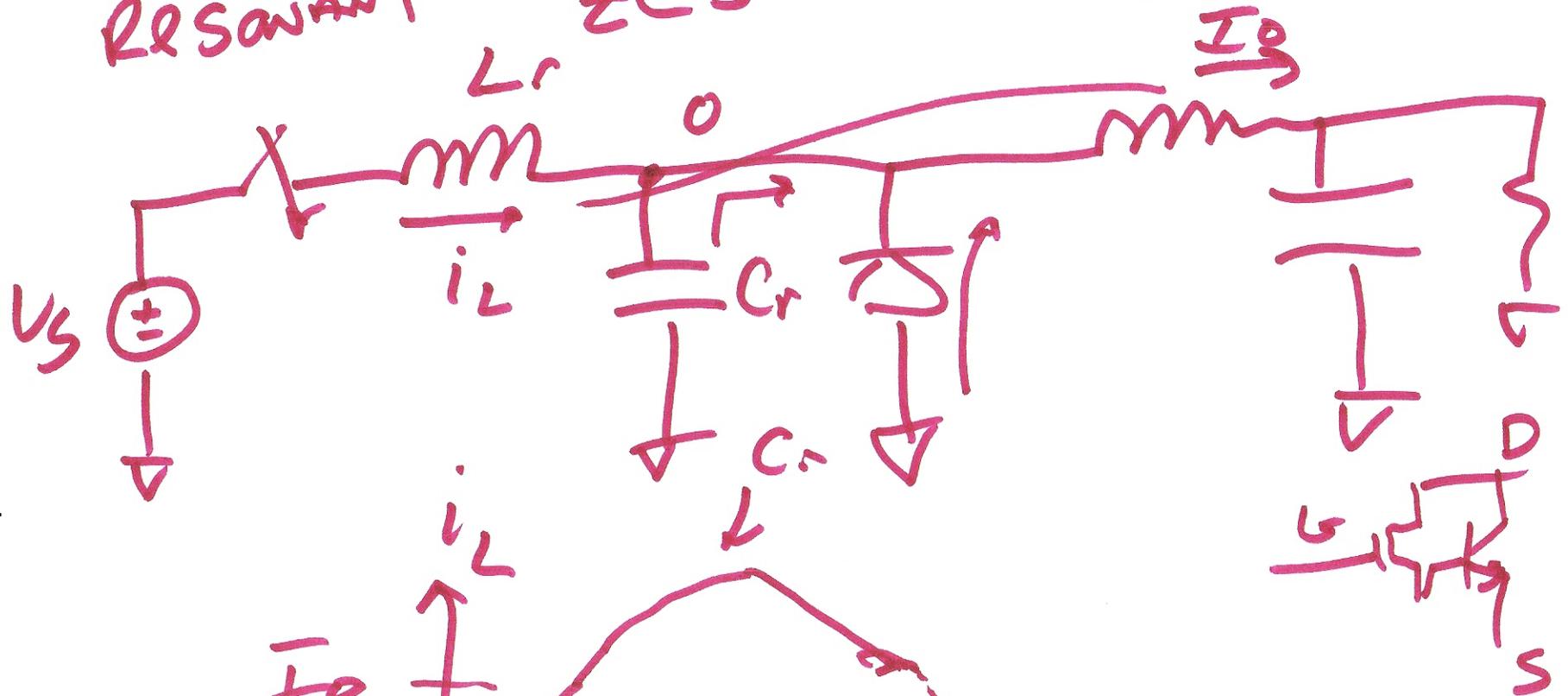


$$\text{Slope} = \frac{V_s}{L_r}$$

off switch


1)

z VS CMOS

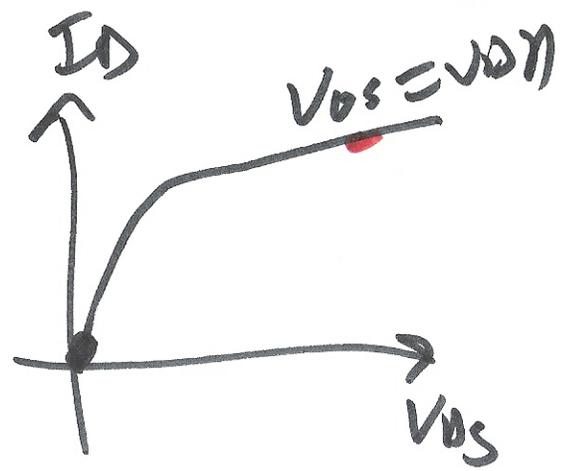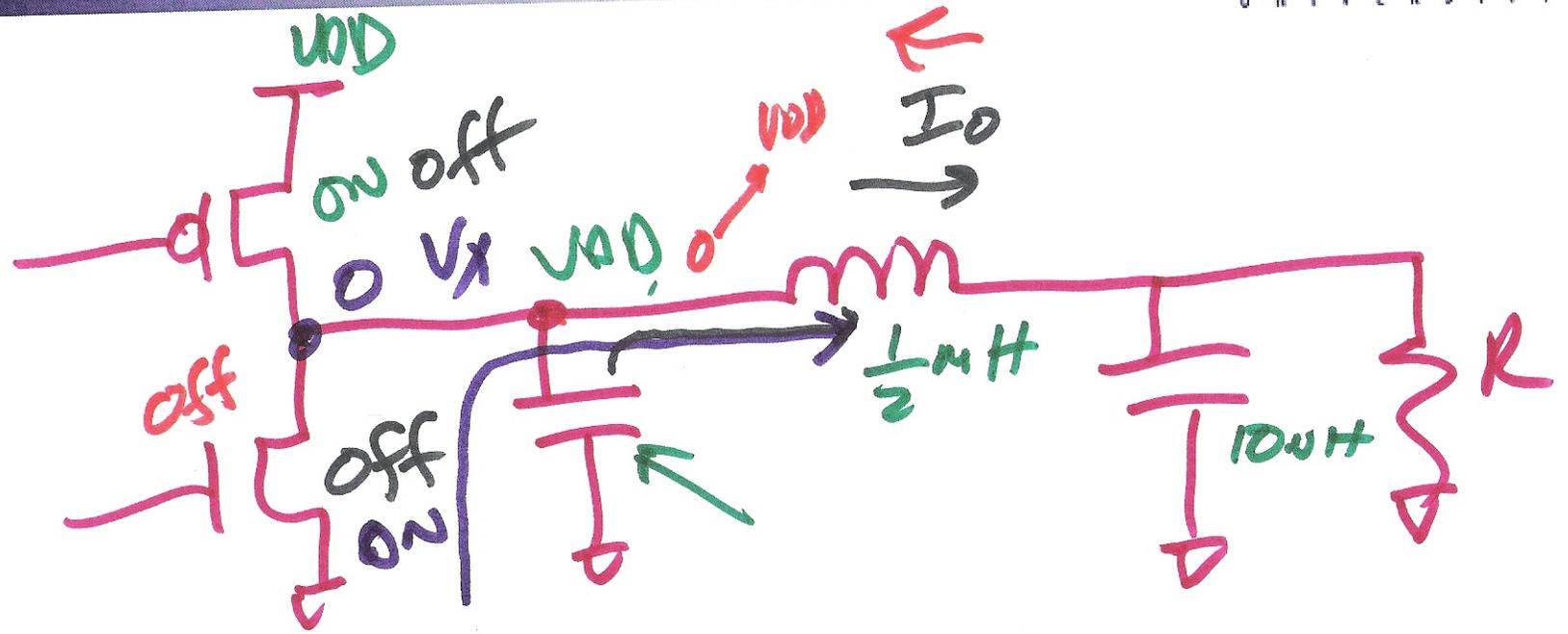

switch
 $f = 1MHz$
 $R_{max} = 2k$
 $L_{min} = 500nH$

2)

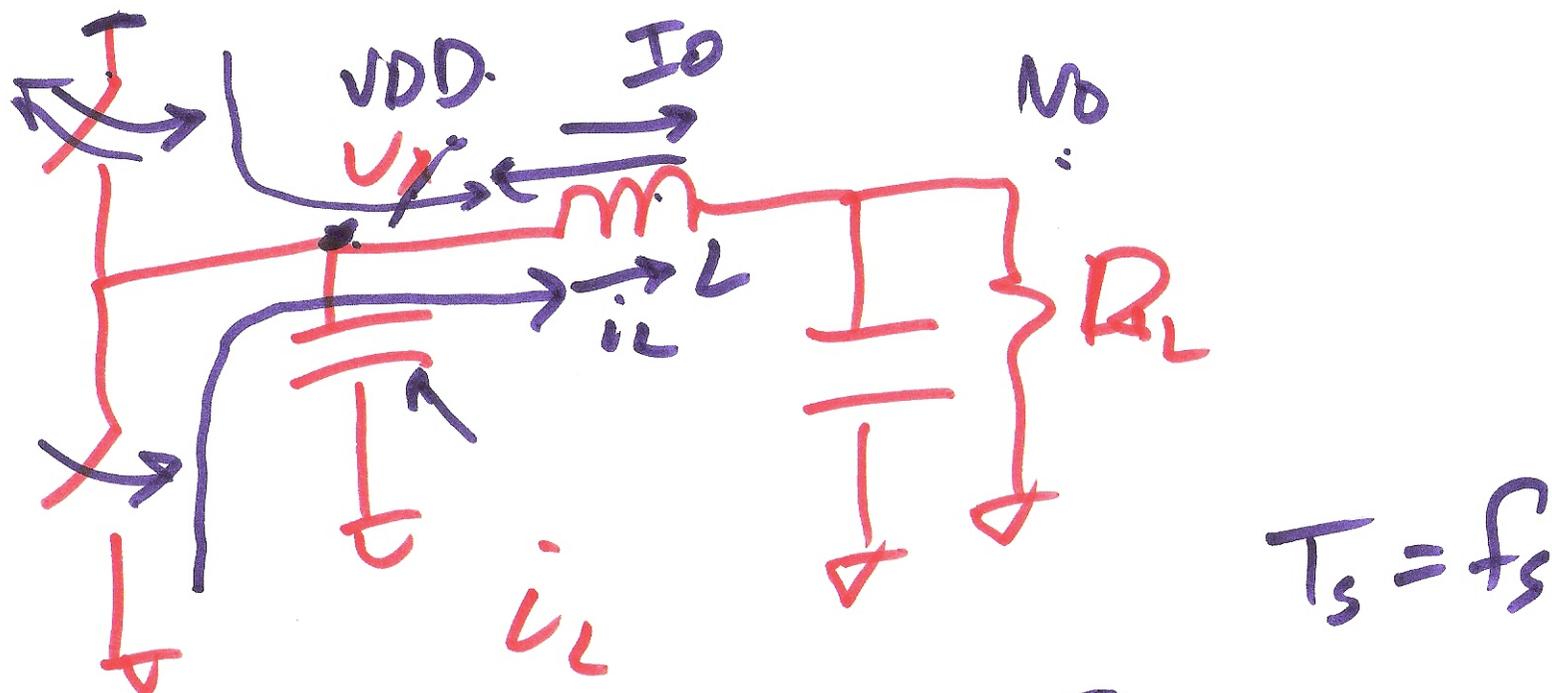

3)

