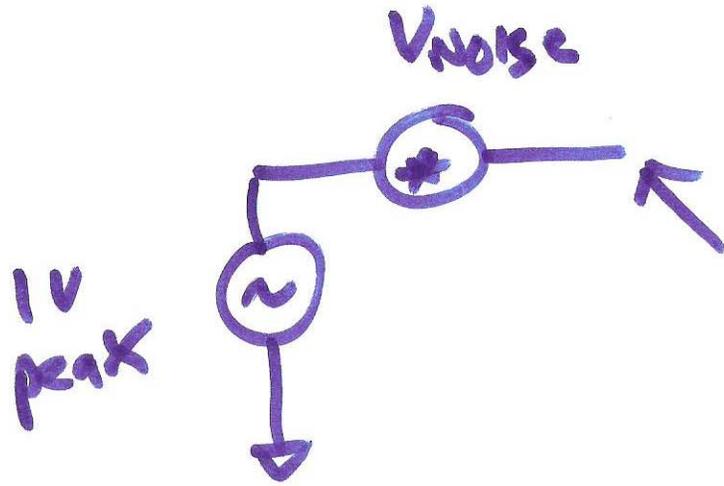


Lecture 13

OCT. 4, 2011




doesn't make sense
 $1V + \frac{1\mu V}{\text{noise}}$
 Signal

$$1 \sin 2\pi 100t + 2 \sin 2\pi 200t = 3 \sin \dots$$

$$= 1.000000001$$

$$SNR = \frac{1}{1\mu}$$


OP-AMP NOISE MODEL

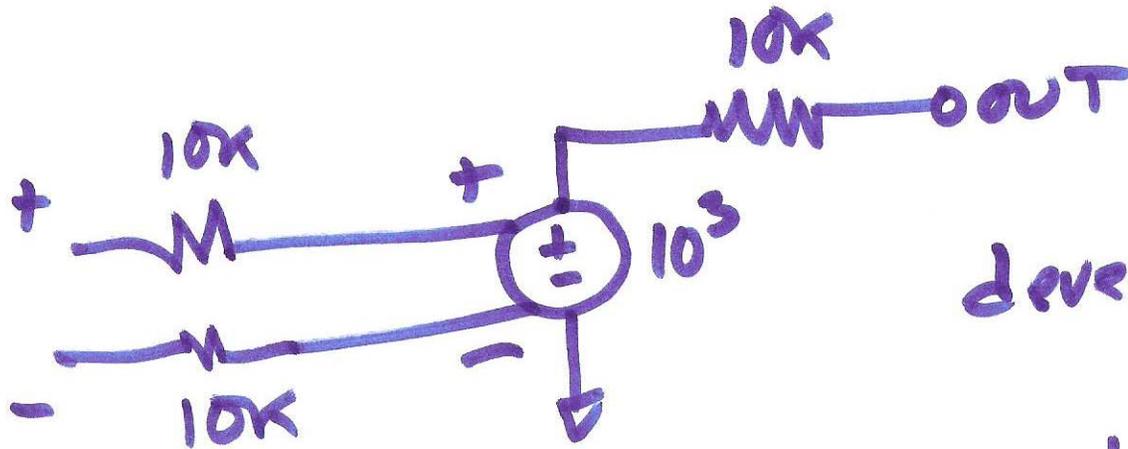

develop noise model

what are $i_{noise}(f)$
 e_n & i_n
 i_v = ?


Fig. 8.47

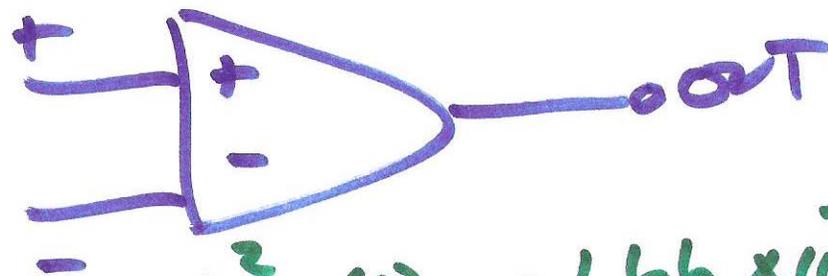

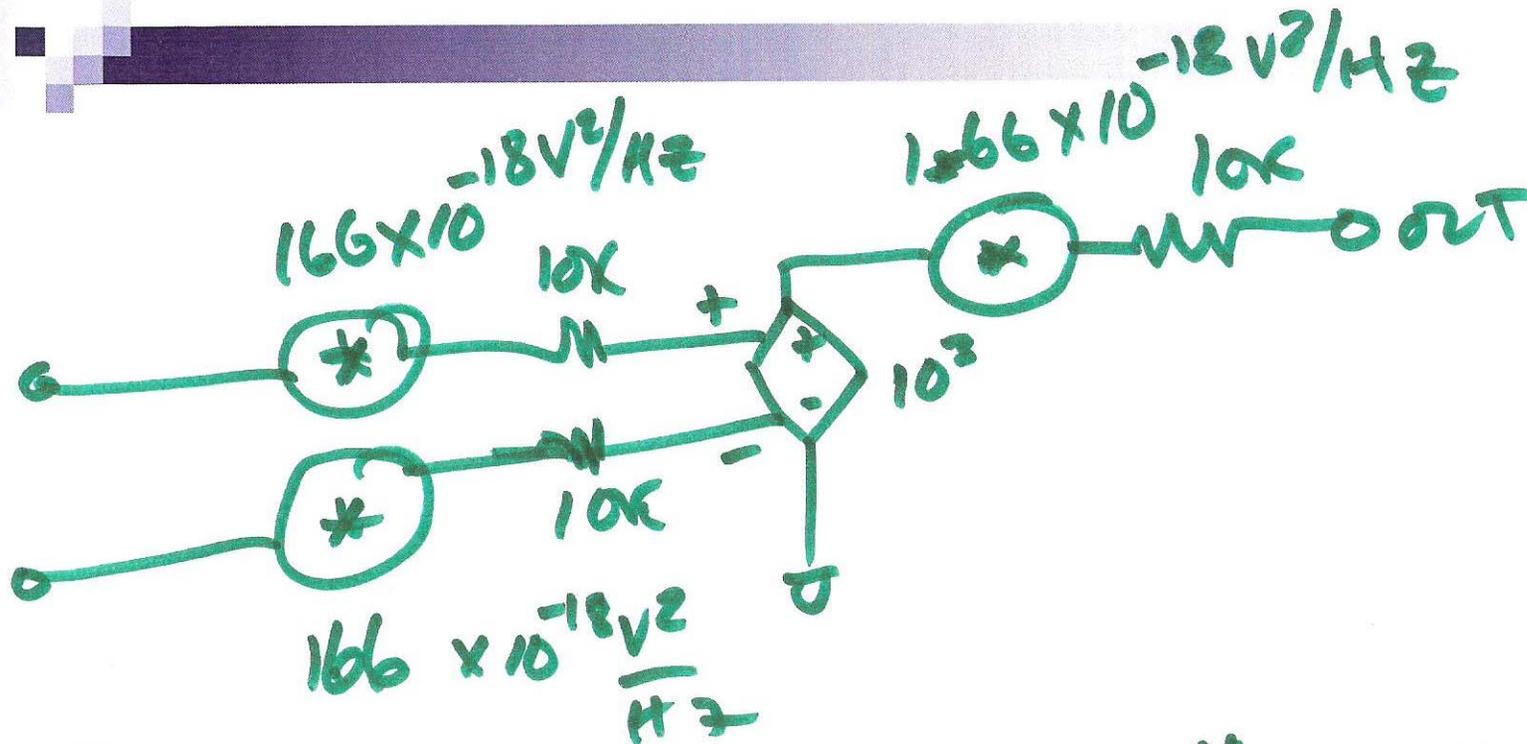2) $10^4^2 = 10^8$



$$i_{10K}^2(f) = 1.66 \times 10^{-24} \frac{A^2}{Hz}$$

$$v_{10K}^2(f) = 1.66 \times 10^{-16} \frac{V^2}{Hz}$$



$$166 \cdot 10^{-18} + 166 \cdot 10^{-12} \cdot 2 = 332 \cdot 10^{-12} \frac{V^2}{Hz}$$

11V

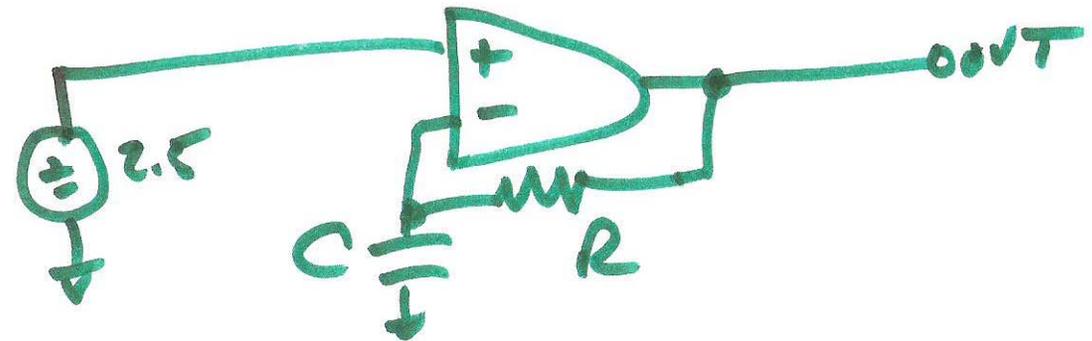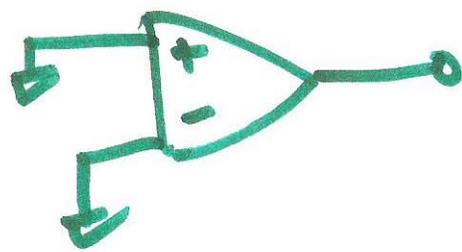

3)

INPUT-referred noise

$e_n(f) = ?$



$v_{noise}(f) = ?$

$= e_n(f) =$


$332 \cdot 10^{-12} \frac{V^2}{Hz}$

$e_n^2(f) = \frac{v_{noise}^2(f)}{10^4}$


v_{noise}

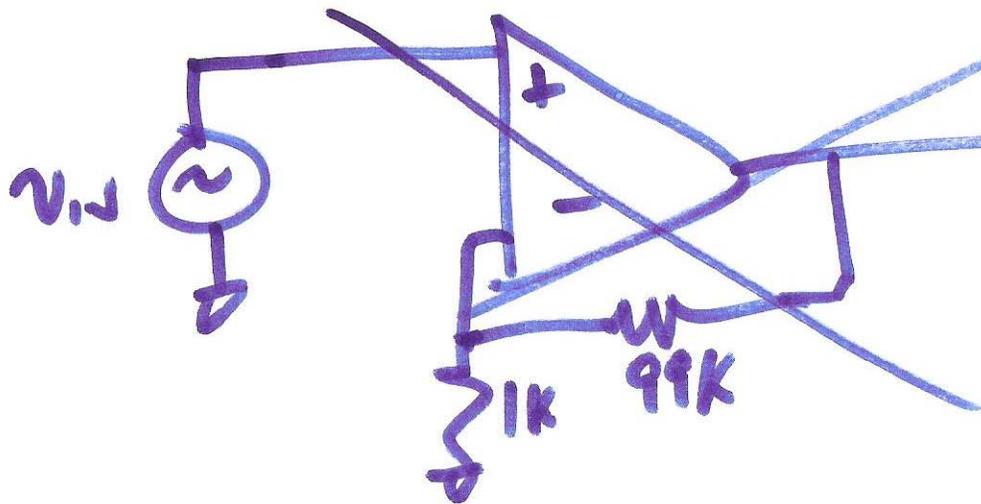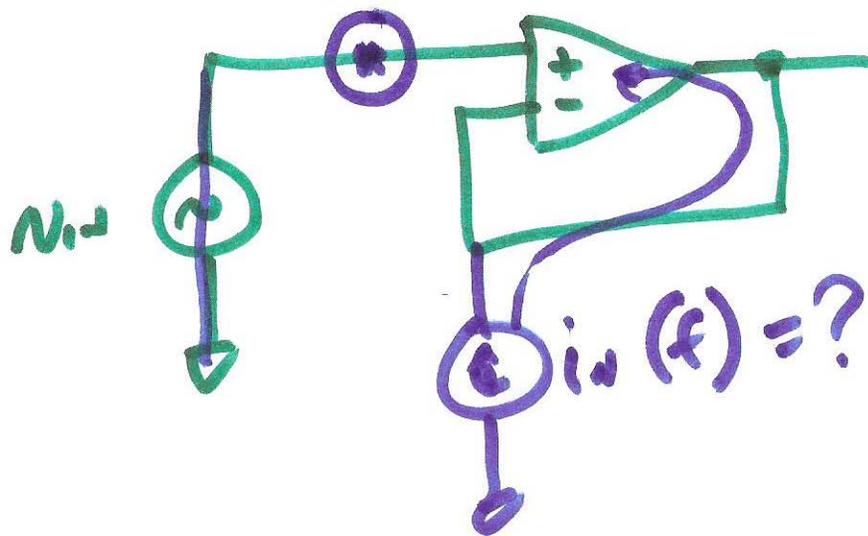

4)

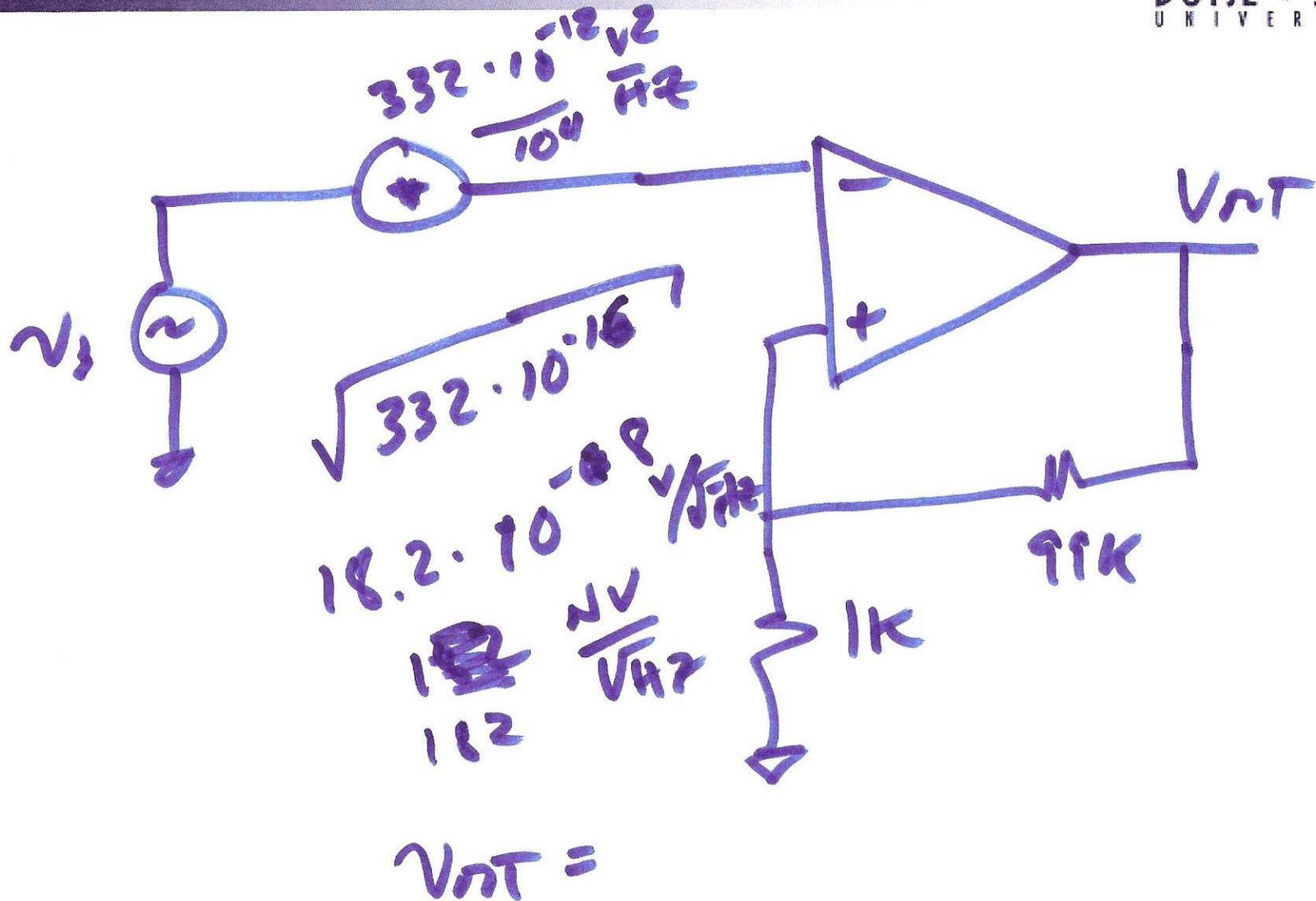


5)

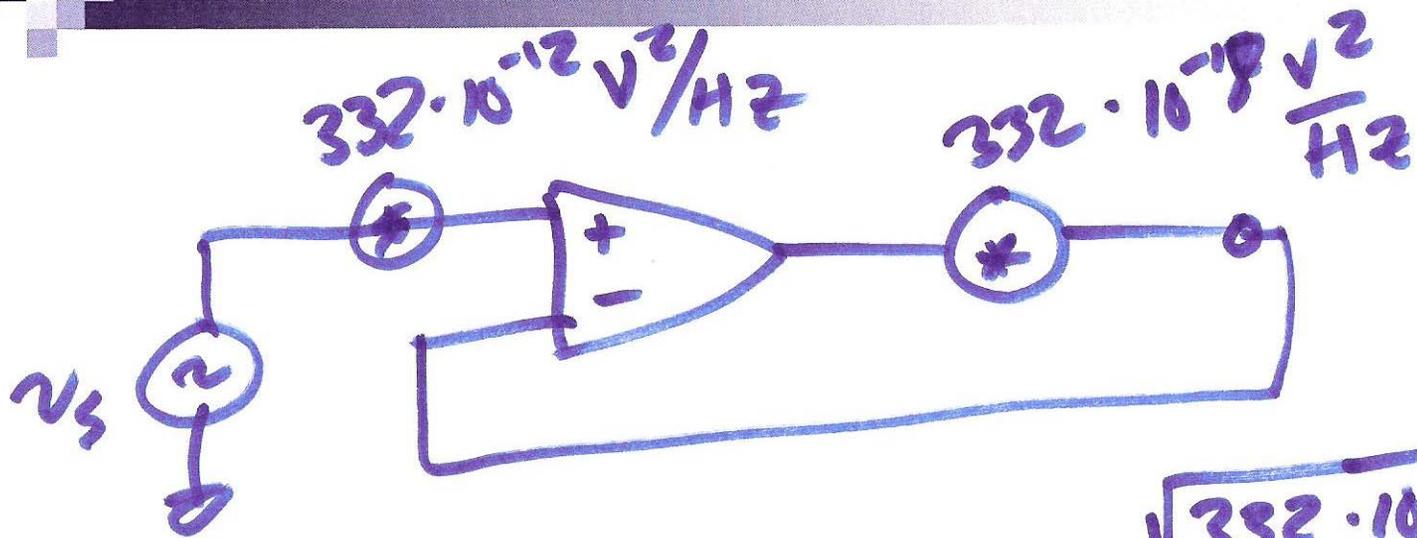




$$\sqrt{332 \cdot 10^{-12}}$$

$$18.2 \cdot 10^{-6} \frac{\text{V}}{\sqrt{\text{Hz}}}$$

6)

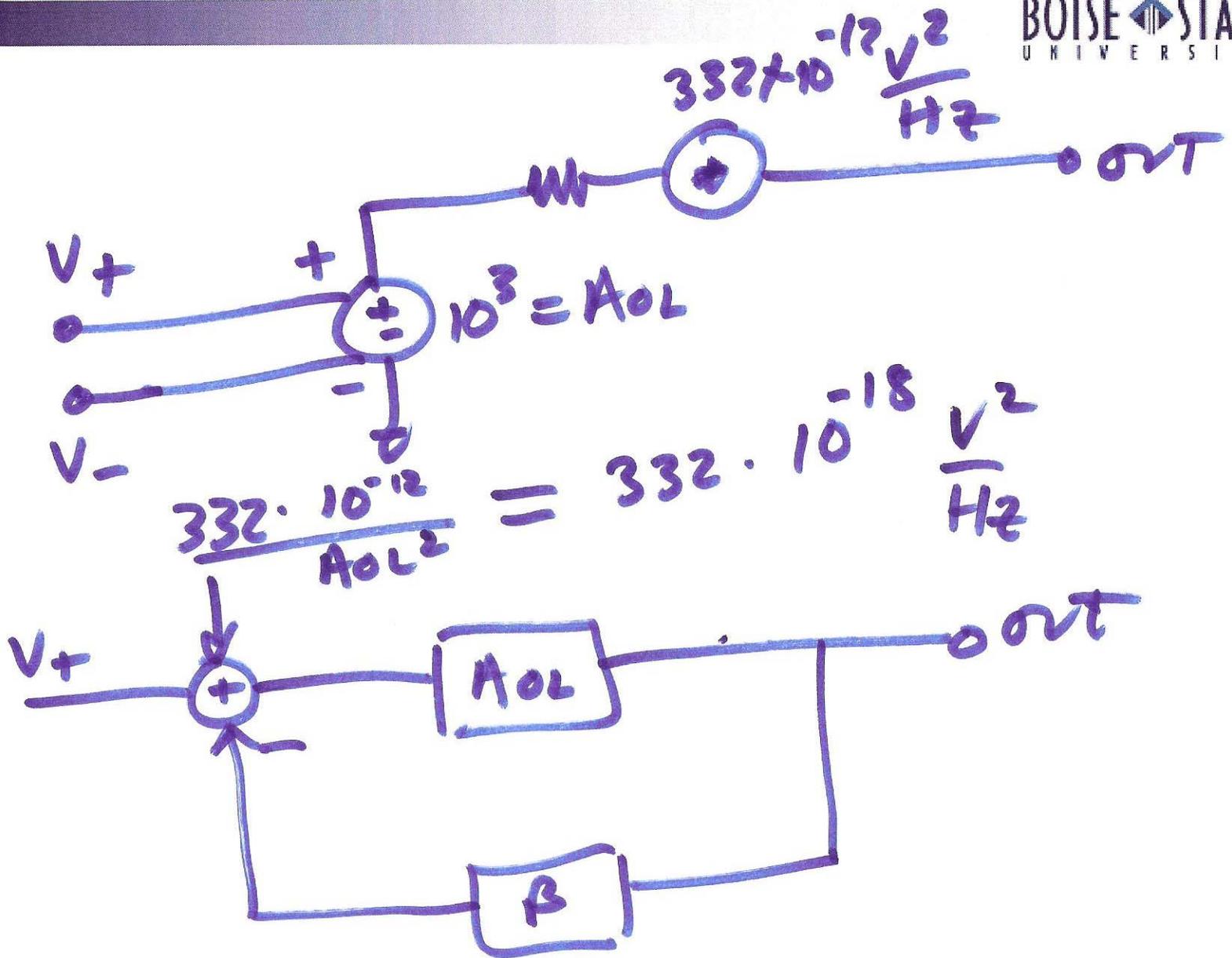

7)

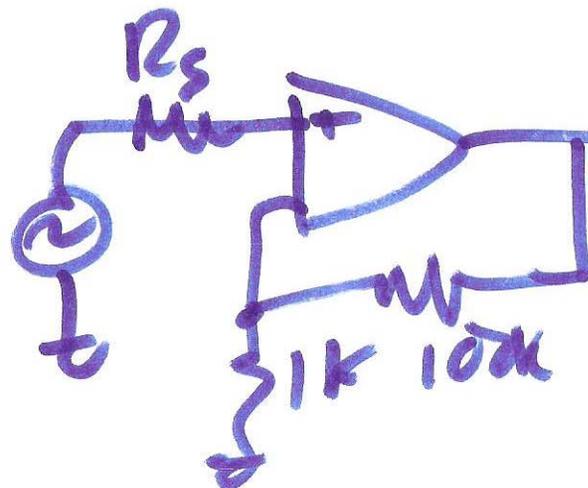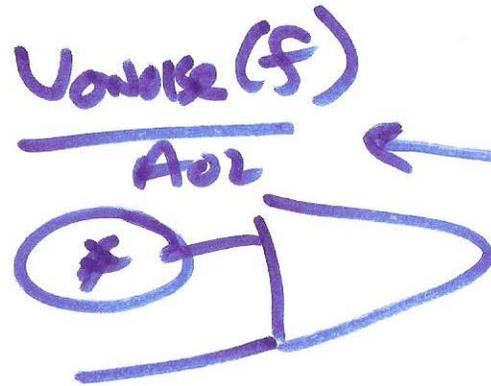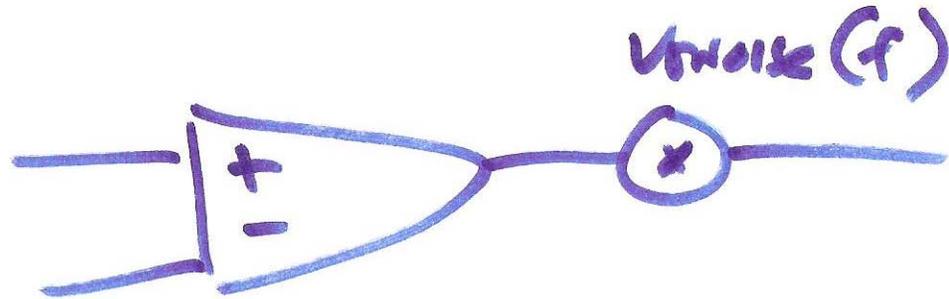

$$V'_{noise}(f) = \frac{V_{noise}(f)}{A_{OL} \cdot \beta}$$

$$\frac{1}{\beta} \approx A_{CL} \cdot \frac{1}{A}$$

INPUT refer.
↓
noise

8)