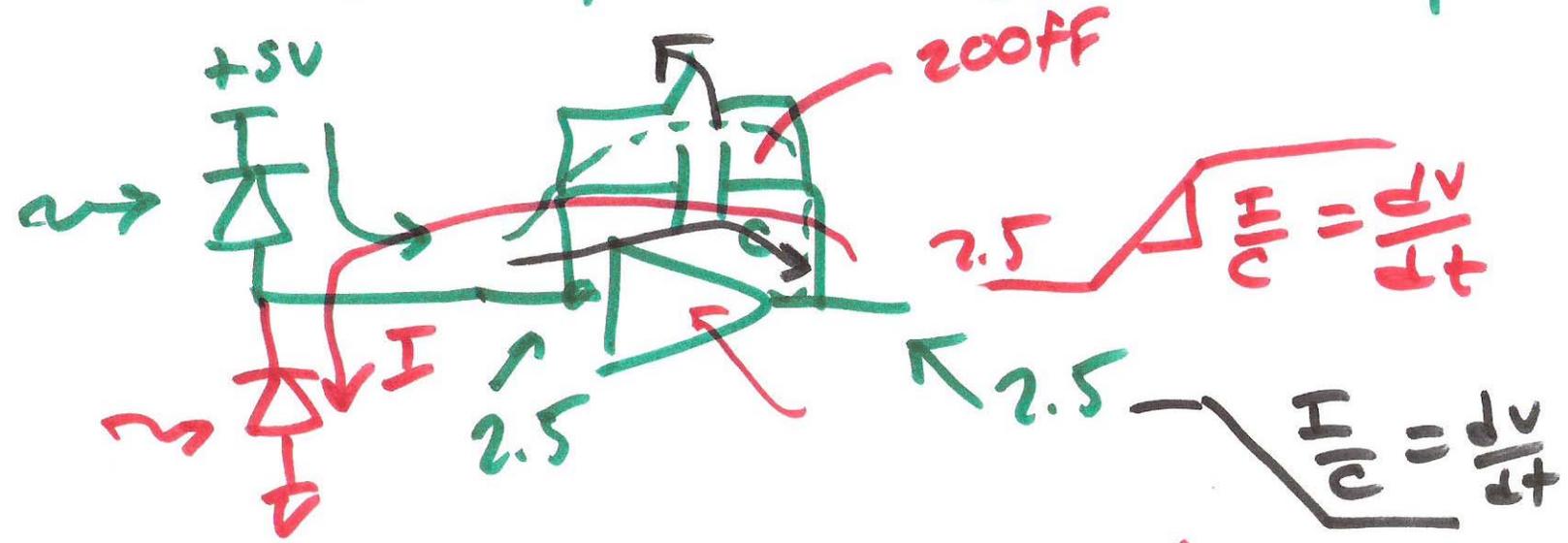


ECE 614 ADVANCE Analog IC Design

OCT. 6, 2011

Lecture 14



$CV = Q$

$200fF \cdot 300mV = 50kV$



$Q = 10,000 \cdot 10^{-18} \text{ Coulombs}$

~~$\sqrt{\frac{K \cdot 200fF \cdot 50kV}{50kV}}$~~

$\sqrt{\frac{K \cdot 50kV}{200f}} = ?$ Kelvin

$50kV = 50$

$Q \cdot \frac{1 \text{ electron}}{1.6 \cdot 10^{-19} C} \Rightarrow \# \text{ of electrons}$

$\# \text{ of electrons} \Rightarrow \# \text{ of electrons}$

peak \rightarrow peak = 300mV

pages 248-249!

$$\frac{10 \cdot 10^{-15} \text{ C}}{1.6 \times 10^{-19} \text{ C/e}} = 100 \text{ electrons (rms)}$$

$$\Delta V = \frac{I}{C} \cdot \Delta t$$

$$200 \text{ pA} \cdot 2 \text{ ms} = 600 \cdot 10^{-12} \text{ C}$$

$$\frac{\Delta V}{I} = \frac{\Delta t}{C}$$

$$\frac{\text{C}}{\text{s}}$$

$$\frac{600 \cdot 10^{-12} \text{ C}}{1.6 \times 10^{-19} \text{ C/e}} =$$



$$100 \text{ electrons} \cdot \frac{1.6 \times 10^{-19} \text{ C}}{\text{elect.}} = 3.7 \times 10^9 \text{ electrons}$$

$$= 160 \times 10^{-19} \text{ Coulombs}$$

$$i_{\text{noise, rms}} = \frac{160 \times 10^{-19}}{2 \text{ ms}} = 80 \cdot 10^{-16} = \underline{\underline{8 \text{ fA}}}$$

2)

Aliasing

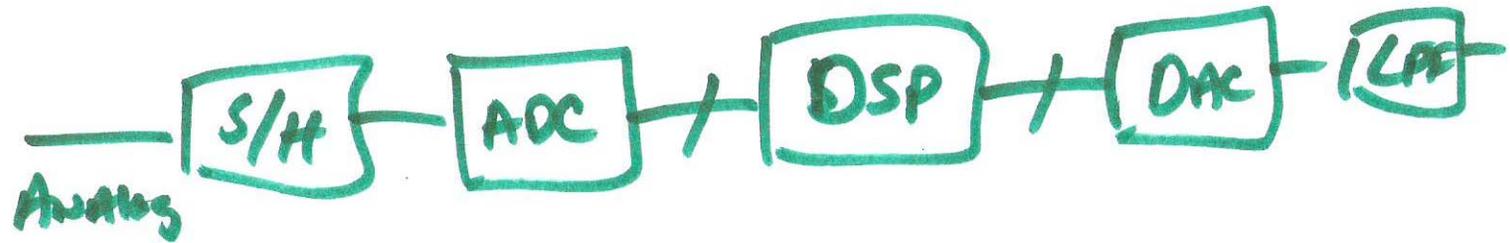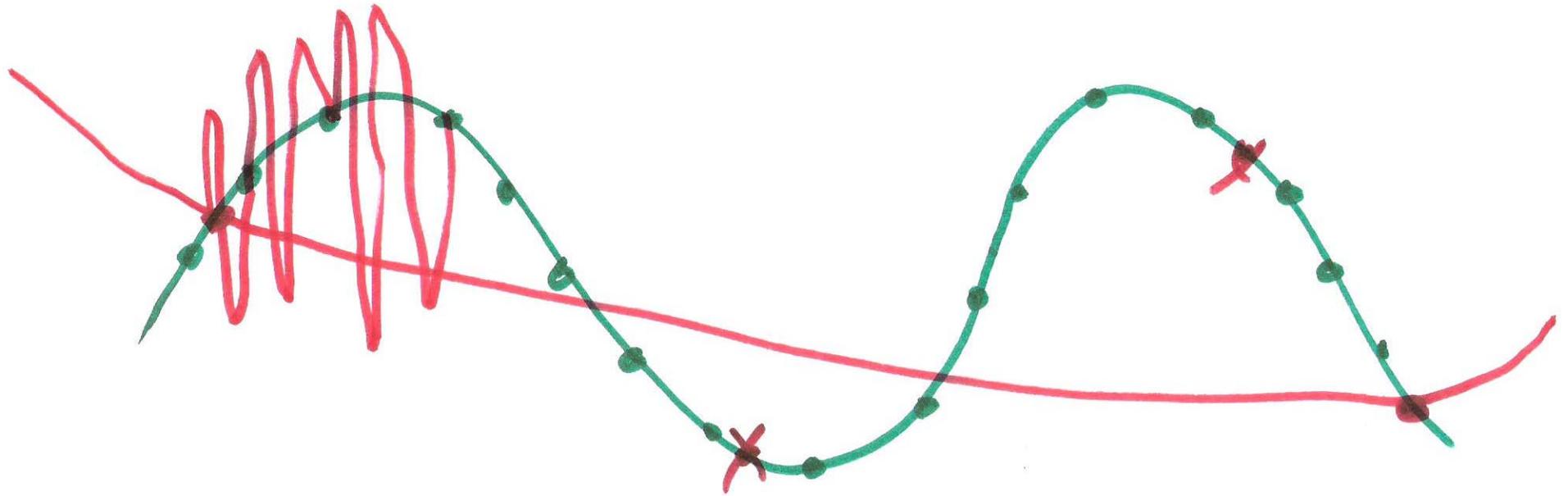

3)

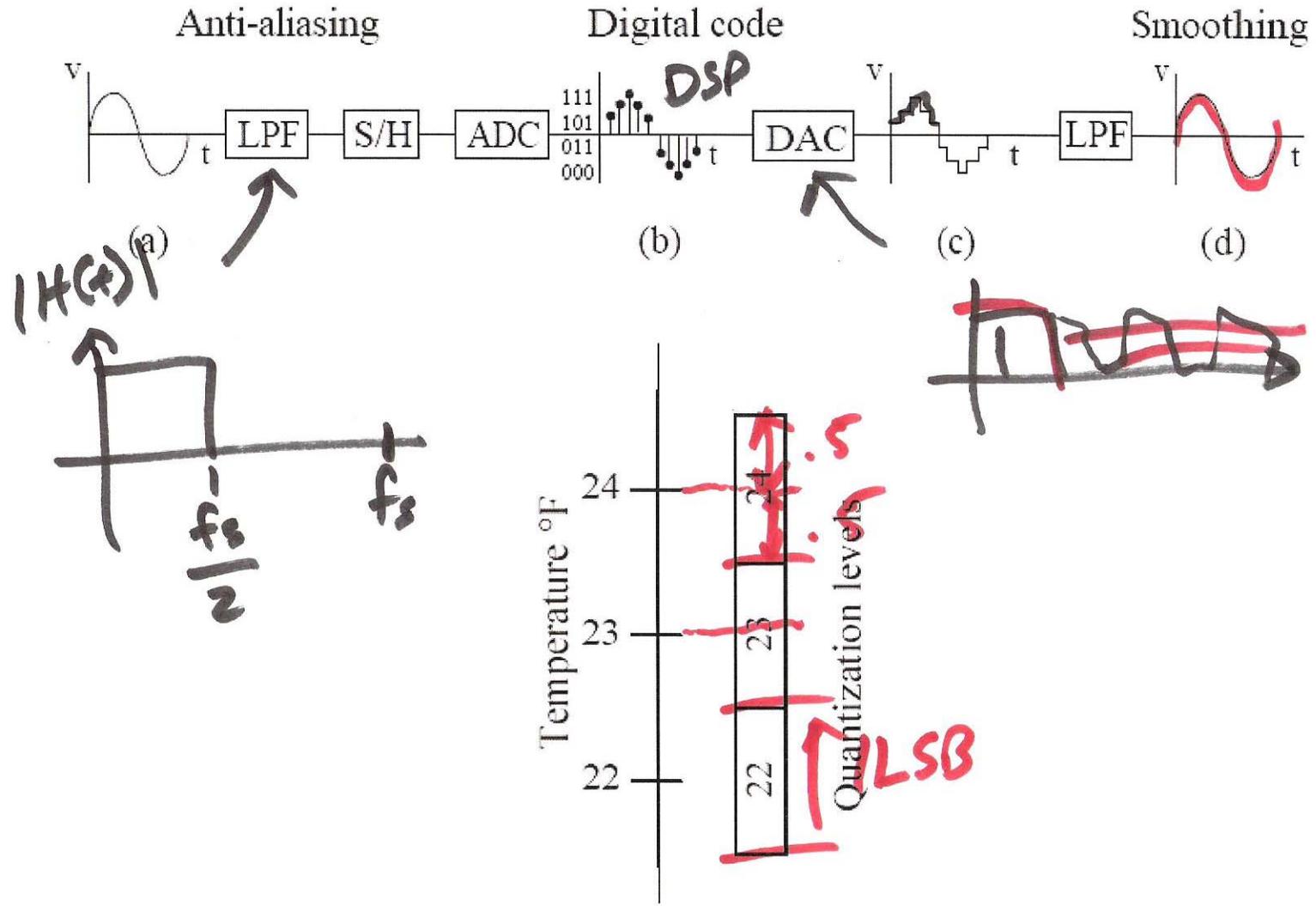


Figure 28.4 Quantization levels overlap actual temperature by $\pm \frac{1}{2}^\circ\text{F}$.

4)


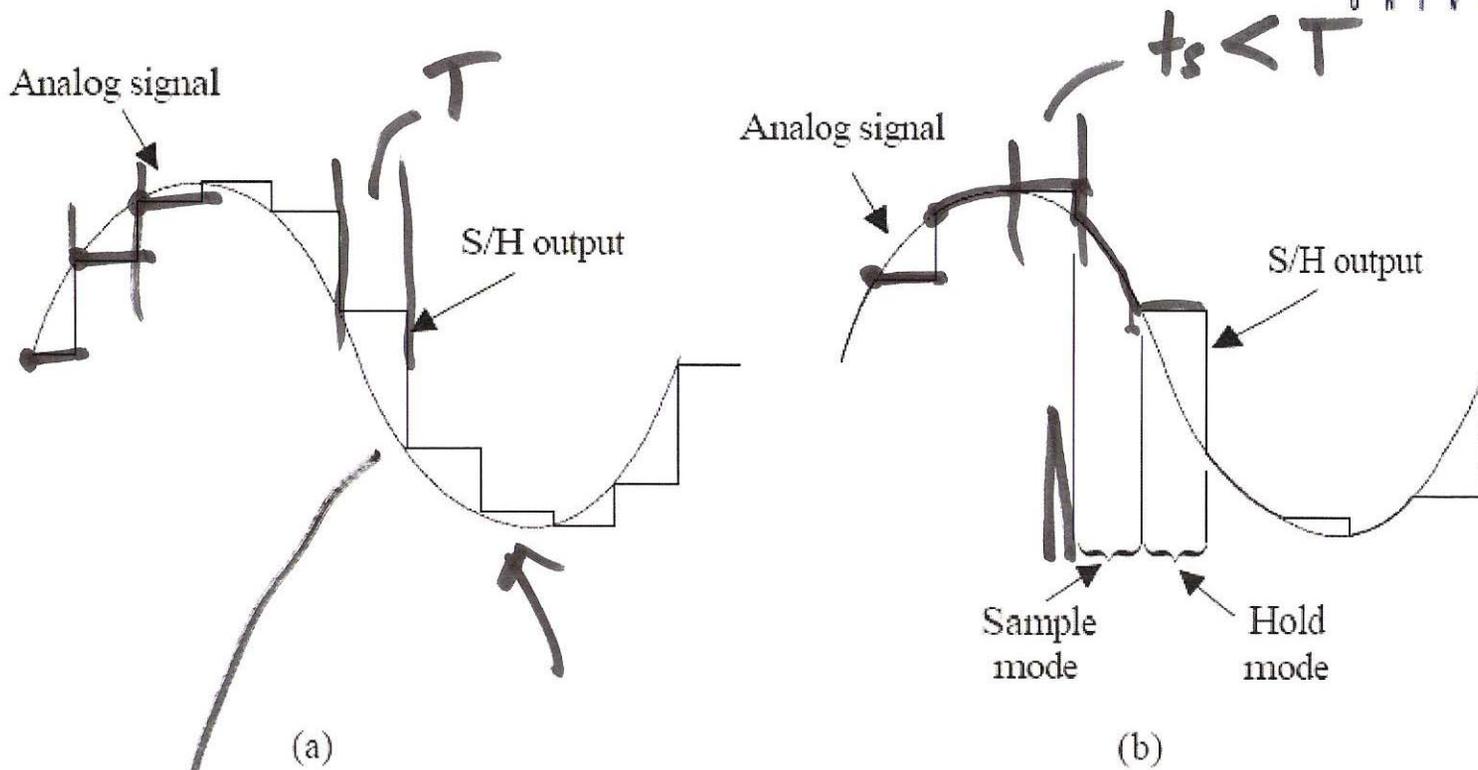



Figure 28.5 The output of (a) an ideal S/H circuit and (b) a track-and-hold (T/H).

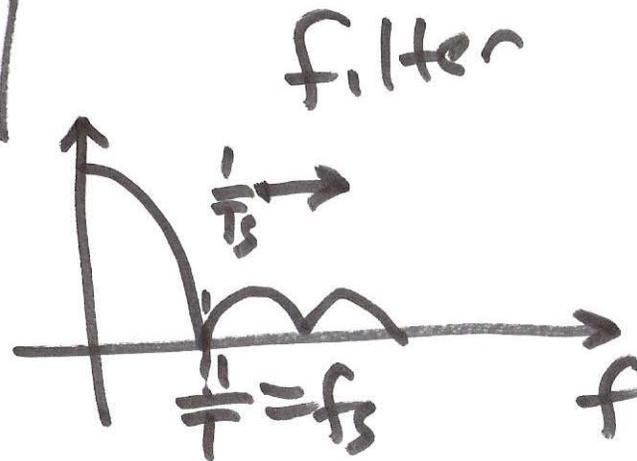


5)

TIMING jitter

Aperture Error

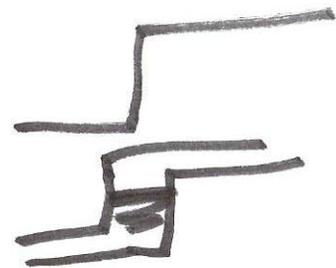

$$A \cdot \sin 2\pi f_{in} \cdot t$$

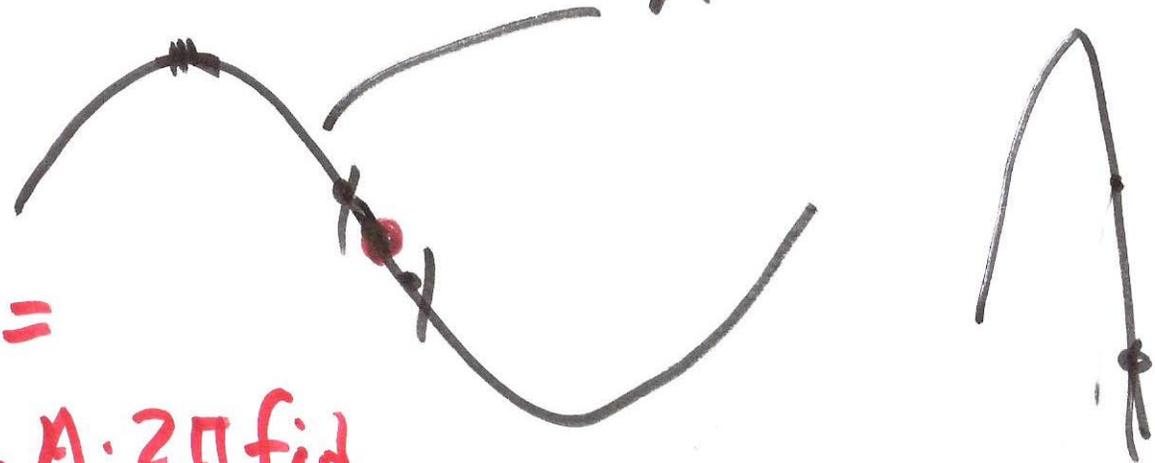

$$\Delta V =$$

$$\Delta t \cdot A \cdot 2\pi f_{in}$$

$$10 \text{ ps} \cdot 2 \cdot 2\pi \cdot 10^9$$

$$10^{-11} \cdot 10^9 \cdot 4\pi$$

$$10^{-2} \cdot 4\pi = \underline{\underline{125 \text{ mV}}}$$

$$\frac{d}{dt} A \sin 2\pi f_{in} \cdot t = A \cdot 2\pi f_{in} \cdot \cos 2\pi f_{in} \cdot t$$

$$\text{MAX error} = A \cdot 2\pi \cdot f_{in} = \frac{\Delta V}{\Delta t}$$


$$2 \cdot 2\pi \cdot 10$$

6)

$$\frac{001}{1000} \cdot V_{REF}$$

$$= 1 \text{ LSB}$$

$$= \frac{1}{8} V_{REF}$$

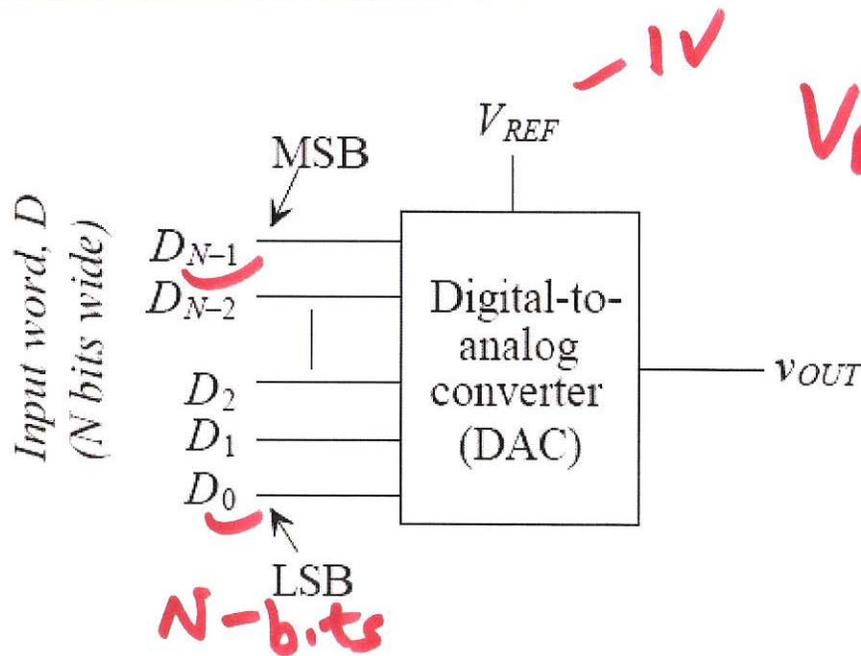


$$V_{REF} \cdot F = V_{REF} \cdot \frac{D}{2^N}$$

$$\frac{000}{1000} \cdot V_{REF} = 0$$

$$\frac{111}{1000} \cdot V_{REF} = \frac{7}{8} V_{REF}$$

Figure 28.9 Block diagram of the digital-to-analog converter.

$$\frac{V_{REF}}{2^N} = 1 \text{ LSB}$$

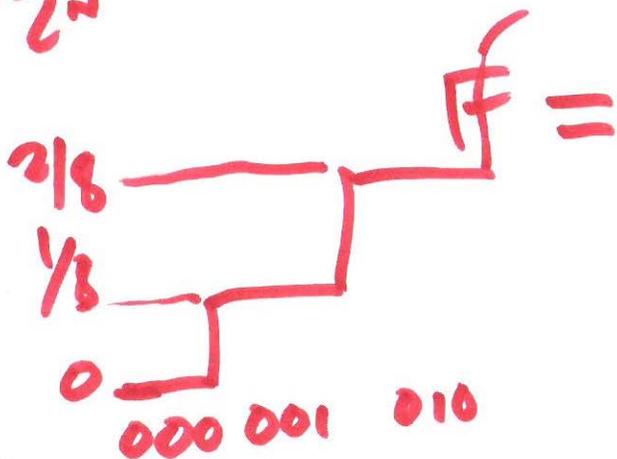

$$\frac{001}{8} \Rightarrow \frac{1}{8}$$

$$N=3$$

$$\frac{010}{8} \Rightarrow \frac{1}{4}$$

7)

$$V_{REF} = V_{REFP} - V_{REFM}$$

$$1 \text{ LSB} = \frac{V_{REFP} - V_{REFM}}{2^N}$$

MINIMUM DAC OUTPUT, all zeroes in,
 V_{REFM}

MAXIMUM DAC OUTPUT, all ones in,


$$V_{REF} - 1 \text{ LSB} = V_{REFP} - \frac{V_{REFP} - V_{REFM}}{2^N}$$

$$V_{REFP} = 900 \text{ mV} \quad 1 \text{ LSB} = 100 \text{ mV} = \frac{800 \text{ mV}}{8}$$

$$V_{REFM} = 100 \text{ mV} \quad N = 3 \text{ DAC}$$

$$\text{MAX OUTPUT} = 800 \text{ mV} \quad \text{min} = 100 \text{ mV} \quad 2^N$$

8)

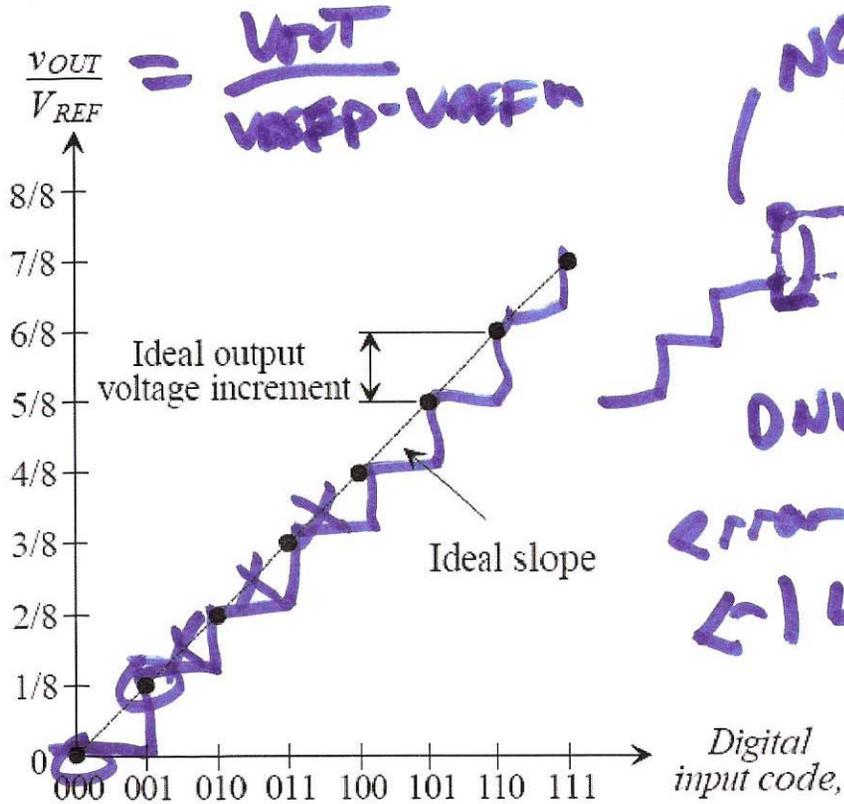

DAC

NOT MONOTONIC

DNL error ≤ 1 LSB

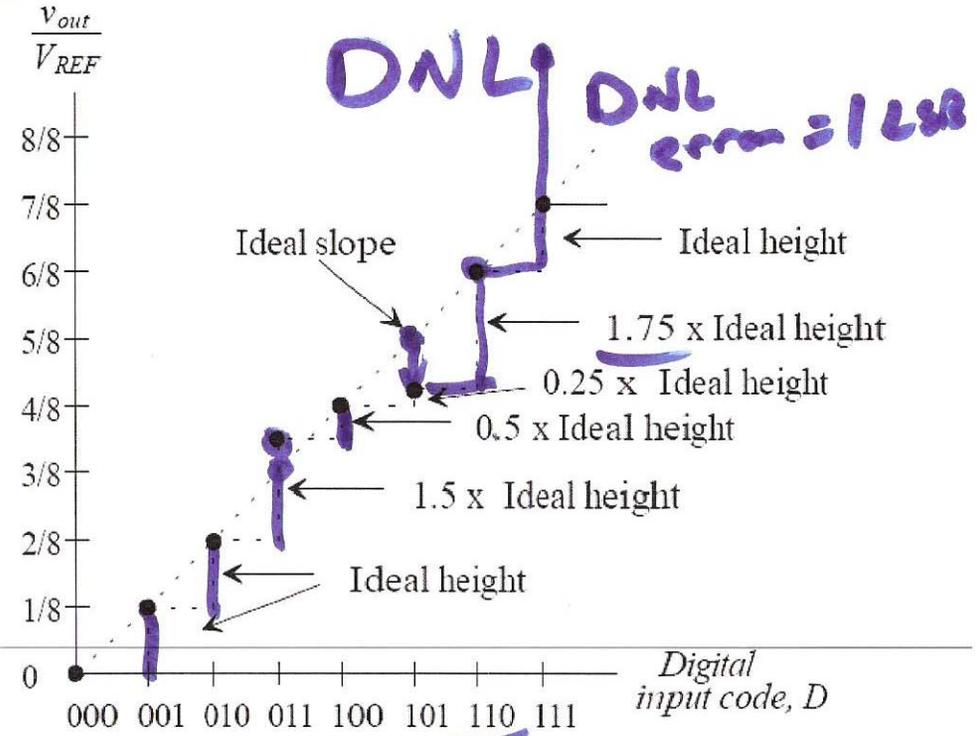


Figure 28.11 Example of differential nonlinearity for a 3-bit DAC.

Figure 28.10 Ideal transfer curve for a 3-bit DAC.

DNL error ≥ 1 LSB

DNL error < 1 LSB

DNL = -1 LSB or less for ADC has a missing code!

DC errors

9)

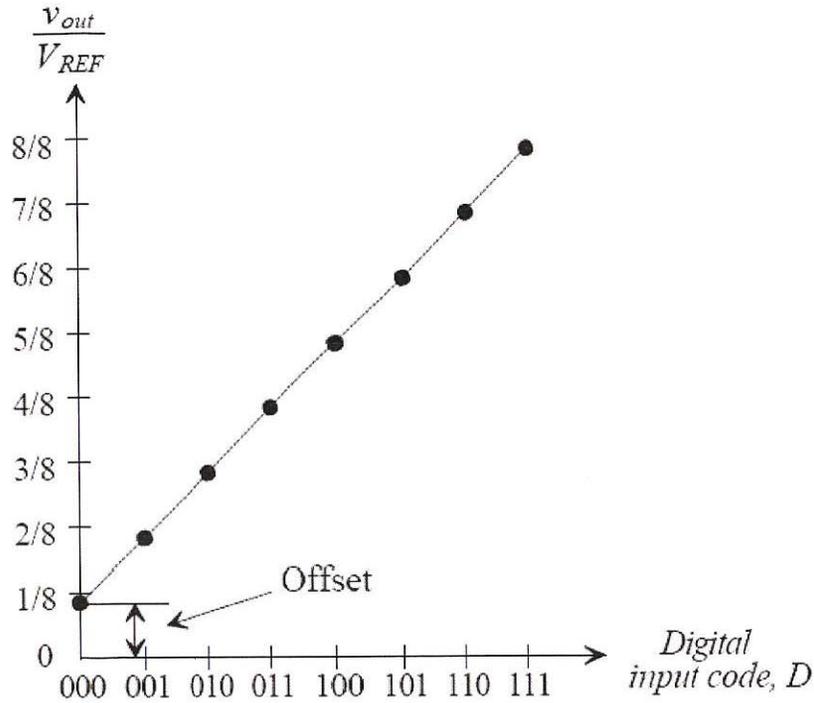


Figure 28.16 Illustration of offset error for a 3-bit DAC.

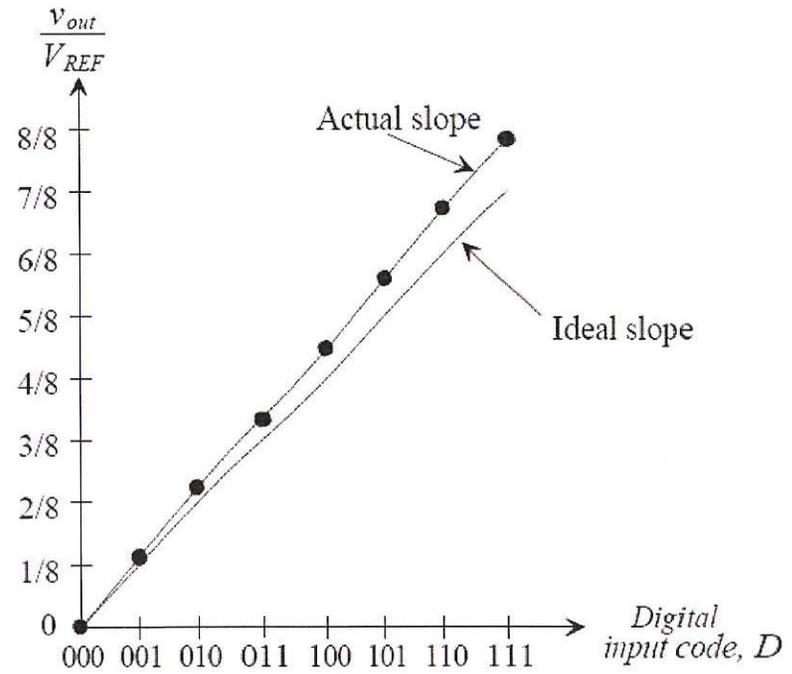


Figure 28.17 Illustration of gain error for a 3-bit DAC.

Integral Nonlinearity

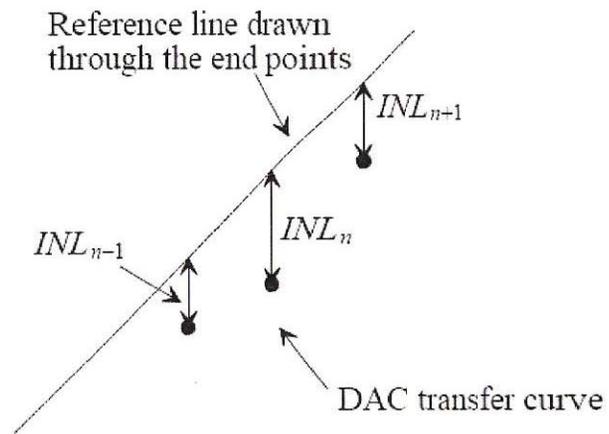


Figure 28.13 Measuring the INL for a DAC transfer curve.


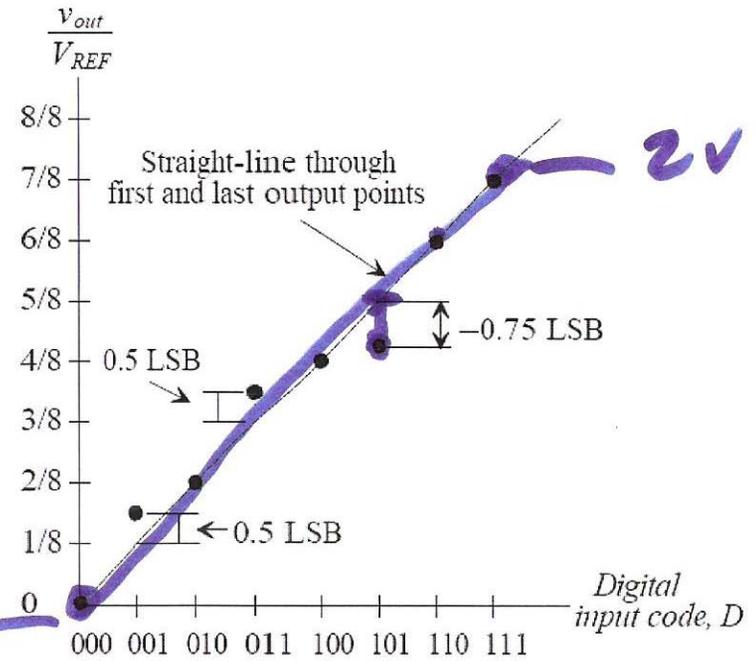


Figure 28.14 Example of integral nonlinearity for a DAC.

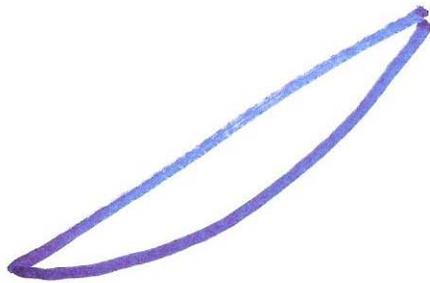

$$ax = y$$

$$ax + bx^2 = y$$

1

111

