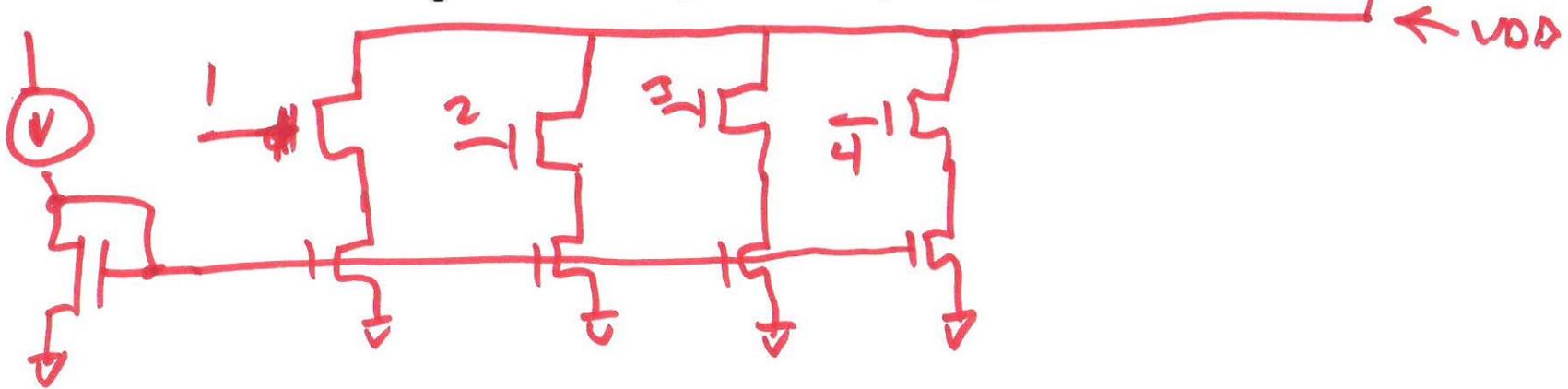


OCT. 20, 2011 LECTURE 17


DAC

Decimal	Binary	Thermometer	Gray	Two's Complement	
<u>0</u>	<u>000</u>	⁴³²¹ <u>0000000</u>	<u>000</u>	<u>000</u>	0 00
1	001	000000 <u>1</u>	001	111	-1
2	010	000001 <u>1</u>	011	110	-2
3	011	000011 <u>1</u>	010	101	-3
4	100	000111 <u>1</u>	110	100	-4
5	101	001111 <u>1</u>	111	011	3 3
6	110	011111 <u>1</u>	101	010	² VDD VDD
7	111	111111 <u>1</u>	100	001	1 1

Figure 29.1 Comparison of digital input codes.



1)

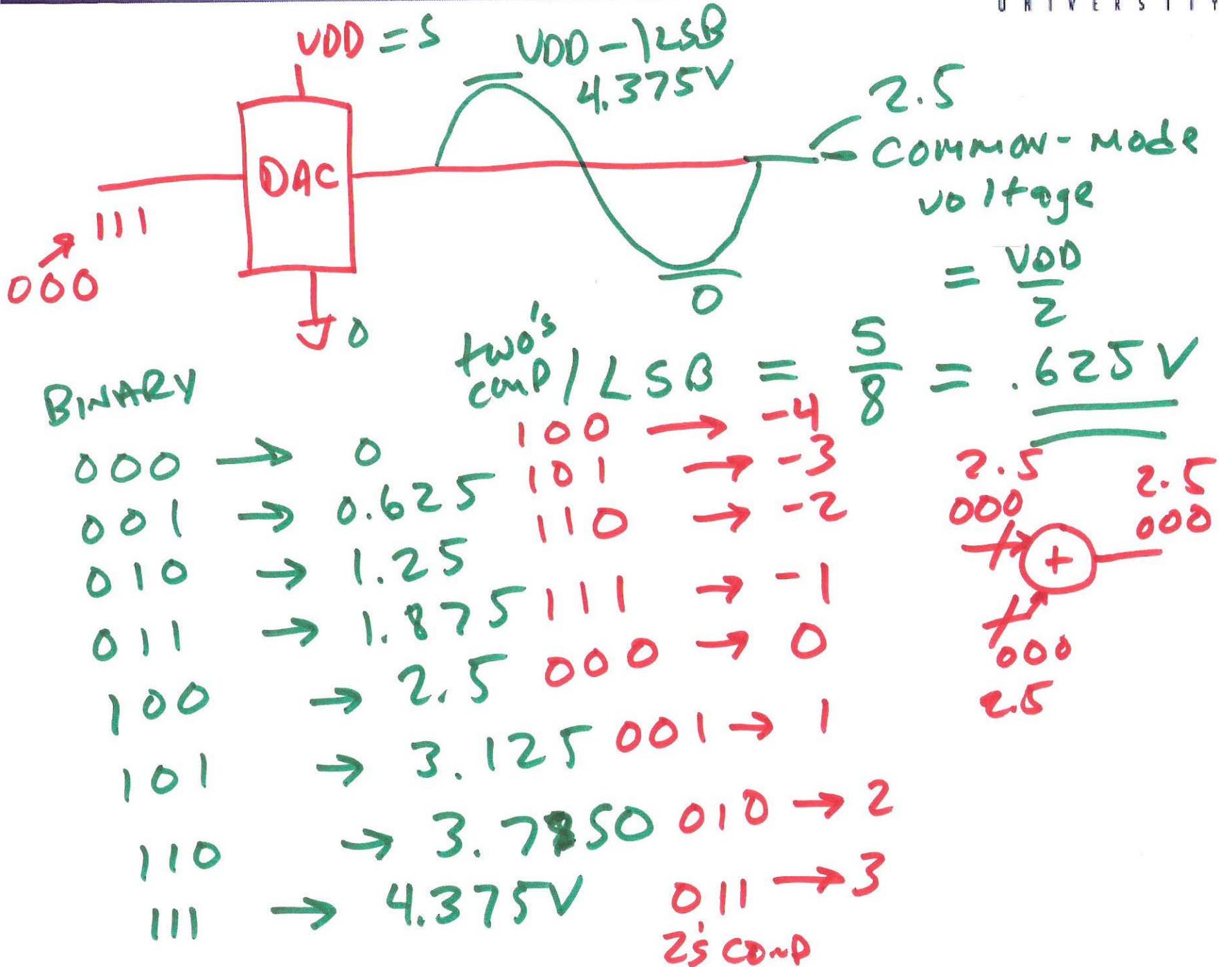

2)

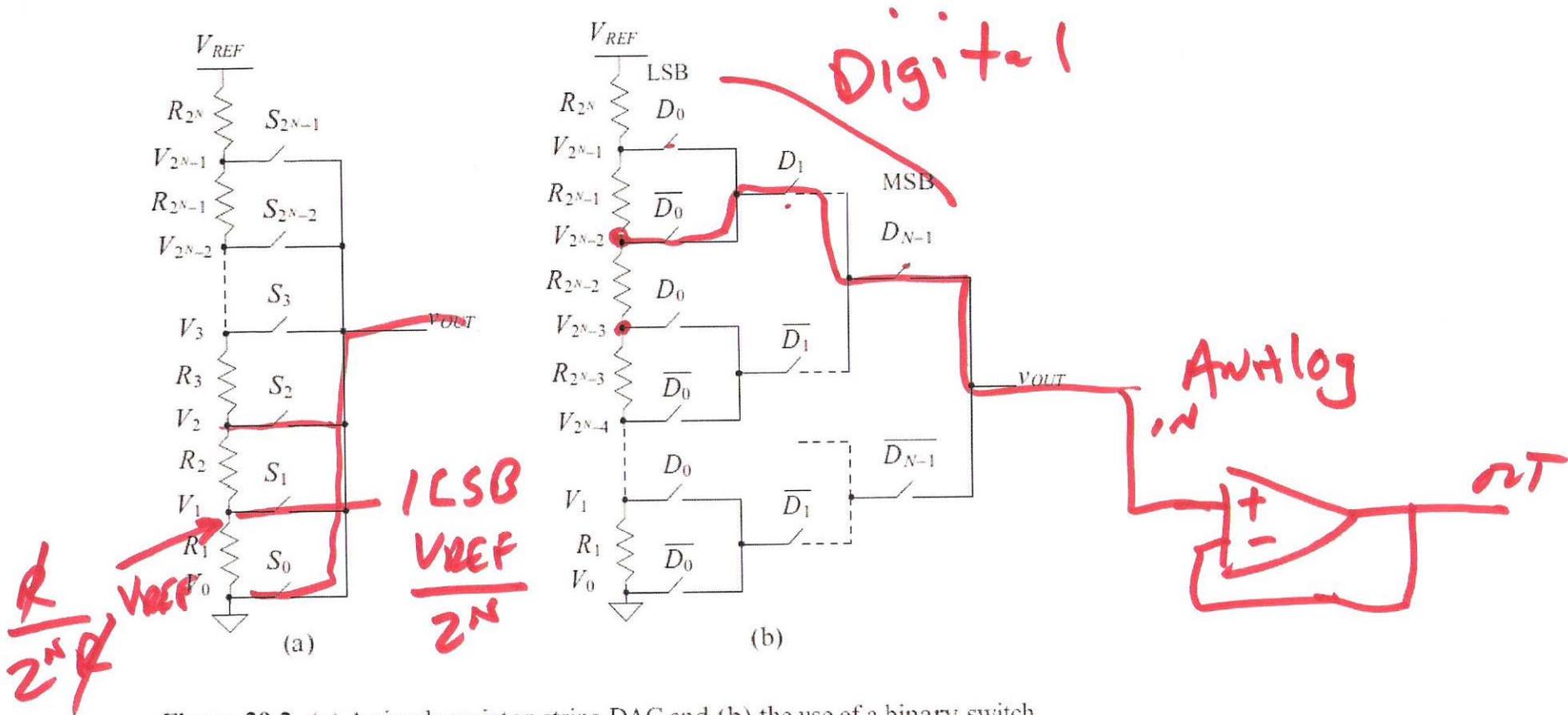


Figure 29.2 (a) A simple resistor-string DAC and (b) the use of a binary switch array to lower the output capacitance.

3)

$D_2D_1D_0$	v_{OUT}
000	0
001	0.625
010	1.25
011	1.875
100	2.5
101	3.125
110	3.75
111	4.375


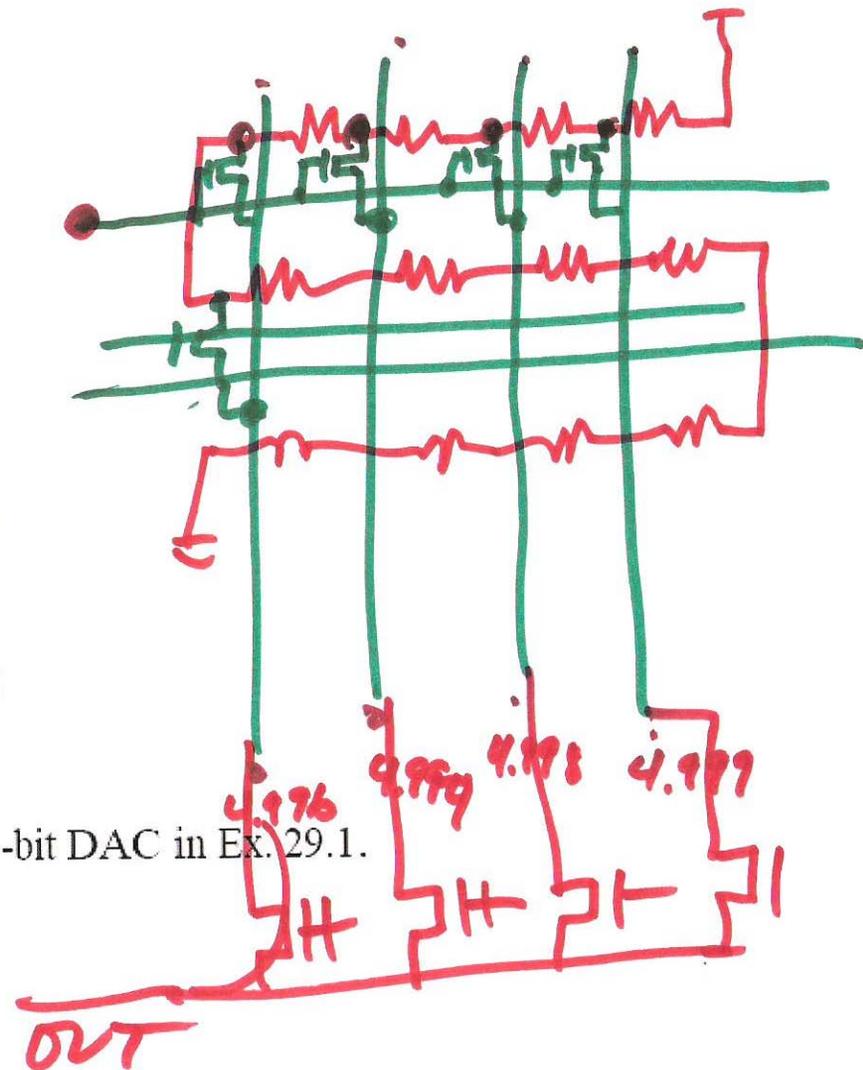


Figure 29.4 Output voltages generated from the 3-bit DAC in Ex. 29.1.

4)



traditional

CURRENT-MODE
R-2R
DAC

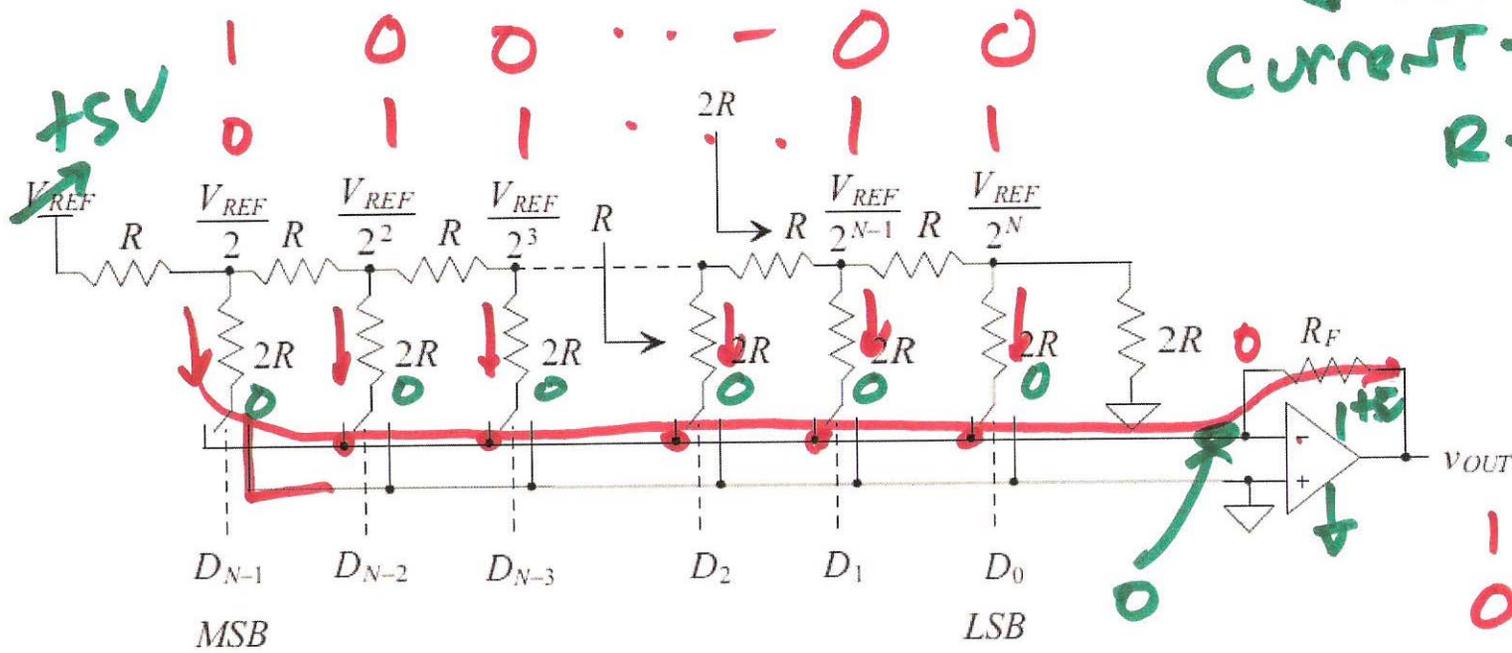

10000
01111

Figure 29.5 An R-2R digital-to-analog converter.

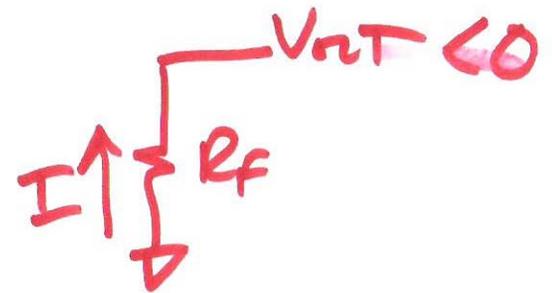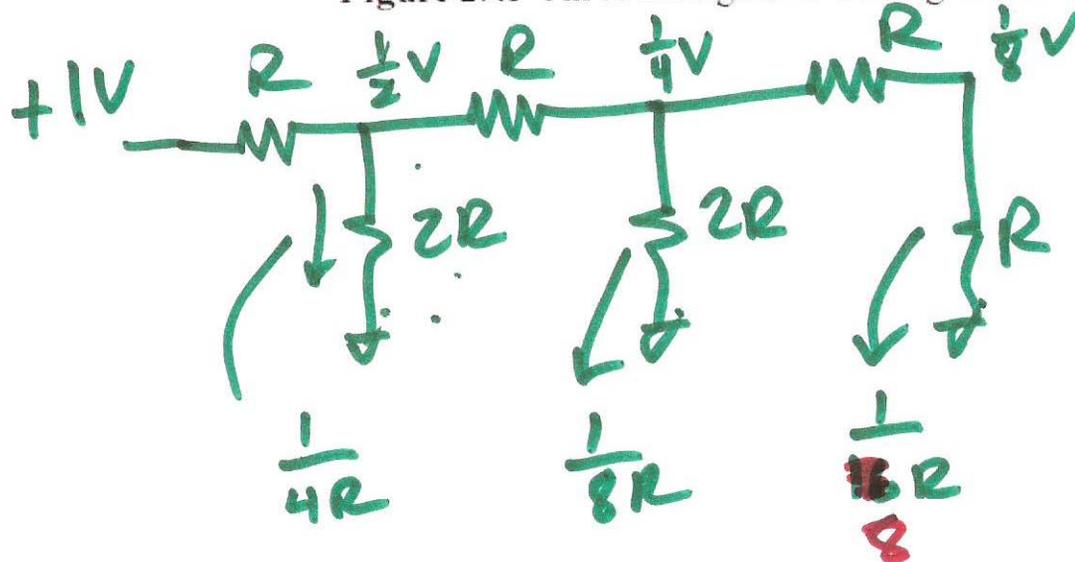

5)


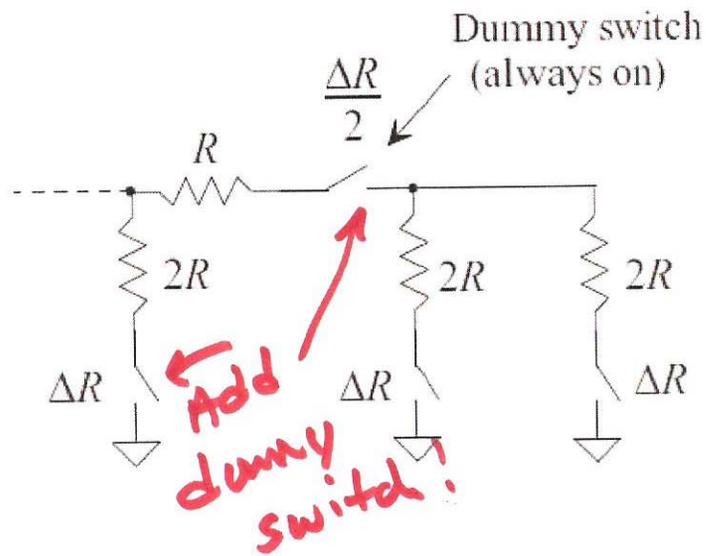
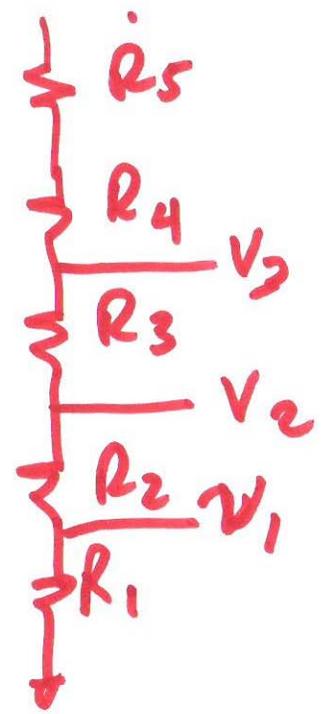
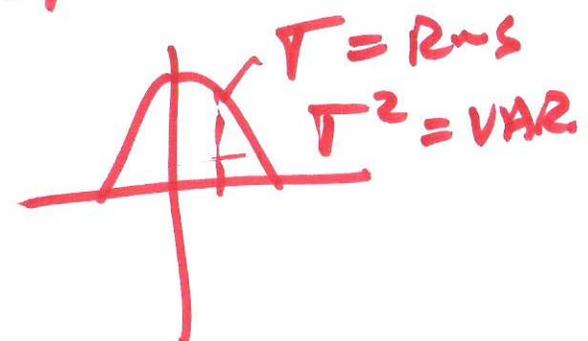


Figure 29.6 Use of dummy switches to offset switch resistance.

6)

Matching

Resistor string, Page 967

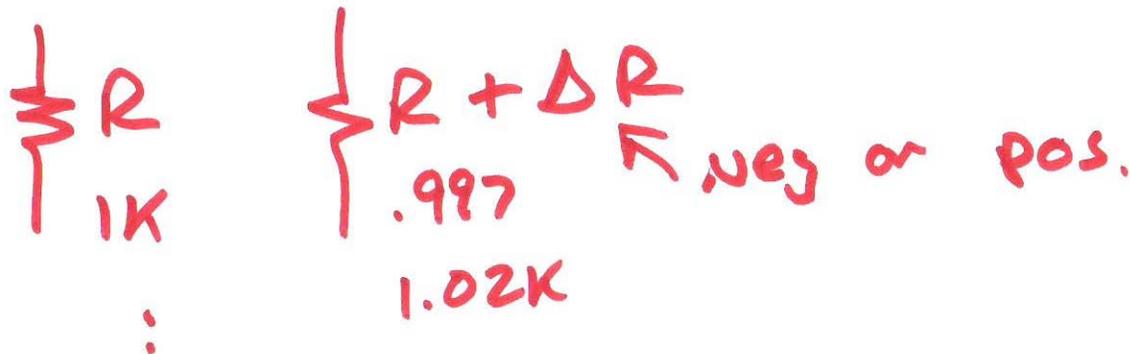

$$R_i = R + \Delta R_i$$

$$\sum_{i=1}^{2^N} \Delta R_i = 0$$

$$\frac{1}{2^N} \sum_{i=1}^{2^N} R_i = R$$

$$V_i = V_{REF} \cdot \frac{\sum_{k=1}^i R + \Delta R_k}{2^N \cdot R}$$

7)

$$V_i = V_{REF} \cdot \sum_{k=1}^i (R + \Delta R_k)$$

$$2^N \cdot R$$

2% mismatch

$$= \frac{V_{REF}}{2^N} \cdot \left[\sum_{k=1}^i \frac{R}{R} + \sum_{k=1}^i \frac{\Delta R_k}{R} \right]$$

1 LSB

$$.02R \leq \Delta R \leq .02R$$

Overall = $\underbrace{1 \cdot \text{LSB} \cdot (i)}_{\text{ideal output } V_{i, \text{ideal}}}$ +

$$1 \text{ LSB} \cdot \sum_{k=1}^i \frac{\Delta R_k}{R}$$

1%
1k
 $\Delta R = 10$

$\frac{\Delta R}{R} = \frac{10}{1000}$
Mismatch
 $= 0.01 = 1\%$

8)

INL


$$i = 256 = V_i - V_{i,ideal}$$

$$N = 8 \quad 2^8$$

$$i = 1 \rightarrow i = 256$$

$$i \cdot 1\text{LSB} = i \cdot \frac{V_{REF}}{2^N}$$
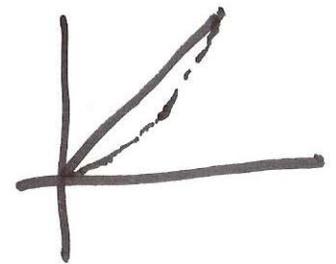
$$INL = \frac{V_{REF}}{2^N} \cdot \sum_{k=1}^N \frac{\Delta R_k}{R}$$



Worst INL occurs when
 $i = \frac{2^N}{2} = 2^{N-1}$

$$< \frac{i}{2} \rightarrow \frac{\Delta R}{R} = -0.01$$

$$> \frac{i}{2} \rightarrow \frac{\Delta R}{R} = +0.01$$

$$INL_{max} = \frac{V_{REF}}{2^N} \sum_{k=1}^{2^N-1} \frac{\Delta R_k}{R}$$

$\frac{1}{2^N} \gg$ Mismatch %

$$= \frac{V_{REF}}{2^N} \cdot 2^{N-1} \cdot \frac{\Delta R_k}{R}$$

1% \rightarrow $\frac{1}{2^N}$
 .01 \rightarrow $\frac{1}{2^N}$
 $N \rightarrow 6\text{bit}$

for $< \frac{1}{2} \text{ LSB}$ INL \rightarrow $\frac{1}{2} \text{ LSB} \cdot 2^N (\% \text{ mismatch})$

$\% \text{ mismatch} \ll \frac{1}{2^N}$

$N = 10$ $\% \text{ mismatch} \ll \frac{1}{1000} = .1\%$

$.02 \gg \frac{1}{2^N}$, $N = 5$ $\% \text{ mismatch}$

10)

DNL

$$V_i - V_{i-1} = 1 \text{ LSB} \left[1 + \frac{\Delta R_i}{R} \right]$$

$$\text{DNL}_i = 1 \text{ LSB} \cdot \frac{\Delta R_i}{R}$$

← DNL
is
good!

-J

11)

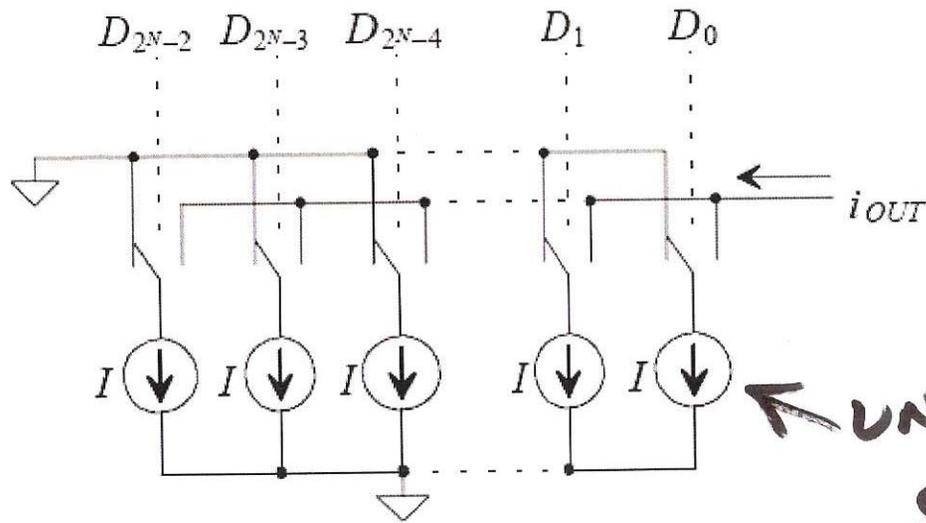


Figure 29.9 A generic current steering DAC.

12)

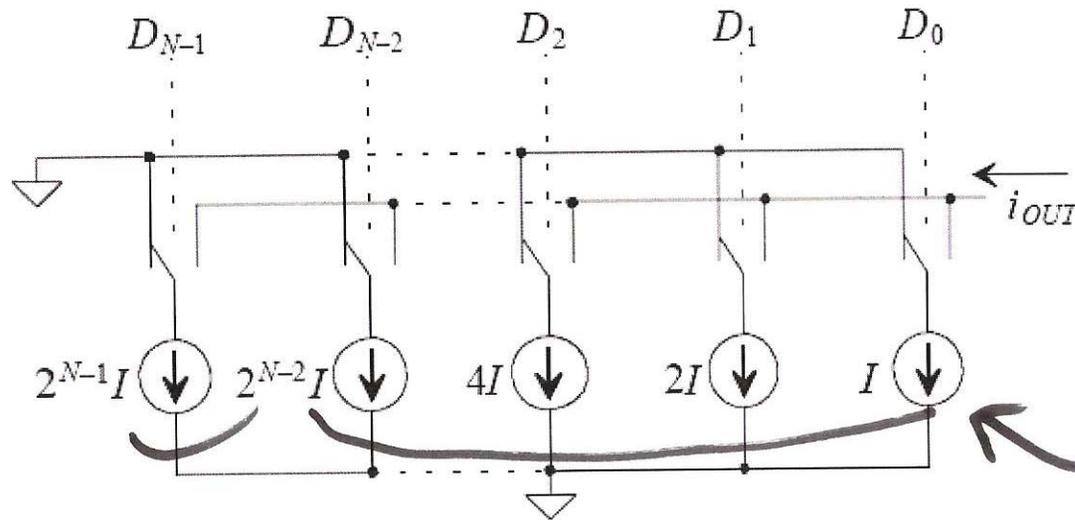


Figure 29.10 A current steering DAC using binary-weighted current sources.

Binary weighted DAC

Smaller AREA

potential for

LARGE

DNV!

13)