

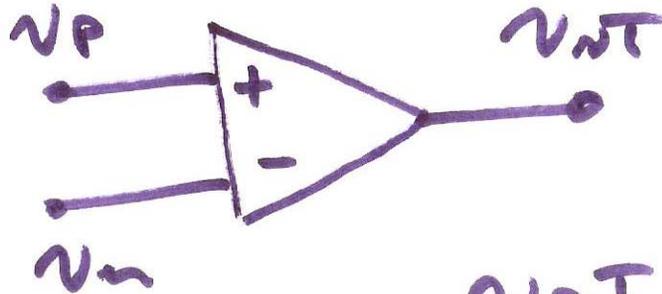


Feed back Cl. 31


SEC. 30.2

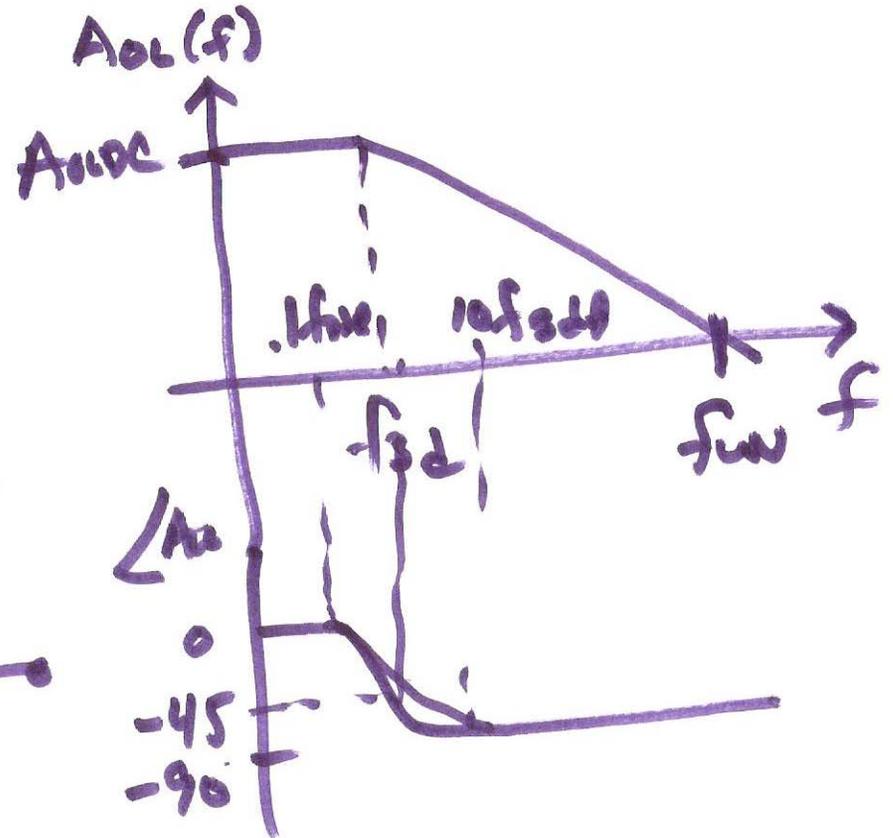

$$A_{OL}(f) = \frac{v_o}{v_p - v_m}$$

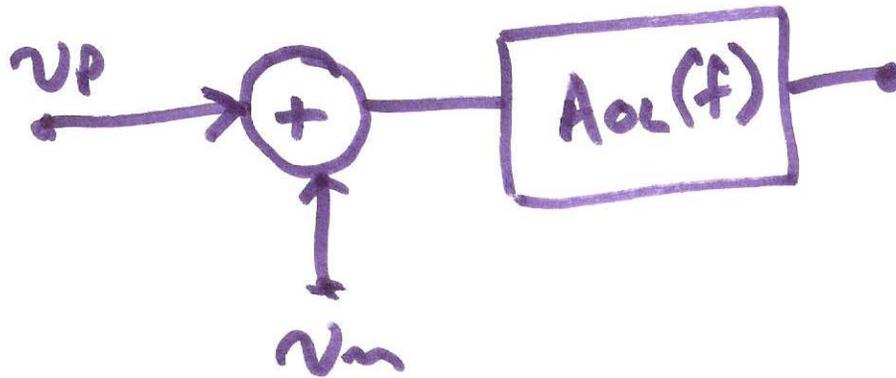

1)

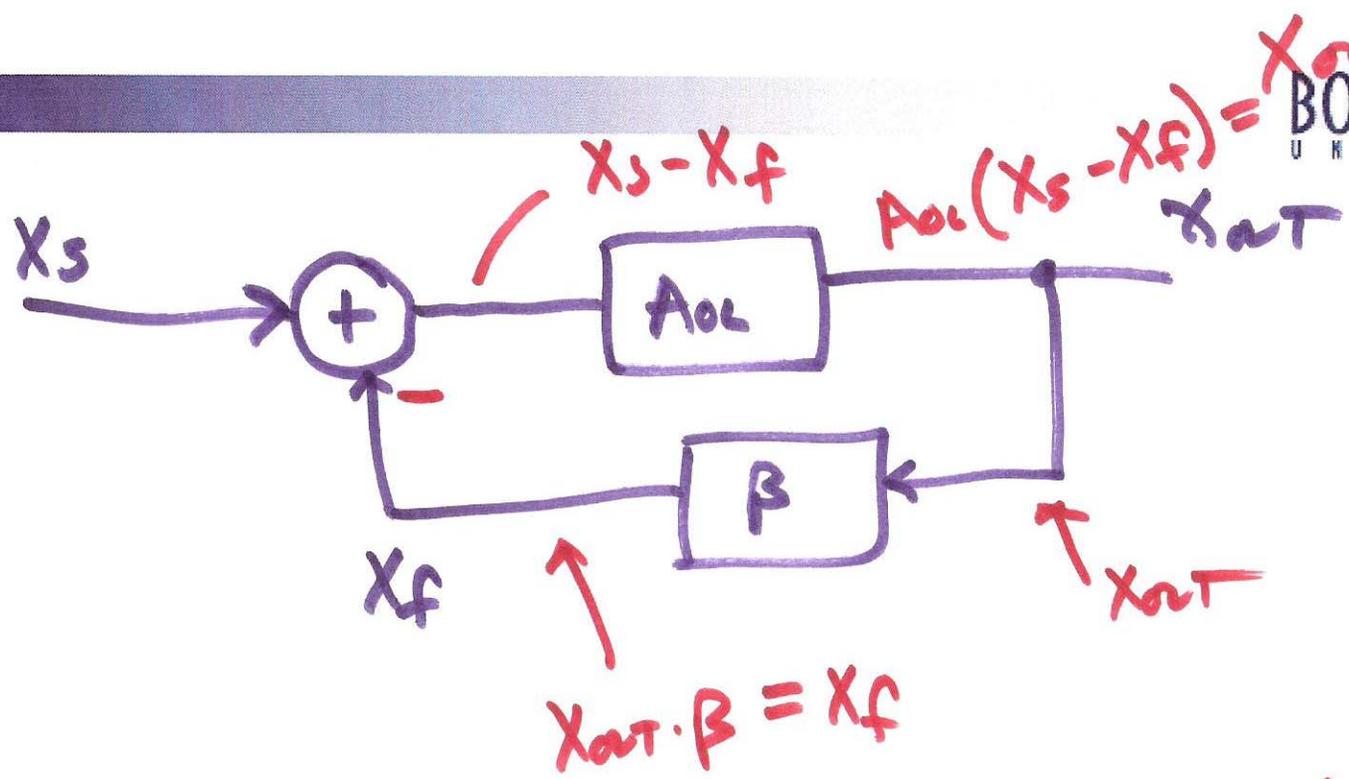

$$X_{out} = A_{ol} (X_s - X_{out} \cdot \beta)$$

$$A_{CL} = \frac{X_{out}}{X_s} = \frac{A_{ol}}{1 + A_{ol} \cdot \beta}, \quad A_{ol} \rightarrow \infty$$

$$A_{CL} \approx \frac{1}{\beta}$$


2)

# NON-INVERTING Amp

$$V_{in} = X_s$$

Voltage - Amp info -

SERIES - SHUNT

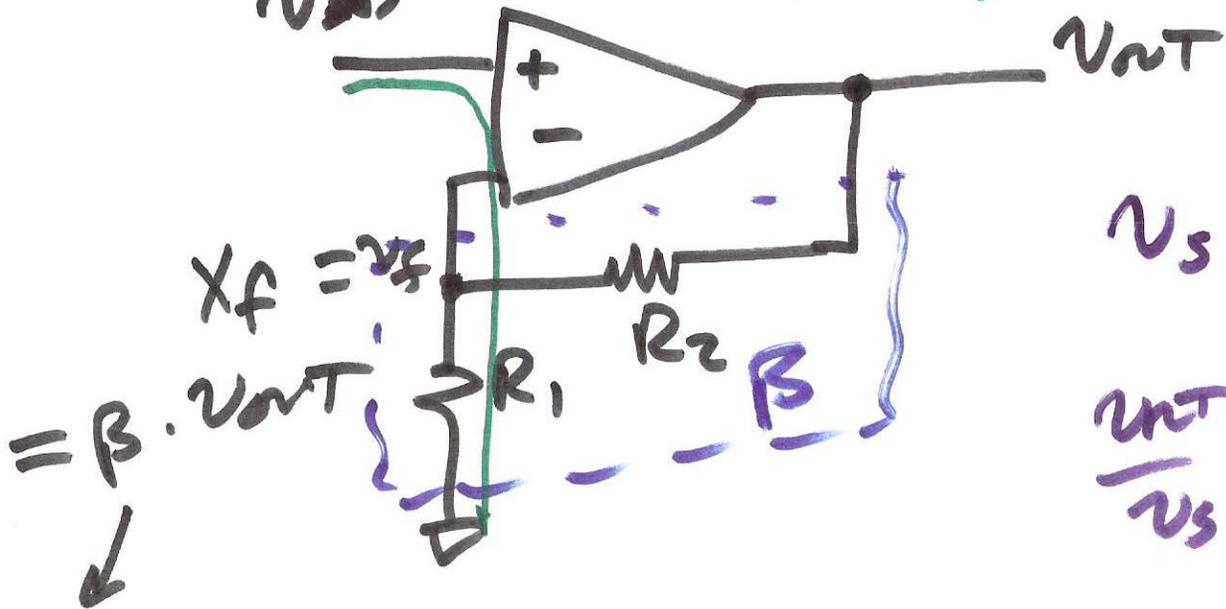

$$V_s = V_{out} \cdot \frac{R_1}{R_1 + R_2}$$

$$\frac{V_{out}}{V_s} = 1 + \frac{R_2}{R_1}$$


$$= \beta \cdot V_{out}$$

$$\downarrow$$

$$\frac{R_1}{R_1 + R_2}$$

SERIES - SHUNT

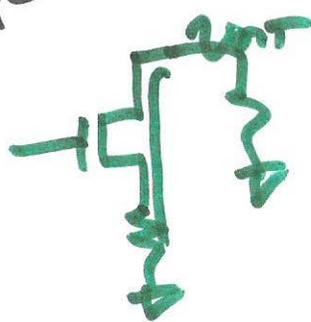
$$A_{CL} \approx \frac{1}{\beta} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$



INPUT SERIES - VOLTAGE - SHUNT  
SHUNT - CURRENT - SERIES


3)

# Inverting Amplifier

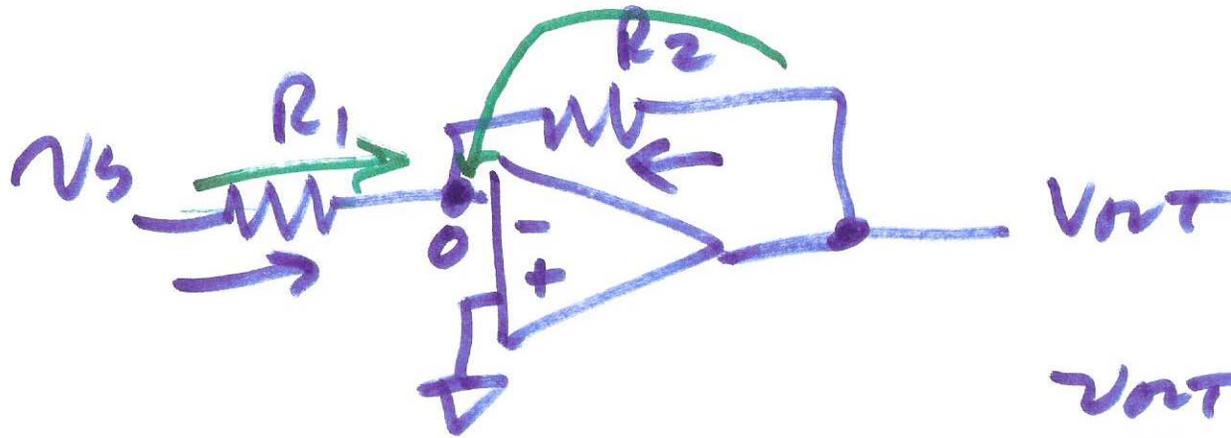

$$\frac{v_{OUT}}{v_s} = -\frac{R_2}{R_1}$$
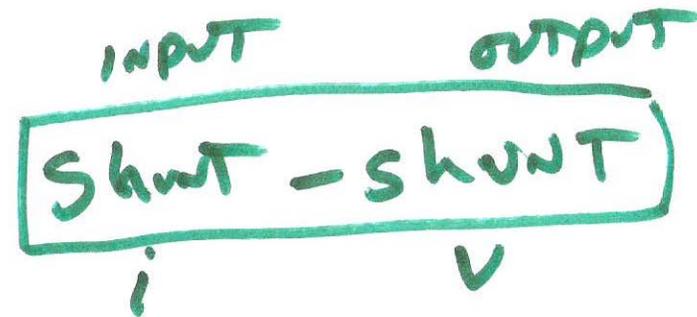
$$\frac{v_s}{R_1} + \frac{v_{OUT}}{R_2} = 0$$




$$-R_2 = A_{CL} = \frac{v}{i} = \text{transimpedance}$$

$$\frac{v_s}{R_1}$$

4)

# Transimpedance Amp

for a photodiode

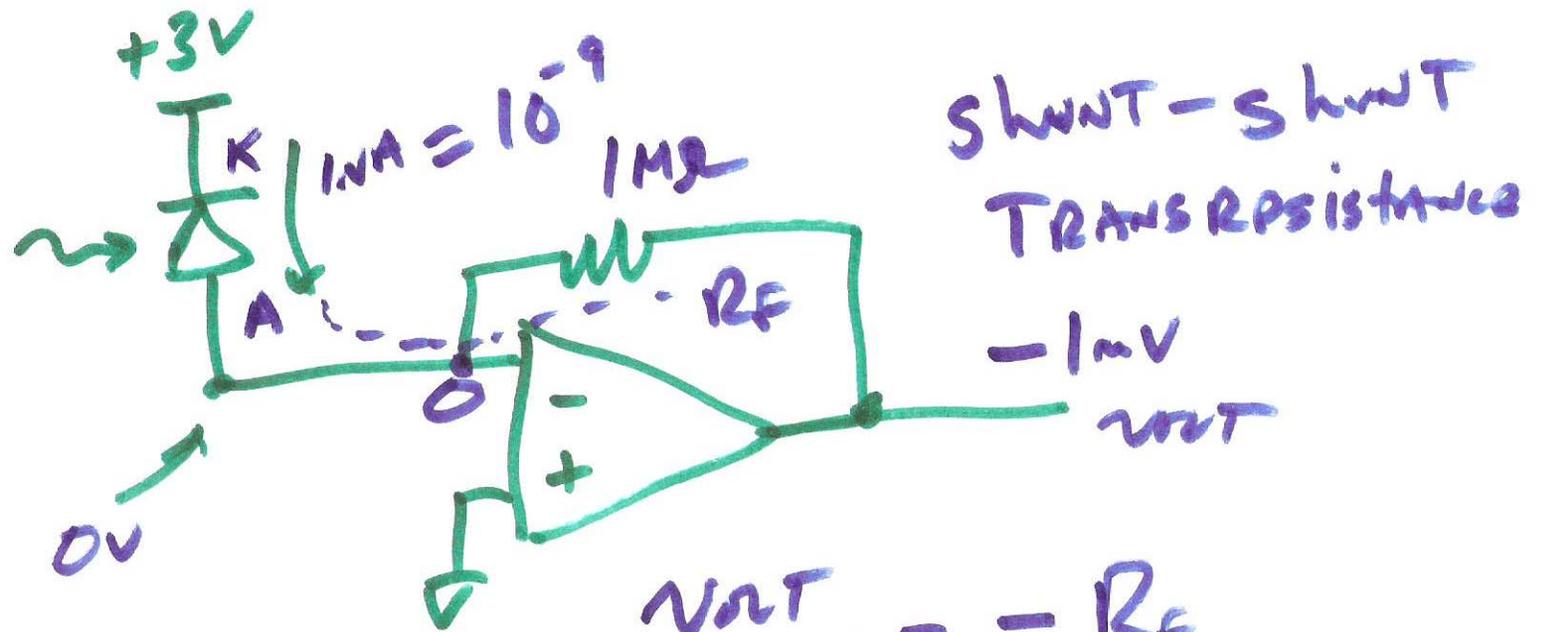


de bias is bad

$$\frac{V_{out}}{i_s} = -R_f$$


$$\begin{aligned} V_{out} &= -R_f \cdot i_s \\ &= -10^6 \cdot 10^{-9} \\ &= \underline{\underline{-1mV}} \end{aligned}$$

s)

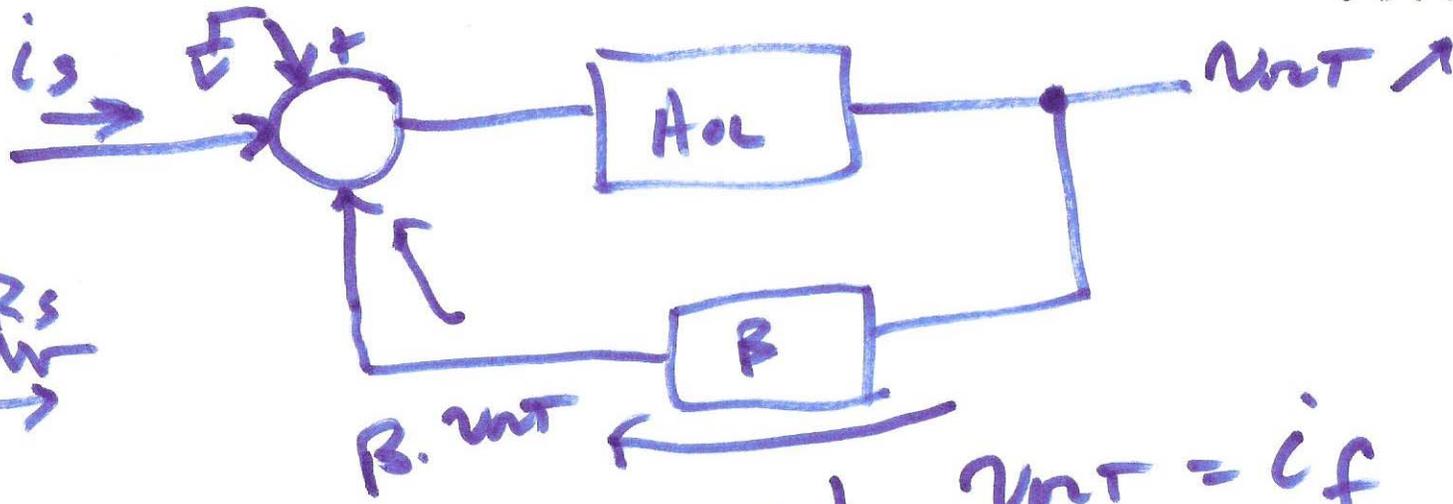


$$\frac{v_s}{R_s} \rightarrow$$

$i_d$

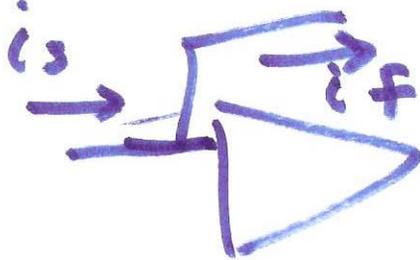


$$-\frac{1}{R_F} \cdot v_{out} = i_f$$

6)

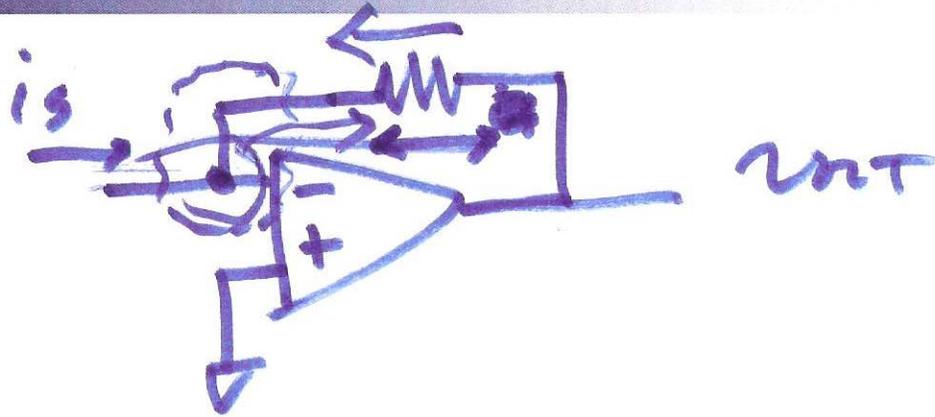



$$A_{CL} = \frac{1}{\beta}$$

ideal

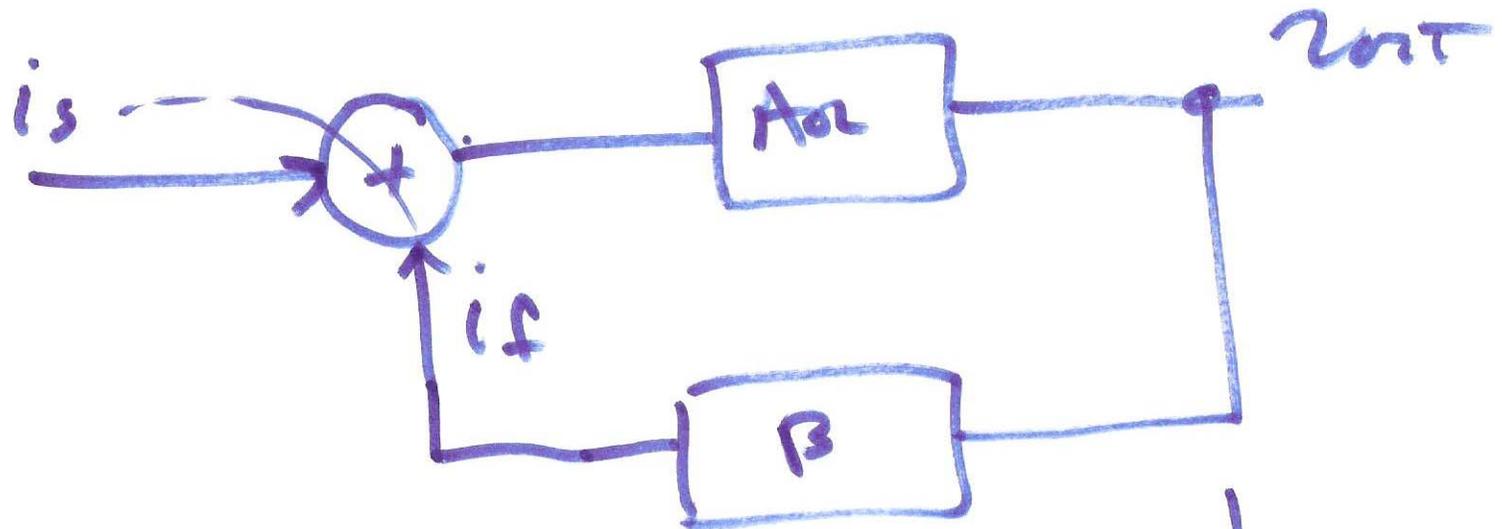


$$i_s = \frac{v_{out}}{\beta} = -i_f \Rightarrow \beta = -\frac{1}{R_2}$$

7)

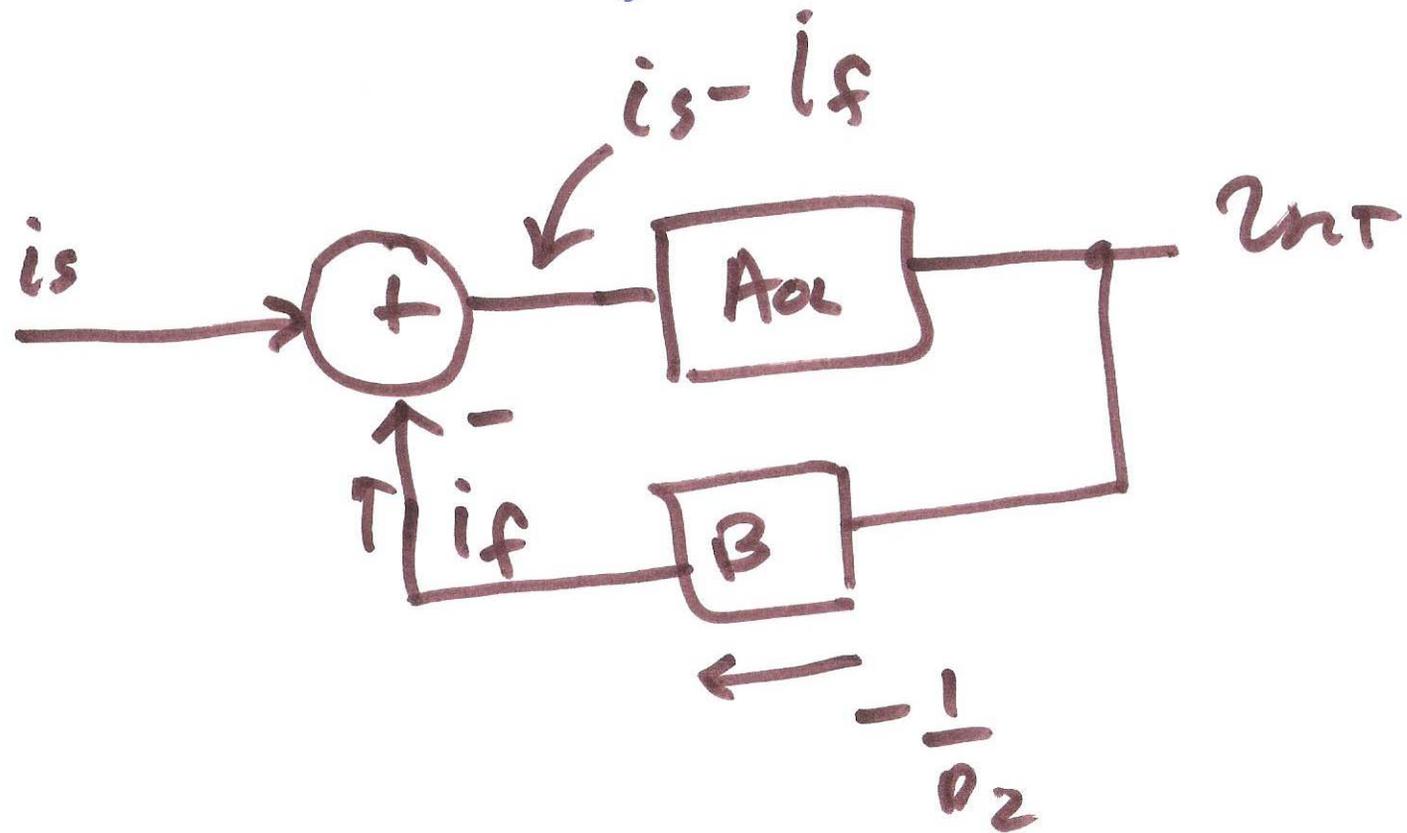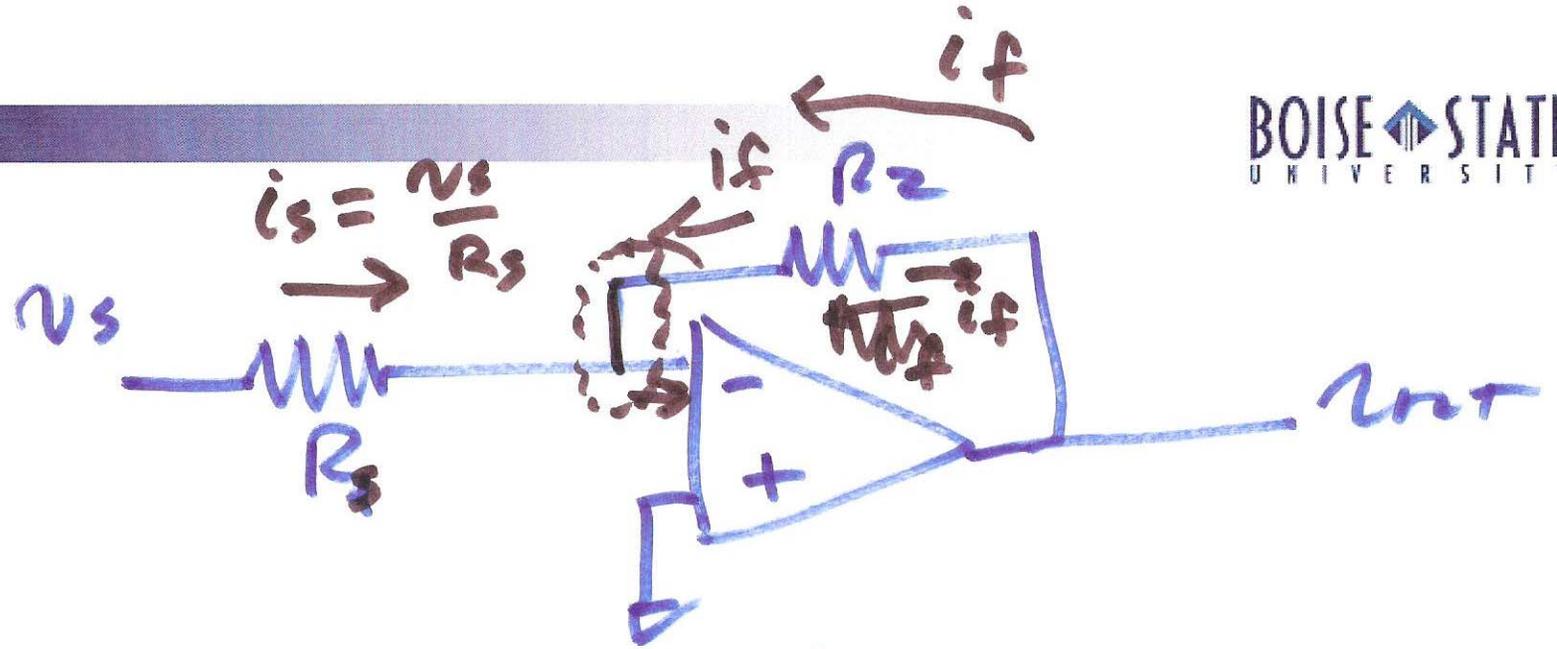

8)

# Non-Inverting

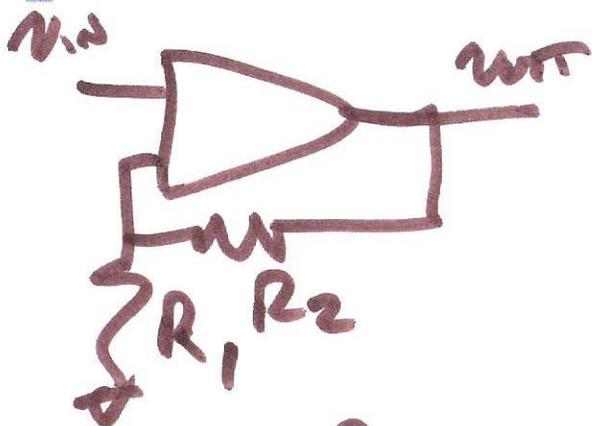


$$\beta = \frac{R_1}{R_1 + R_2}$$

$$A_{OL} = \frac{A_{OLDC}}{1 + j \frac{f}{f_{3dB}}}$$

$$f \gg f_{3dB}$$
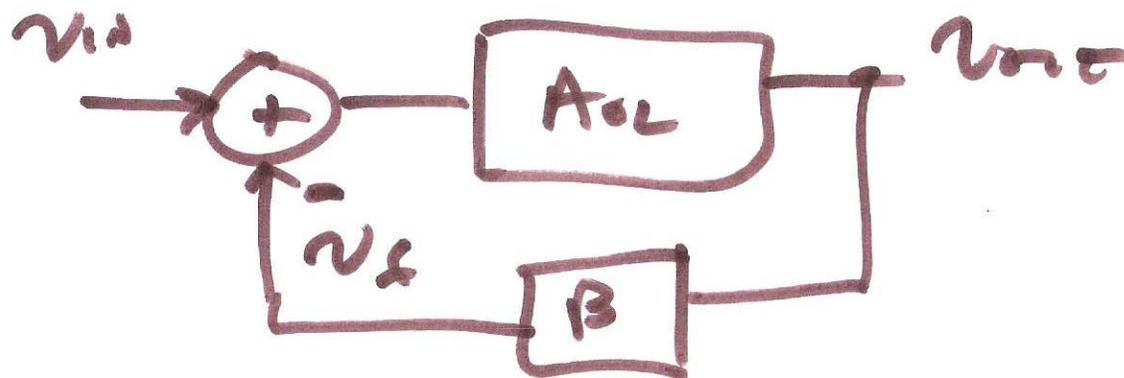
$$A_{OL} \approx \frac{1}{j \cdot \frac{f}{f_{3dB}}}$$



$$A_{CL} = \frac{A_{OL}}{1 + \beta \cdot A_{OL}}$$

$$|A_{OL}| = \frac{f_{3dB}}{f}$$

100 MHz

$$f_{3dB} = f_{3dB} \cdot A_{OLDC}$$



9)

$$A_{cl}|_{DC} = \left(1 + \frac{R_2}{R_1}\right) = \frac{1}{\beta}, f_{un}$$

$$1 + \frac{R_1}{R_2}$$

$$A_{cl}(f) = \frac{f}{f_{un}} + \beta$$

$f \gg f_{3dB}$

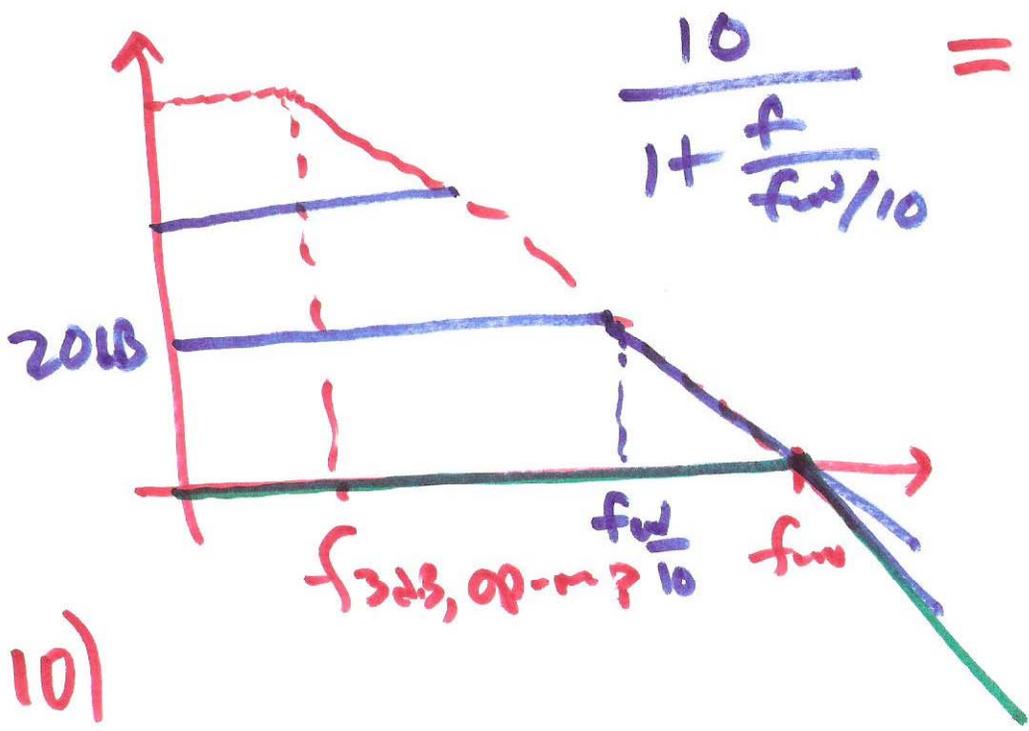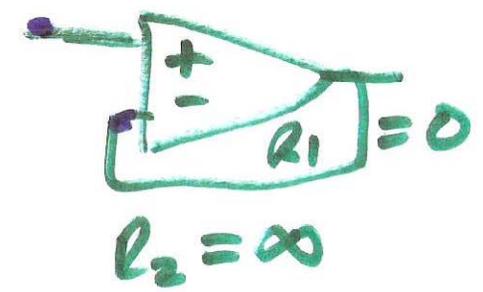

$$\frac{10}{1 + \frac{f}{f_{un}/10}} =$$

$$\frac{1}{\beta} \frac{1}{1 + \frac{f}{f_{un}\beta}}$$

$A_{cl}|_{DC}$




$$= \frac{1}{1 + \frac{f}{f_{un}/A_{cl}'}}$$



10)

# INVERTING topology

$$A_{CL} = \frac{1}{\beta}$$

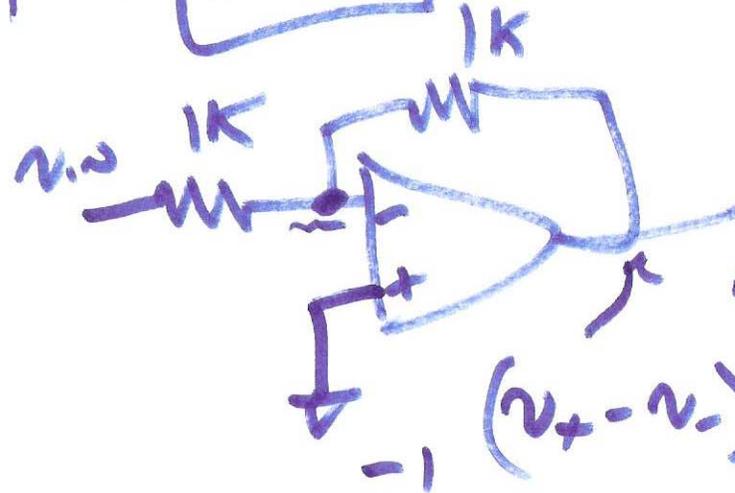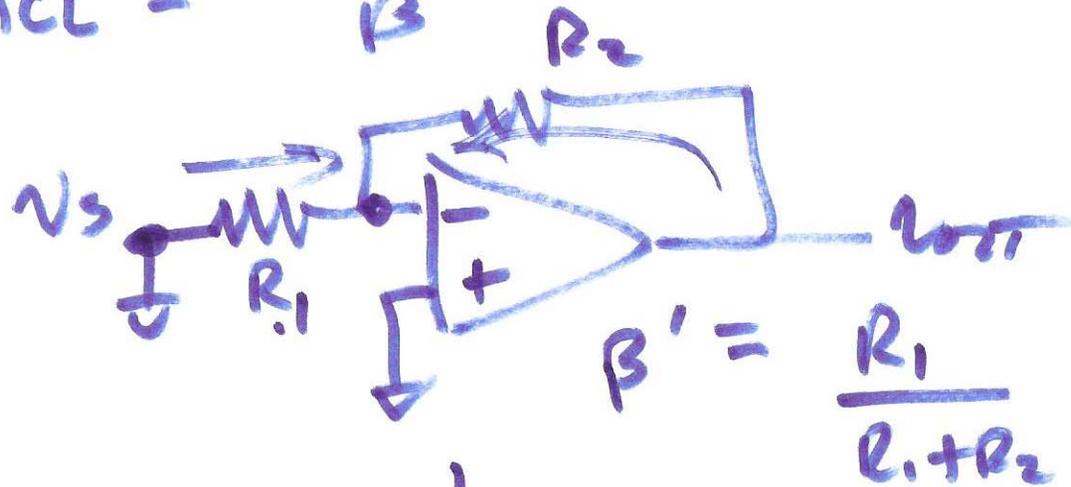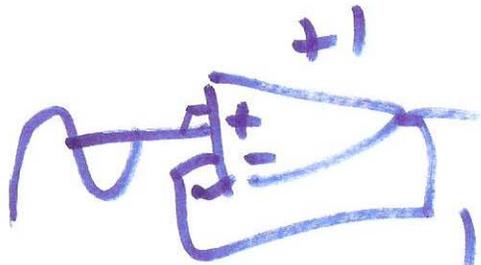

$$A_{CL} = \frac{\frac{1}{\beta'}}{1 + \frac{f}{\text{gain} \cdot \beta'}}$$

$$A_{CL} \Big|_{\text{inverting}} = \frac{1}{\beta} = -R_2$$

11)