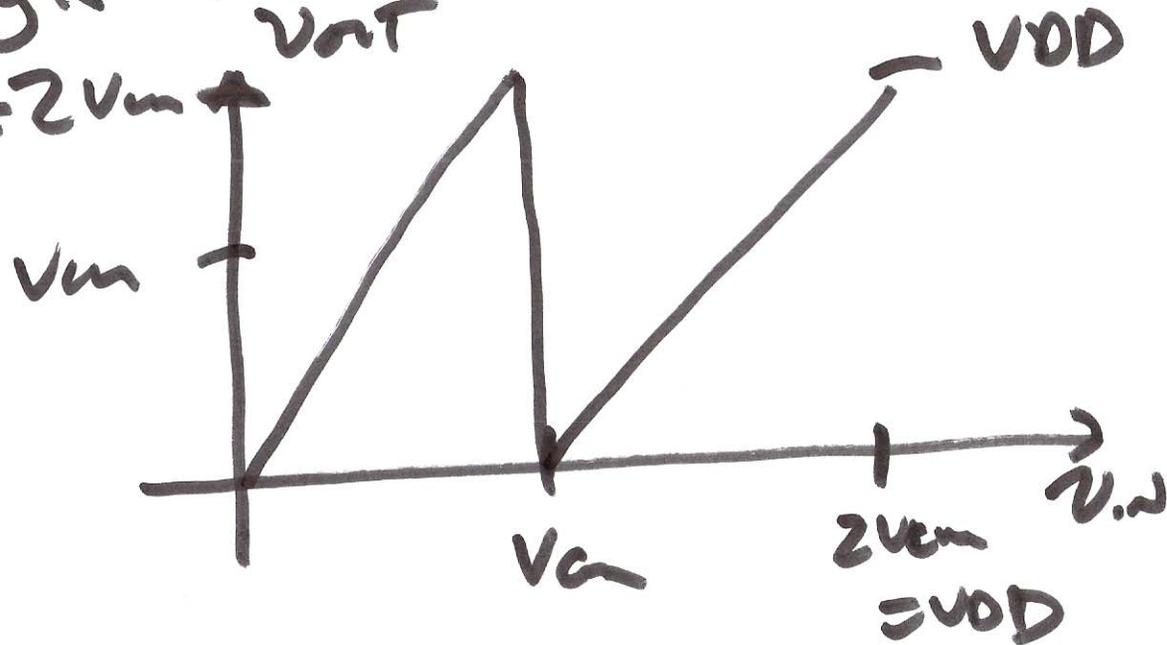


$$v_{out} |_{\text{stage}} = 2 (v_{in} + \bar{b} \cdot 0 - b \cdot v_{cm})$$

$b \rightarrow$ output of the comparator

\rightarrow Single-ended v_{out}

$$v_{DD} = 2v_{cm}$$



$$0 \leq v_{in} \leq v_{cm}$$

2)


Eq. (30.56)

$$V_{AT} = V_{AT+} - V_{AT-} =$$

$$\bar{b} \cdot V_{in} + 2 \left(\overbrace{V_{in+} - V_{in-}}^{V_{id}} + \bar{b} \cdot 0 - \bar{b} \cdot V_{in} \right)$$


$$+ b \cdot V_{in}$$

$$= V_{in}$$

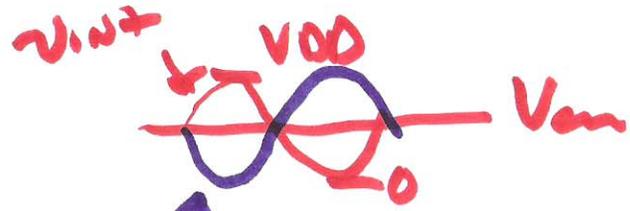

$V_{in} > 0$
SUBTRACT

$V_{in} < 0$
~~ADD~~
SUB
Nothing

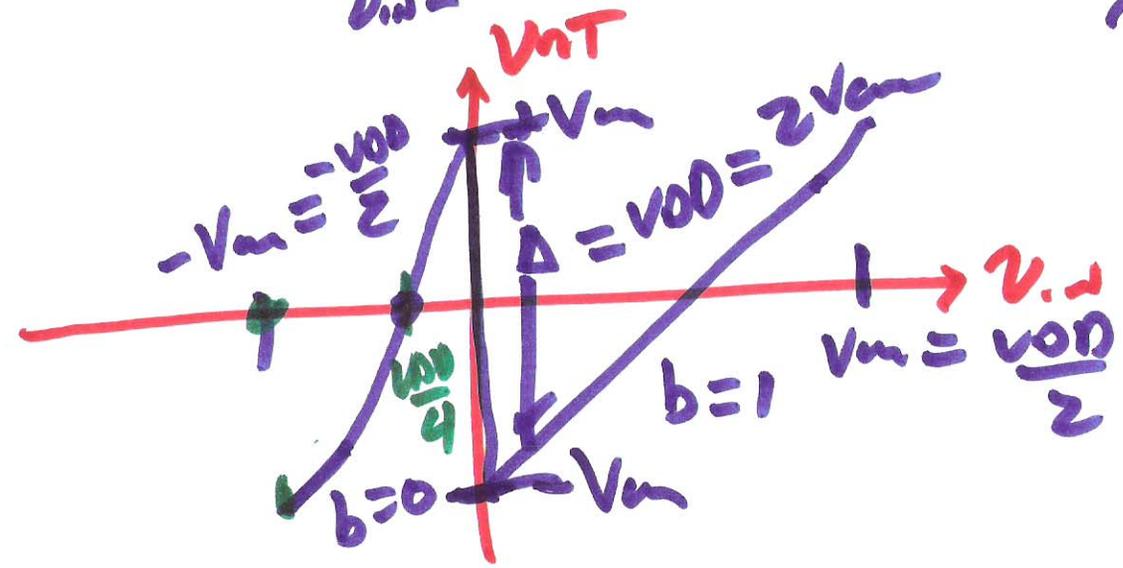

3)

$$V_{out+} - V_{out-} = 2(V_{in+} - V_{in-} + \bar{b} \cdot 0 - b \cdot V_{cm}) + \bar{b} \cdot V_{cm} + b \cdot V_{cm}$$

$$V_{out+} - V_{out-} = 2\left(V_{in+} - V_{in-} + \bar{b} \cdot 0 + \bar{b} \cdot \frac{V_{cm}}{2} - b \cdot V_{cm} + b \cdot \frac{V_{cm}}{2}\right)$$

$$\underbrace{V_{out+} - V_{out-}}_{V_{out}} = 2\left(\underbrace{V_{in+} - V_{in-}}_{V_{in}} + \bar{b} \cdot \frac{V_{cm}}{2} - b \cdot \frac{V_{cm}}{2}\right)$$

$\frac{-V_{DD}}{4} \cdot \frac{V_{cm}}{2} + V_{cm}/2$
 $-V_{cm}$
 $-2 \cdot \frac{-V_{cm}}{2} = -V_{cm}$

4)

Thermometer, ad Decimals


1
0.75
0.25
0

11
01
00

3
1
0

0 Single-ended

Differential

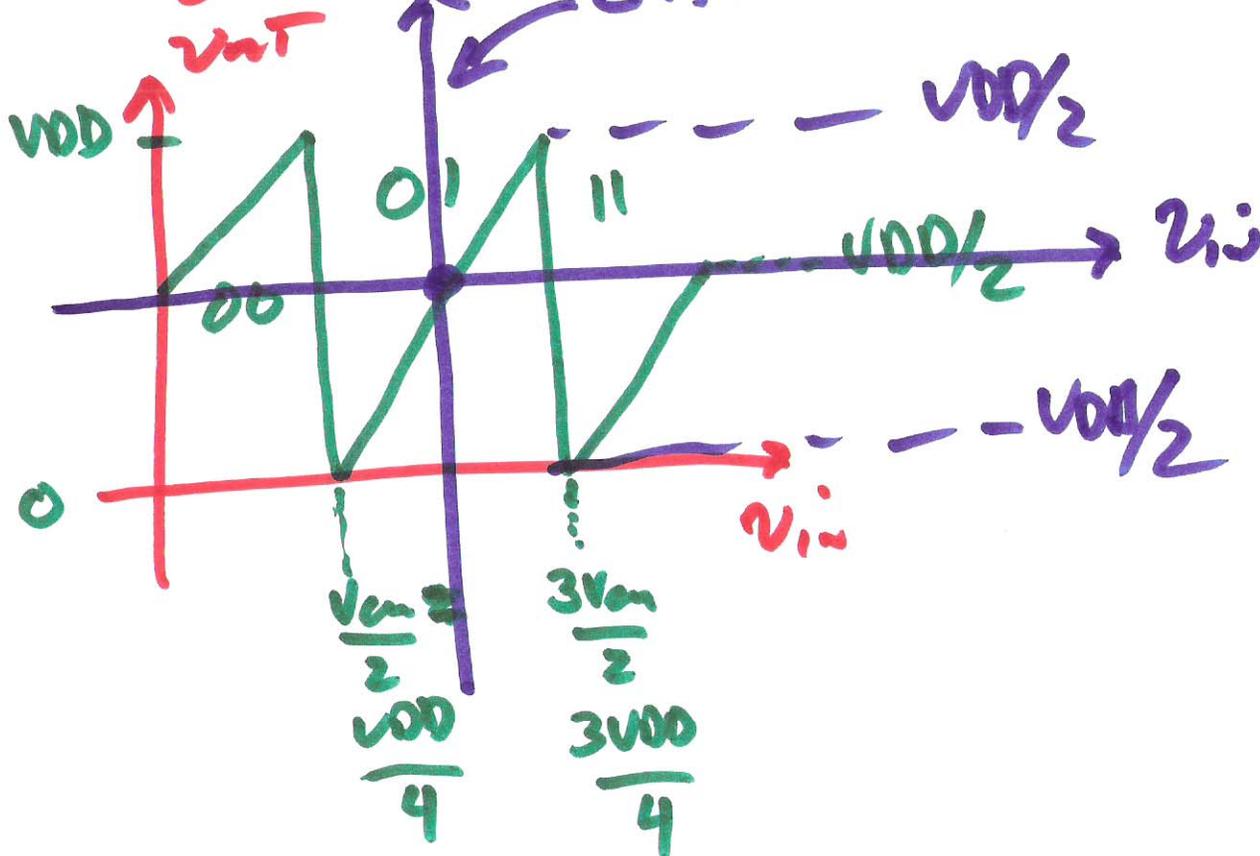

5)

$$v_{out} = 2 \cdot (v_{in} - \bar{a}\bar{b} \cdot 0 - \bar{a}b \cdot V_{cm} - ab \cdot 2V_{cm}) + V_{cm}$$

$$v_{out} = 2 \cdot \left(v_{in} + \bar{a}\bar{b} \cdot \frac{V_{cm}}{2} - \bar{a}b \cdot \frac{V_{cm}}{2} - ab \cdot \frac{3V_{cm}}{2} \right)$$

Single-ended

$$0 \leq v_{in} \leq \frac{V_{cm}}{2} \quad \frac{ab}{00}$$

$$\frac{V_{cm}}{2} \leq v_{in} \leq \frac{3V_{cm}}{2} \quad 01$$

$$\frac{3V_{cm}}{2} \leq v_{in}$$

11


b)

Differential

$$V_{out+} - V_{out-} = 2 \cdot (V_{in+} - V_{in-} + \bar{a}\bar{b} \cdot V_{cm} - \bar{a}b \cdot 0 - ab \cdot V_{cm})$$

Fig 30.40

$$C_I = C_F$$

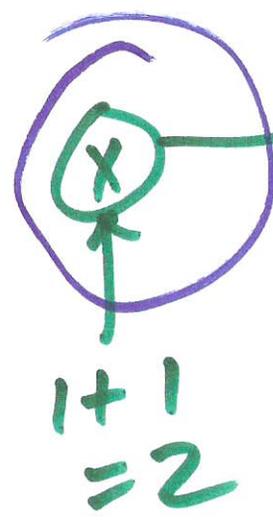

Add $2V_{cm}$

to Add V_{cm}

$$V_{ci+} = \frac{V_{cm}}{4}$$


$$V_{ci-} = \frac{3}{4}V_{cm}$$

$$1 \cdot (V_{ci+} - V_{ci-})$$

$-V_{cm}$

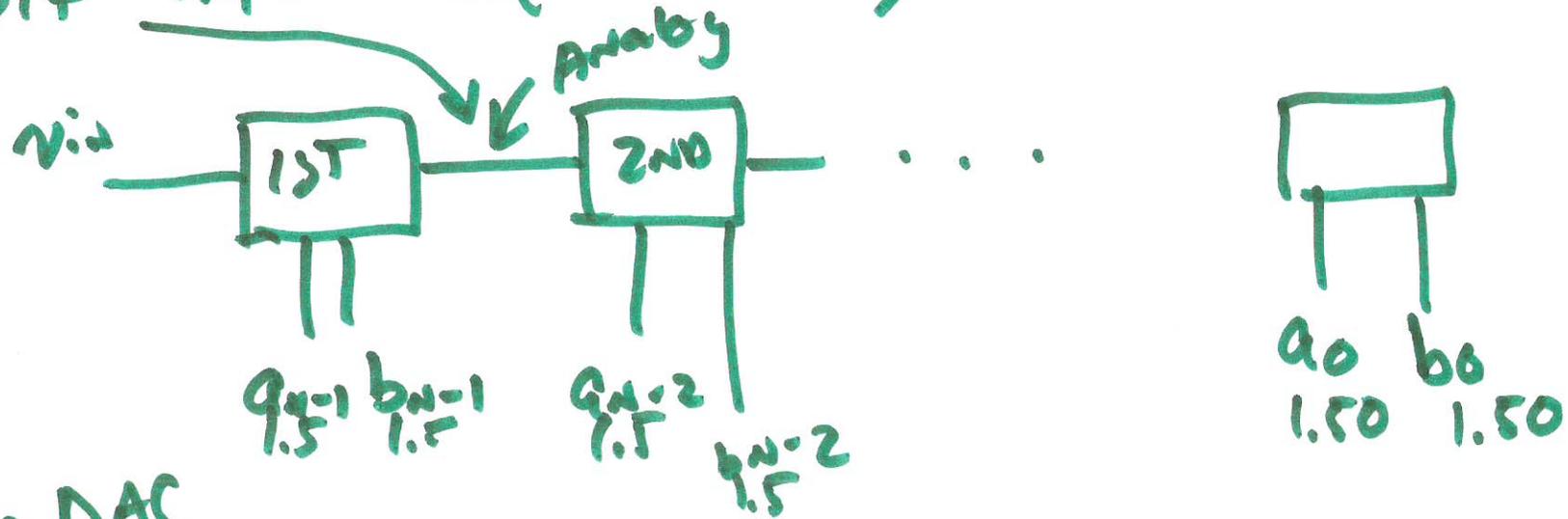1)

$$V_{out+} - V_{out-} = 2(V_{in+} - V_{in-}) + \bar{a} \bar{b} \cdot 2V_{cm} - a \bar{b} \cdot 2V_{cm}$$



for a DAC

$$V_{out} = b_{N-1} \cdot V_{cm} + b_{N-2} \cdot \frac{V_{cm}}{2} + b_{N-3} \cdot \frac{V_{cm}}{4} + \dots + b_0 \cdot \frac{2V_{cm}}{2^N}$$

Remember this

$\frac{V_{cm}}{2^{N-1}}$ $\frac{1 \text{ LSB}}{2^N}$
 $\frac{V_{DD}}{2^N}$

8)

$$V_{IN} = a_{1.5N-1} b_{1.5N-1} \cdot V_{an} + a_{1.5N-1} b_{1.5N-1} \cdot 2 \frac{V_{an}}{2}$$

30.59

$$\frac{V_{OUT}}{2} = \left(V_{IN} - \bar{a}\bar{b} \cdot 0 - \bar{a}b \cdot V_{an} - ab \left(\frac{V_{an}}{2} + \frac{V_{an}}{2} \right) \right)$$

$$-\frac{V_{an}}{2} - \frac{V_{an}}{4} - \frac{V_{an}}{8} - \dots = -V_{an} \cdot \frac{2^{N-1}}{2^N}$$

$$= -V_{an} + \frac{1}{2} \text{LSB} + \frac{V_{REF-}}{2^N}$$

9)

~~Handwritten scribbles~~

$$\frac{V_{\text{out}}}{2^N} = \frac{V_{\text{REF}+} + V_{\text{REF}-}}{2} = \frac{V_{\text{out}}}{2^{N+1}}$$


$$= \frac{V_{\text{REF}+} - V_{\text{REF}-}}{2^{N+1}} + \frac{2V_{\text{REF}-}}{2^{N+1}}$$

$$= \frac{1}{2} \text{LSB} + \frac{V_{\text{REF}-}}{2^N}$$

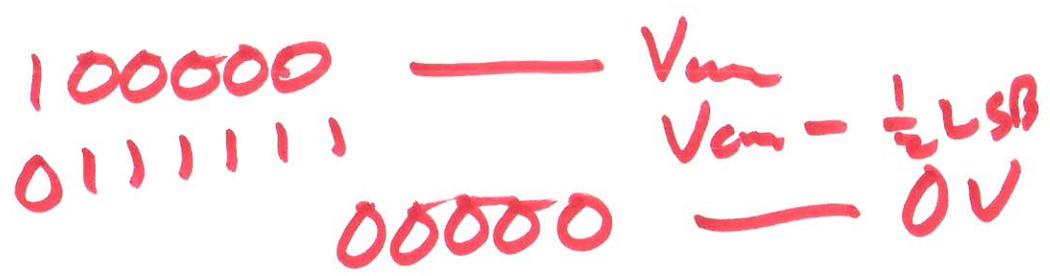10)

Addition, not an "OR"

$$V_{IN} = \left(\overline{a_{1.5N-1} b_{1.5N-1}} + a_{1.5N-2} b_{1.5N-2} \right) \cdot V_{cm} +$$



11)