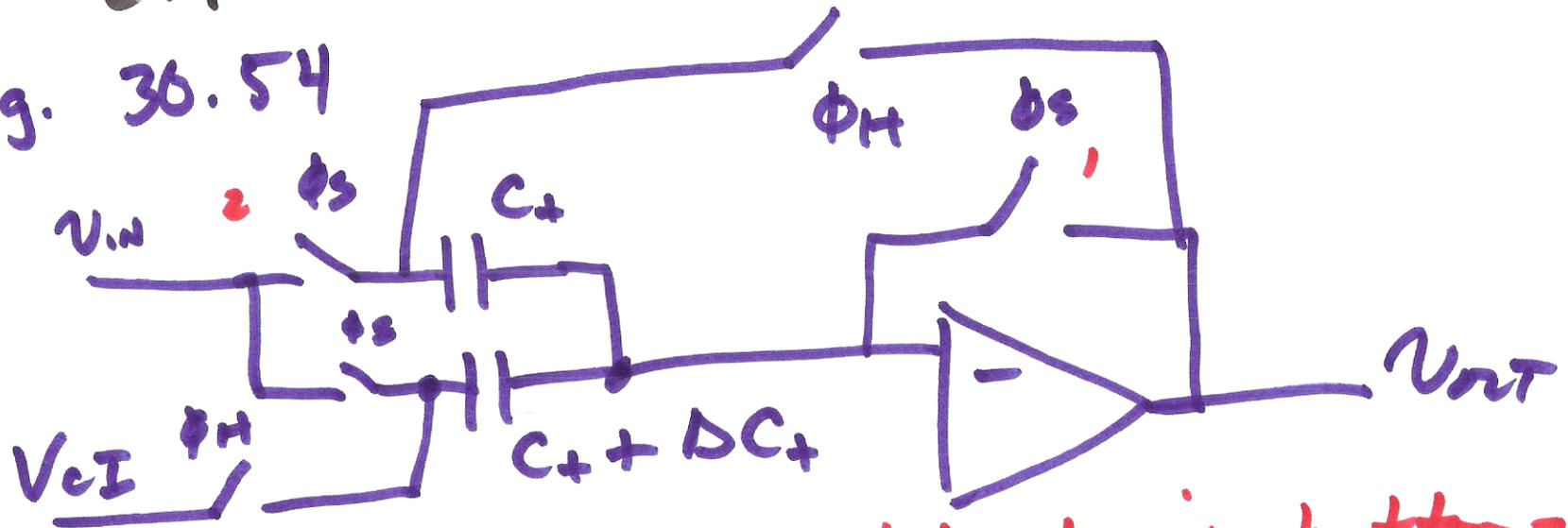


NOV. 17, 2011

Lecture 24

Capacitor Error Averaging

Fig. 30.54



$$V_{out} = \left(1 + \frac{C_+ + DC_+}{C_+} \right) \cdot V_{in} \neq$$

$$- V_{cI} \left(1 + \frac{DC_+}{C_+} \right)$$

Not showing bottom-plate sampling

1 shuts off before 2

EQ. 30.74

1)

$$V_{out+} = \left(2 + \frac{\Delta C_{+-}}{C_{+-}} \right) \cdot V_{in+} -$$

$$\left(1 - \frac{\Delta C_{+-}}{C_{+-}} \right) V_{CI+}$$

$$V_{out+} = \underbrace{2V_{in+} - V_{CI+}}_{\text{ideal response}} + \frac{\Delta C_{+}}{C_{+}} V_{in+} + \frac{\Delta C_{+}}{C_{+}} \cdot V_{CI+}$$

$$V_{out+h} = \left(1 + \frac{C_{+}}{C_{+} + \Delta C_{+}} \right) V_{in} - V_{CI}$$

\rightarrow see Eq. 30.80 $\left(\neq \frac{C_{+}}{C_{+} + \Delta C_{+}} \right)$

2)

$$V_{out} = V_{CI} + \frac{C_+}{C_+ + \Delta C_+} \cdot V_{in} +$$

$$- \frac{C_+}{C_+ + \Delta C_+} \cdot V_{CI}$$

$$\frac{C_+}{C_+ + \Delta C_+} = \frac{1}{1 + \frac{\Delta C_+}{C_+}} \approx 1 - \frac{\Delta C_+}{C_+}$$

$$\frac{1}{1+x} \approx 1 - x$$

\uparrow
 x is small

3)

$$V_{out} = \left(1 - \frac{\Delta C_+}{C_+}\right) \cdot V_{out} + \frac{\Delta C_+}{C_+} \cdot V_{in}$$

$$V_{out} = 2 \cdot V_{in} - V_{out} + \frac{\Delta C_+}{C_+} (V_{in} - V_{out})$$


$$V_{out} = 2V_{in} - V_{out} + \frac{\Delta C_+}{C_+} (V_{in} - V_{out})$$

$$\cancel{+} - \frac{\Delta C_+}{C_+} (2V_{in} - \cancel{2}V_{out}) + \cancel{V_{out}} \cdot \frac{\Delta C_+}{C_+}$$

$$V_{out} = 2V_{in} - V_{out} - \frac{\Delta C_+}{C_+} (V_{in} - V_{out})$$

$$\frac{V_{out} + V_{out}}{2} = 2V_{in} - V_{out}$$

4)

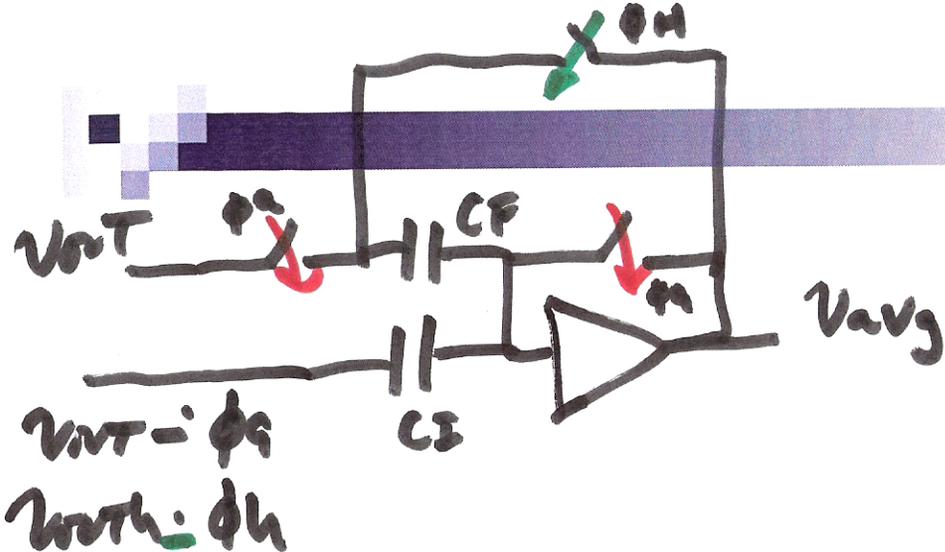

$$Q_{+}^{\phi_g} = (V_{INTa+} - V_{in \pm V_{os}}) C_F + (V_{INTa-} - V_{in \pm V_{os}}) C_I$$

$$Q_{+}^{\phi_h} = (V_{avg+} - V_{in \pm V_{os}}) C_F + (V_{INTb-} - V_{in \pm V_{os}}) C_I$$

$$Q_{+}^{\phi_g} = Q_{+}^{\phi_h}$$

$$V_{INTa+} \cdot C_F + V_{INTa-} \cdot C_I =$$

$$V_{avg+} \cdot C_F + V_{INTb-} \cdot C_I$$

$$V_{avg+} = V_{INTa+} + \frac{C_I}{C_F} V_{INTb-} - \frac{C_I}{C_F} V_{INTa-}$$

5)

$$V_{avg+} = V_{out+} + \frac{C_I}{C_F} (V_{in+} - V_{in-})$$

$$V_{avg} = V_{avg+} - V_{avg-} = V_{out+} - V_{out-}$$

$$V_{avg+} - V_{avg-} = \underbrace{2(V_{in+} - V_{in-}) - (V_{CI+} - V_{CI-})}_{\text{wanted}}$$

$$+ (V_{in+} - V_{CI+}) \frac{DC_+}{C_+} - (V_{in-} - V_{CI-}) \frac{DC_-}{C_-}$$

$$\frac{2(V_{in+} - V_{CI+})}{C_F/C_I} \cdot \frac{DC_+}{C_+} + \frac{DC_- 2(V_{in-} - V_{CI-})}{C_- C_F/C_E}$$

b)