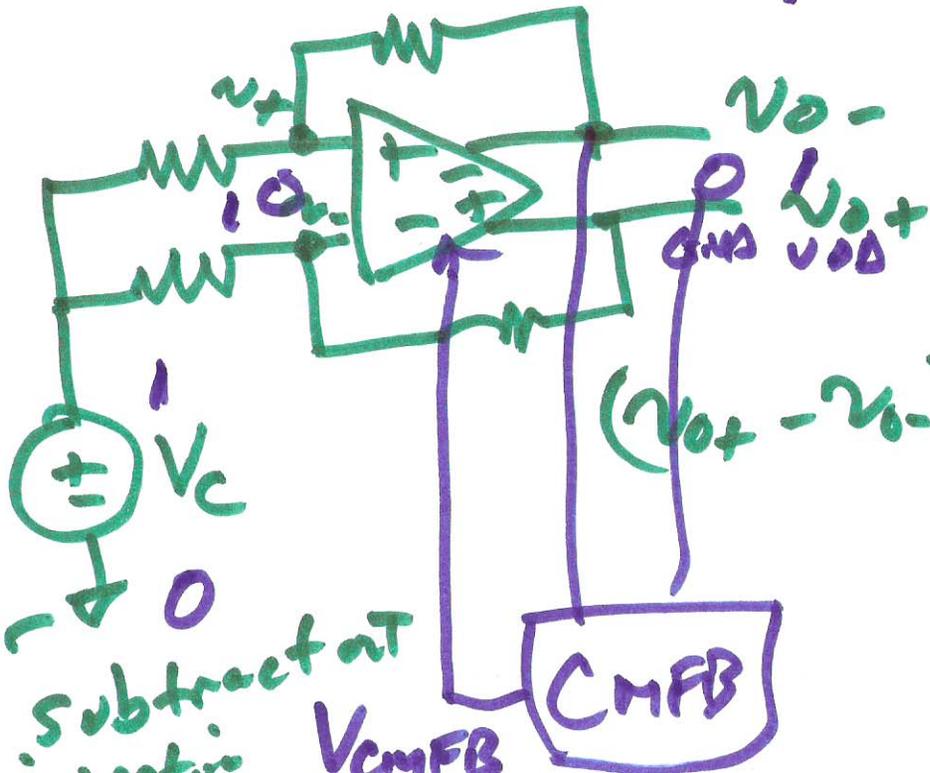


Lecture 26, ~~DEC~~ DEC. 4, 2011

Talk CMFB




$$(v_{out+} - v_{out-}) = A_{OL}(v_{in+} - v_{in-})$$

$$v_{in+} \approx v_{in-}$$

$-x^2 - x^4$   
 $\sim x^2 - x^4$   
 \* REJECT CM NOISE

\* even-order harmonics subtract out  
 \* change injection cap. feedback  $\omega_p$  CM so they subtract out.

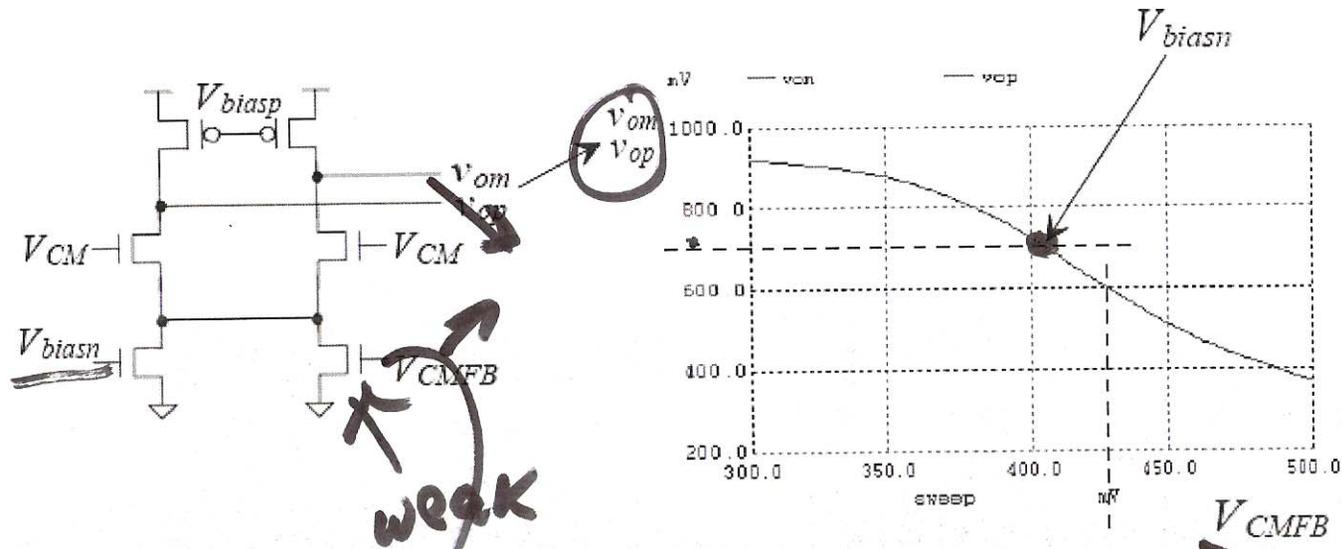
1) \* change injection cap. feedback  $\omega_p$  CM so they subtract out.



NMOS 10/1  
 PMOS 20/1  
 Bias circuit from Fig. 26.3

Value of CM feedback voltage when the outputs are 600 mV.

Figure 26.17 Plotting the output voltages as a function of the CM feedback voltage.

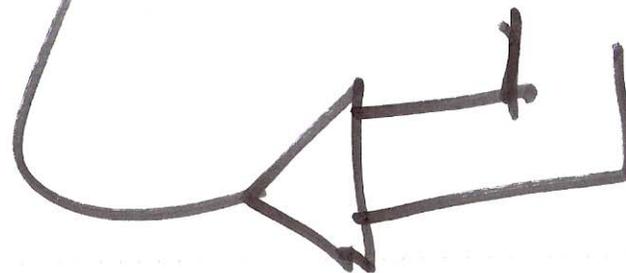

$A_{cm} < 1$

2)

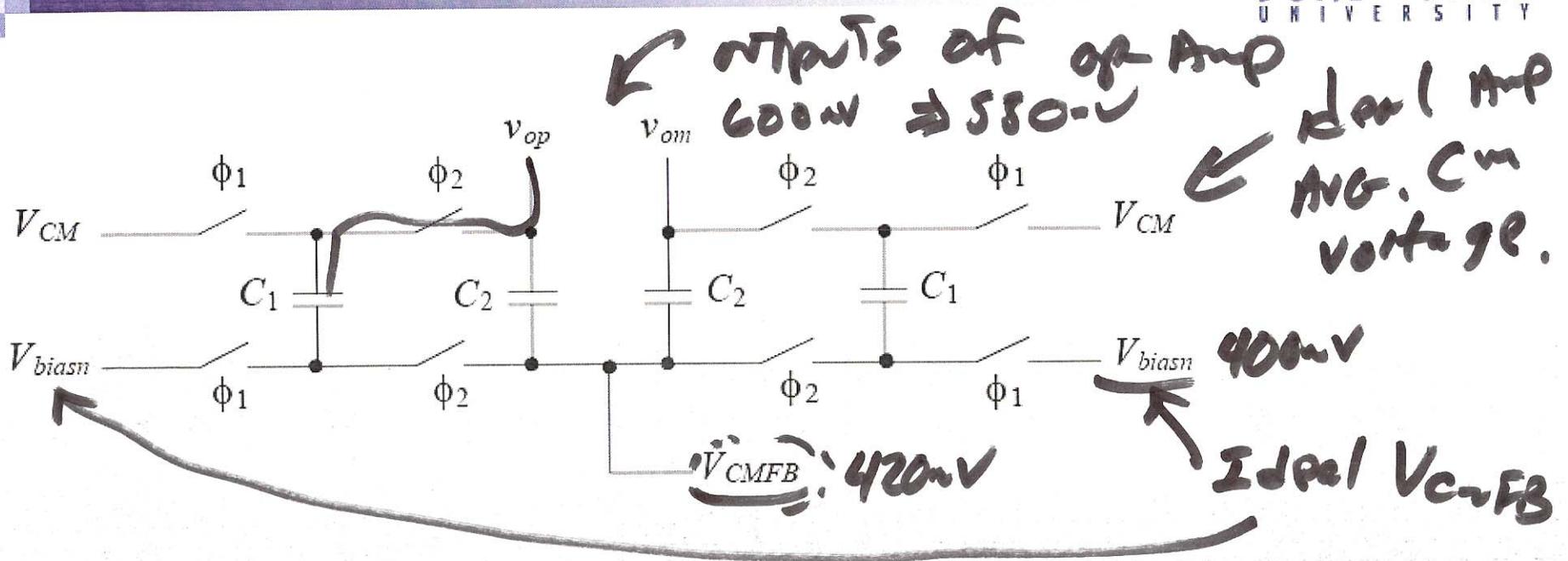


Figure 26.16 A switched-capacitor CMFB circuit.

$\phi_1$  closed

$$q_1 = 2C_1 (V_{biasn} - V_{cm})$$



$\phi_2$  closed

$$q_2 = (-v_{op} + V_{cmFB}) \cdot C_1 + C_1 (V_{cmFB} - v_{om})$$

$$\Delta V_{cmFB} = q_1 - q_2 = 2C_1 \left( V_{biasn} - V_{cmFB} + \frac{v_{op} + v_{om}}{2} - V_{cm} \right)$$

3)

134A

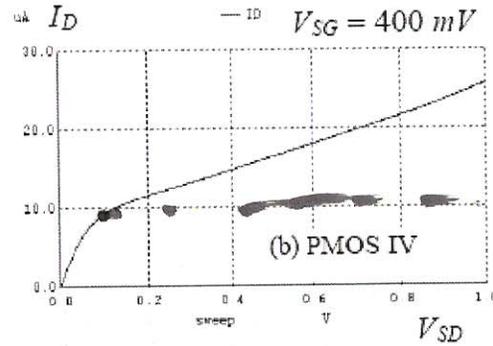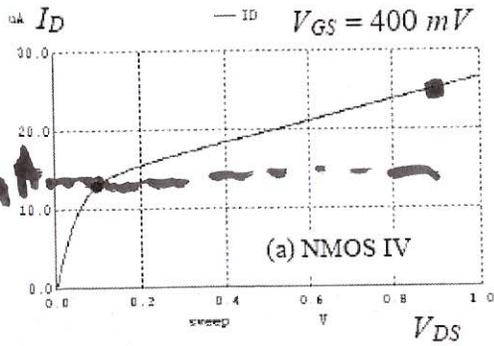



going for speed  
and low-power

$V_{ov} \uparrow$



$L \rightarrow$  minimum

$V_{os} = 400\text{mV}$

$V_{sg} = 400\text{mV}$

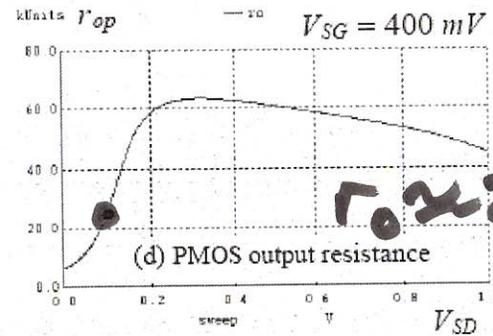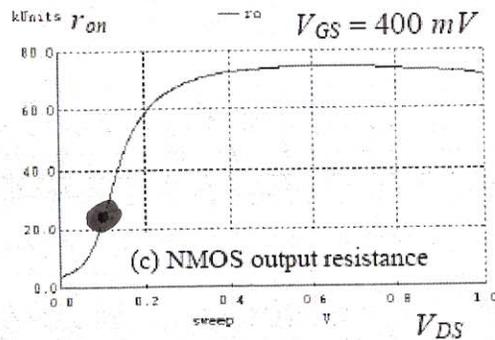

$r_{o} \approx 25\text{k}$

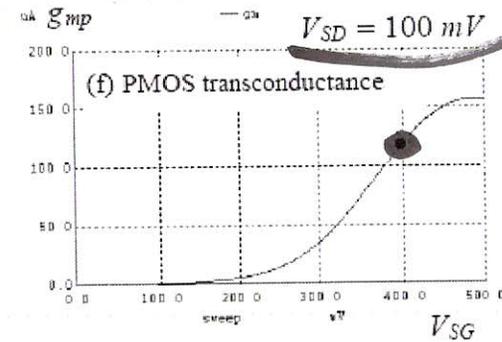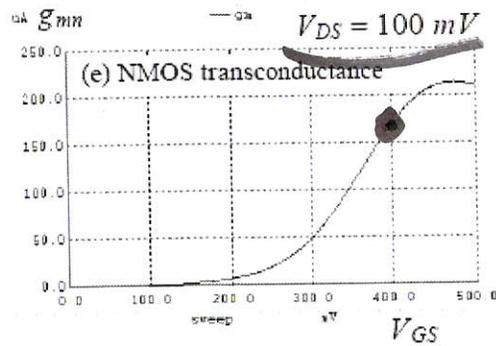


$g_m = 150 \mu\text{A/V}$

$g_m r_o = 150 \mu\text{A/V} \cdot 25\text{k}$

$\approx 6$

Figure 26.18 Characteristics of NMOS (10/1) and PMOS (20/1) devices.

4)

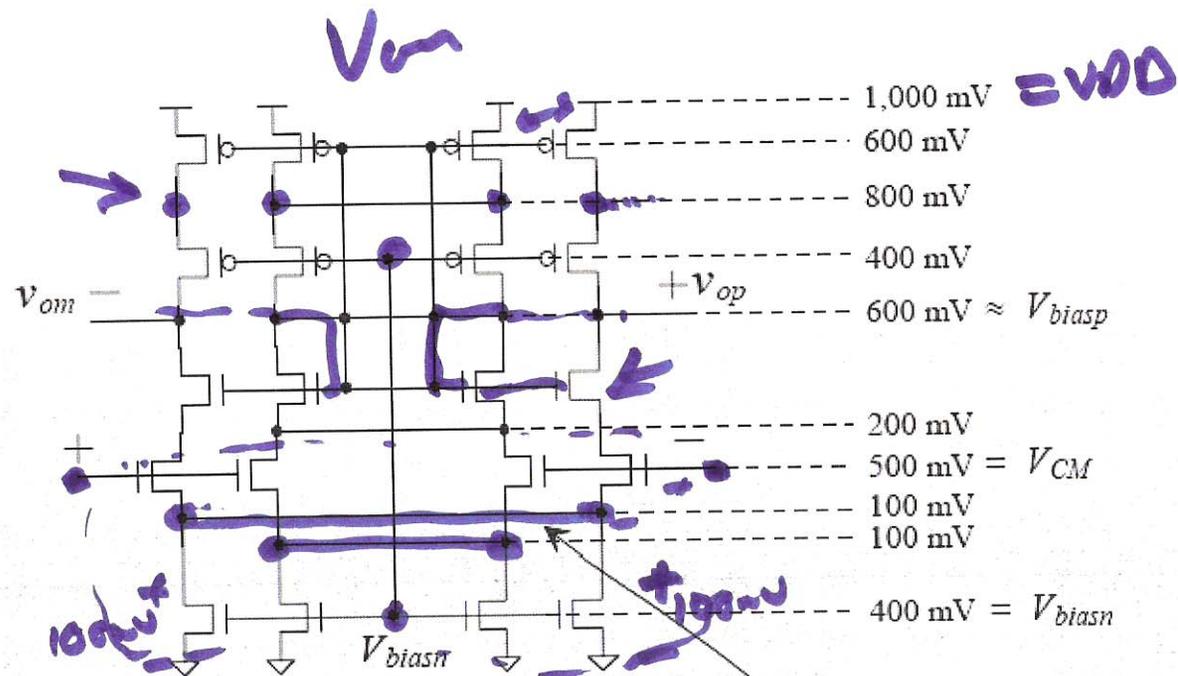

NMOS are 10/1  
 PMOS are 20/1  
 Bias circuit in Fig. 26.3

Note separate diff-amp connections.

Figure 26.19 Fully-differential cascode diff-amp.

s)


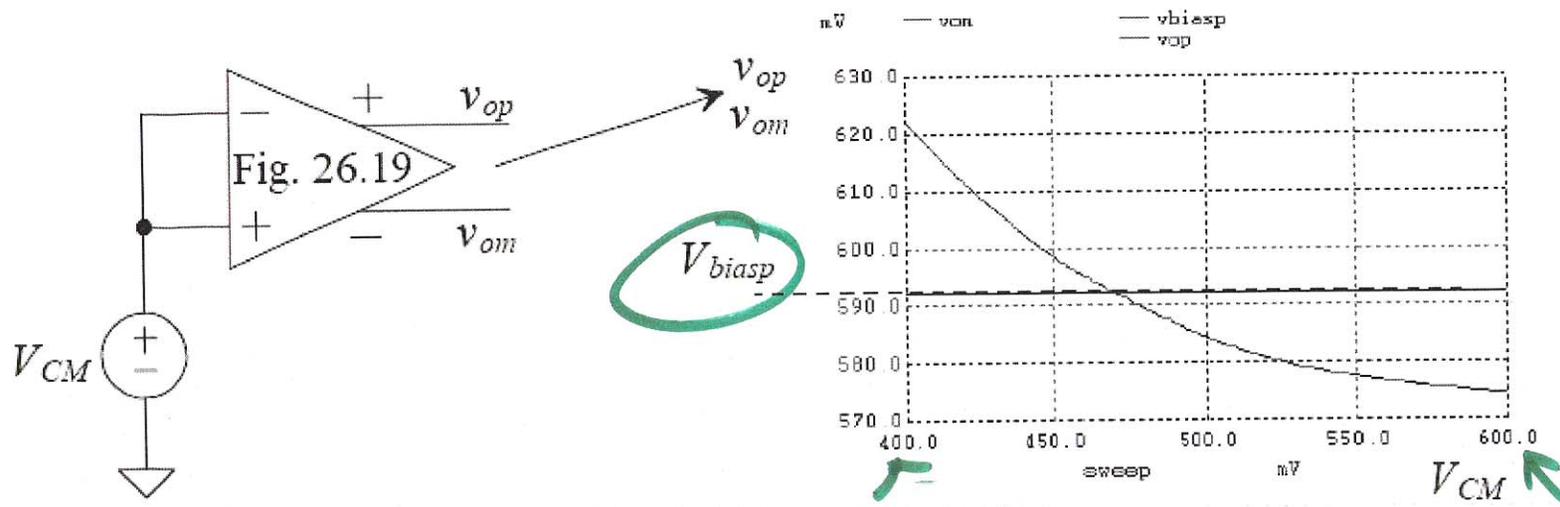


Figure 26.20 Varying the common-mode voltage and looking at the output.





b)

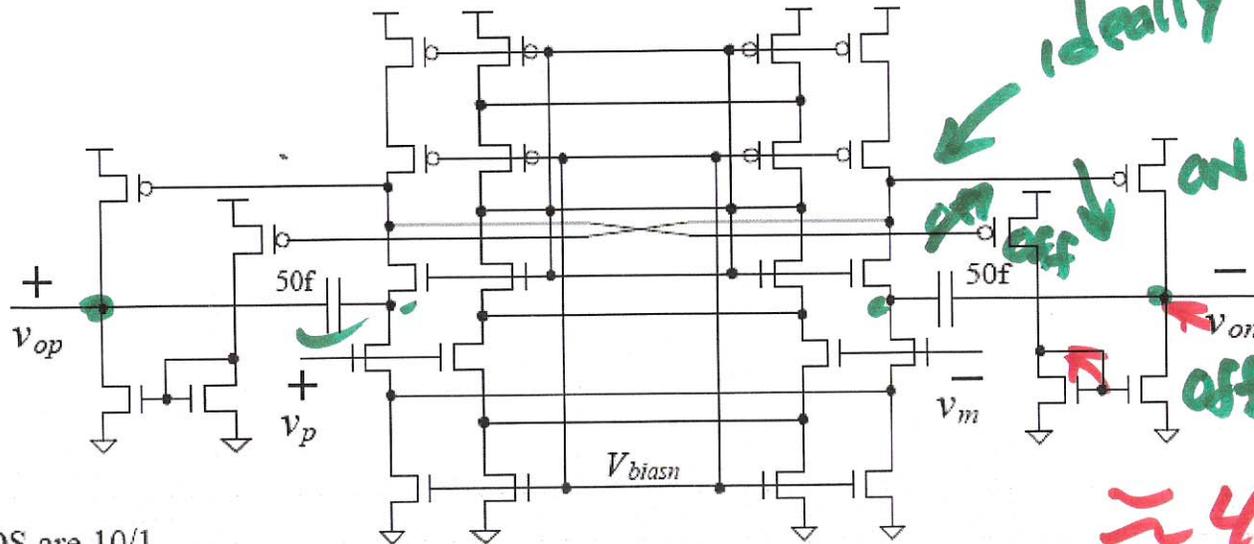

NMOS are 10/1  
 PMOS are 20/1  
 Bias circuit in Fig. 26.3

Figure 26.22 Basic two-stage op-amp without CMFB.

7)

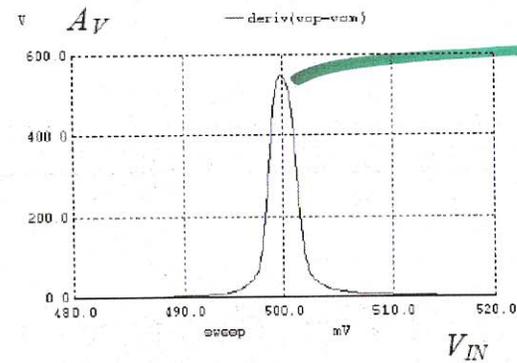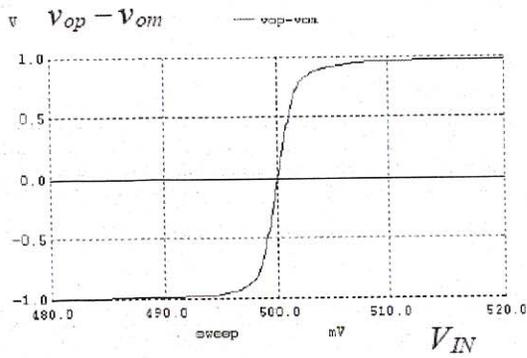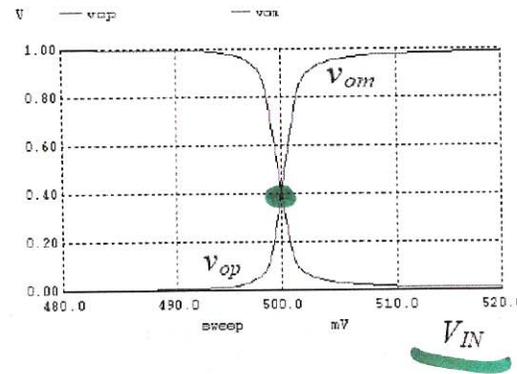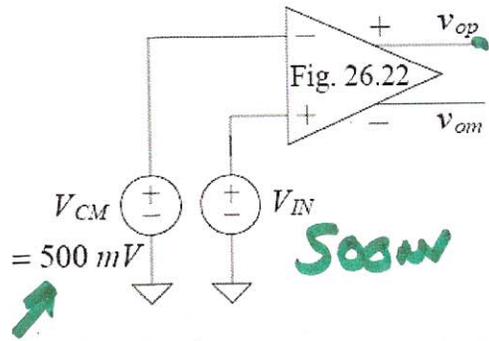

$\sim 550 \rightarrow V/V$

Figure 26.23 DC behavior and gain of the op-amp in Fig. 26.22.

87

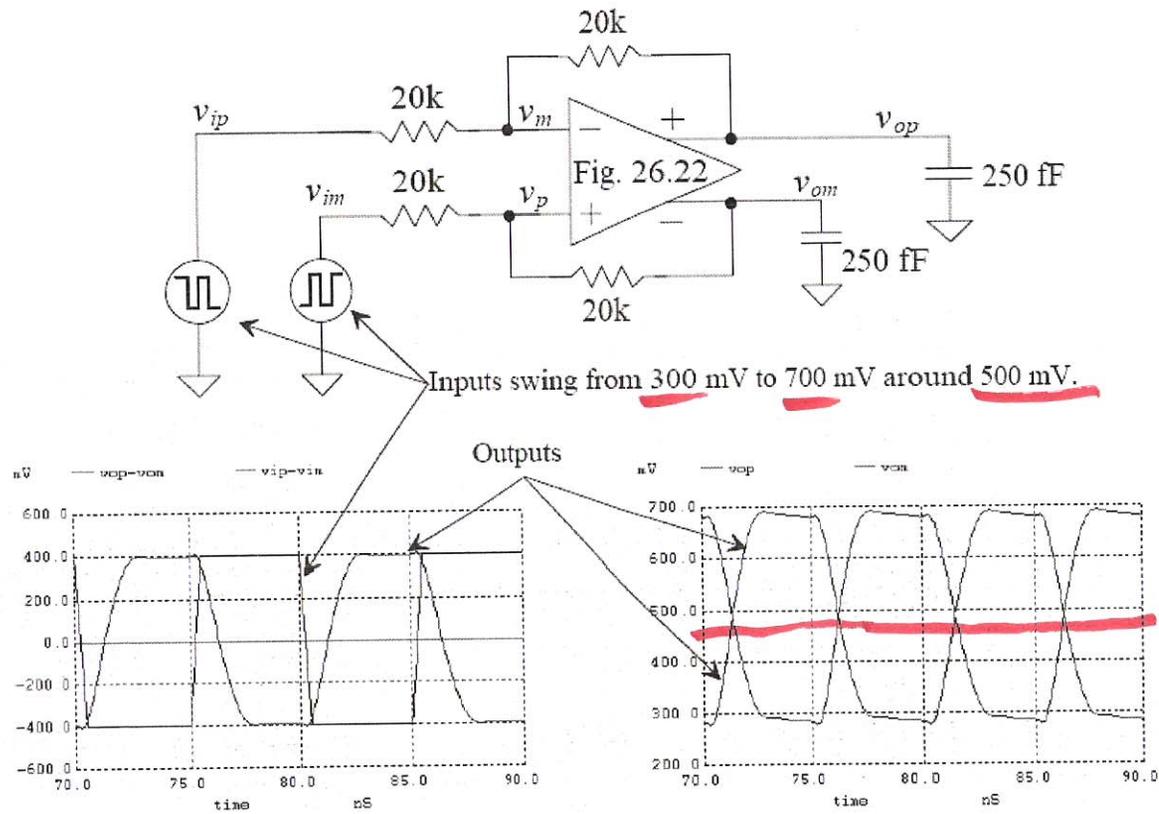


Figure 26.24 Step response of the op-amp in Fig. 26.22 driving 250 fF load capacitors and 20k feedback resistors.

Bottom plate  
S/H

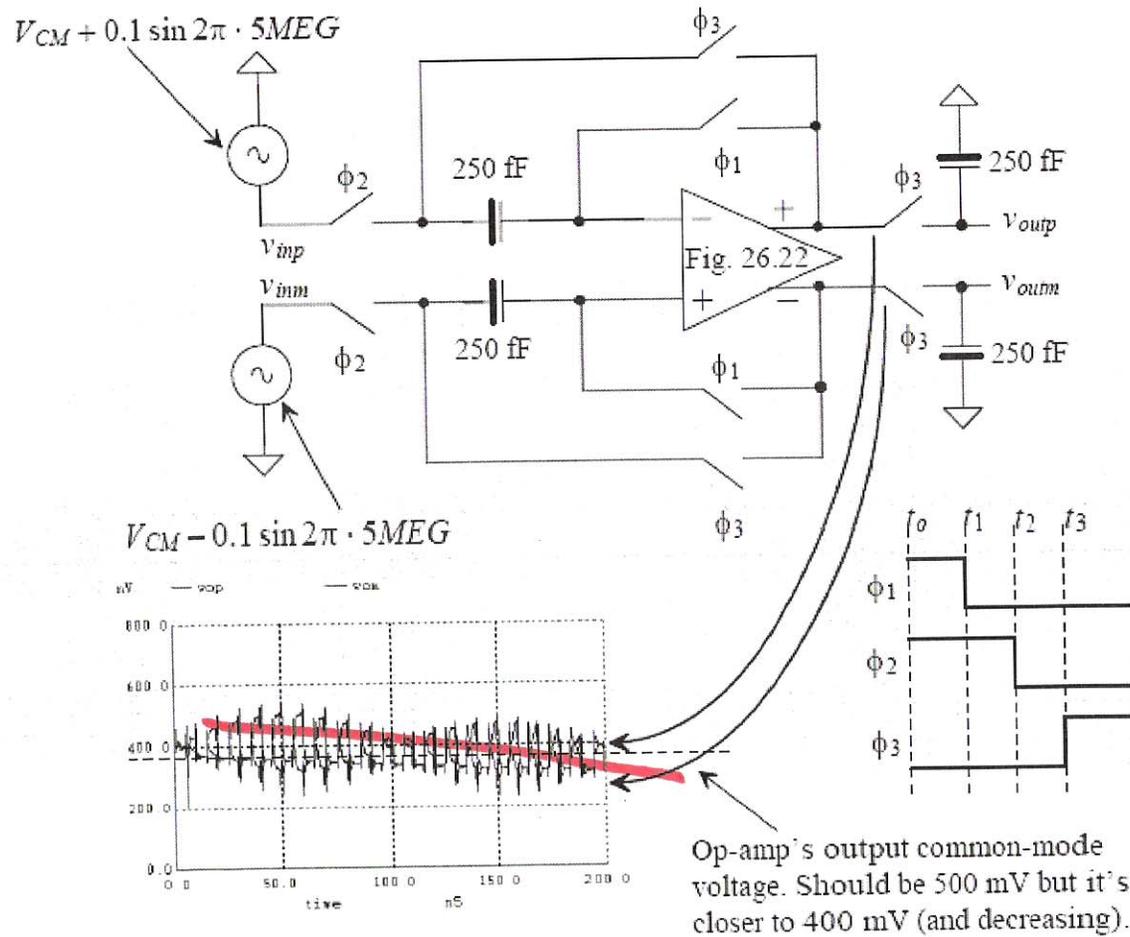


Figure 26.25 A sample-and-hold circuit. Notice how the output common-mode voltage is wandering.


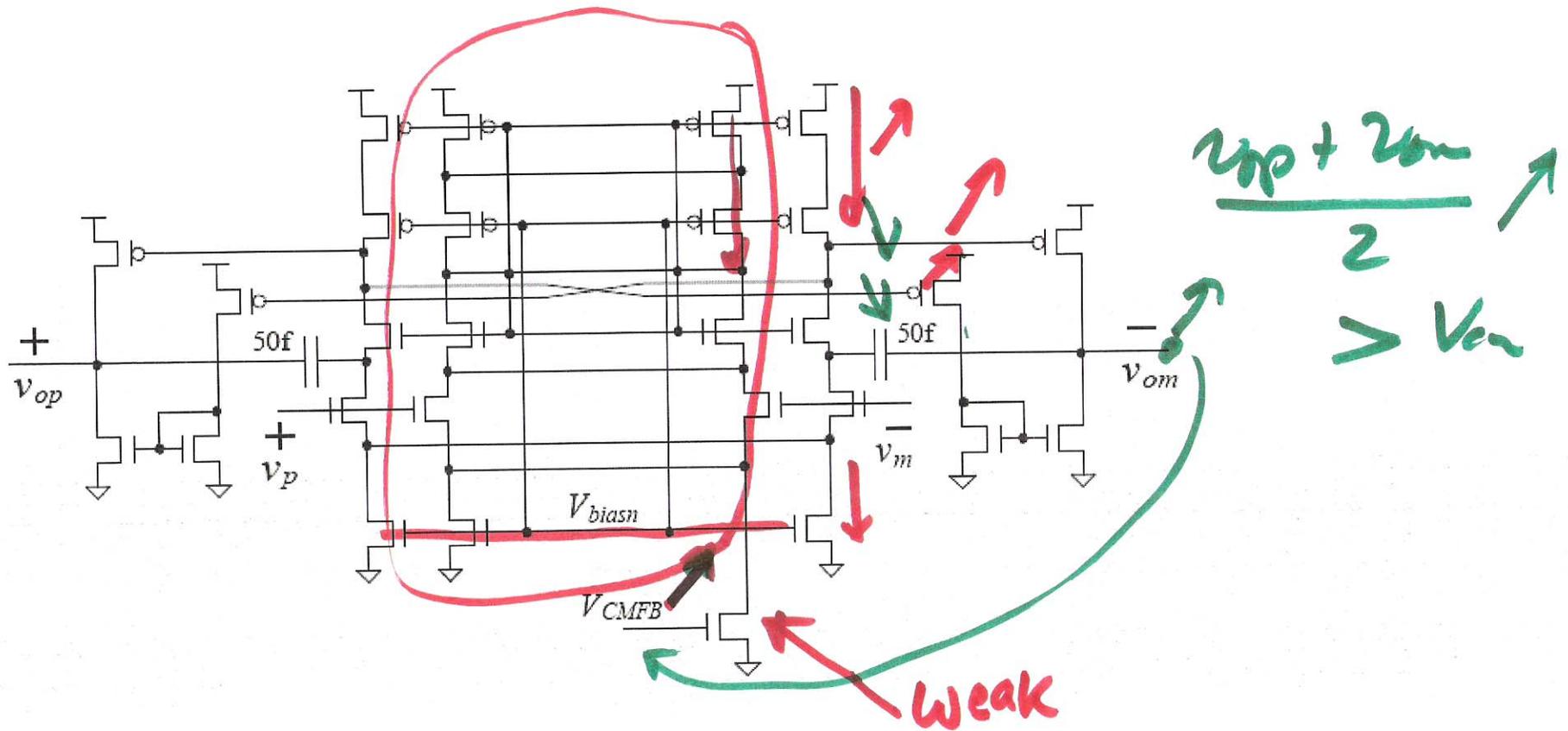


Figure 26.26 Modifying the op-amp for a CMFB input signal.

m)

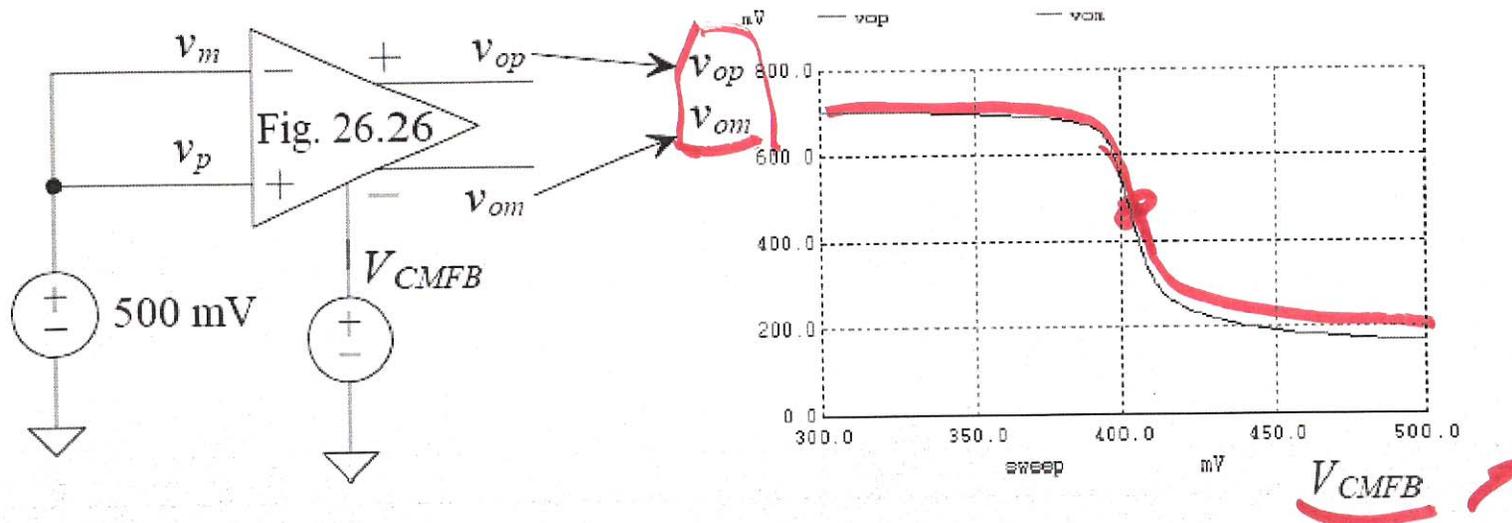

**Figure 26.27** The CMFB input to output relationship. The gain is approximately 25 (considerably less than the forward differential gain).

$$A_{cm} < 1$$

↑ CMFB Amplifier gain

12)

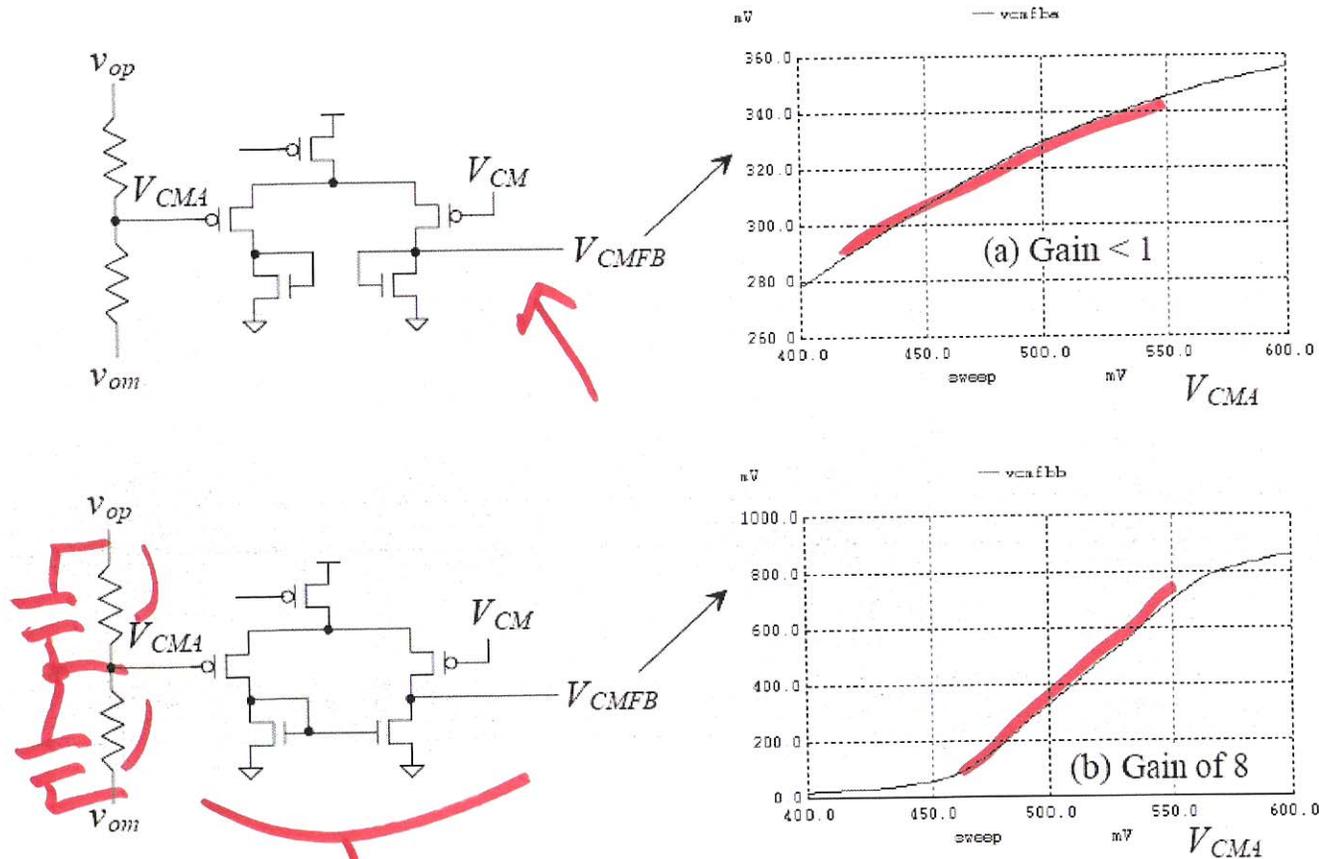


Figure 26.28 Gains of CMFB amplifiers.

CAN use only if CMFB signal goes to a weak transistor!

13)

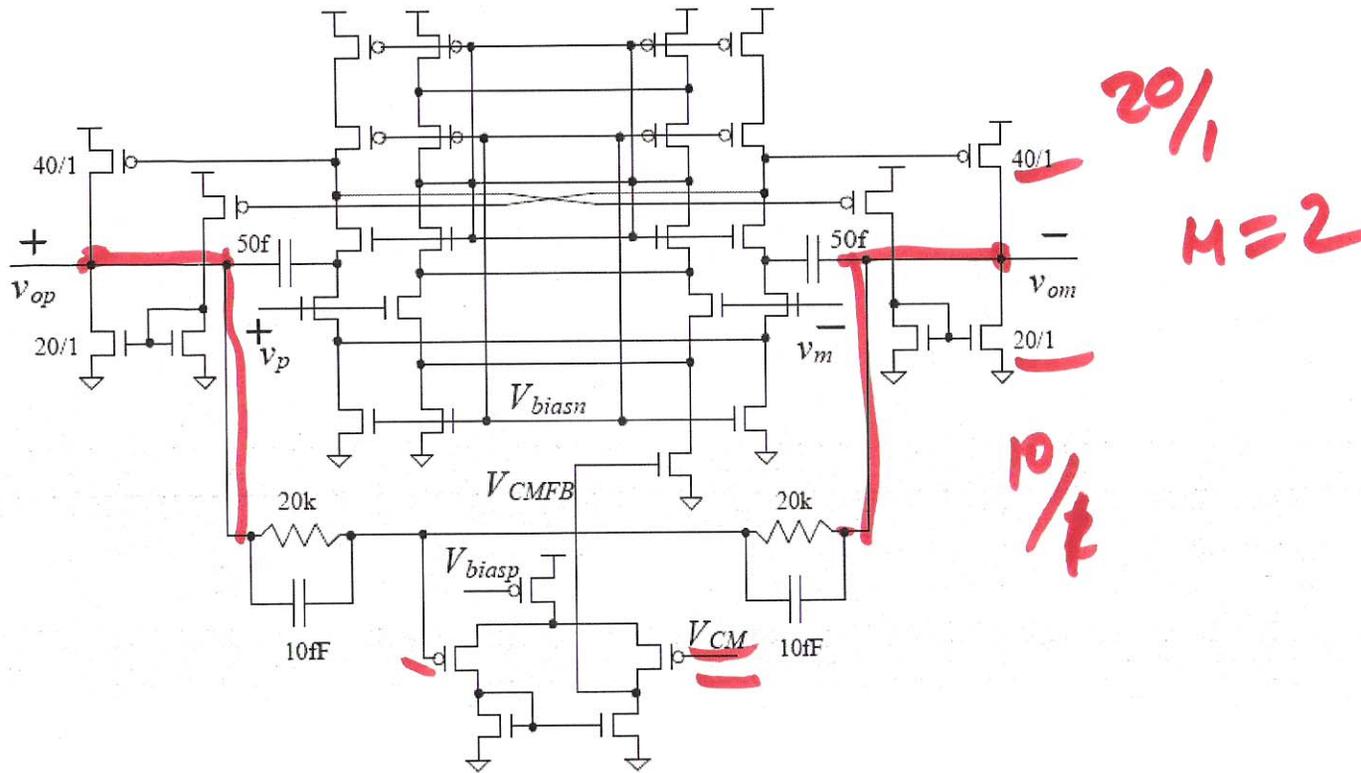


Figure 26.29 Complete schematic of op-amp with CMFB.

14)