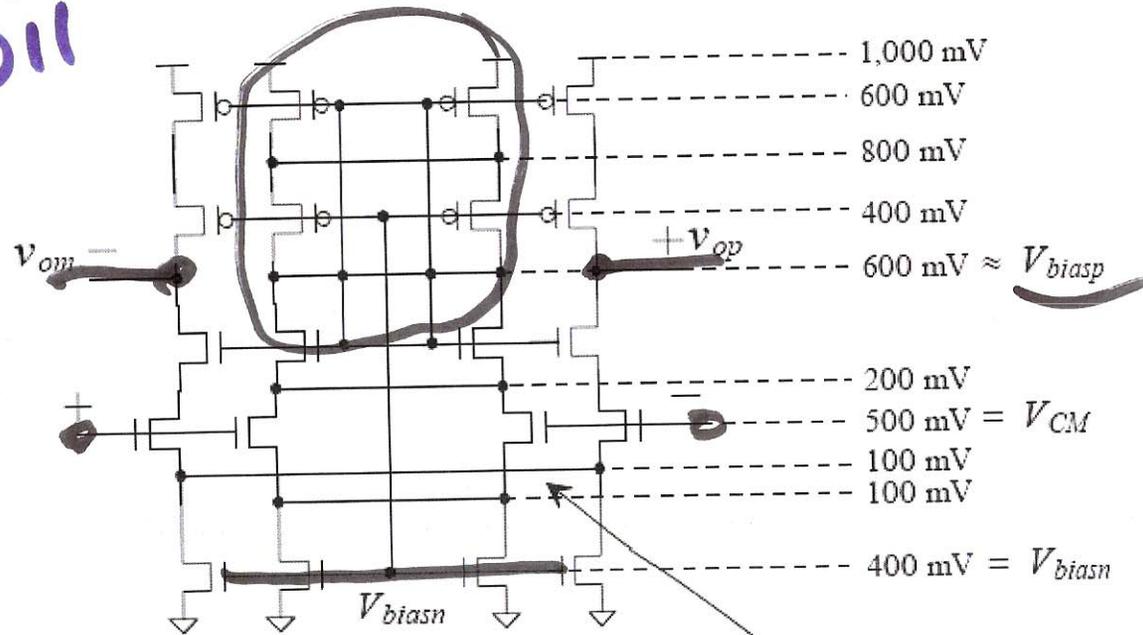


Lecture 27
Dec. 6, 2011




NMOS are 10/1
PMOS are 20/1
Bias circuit in Fig. 26.3

Note separate diff-amp connections.

Figure 26.19 Fully-differential cascode diff-amp.
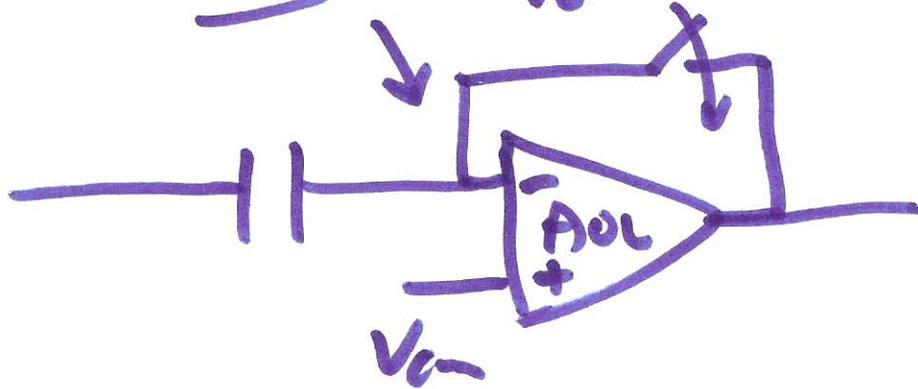
$$V_- = -\frac{A_{OL}}{V_{cm}} + V_{cm} =$$



$$V_{OUT} = A_{OL}(V_+ - V_-)$$

$$\frac{V_{OUT}}{A_{OL}} = V_+ - V_-$$


$$\frac{V_{cm}}{A_{OL}} - \frac{V_{cm}}{A_{OL}}$$

$$(A_{OL} + 1)V_- = V_+$$

$$V_- = \frac{V_{cm}}{A_{OL} + 1}$$

$$\approx \frac{V_{cm}}{A_{OL}}$$

2)

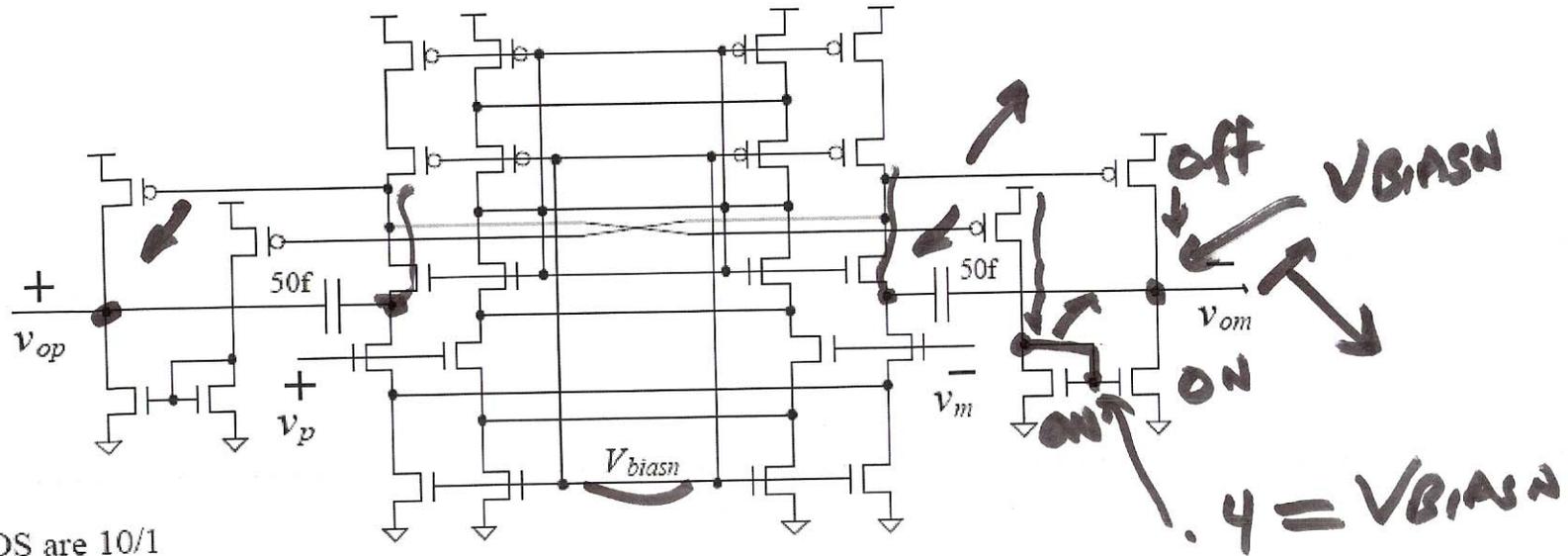

NMOS are 10/1
 PMOS are 20/1
 Bias circuit in Fig. 26.3

Figure 26.22 Basic two-stage op-amp without CMFB.

3)

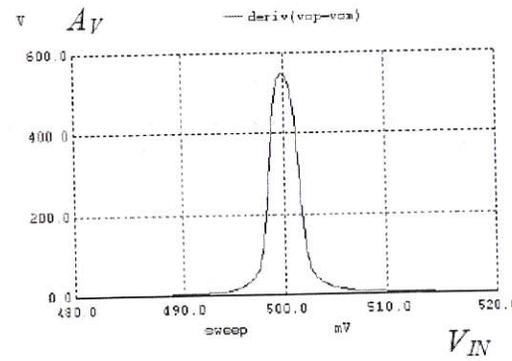
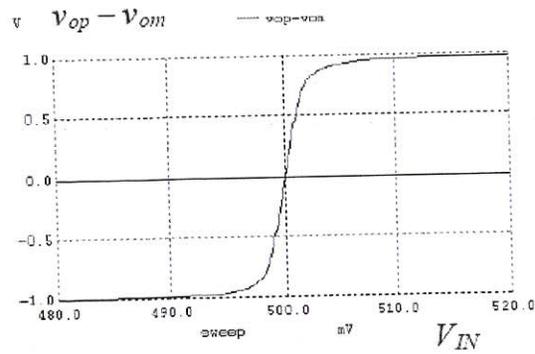
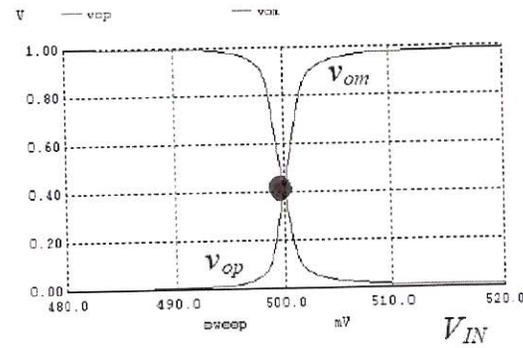
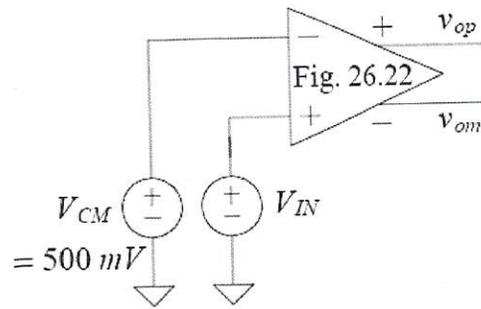


Figure 26.23 DC behavior and gain of the op-amp in Fig. 26.22.

4)

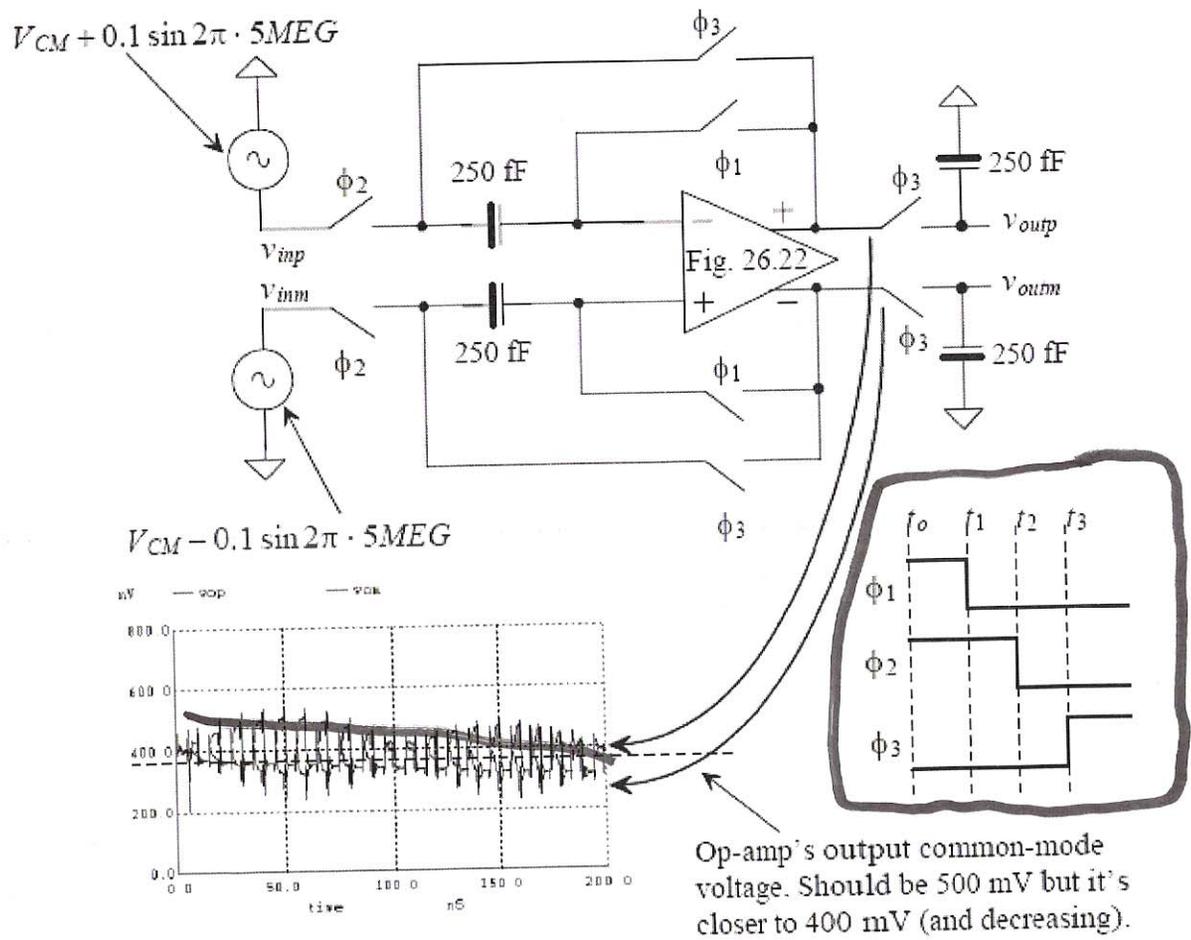


Figure 26.25 A sample-and-hold circuit. Notice how the output common-mode voltage is wandering.

S)

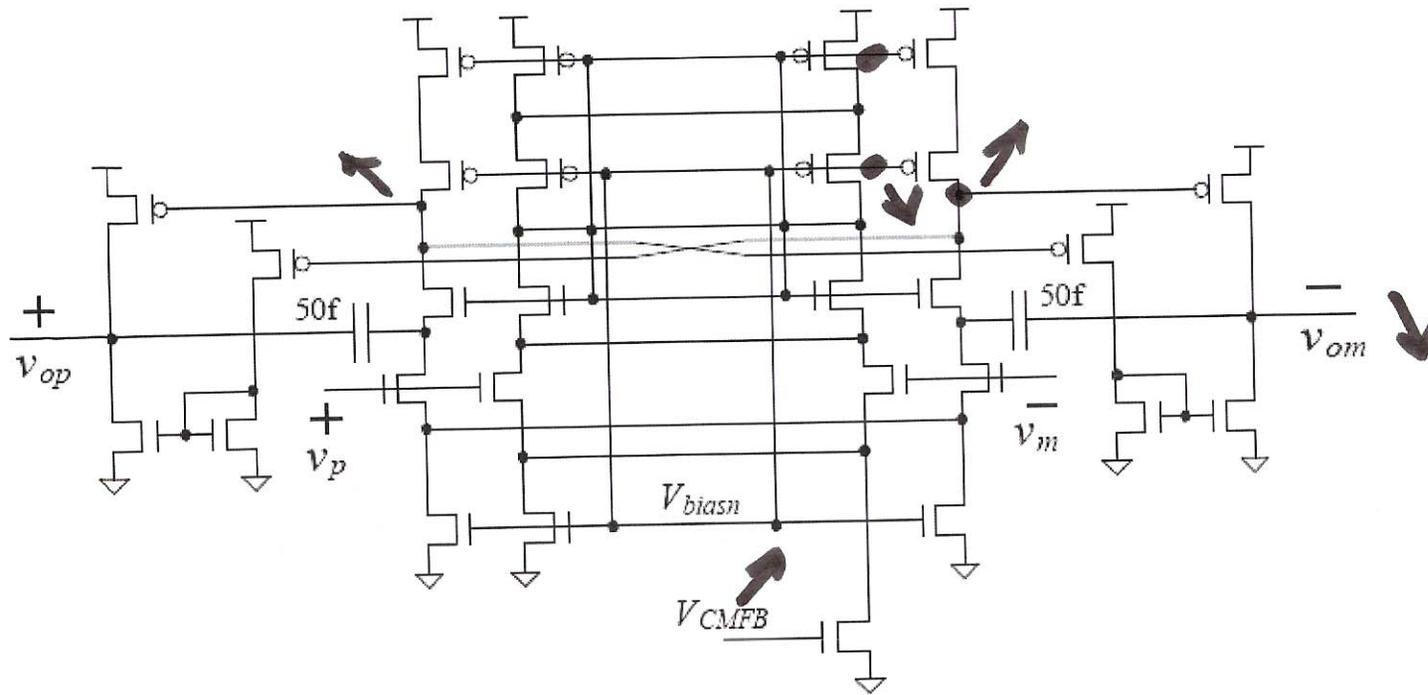


Figure 26.26 Modifying the op-amp for a CMFB input signal.

6)

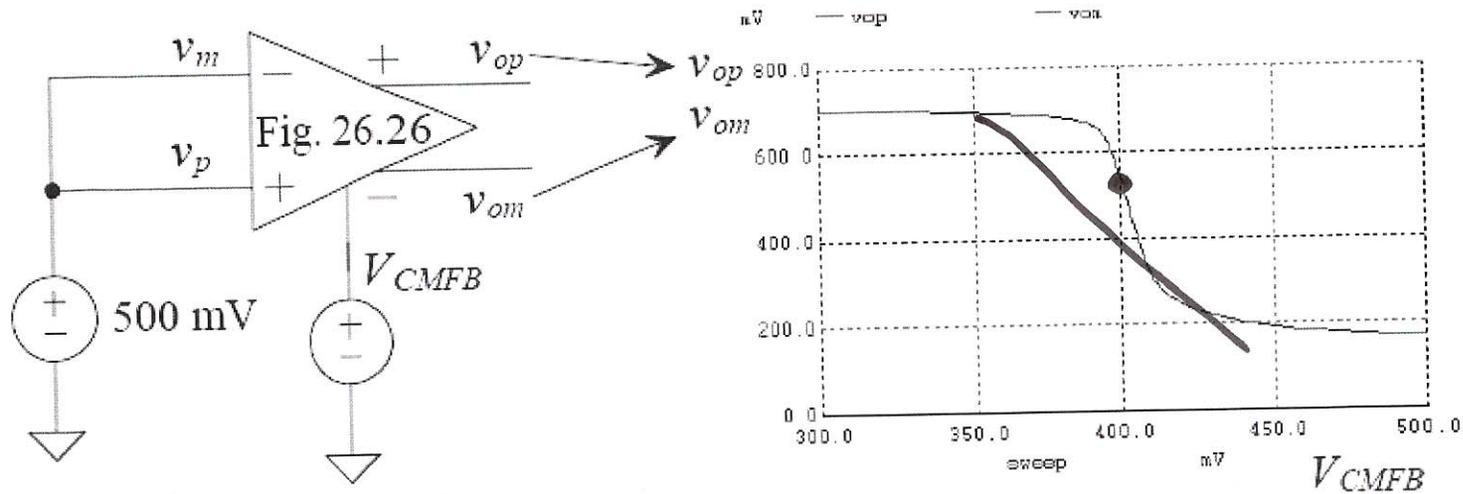


Figure 26.27 The CMFB input to output relationship. The gain is approximately 25 (considerably less than the forward differential gain).

7)



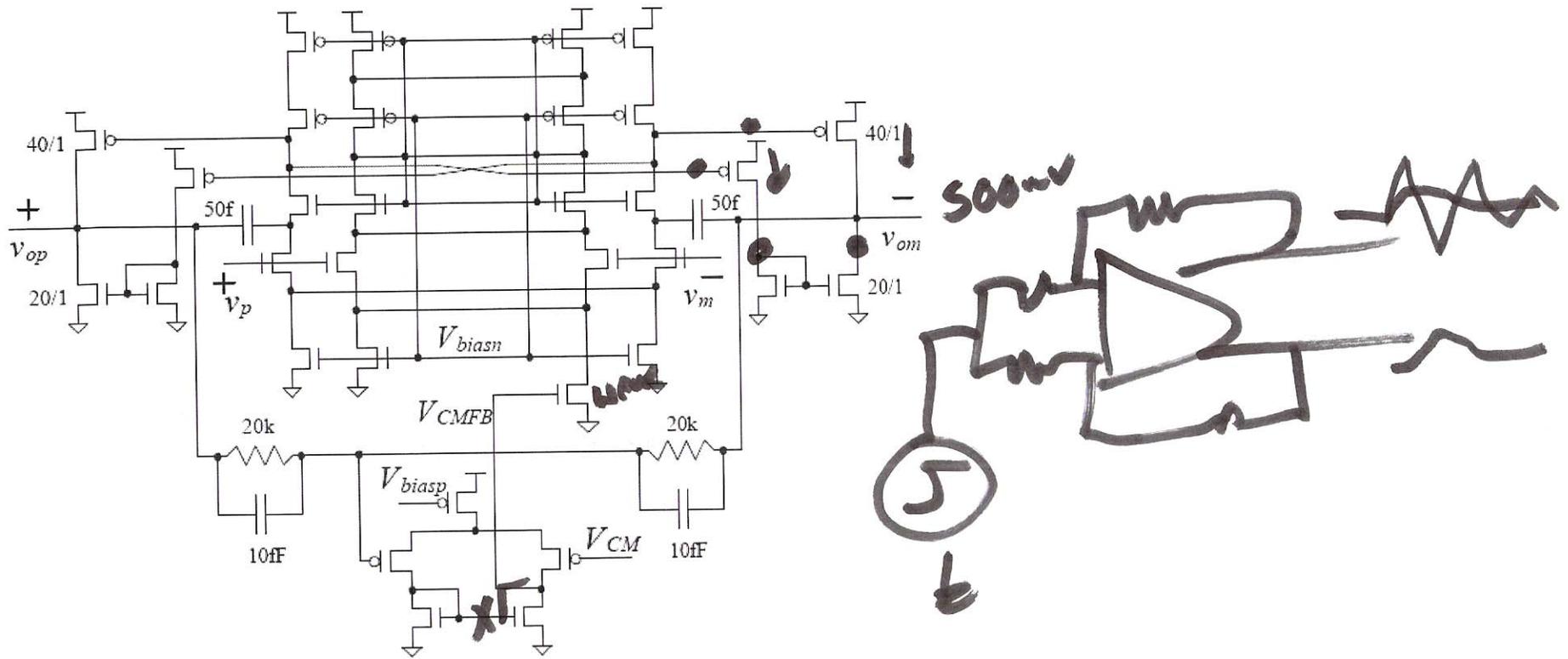


Figure 26.29 Complete schematic of op-amp with CMFB.

8)

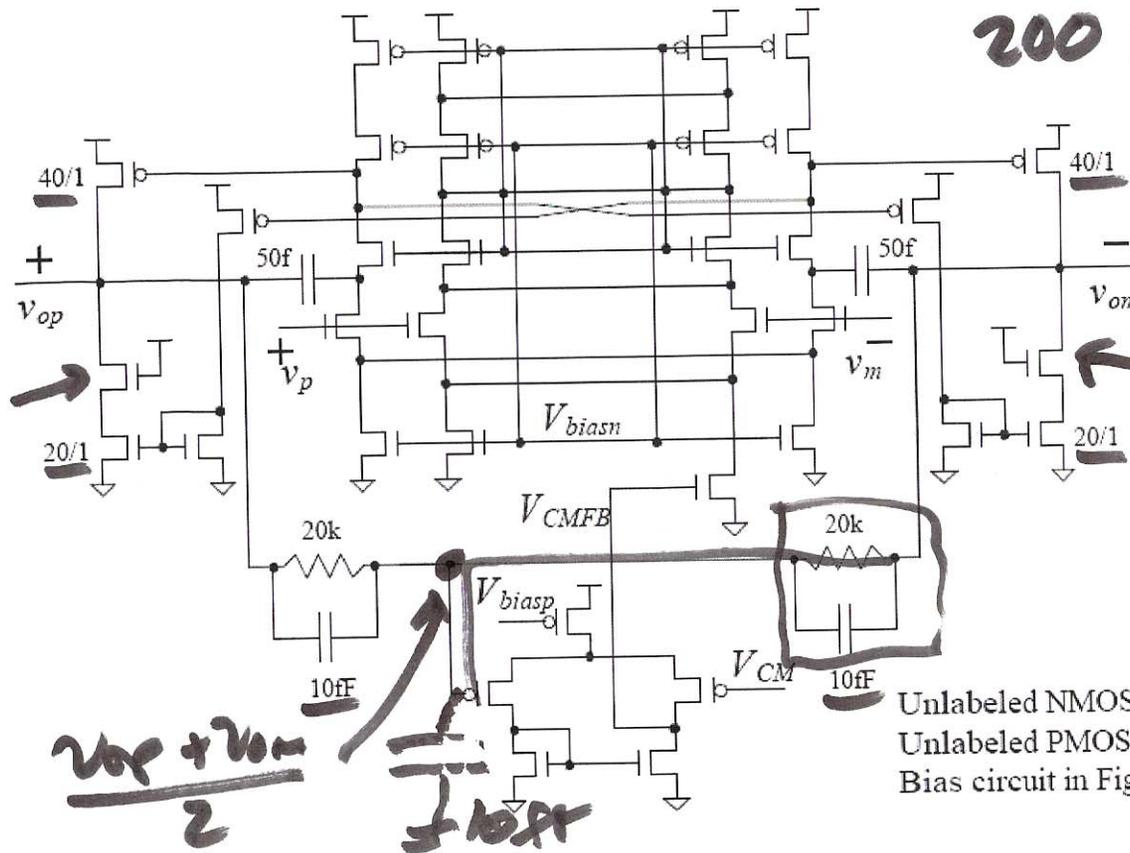

20k · 10fF
200 pS

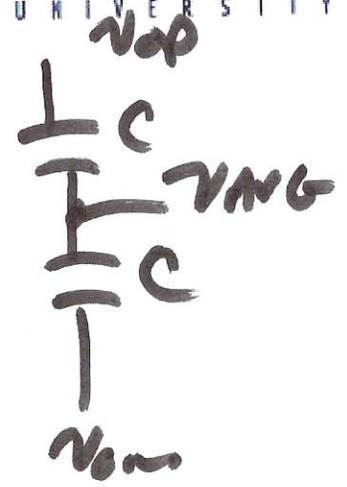

added device

$$\frac{v_{op} - v_{avg}}{I_{DQ}} =$$

~~$\frac{v_{op} - v_{om}}{I_{DQ}}$~~

$$\frac{v_{avg} - v_{om}}{I_{DQ}}$$

~~$\frac{v_{op} - v_{om}}{I_{DQ}}$~~

$$2v_{avg} = v_{op} + v_{om}$$

$$v_{avg} = \frac{v_{op} + v_{om}}{2}$$

$$\frac{v_{op} + v_{om}}{2}$$

10fF

Unlabeled NMOS are 10/1
Unlabeled PMOS are 20/1
Bias circuit in Fig. 26.3

Figure 26.33 Op-amp with modified output buffer.

10)

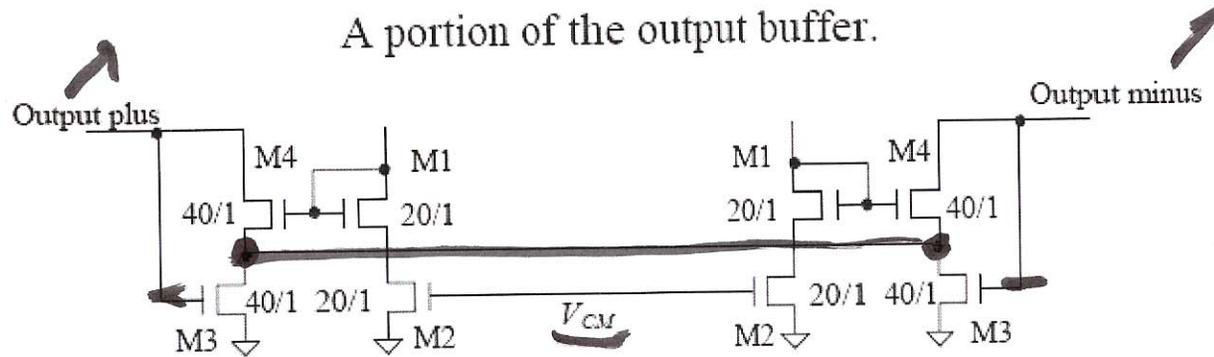


Figure 26.37 Using triode-operating MOSFETs to balance the outputs (bad).

11)


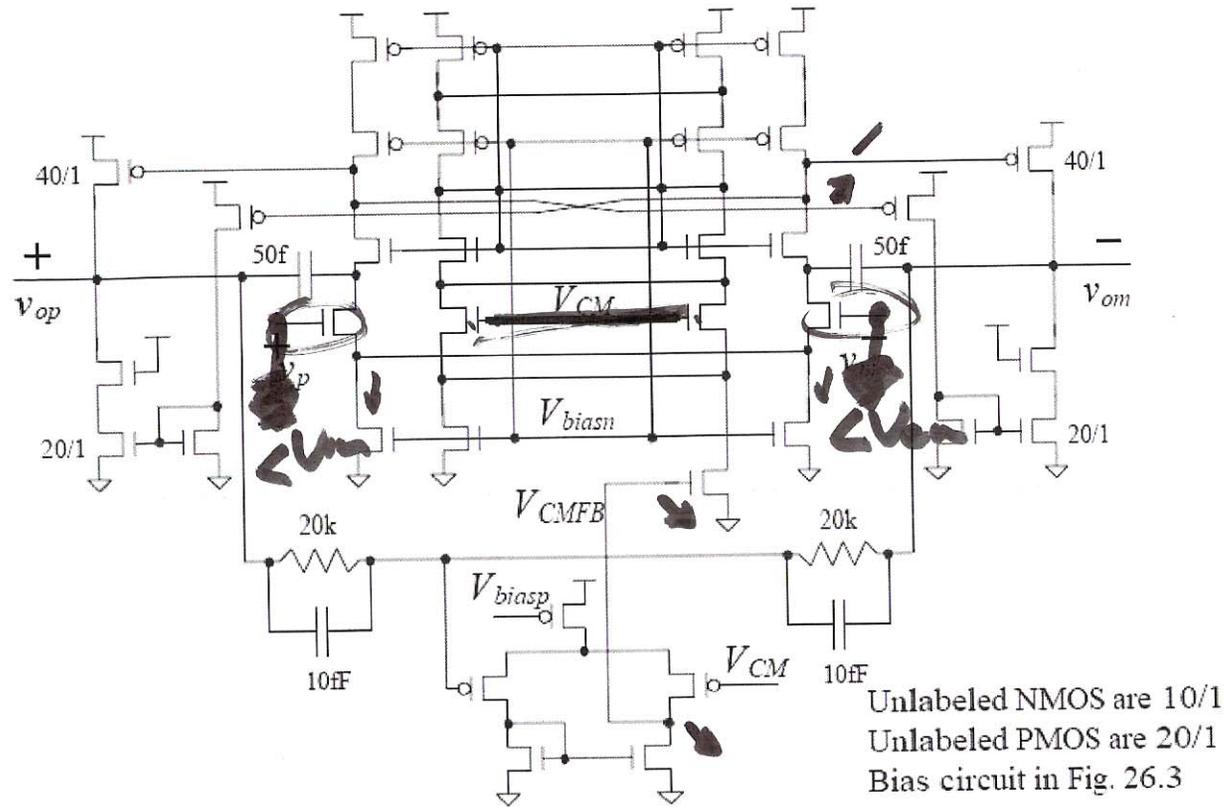


Figure 26.39 Connecting the bias circuit diff-amp's inputs to the common-mode voltage.

12)

simplify the design

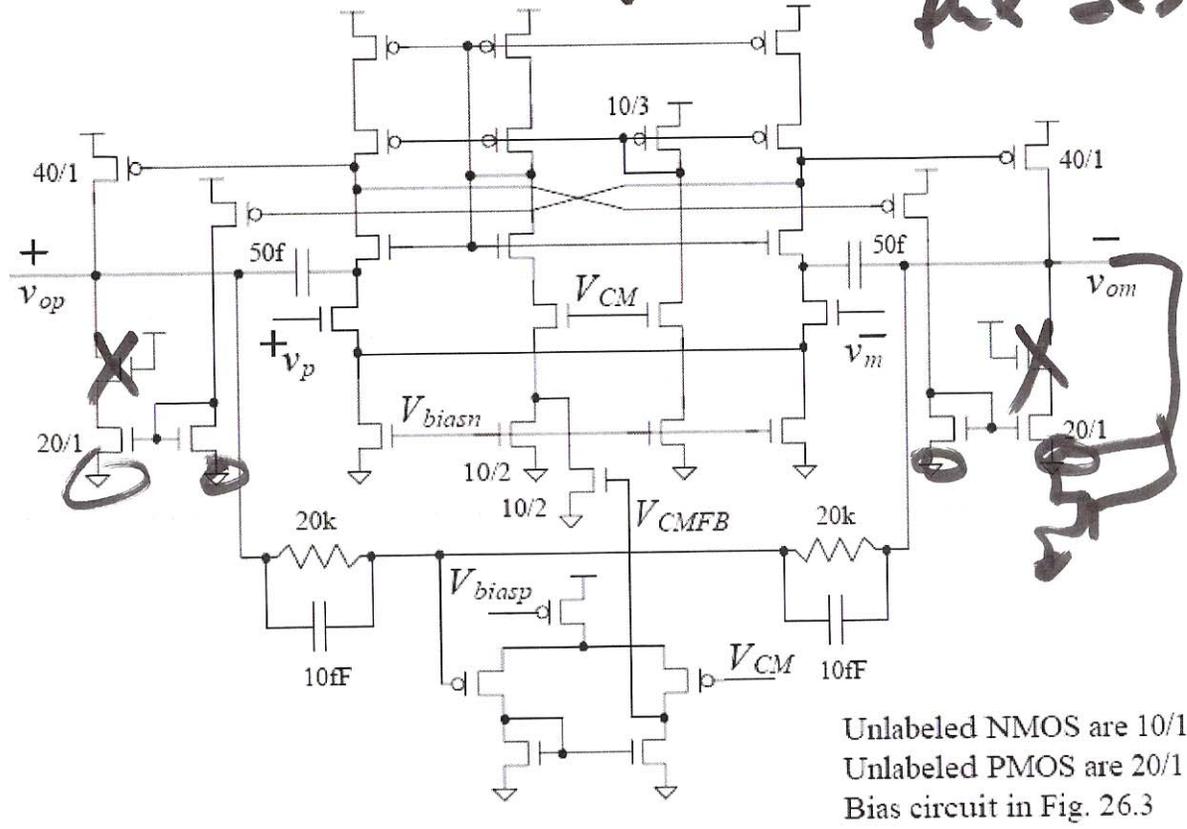

Unlabeled NMOS are 10/1
 Unlabeled PMOS are 20/1
 Bias circuit in Fig. 26.3

Figure 26.40 Making the op-amp more practical.

137

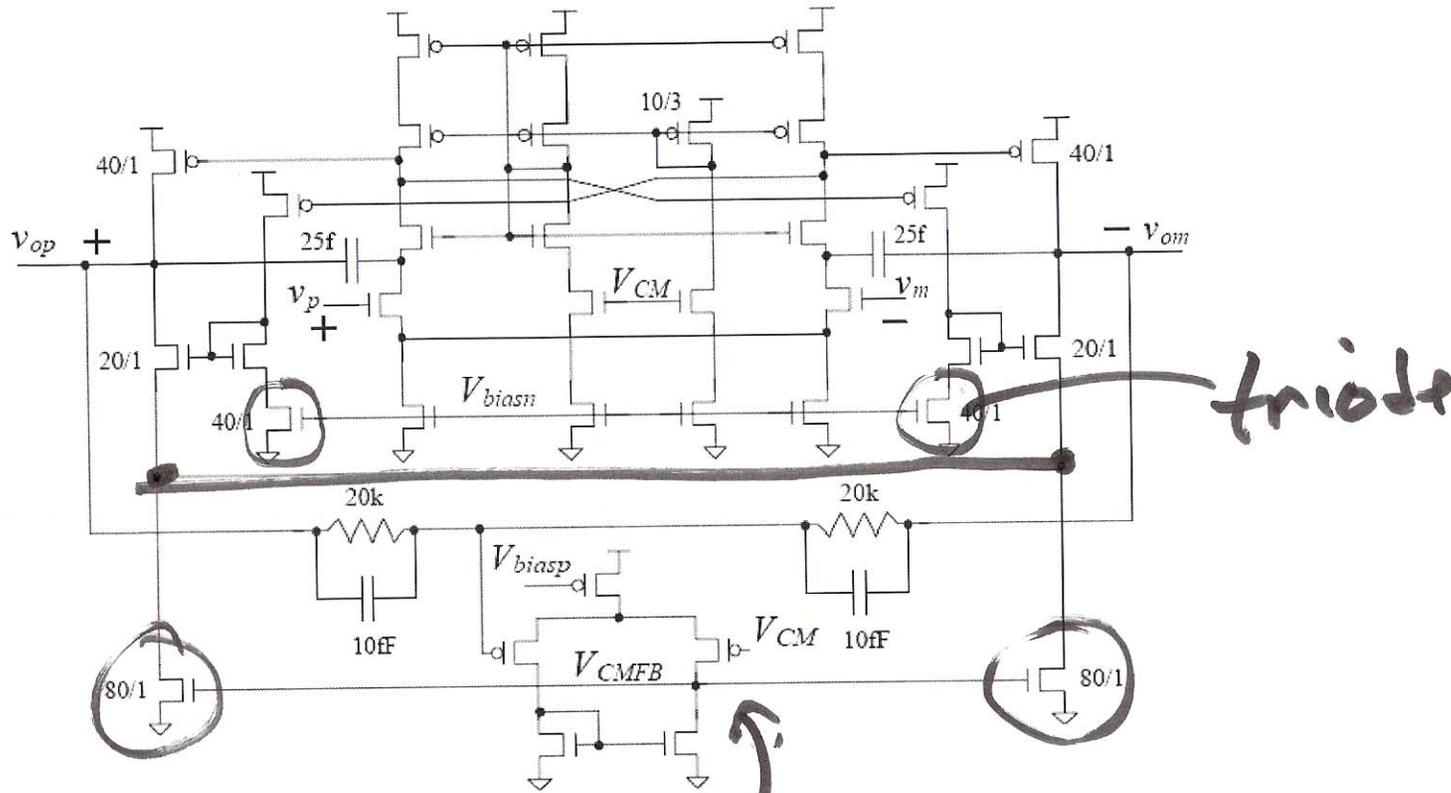


Figure 26.43 Providing CMFB through just the output buffer. Using an amplifier with triode-operating MOSFETs for CMFB (good).

Amplifier with gain

op-amp

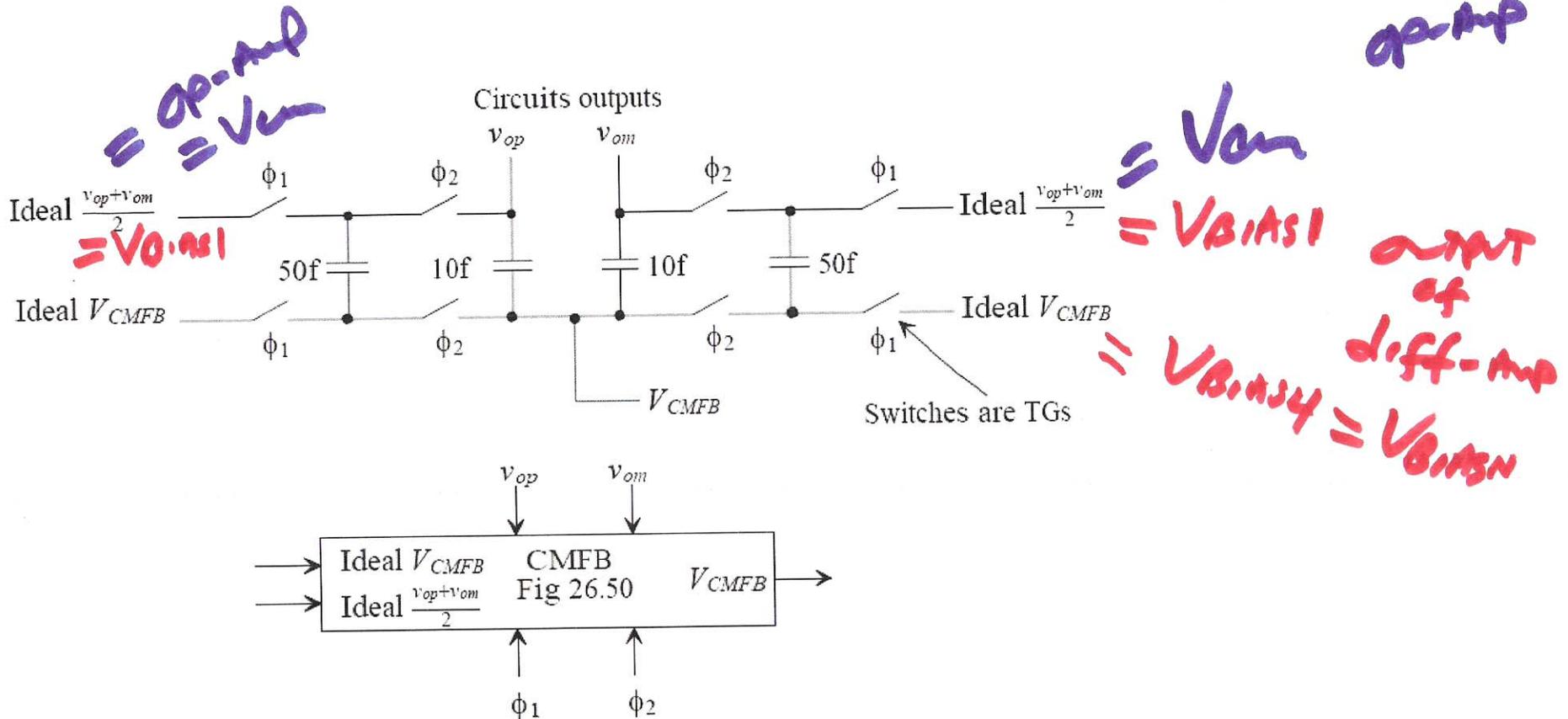


Figure 26.50 A switched-capacitor CMFB circuit (see Fig. 26.16).
Switches implemented with transmission gates.

15)

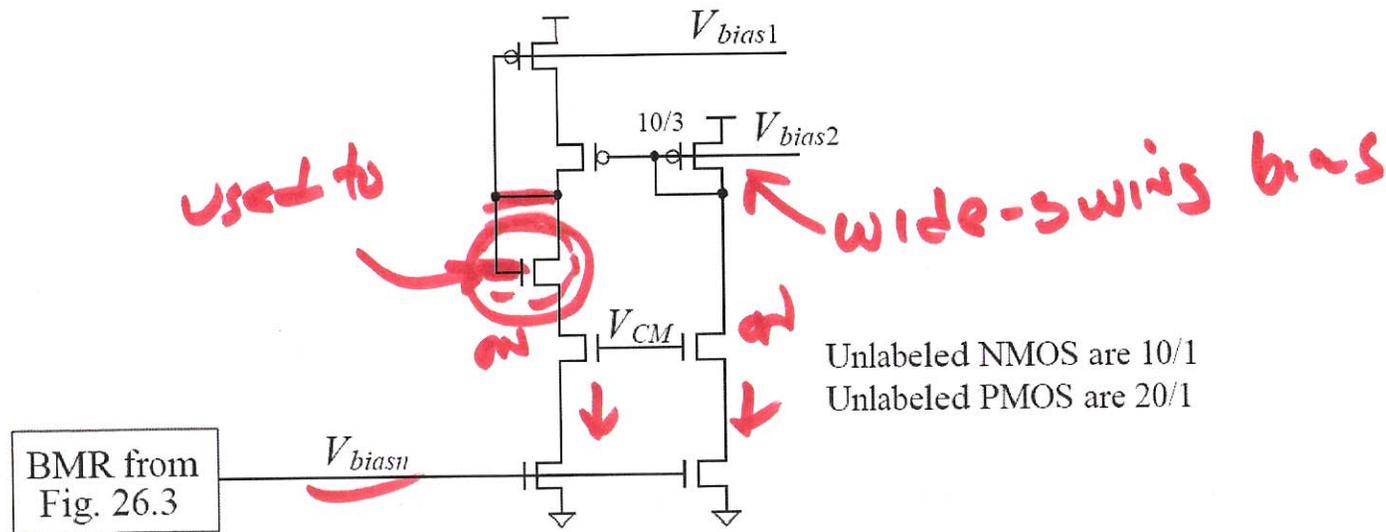


Figure 26.52 Biasing circuit for the op-amp developed in this section.

14)


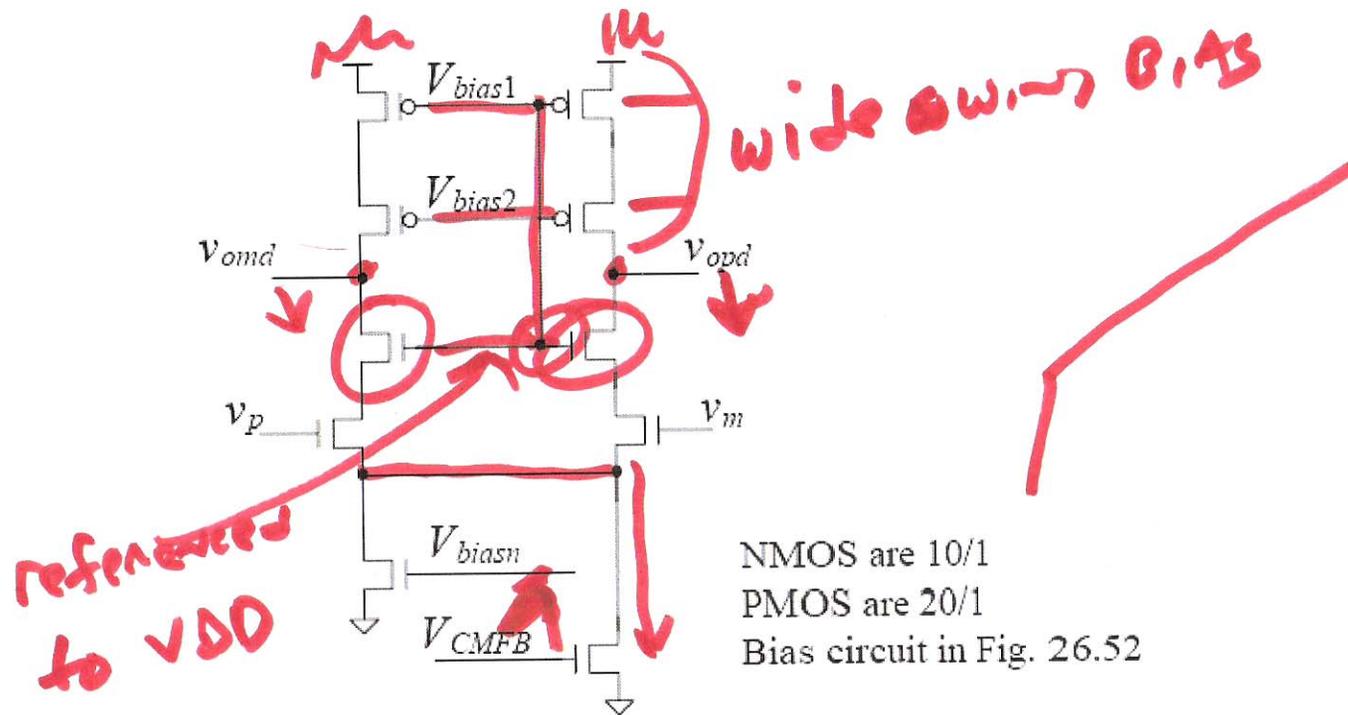


Figure 26.53 Diff-amp used with the bias circuit of Fig. 26.52.

17)

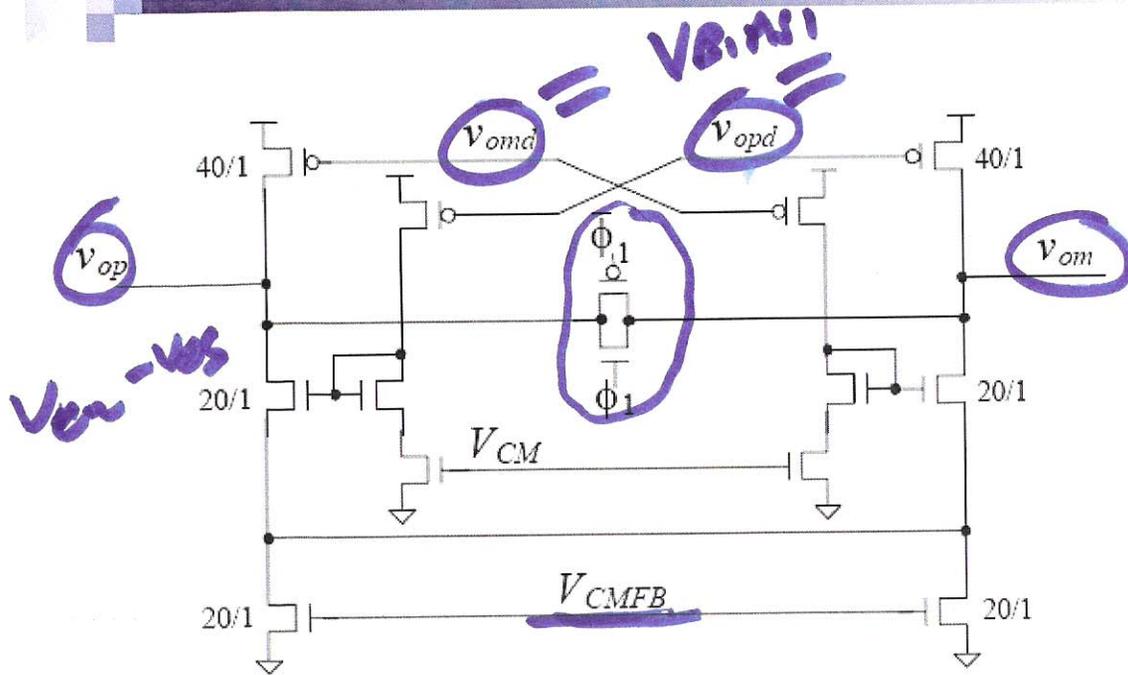

$v_{om} + v_{os}$

Will not cancel the offset


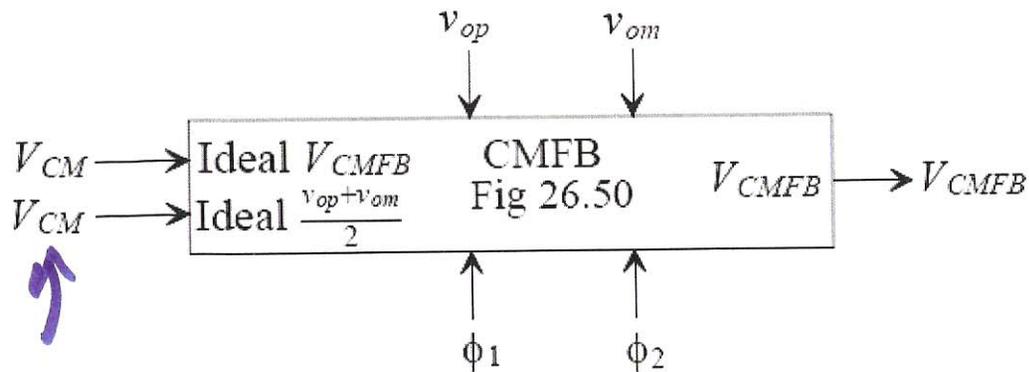


Figure 26.56 Output buffer and CMFB.

17)

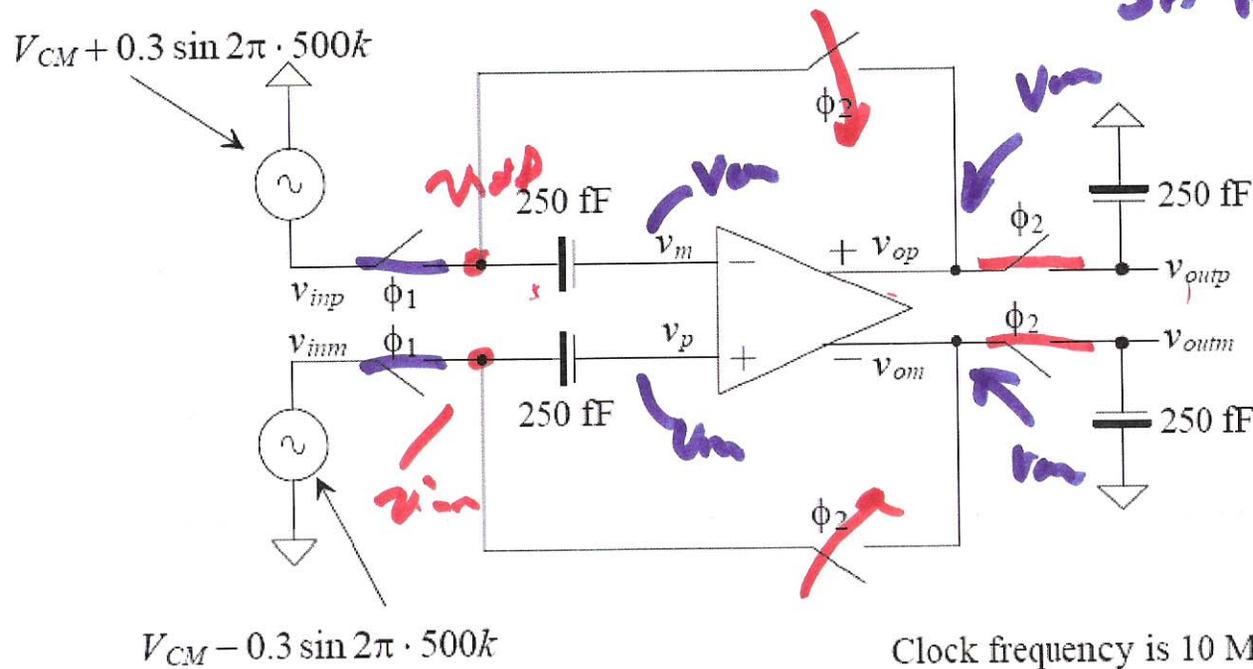

SAMPLE ϕ_1 is
 closed
 open ϕ_1
 switches
 close
 ϕ_2 switches

Figure 26.58 Simulating the operation of the op-amp formed with the diff-amp in Fig. 26.54 and buffer in Fig. 26.56.

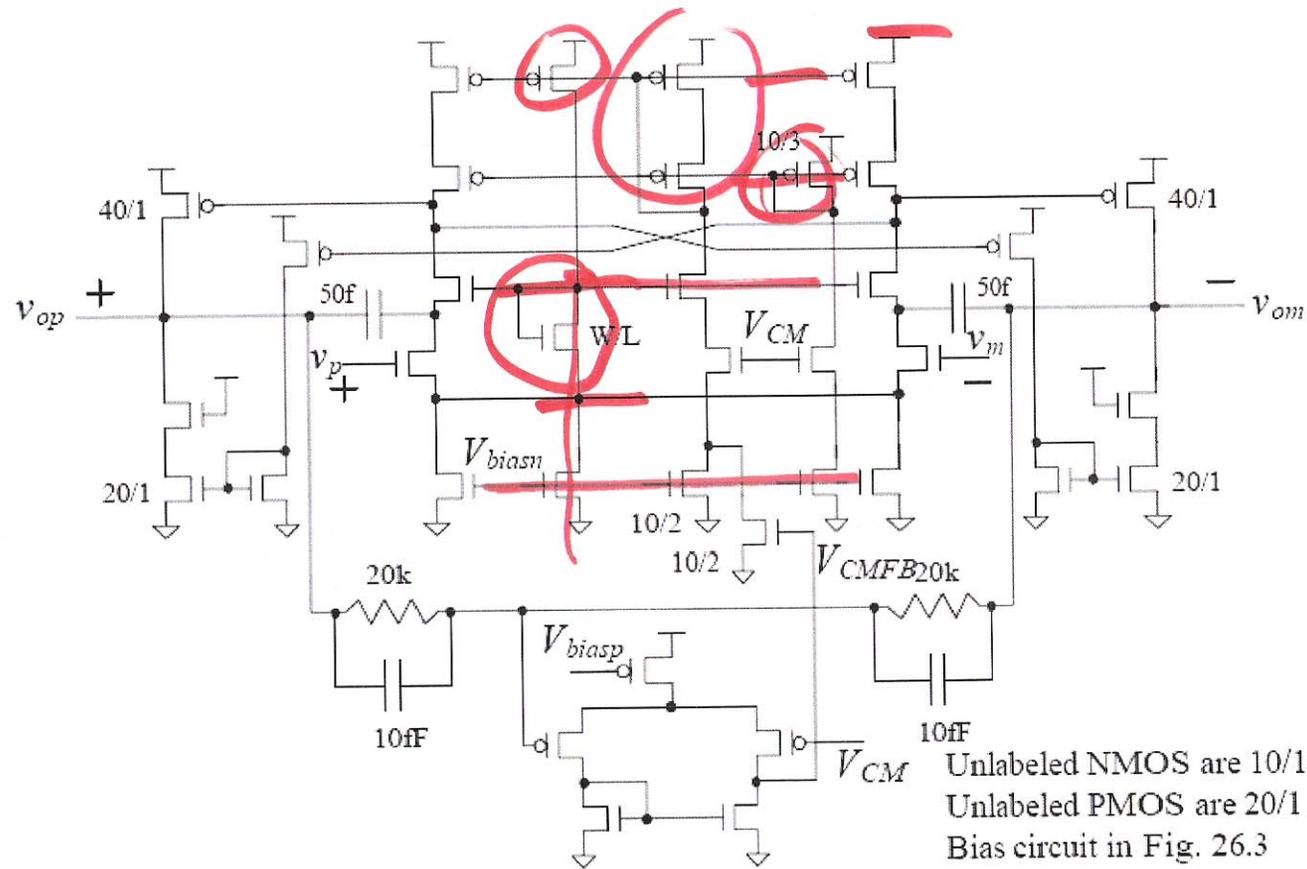


Figure 26.62 An op-amp with better biasing (but more power) for lower VDD operation.

21)

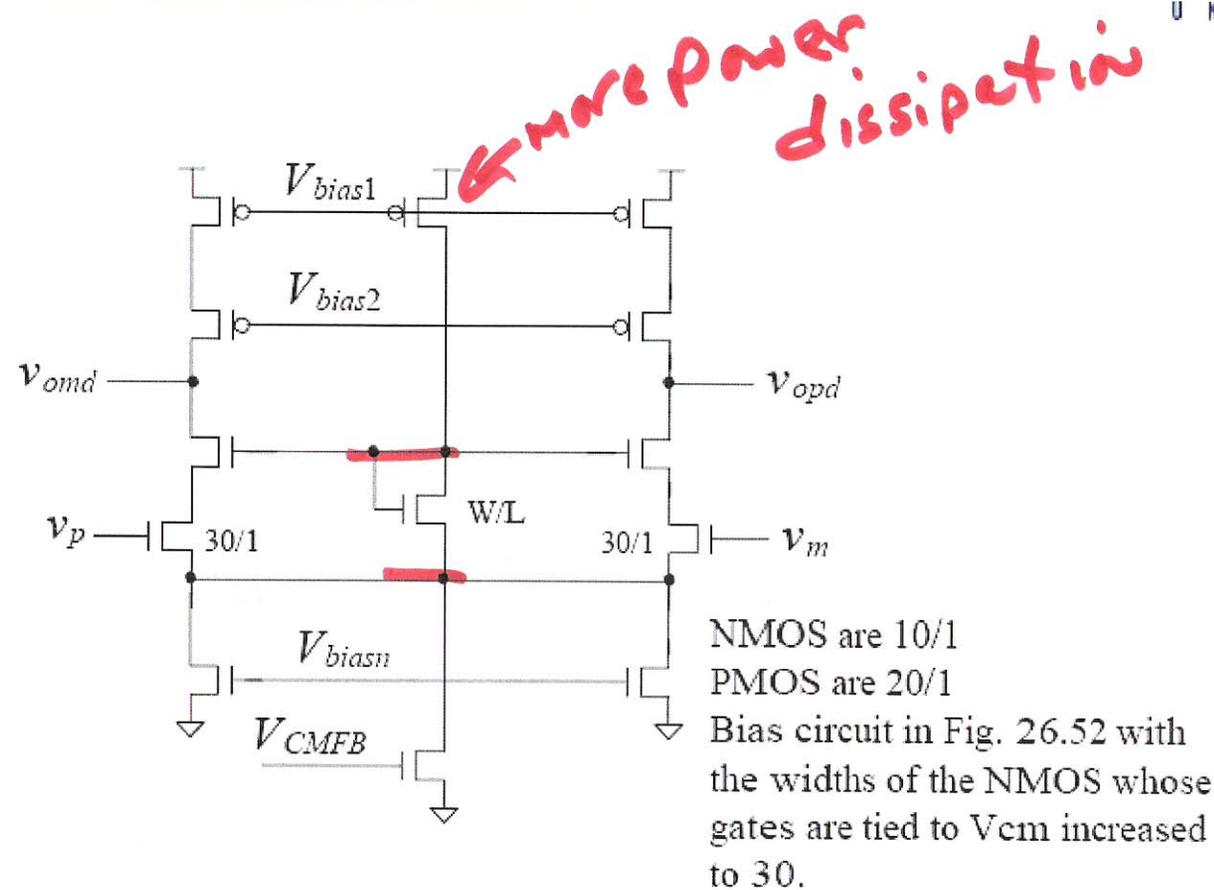


Figure 26.63 Modifying the diff-amp seen in Fig. 26.53 for wider swing operation.

22)