

ECE 614 Advanced Analog IC

Sept. 1, 2011 DPSign

Lecture 4

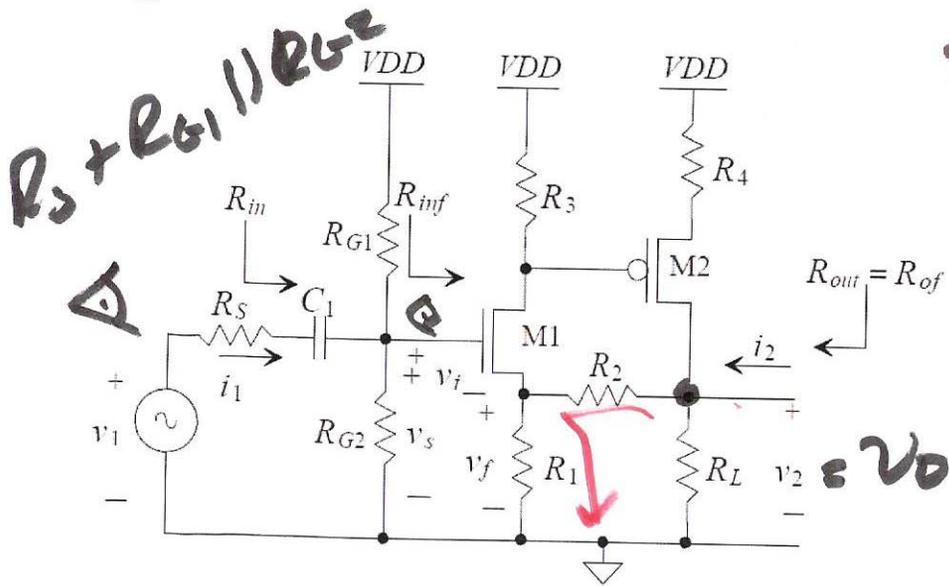


Figure 31.13 Transistor-level series-shunt feedback amplifier.

Handwritten equations for the feedback amplifier analysis:

$$i_d = g_m \cdot v_{gs}$$

$$-i_d = g_m \cdot (-v_{gs}) = g_m \cdot v_{gs}$$

$$-(v_g - v_s) = v_s - v_g$$

$$v_f = \beta \cdot v_o$$

Handwritten equations for input and output resistances:

$$R_{inf} = R_{in} = \infty$$

$$R_{in} = R_{L1} \parallel R_{G2}$$

$$R_{out} = \frac{R_o (1 + \beta A_{CL})}{\beta}$$

Handwritten equation for the output resistance with feedback:

$$R_{outf} = \frac{R_o}{1 + \beta A_{CL}}$$

Handwritten equation for the feedback factor beta:


$$\beta = \left(\frac{R_1 + R_2}{R_1} \right)^{-1}$$

Handwritten equation for the ideal closed-loop gain:

$$A_{CL} /_{ideal} = \frac{1}{\beta}$$

17

OPEN-LOOP gain

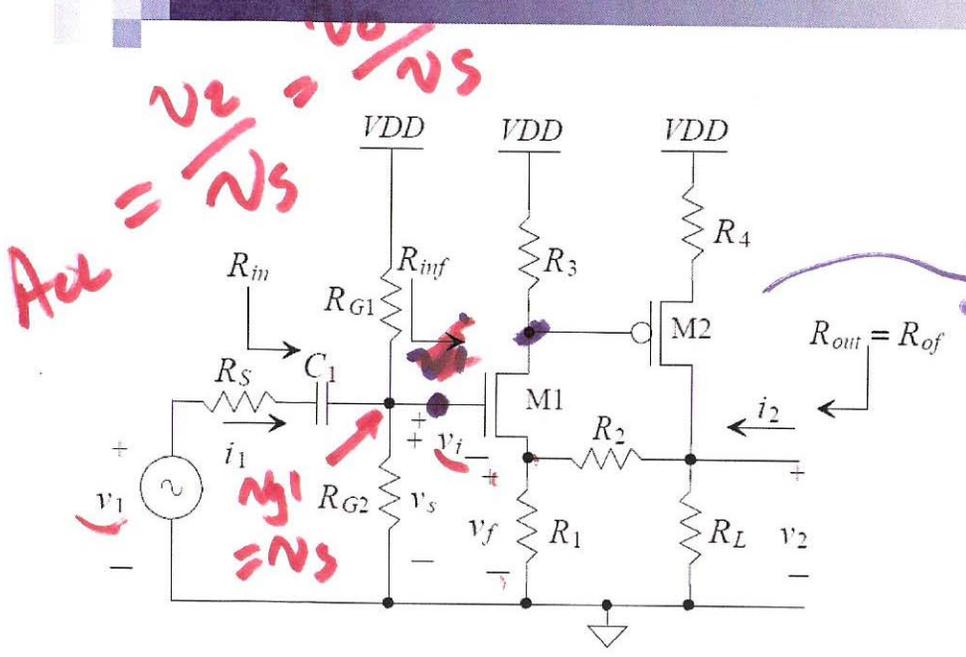

include loadings from β network

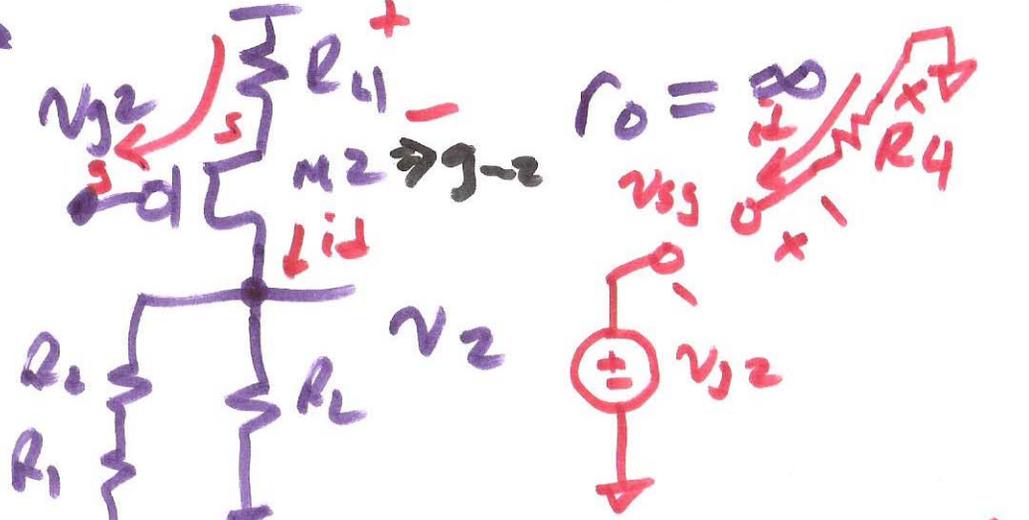


Figure 31.13 Transistor-level series-shunt feedback amplifier.

$$R_4 \cdot i_d - v_{sg} - v_2 = 0$$


$$v_s - v_f = v_i \quad i_d = g_{mP} \cdot v_{sg}$$

$$\frac{v_2}{v_{sg2}} = -g_{m2} (R_L \parallel (R_1 + R_2))$$

$$\frac{v_2}{v_{sg2}} = \frac{i_d \cdot (R_L \parallel (R_1 + R_2))}{i_d \left(\frac{1}{g_{mP}} + R_4 \right)}$$

$$\frac{v_2}{v_{sg2}} = \frac{i_d (R_L \parallel (R_1 + R_2))}{i_d \left(-\frac{1}{g_{mP}} \right)}$$

2)

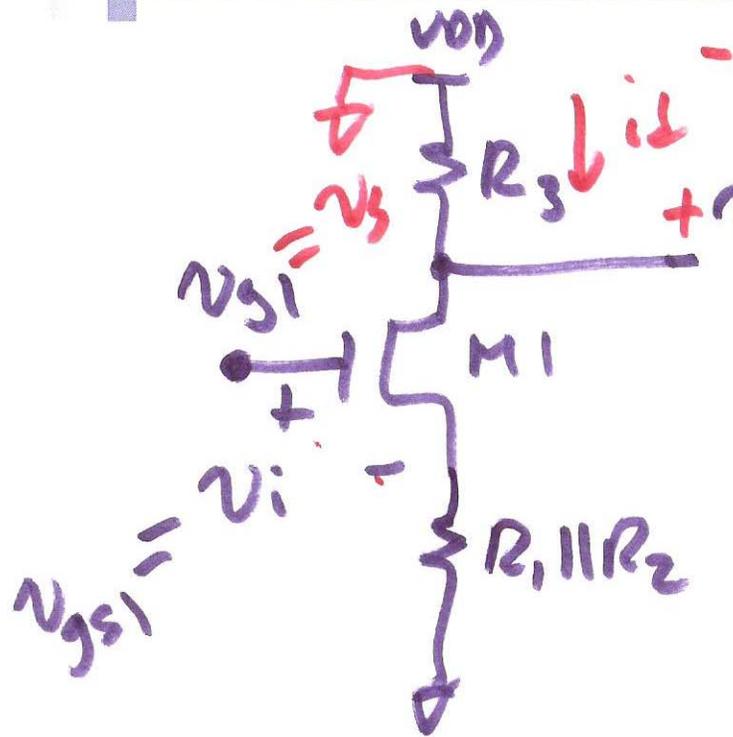

$$\frac{v_{gs2}}{v_{gs1}} = \frac{v_{gs2}}{v_s} = \frac{-i_d \cdot R_3}{i_d \left(\frac{1}{g_{m1}} + R_1 || R_2 \right)}$$

$$\frac{v_{gs2}}{v_{gs1}} = \frac{-R_3}{\frac{1}{g_{m1}}}$$

$$v_{gs1} = \frac{i_d}{g_{m1}}$$

$$\frac{v_{gs2}}{v_s} = \frac{g_{m1} R_3}{1 + g_{m1} \cdot (R_1 || R_2)}$$

3)



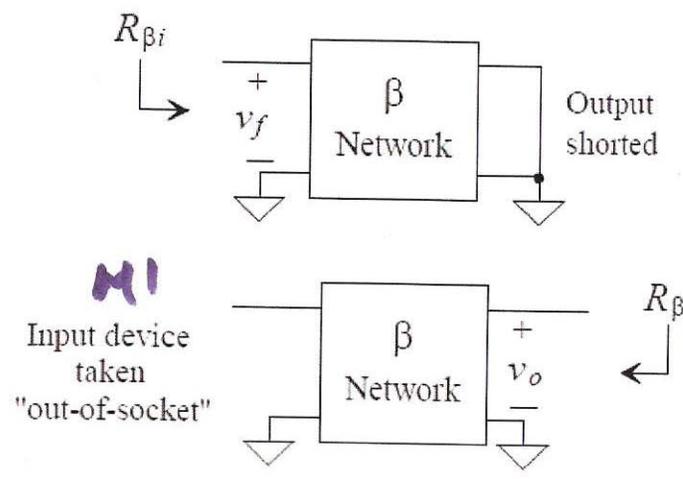


Figure 31.15 Determining the loading due to the feedback network for a series-shunt amplifier.

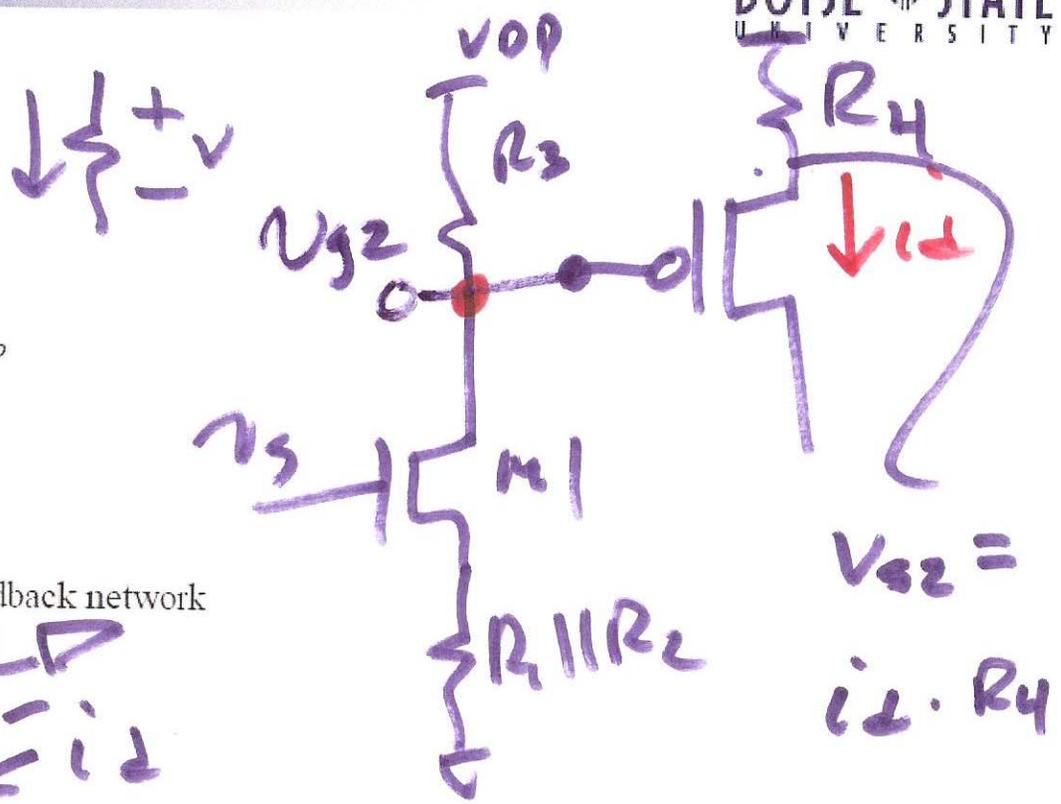


$v_{s2} = i_d \cdot R_4$

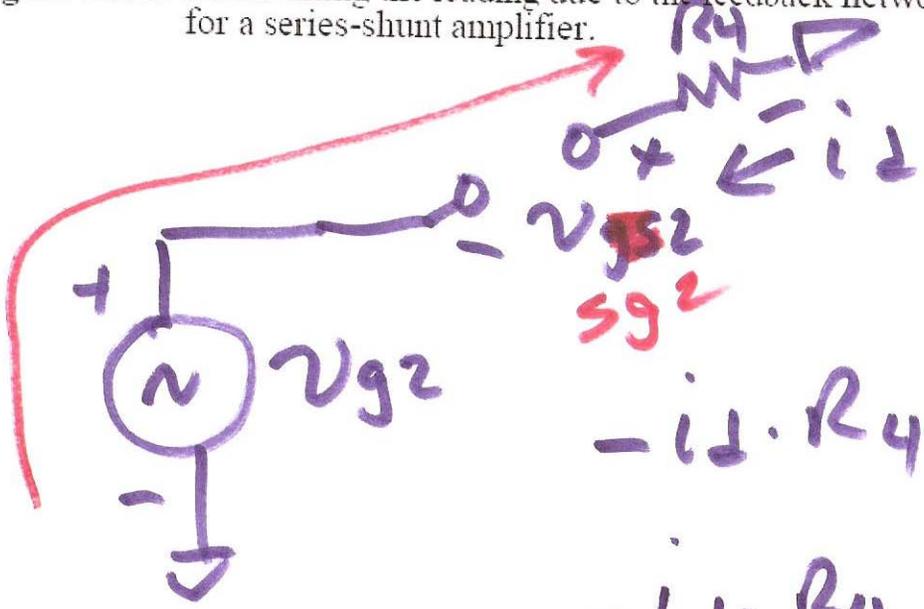

$$-i_d \cdot R_4 + v_{s2} + v_{g2} = 0$$

$$-i_d \cdot R_4 + v_{s2} - v_{g2} + v_{g2} = 0$$

4)

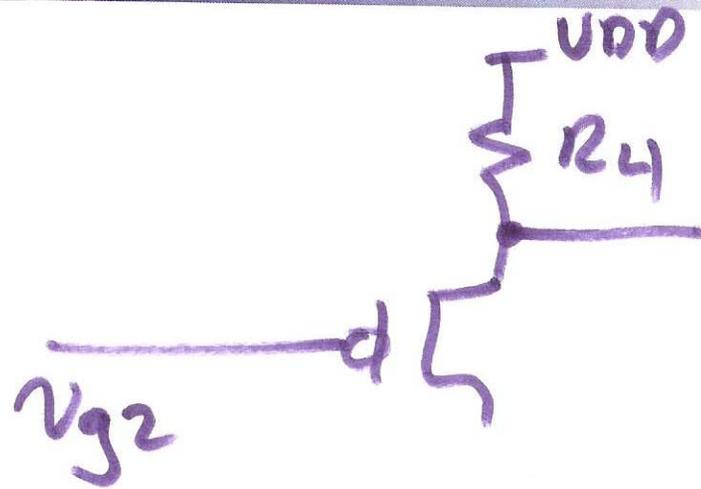

$$v_{s2} = -i_d \cdot R_4$$

$$v_{sg2} = v_{s2} - v_{g2}$$

$$= -i_d \cdot R_4 - v_{g2}$$


$$v_{sg2} \cdot g_{m2}$$

$$-v_{g2} = v_{sg2} \underbrace{(1 + g_{m2} R_4)}$$

$$\Rightarrow (1 + g_{m2} R_4)$$

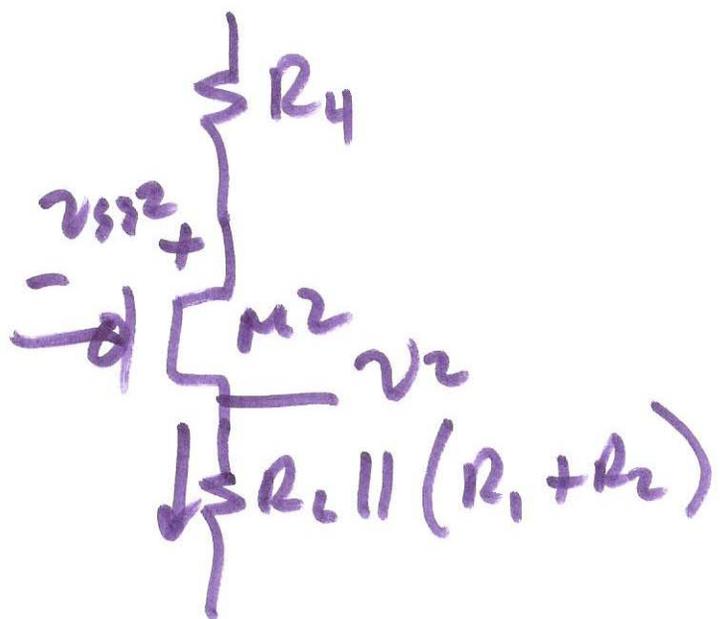5)


$$\left(\frac{v_2}{v_{sg2}} \right) = \frac{+R_2 \parallel (R_1 + R_2)}{-1/g_{m2}} = -g_{m2} R_2 \parallel (R_1 + R_2)$$



b)

$$\frac{v_{sg2}}{v_{gs1}}$$

$$v_{g2} = -\frac{R_3}{1/g_{m1}}$$

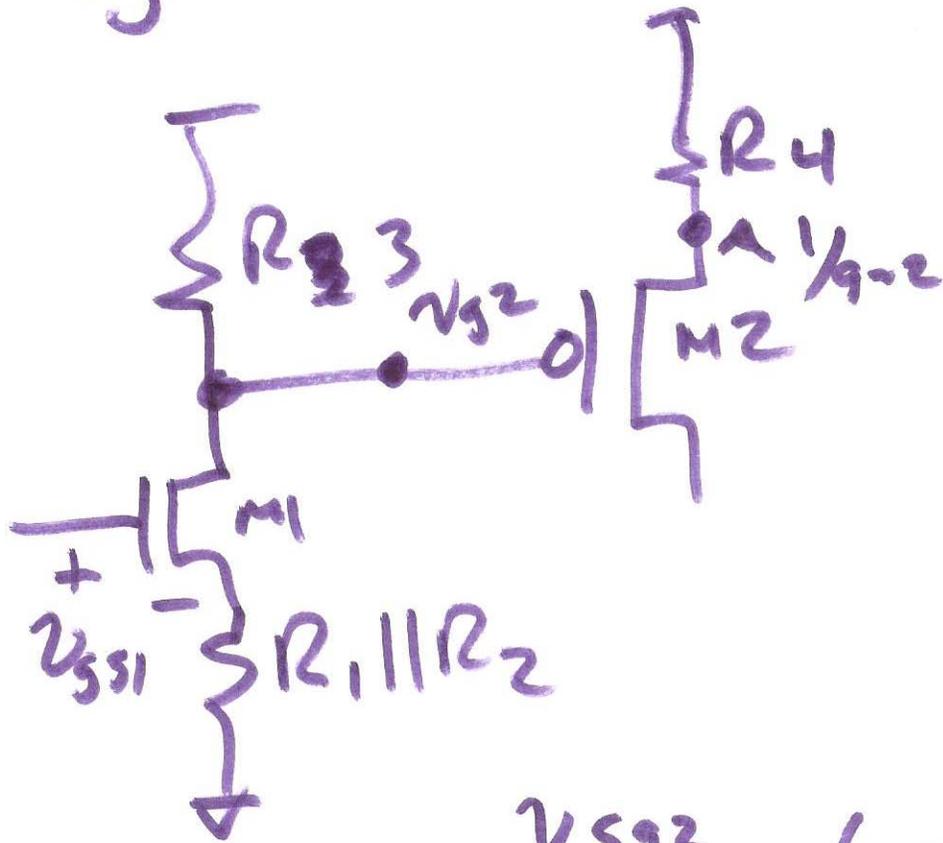


$$v_{s2} = v_{g2} \cdot \frac{R_4}{R_4 + 1/g_{m2}}$$

$$\frac{v_{sg2}}{v_{g2}} = \frac{1}{g_{m2}} \cdot \frac{1}{R_4 + 1/g_{m2}}$$

$$\frac{v_{sg2}}{v_{gs1}} = (-g_{m1} R_3) \cdot \left(\frac{1}{1 + g_{m2} R_4} \right)$$


→

$$\frac{V_{sg2}}{V_{g2}}$$

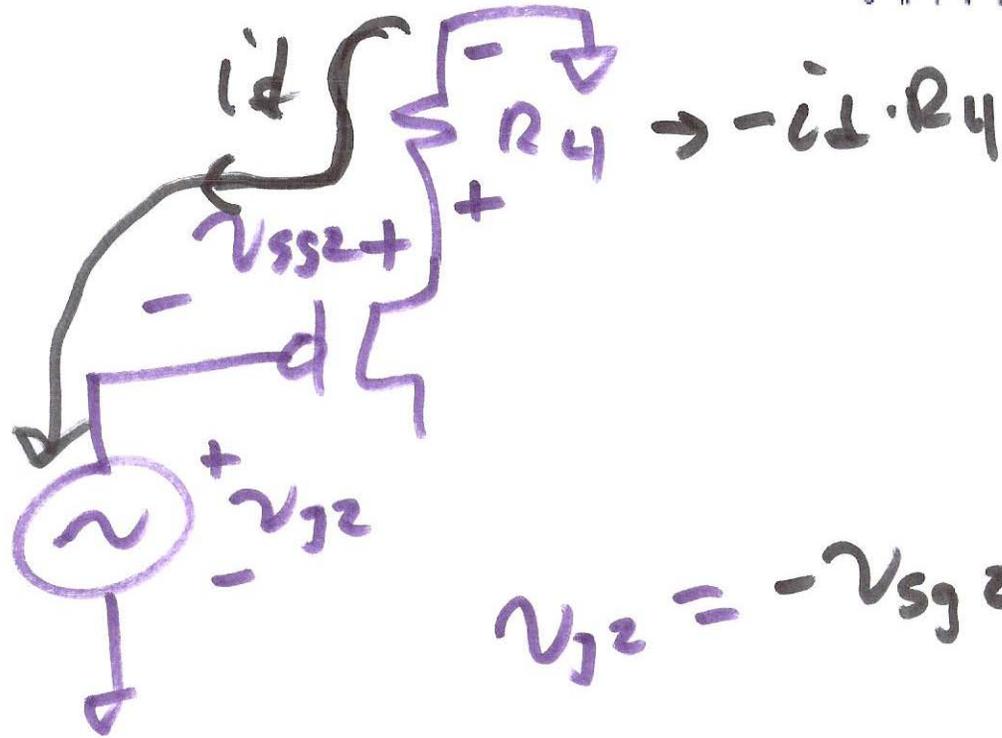

$$V_{g2} = -V_{sg2} - i_d R_4$$

8)

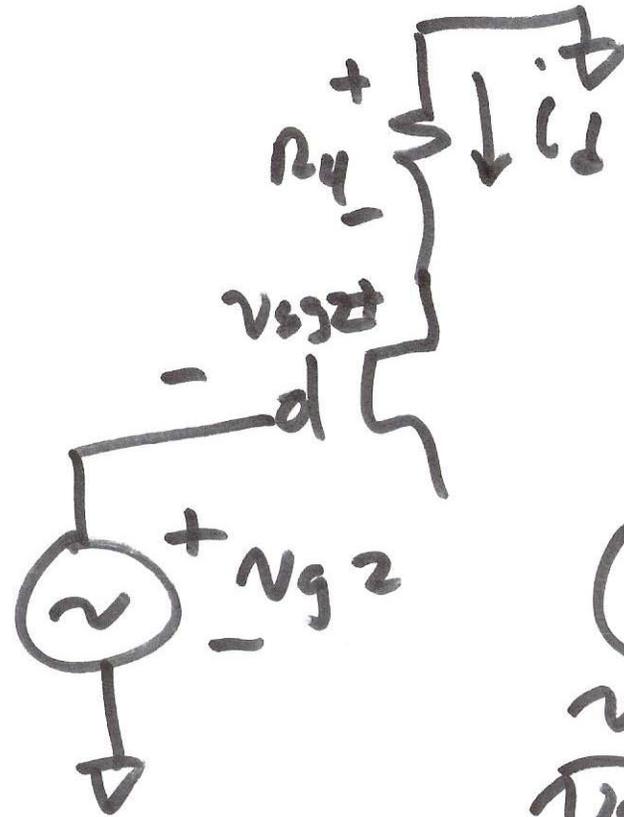

$$g_m v_{sg2} = i_d$$

$$R_4 \cdot i_d + v_{sg2} + v_{gs2} = 0$$

$$(R_4 g_m + 1) v_{sg2} = -v_{gs2}$$

$$\frac{v_{sg2}}{v_{gs2}} = \frac{1}{1 + g_m R_4}$$

9)

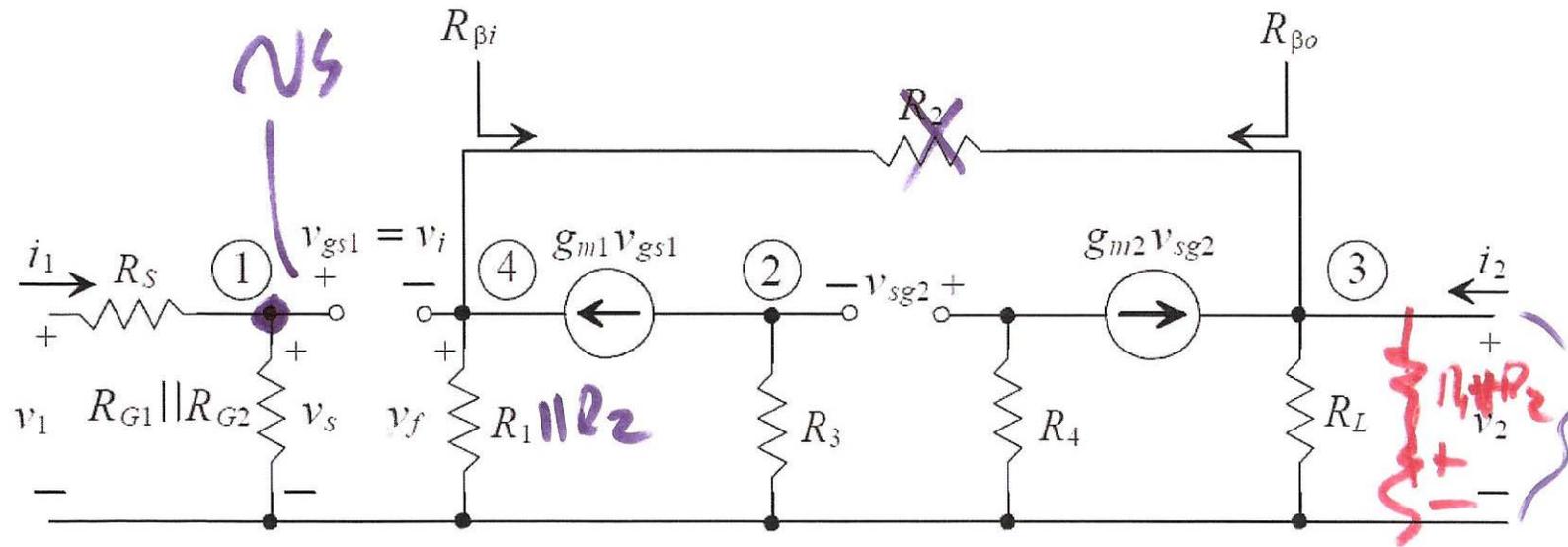


Figure 31.14 Closed-loop small-signal model of Fig. 31.13.

10)


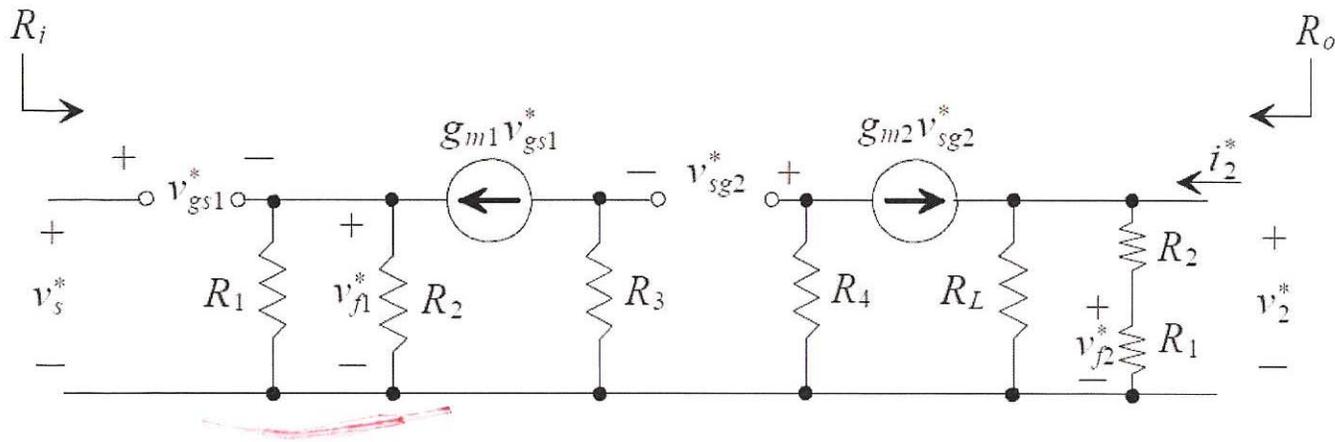


Figure 31.16 Open-loop small-signal model of Fig. 31.13.

11)

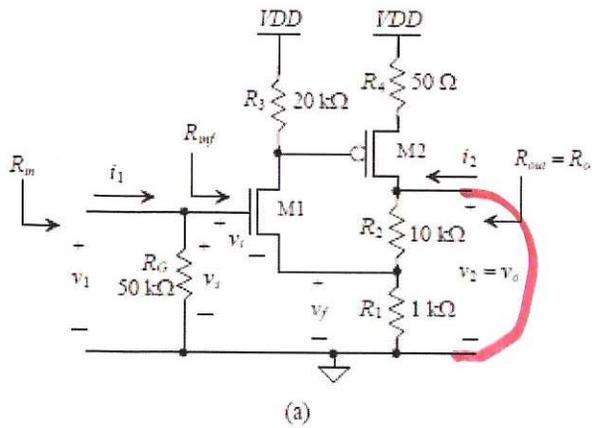

$$v_o \cdot \beta = \left(\frac{20k\Omega + 1k\Omega}{10k\Omega} \right)^{-1} = v_f$$

$$v_f = v_o \cdot \frac{1k\Omega}{1k\Omega + 10k\Omega}$$

$$A_{cl} \approx \frac{1}{\beta} = 11 \beta$$

$$R_{in} = R_{inf} = \infty$$

$$R_o = 11k\Omega$$



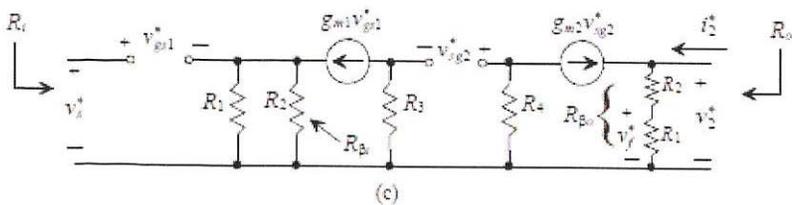
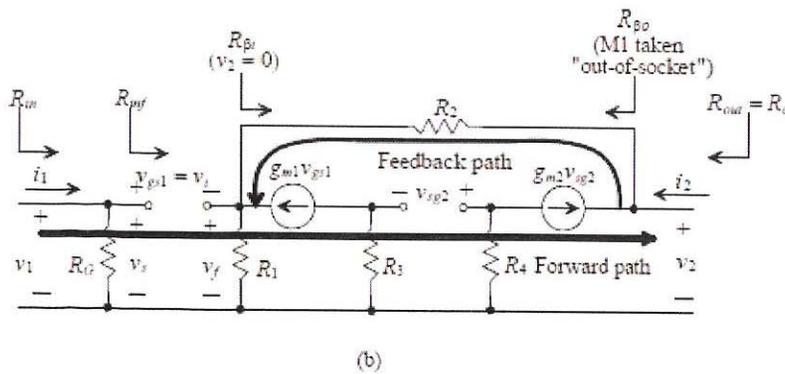


Figure 31.17 (a) Series-shunt circuit used in Ex. 31.1; (b) its closed-loop small-signal model; and (c) the resulting open-loop model.


(2)

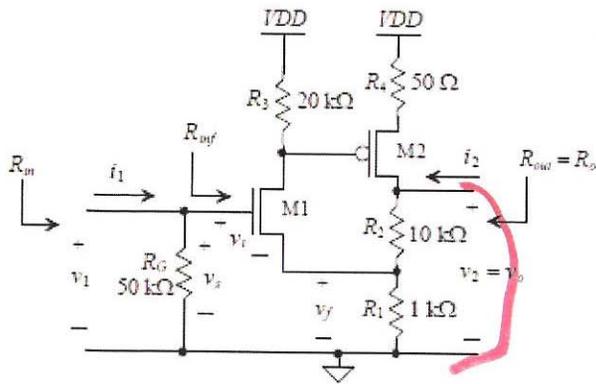

(a)

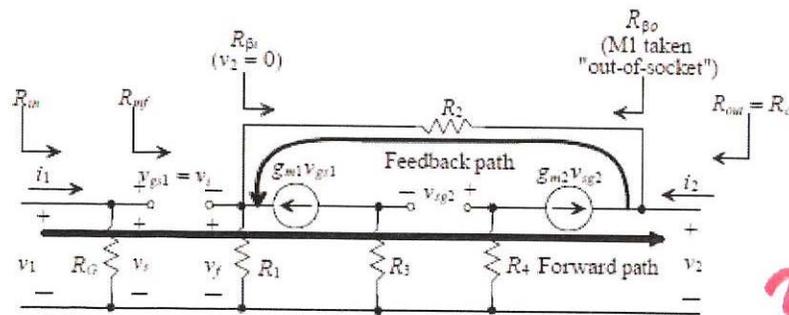

(b)

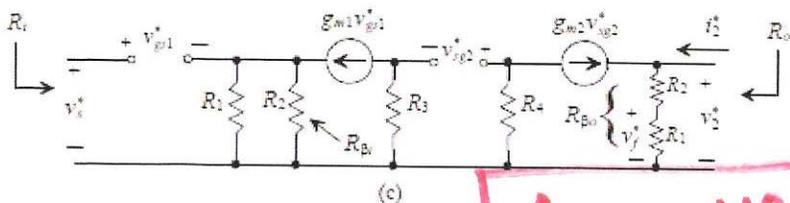

(c)

$A_{OL} = 110$

Figure 31.17 (a) Series-shunt circuit used in Ex. 31.1; (b) its closed-loop small-signal model; and (c) the resulting open-loop model.

$$\frac{v_s}{v_{gs2}} = \frac{20k}{10k \parallel 1k}$$

$$\frac{v_{gs2}}{v_s} = \frac{-20k}{1k + 10k \parallel 1k}$$

$$g_{-1,2} = 1 - \frac{v_{gs2}}{v_s}$$

$$\frac{1}{g_{-1,2}} = 1k$$

$$\frac{v_o}{v_{gs2}} = \frac{50}{-11k}$$

$$\frac{v_o}{v_s} = \frac{50 + \frac{1}{g_{-2}}}{20k \cdot 11k}$$

$$= \frac{220 \cdot 10^6}{2 \cdot 10^6} \approx 110$$

$$A_{OL} = \frac{v_o}{v_s} = \frac{v_o}{v_{gs2}} \cdot \frac{v_{gs2}}{v_s} = \frac{110}{(1k + 9k)(1,050)}$$

13)

$$\beta = \frac{1\text{K}}{1\text{K} + 10\text{K}} = .09$$

$$A_{CL} = \frac{110}{1 + .09 \cdot 110} = \frac{1}{\frac{1}{110} + .09} \approx 10$$

$$R_{of} = \frac{11\text{K}}{1 + 0.09 \cdot 110} = \underline{\underline{1\text{K}}}$$

14)

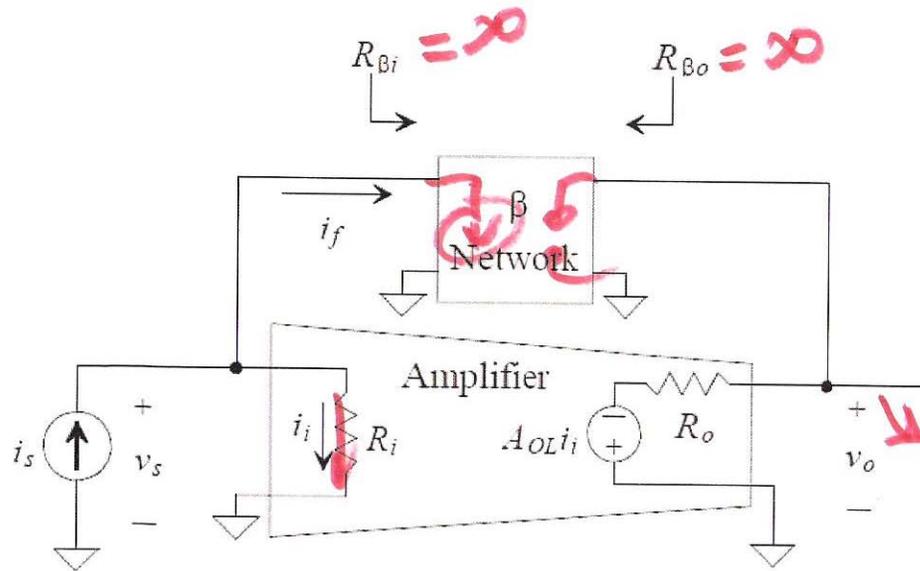


Figure 31.18 An ideal transimpedance (shunt-shunt) amplifier.

CURRENT - VOLTAGE

$$R_{if} = \frac{R_i}{1 + \beta A_{OL}}$$

$$R_{of} = \frac{R_o}{1 + \beta A_{OL}}$$

15)

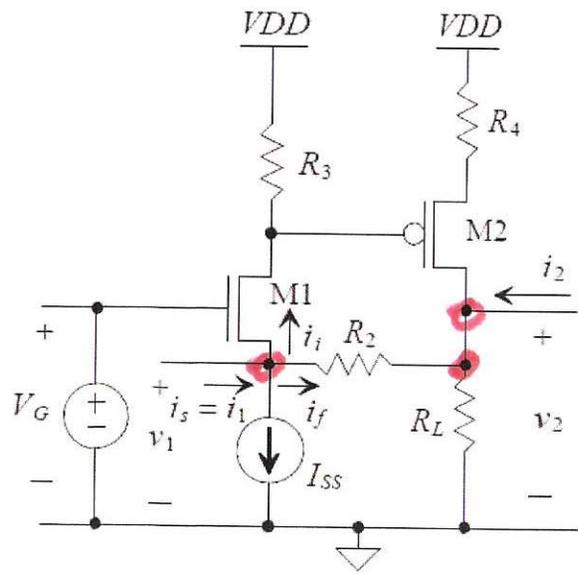


Figure 31.19 Shunt-shunt feedback amplifier.

trans resistance.

1b)